

# [CS M51A FALL 18] MIDTERM EXAM

Date: 10/30/18

- The midterm is closed book, and up to 4 sheets (= 8 pages) of summary notes are allowed. You can use a calculator but not smart phones.
- For multiple choice questions, wrong answers may have a negative score value so choose carefully. It is possible that questions can have multiple answers.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- **This should strictly be your own work; any form of collaboration will be penalized.**

Name : Yinghao Wang

Student ID : 204953840

Problem	Points	Score
1	10	10
2	15	15
3	15	13
4	15	10
5	20	15
6	10	7
7	15	3
Total	100	73

94

Problem 1 (10 points)

1. (4 points) How many bits are required to encode a color spectrum capable of supporting 16 million colors using:

20 bits =  $10^5$   
5 chunks =  $10^5$

$10^7 = 100,000,000$

a. Decimal digits in BCD

$8 \cdot 4 = 32$

32 bits

b. Hexadecimal representation

24 bits

$16^5 \cdot 16^4 \cdot 16^3 \cdot 16^2 \cdot 16^1 \cdot 16^0$   
In binary, requires 24 bits  
 $2^{24} > 16 \text{ mil}$

Which representation is more efficient? Why?

Hexadecimal because it requires less bits

2. (6 points) Fill in the missing entries in the table.

$5 \times 16^2 + 1 \times 16^1 + 7 \times 16^0$

Radix	Digit vector $\underline{x}$	Value $x$ in decimal
16	(5, 1, 7)	1303
8	(5, 1, 7)	335
7	(4, 5, 3, 2)	1640

~~$5 \times 8^2 + 1 \times 8^1 + 7 \times 8^0$~~   
 $5 \times 8^2 + 1 \times 8 + 7 \times 8^0$

23

$\frac{4}{5} \frac{3}{2}$   
3 2 1 0

Problem 2 (15 points)

$a + b = b + a$	$ab = ba$	Commutativity
$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
$a + (b + c) = (a + b) + c = a + b + c$	$a(bc) = (ab)c = abc$	Associativity
$a + a = a$	$aa = a$	Idempotency
$a + a' = 1$	$aa' = 0$	Complement
$1 + a = 1$	$0a = 0$	
$0 + a = a$	$1a = a$	Identity
$(a')' = a$		Involution
$a + ab = a$	$a(a + b) = a$	Absorption
$a + a'b = a + b$	$a(a' + b) = ab$	Simplification
$(a + b)' = a'b'$	$(ab)' = a' + b'$	DeMorgan's law

Given  $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)'$ , which of the following represents the same function as  $E(a, b, c, d)$ ? Show all your work.

1.  $a + b + c + d'$
2.  $a' + b + c$
3.  $b + c' + d$
4.  $a'b'c'd$
5.  $ab'c'$
6.  $b'cd'$

$$\begin{aligned}
 & (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)' \\
 & (a'b'c' + abc)'(ac + bca + bcc' + bcd') + a(bb + bd + bc + cd + c)' \quad \text{De Morgan's Law} \\
 & (a'b'c' + b'c')(ac + abc + bcc' + bcd') + a(bb + bd + bc + cd + c)' \quad \leftarrow \begin{matrix} \text{distributivity} \\ \text{commutativity} \end{matrix} \\
 & (a'b'c' + b'c')(ac + abc + 0 + bcd') + a(bb + bd + bc + cd + c)' \quad \text{complement} \\
 & (a'b'c' + b'c')(ac + abc + bcd') + a(b + bd + bc + cd + c)' \quad \text{idempotency \& identity} \\
 & (a'b'c' + b'c')(ac + bcd') + a(b + bc + c)' \quad \text{absorption} \\
 & (a'b'c'ac + b'c'ac + a'b'c'bcd' + b'c'bcd') + a(b + bc + c)' \quad \text{distributivity} \\
 & (a'a'b'c'c + ab'c'c + a'b'c'cd' + b'bc'cd') + a(b + bc + c)' \quad \text{commutativity} \\
 & (0 + 0 + 0 + 0) + a(b + bc + c)' \quad \text{complement} \\
 & a(b + bc + c)' \\
 & a(b + c)' \\
 & \boxed{a(b'c')} \\
 & a + b
 \end{aligned}$$

z: 01  
u: 100

$$ab + ac' + b'b + b'c'$$

6: 116  
7: 111

**Problem 3 (15 points)**

Show if the gate G, described by  $G(x, y, z) = \text{one-set}\{3, 4, 6, 7\}$ , can implement NOT and AND gates. Assume that 0 and 1 are available. If it can, then use G gates to implement the following expression and show the corresponding network of G gates


$$(a'b)' - (b'c)'$$

$$E(a, b, c) = (a + b')(b + c')$$

$$\begin{aligned} G &= x'yx + xy'z' + xyz' + xyz \\ &= yz(x' + x) + xz'(y' + y) \\ G &= yz + xz' \end{aligned}$$

AND(a, b) = G(0, a, b) ✓  
NOT(a) = G(1, 0, a) ✓
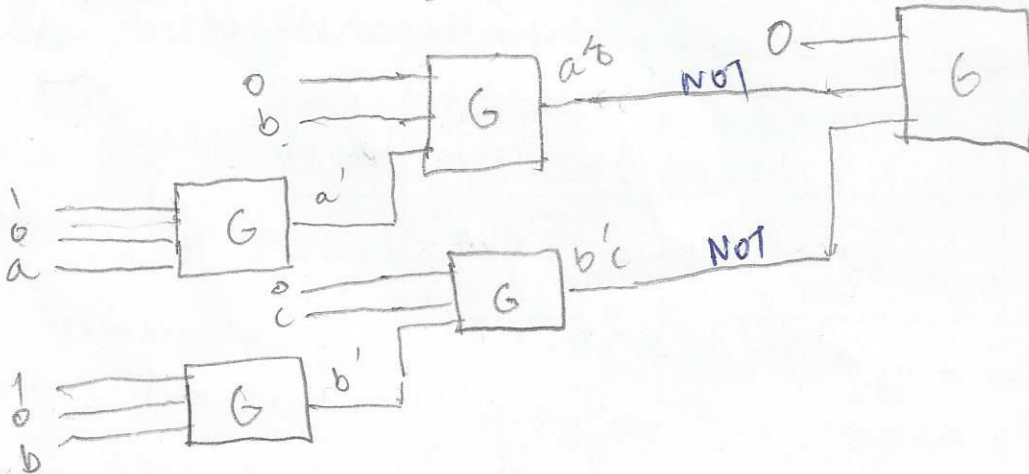
$$\begin{aligned} E(a, b, c) &= (a + b')(b + c') \\ &= (a'b)'(b'c)' \end{aligned}$$




$$(a'b)'(b'c)' =$$

$$G(1, 0, G(0, G(1, 0, a), b)) \text{ and } G(1, 0, G(0, G(1, 0, b), c))$$

$$G(0, G(1, 0, G(0, G(1, 0, a), b)), G(1, 0, G(0, G(1, 0, b), c)))$$

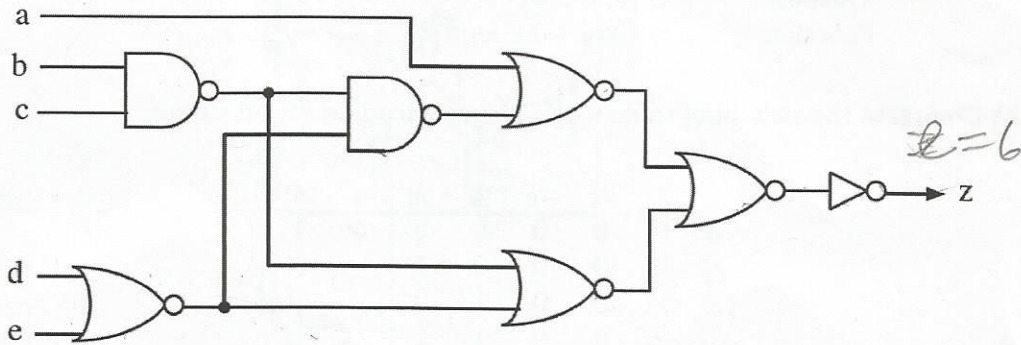**Problem 4 (15 points)**

With the help of the table below, determine the low to high propagation delay  $t_{pLH}(d, z)$  of the output  $z$  of the network shown below. Assume the network output has a load of 6.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		$t_{pLH}$	$t_{pHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

LH 1+L LH LH LH

$$0.06 + 0.075(2) + 0.05 + 0.038(1) + 0.08 + 0.027 \times 1$$

$$0.06 + 0.075(1) + 0.07 + 0.016(1) + 0.02 + 0.038(6) =$$

= 0.767 ns

**Problem 5 (20 points)**

Obtain a two-level gate network of the following system.

Inputs:  $x, y \in \{0, 1, 2, 3\}$   
 Outputs:  $z \in \{0, 1, 2, 3\}$   
 Function:  $z = \{3xy + 1\} \pmod 4$

x y  
 0 0  
 0 1  
 1 2  
 1 3

1. (2 points) Complete the switching table using binary encoding for all values.


		$x_1$	$x_0$	$y_1$	$y_0$	$z_1$	$z_0$
0	0	0	0	0	0	0	1
0	1	0	0	0	1	0	1
0	2	0	0	1	0	0	1
0	3	0	0	1	1	0	1
1	0	0	1	0	0	0	1
1	1	0	1	0	1	0	0
1	2	0	1	1	0	1	1
1	3	0	1	1	1	1	0
2	0	1	0	0	0	0	1
2	1	1	0	0	1	0	1
2	2	1	0	1	0	0	1
2	3	1	0	1	1	1	1
3	0	1	1	0	0	0	1
3	1	1	1	0	1	1	0
3	2	1	1	1	0	1	1
3	3	1	1	1	1	0	0

2. (5 points) Show the switching expressions of  $z_1$  and  $z_0$  in sum of minterms form.


$$z_1 = x_1' x_0 y_1 y_0' + x_1' x_0 y_1 y_0 + x_1 x_0' y_1 y_0 + x_1 x_0 y_1' y_0 + x_1 x_0 y_1 y_0'$$

$$z_0 = x_1' x_0' y_1' y_0' + x_1' x_0' y_1' y_0 + x_1' x_0' y_1 y_0' + x_1' x_0' y_1 y_0 + x_1' x_0 y_1' y_0' + x_1' x_0 y_1' y_0 + x_1' x_0 y_1 y_0' + x_1' x_0 y_1 y_0 + x_1 x_0 y_1' y_0' + x_1 x_0 y_1' y_0 + x_1 x_0 y_1 y_0'$$

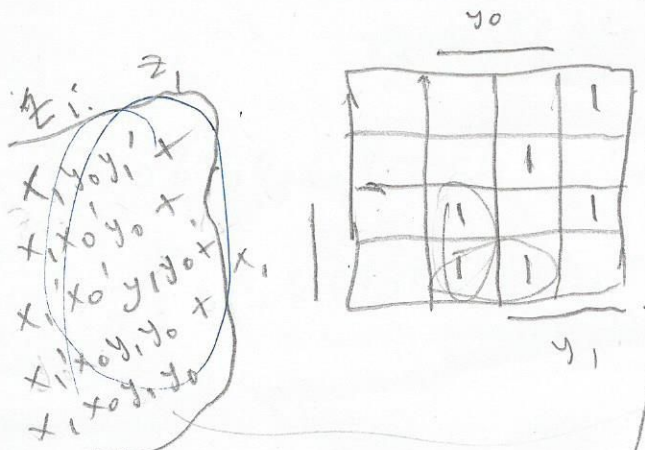3. (8 points) Show the minimal sum of products expressions of  $z_1$  and  $z_0$ . In each case, show a K-map, indicate all prime implicants, and all essential prime implicants. Show NAND-NAND networks.




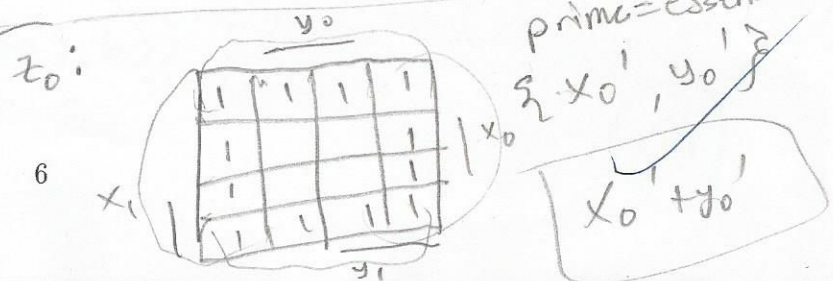prime = essential =  
 $\{x_1 y_0 y_1', x_1 x_0' y_0, x_1 x_0' y_1 y_0', x_1' x_0 y_1 y_0, x_1' x_0 y_1 y_0'\}$



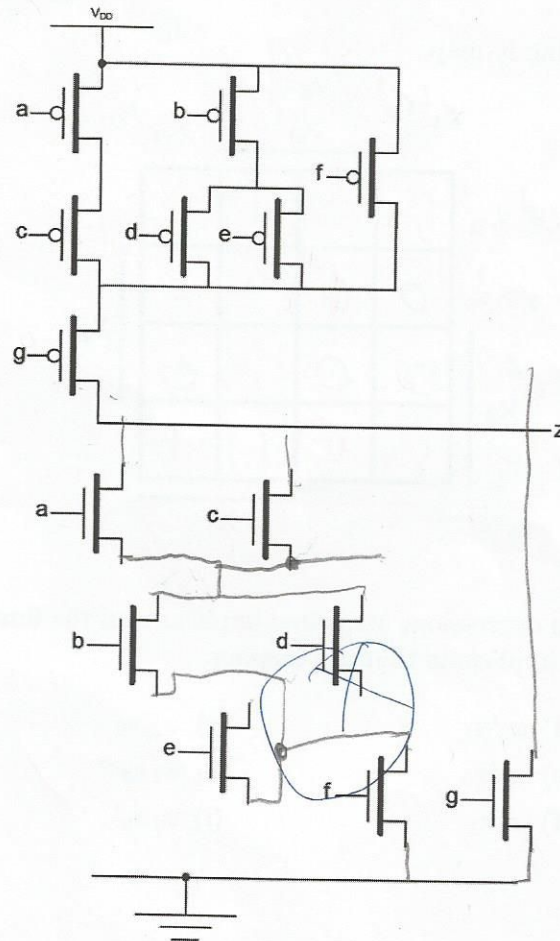**Problem 6 (10 points)**

We are given the following partial CMOS network.



1. (5 points)

Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

2. (5 points) Connect NMOS transistors to complete the circuit according to the pull-down expression. Please only add missing wires.

$$1) z = a'c'g' + b'(d' + e') + f'$$

$$2) z' = (a'c'g' + b'd' + b'e' + f')' = (a + c + g)(b + d)(b + e)(f) =$$

$M(4, 5, 6, 12, 13, 14)$   
 $= \sum m$

**Problem 7 (15 points)**

For  $f(x_3, x_2, x_1, x_0) = (x_3 + x_2' + x_1 + x_0)(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2' + x_1 + x_0)(x_3' + x_2' + x_1 + x_0')(x_3' + x_2' + x_1' + x_0)$

1. (2 points) Fill out the following K-map.

$x_1'x_0' \quad x_1'x_0 \quad x_1x_0' \quad x_1x_0$

$x_3'x_2'$	$x_3'x_2$	$x_2x_1$	$x_2x_1'$	$x_3$
$x_3'x_2'$	$x_3'x_2$	$x_2x_1$	$x_2x_1'$	$x_3$
$x_2x_1$	$x_2x_1'$	$x_3$	$x_3'$	$x_1$
$x_3'x_2'$	$x_3'x_2$	$x_2x_1$	$x_2x_1'$	$x_3$
$x_3'x_2'$	$x_3'x_2$	$x_2x_1$	$x_2x_1'$	$x_3$

$x_1$

2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Write down any prime implicants that are missing.

- |                |               |                |                    |
|----------------|---------------|----------------|--------------------|
| (a) $x_1$      | (d) $x_3'x_1$ | (g) $x_2'x_0$  | (j) $x_3'x_2'x_1$  |
| (b) $x_3x_1$   | (e) $x_3'x_0$ | (h) $x_1x_0$ ✓ | (k) $x_2x_1x_0$    |
| (c) $x_3'x_2'$ | (f) $x_2x_1$  | (i) $x_1x_0'$  | (l) $x_3x_2x_1x_0$ |

- 3

3. (2 points) Write down the complete set of essential prime implicants.

$x_1x_0, x_2'$

- 2

4. (1 point) Write the minimal sum of products expression for  $f$ . Is it unique?

$x_1x_0 + x_2'$ , is unique