

$$x \oplus y = xy' + x'y$$

$$ad(b') + (ad')b' = ad'b + (a'+d)b'$$

$$ad' = x \quad y = b'$$

Problem 1 (20 points)

1. (8 points) Using algebraic identities obtain a simplified sum of product for the following switching expression:

$$E_1(a, b, c, d) = (ad' \oplus b')(c+d) + (a' + bc)'cd'$$

Show each step of your work on a separate line and indicate which identity was used.

$$(ad'b + (a'+d)b')(c+d) + (a'+bc)'cd' \quad \text{expression for XOR (and DeMorgan's)}$$

$$(ad'b + a'b + db')(c+d) + (a \cdot (b+c))cd' \quad \text{DeMorgan's and distributivity}$$

$$(ad'bc + a'b'c + db'c + ad'db + a'b'd + ddb') + (ab' + ac)'cd' \quad \text{distributivity}$$

$$(ad'bc + a'b'c + db'c + a'b'd + db') + (ab'cd' + ac'd') \quad \text{distributivity}$$

$$= ad'bc + a'b'c + db'c + a'b'd + db' + ab'cd' \quad \text{commutativity}$$

$$= db'(c+1) + ad'bc + a'b'c + a'b'd + ab'cd'$$

$$= db'(1+a') + ad'bc + a'b'c + ab'cd'$$

$$= db' + ad'bc + a'b'c + ab'cd' = b'c(a'+ad') + db' + ad'bc$$

$$= b'c(a'+d') + db' + ab'cd' = a'b'c + b'cd' + b'd + ab'cd'$$

$$= b'cd'(a+1) + a'b'c + b'd$$

$$= \underline{b'cd'} + \underline{a'b'c} + b'd$$


$$= b'(cd' + d) + abc$$

$$= b'c + b'd + a'b'c$$

6

| | | | |
|-----|-----------------------------|--------------------------|----------------|
| 1. | $a + b = b + a$ | $ab = ba$ | Commutativity |
| 2. | $a + (bc) = (a + b)(a + c)$ | $a(b + c) = (ab) + (ac)$ | Distributivity |
| 3. | $a + (b + c) = (a + b) + c$ | $a(bc) = (ab)c$ | Associativity |
| | $= a + b + c$ | $= abc$ | |
| 4. | $a + a = a$ | $aa = a$ | Idempotency |
| 5. | $a + a' = 1$ | $aa' = 0$ | Complement |
| 6. | $1 + a = 1$ | $0a = 0$ | |
| 7. | $0 + a = a$ | $1a = a$ | Identity |
| 8. | $(a')' = a$ | | Involution |
| 9. | $a + ab = a$ | $a(a + b) = a$ | Absorption |
| 10. | $a + a'b = a + b$ | $a(a' + b) = ab$ | Simplification |
| 11. | $(a + b)' = a'b'$ | $(ab)' = a' + b'$ | DeMorgan's Law |

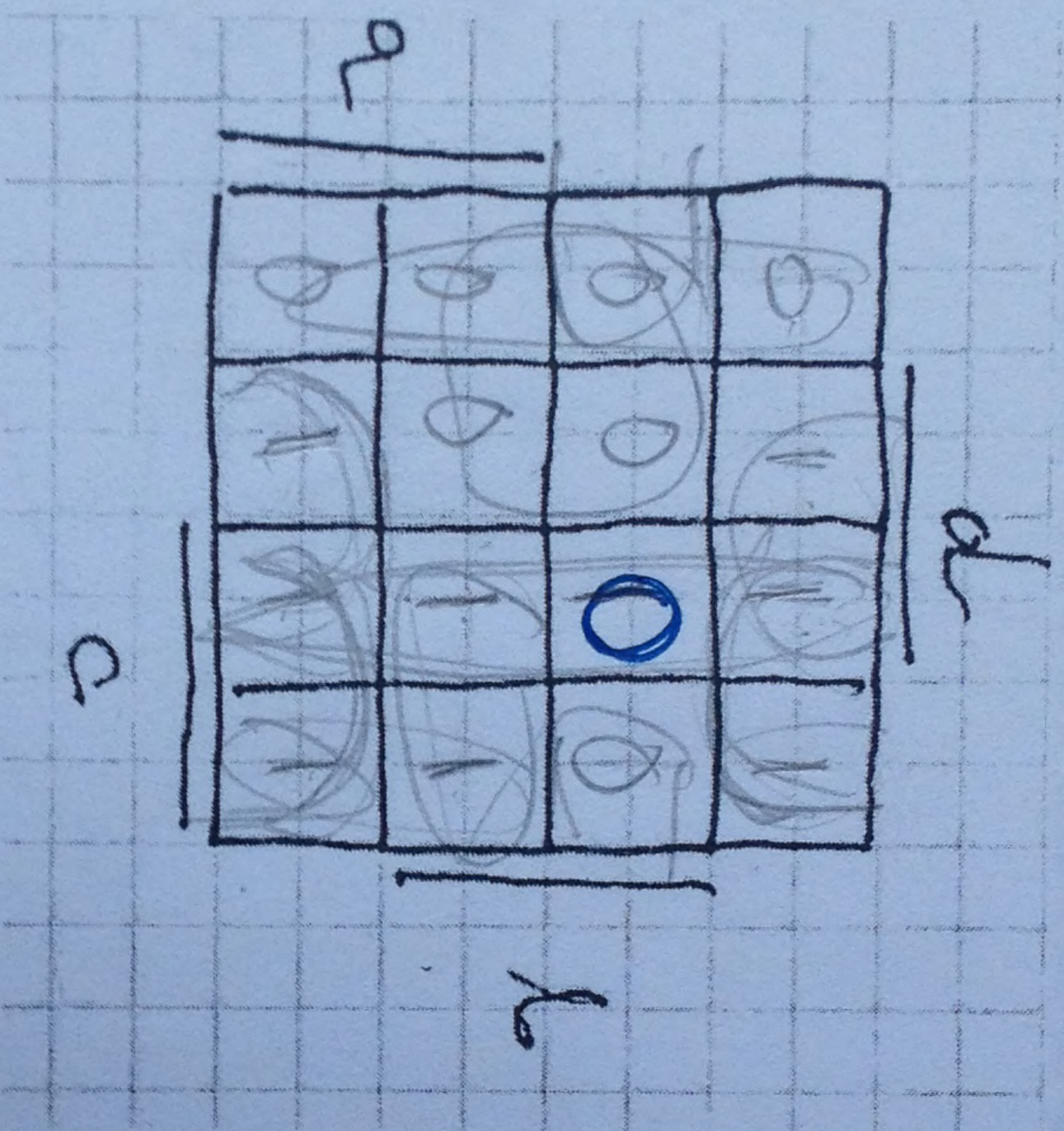2. (4 points) Using a K-map, obtain minimal sum of products and product of sums. Compare the minimal SOP with the SOP in (1).



$$bcd' + a'bc + b'd$$

$$ad'b'c + a'b'c + db'c + a'b'd + db' + a'b'cd'$$


(2)

SOP: $d'c + cb' + db' + bac$

POS: $(c+d)(b'+c)(b'+a+d)$

3. (8 points) Show implementation of min SOP and min POS expressions using NAND and NOR gates. Inverted inputs are not available, and no constant inputs are allowed. Compare the two networks with respect to the number of gates and the total number of inputs. (You are allowed to use NOT gates.)


SOP!

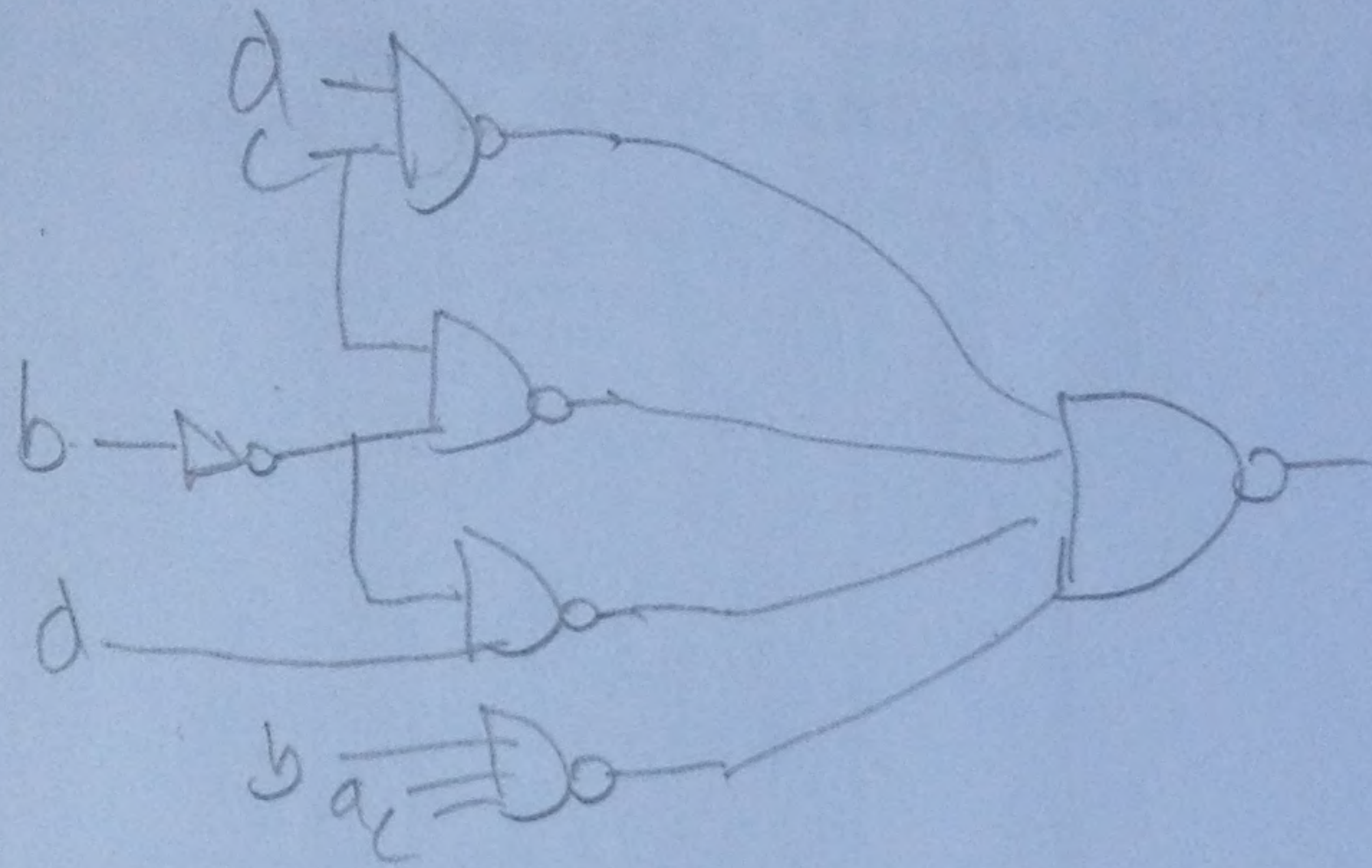

6 gates 13 inputs

4

POS

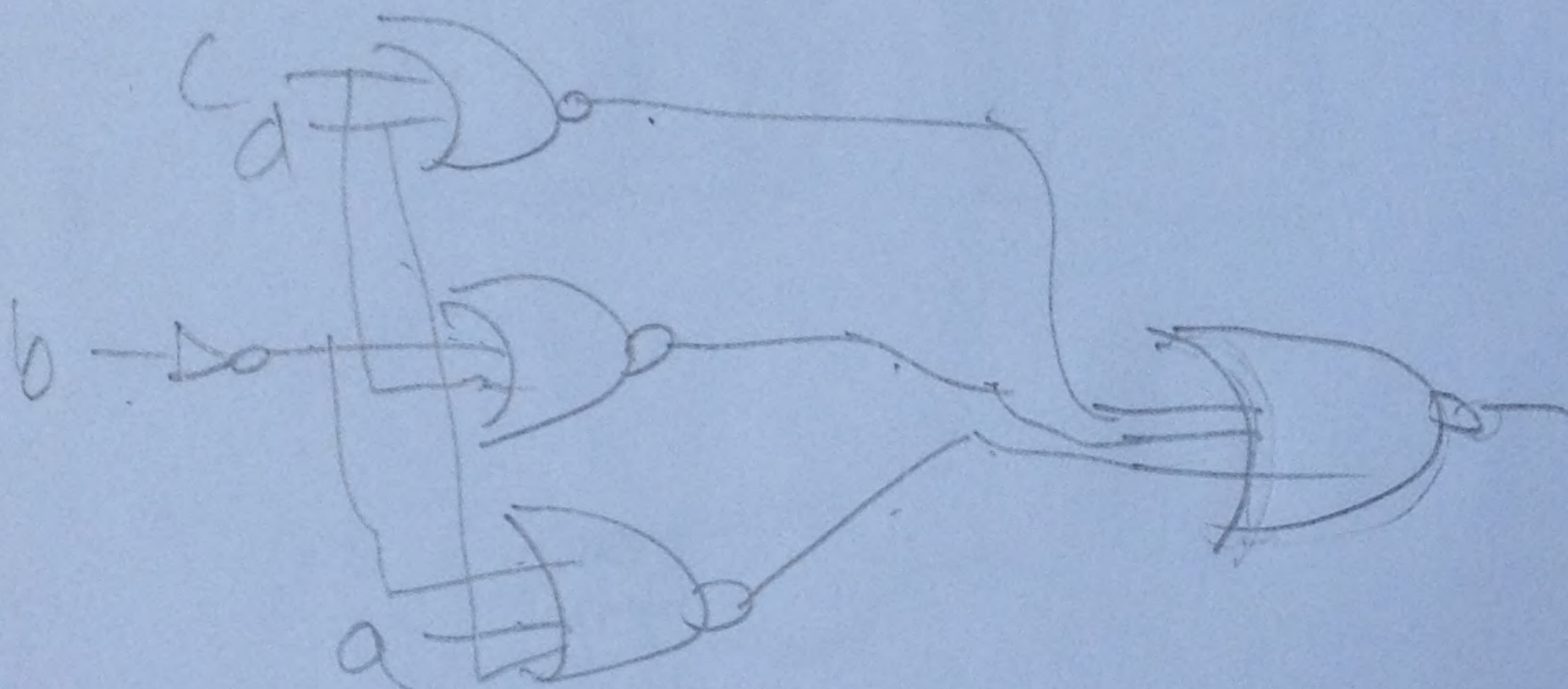

4 gates, 10 inputs


POS is better

Problem 2 (15 points)

17

We want to design a gate network to implement a 4-input multiplexer module MUX. This module has four data inputs $\underline{x} = (x_3, x_2, x_1, x_0)$, two select inputs $\underline{s} = (s_1, s_0)$ and the output y , all in binary code. The output is connected to one of the data inputs determined by the select inputs. Formally, the MUX function is specified as
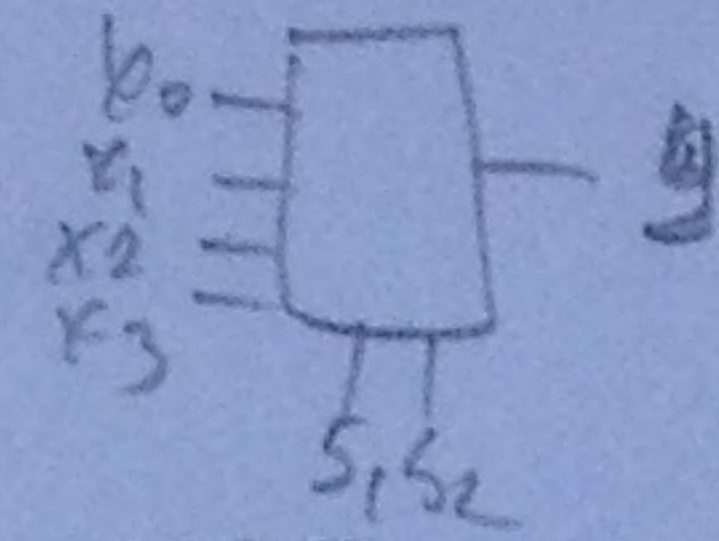
$$y = MUX(\underline{x}, \underline{s}) = x_i \text{ if } s = i, i = 0, 1, 2, 3. \text{ For example, if } s = 2, y = x_2.$$




- Show a sum of products expression for y . *4 transistors*
- Implement MUX module using CMOS NAND gates (with fanin as needed) and NOT gates. How many transistors are used? *2 transistors*

| x_3 | x_2 | x_1 | x_0 | s_1 | s_0 | y |
|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | x_0 |
| 0 | 0 | 0 | 1 | 0 | 0 | x_1 |
| 0 | 0 | 1 | 0 | 0 | 1 | x_2 |
| 0 | 0 | 1 | 1 | 0 | 1 | x_3 |
| 0 | 1 | 0 | 0 | 1 | 0 | x_0 |
| 0 | 1 | 0 | 1 | 1 | 0 | x_1 |
| 0 | 1 | 1 | 0 | 1 | 1 | x_2 |
| 0 | 1 | 1 | 1 | 1 | 1 | x_3 |
| 1 | 0 | 0 | 0 | 0 | 0 | x_0 |
| 1 | 0 | 0 | 1 | 0 | 0 | x_1 |
| 1 | 0 | 1 | 0 | 0 | 1 | x_2 |
| 1 | 0 | 1 | 1 | 0 | 1 | x_3 |
| 1 | 1 | 0 | 0 | 1 | 0 | x_0 |
| 1 | 1 | 0 | 1 | 1 | 0 | x_1 |
| 1 | 1 | 1 | 0 | 1 | 1 | x_2 |
| 1 | 1 | 1 | 1 | 1 | 1 | x_3 |

$s=0(00) \quad y=x_0$
 $s=1(01) \quad y=x_1$
 $s=2(10) \quad y=x_2$
 $s=3(11) \quad y=x_3$

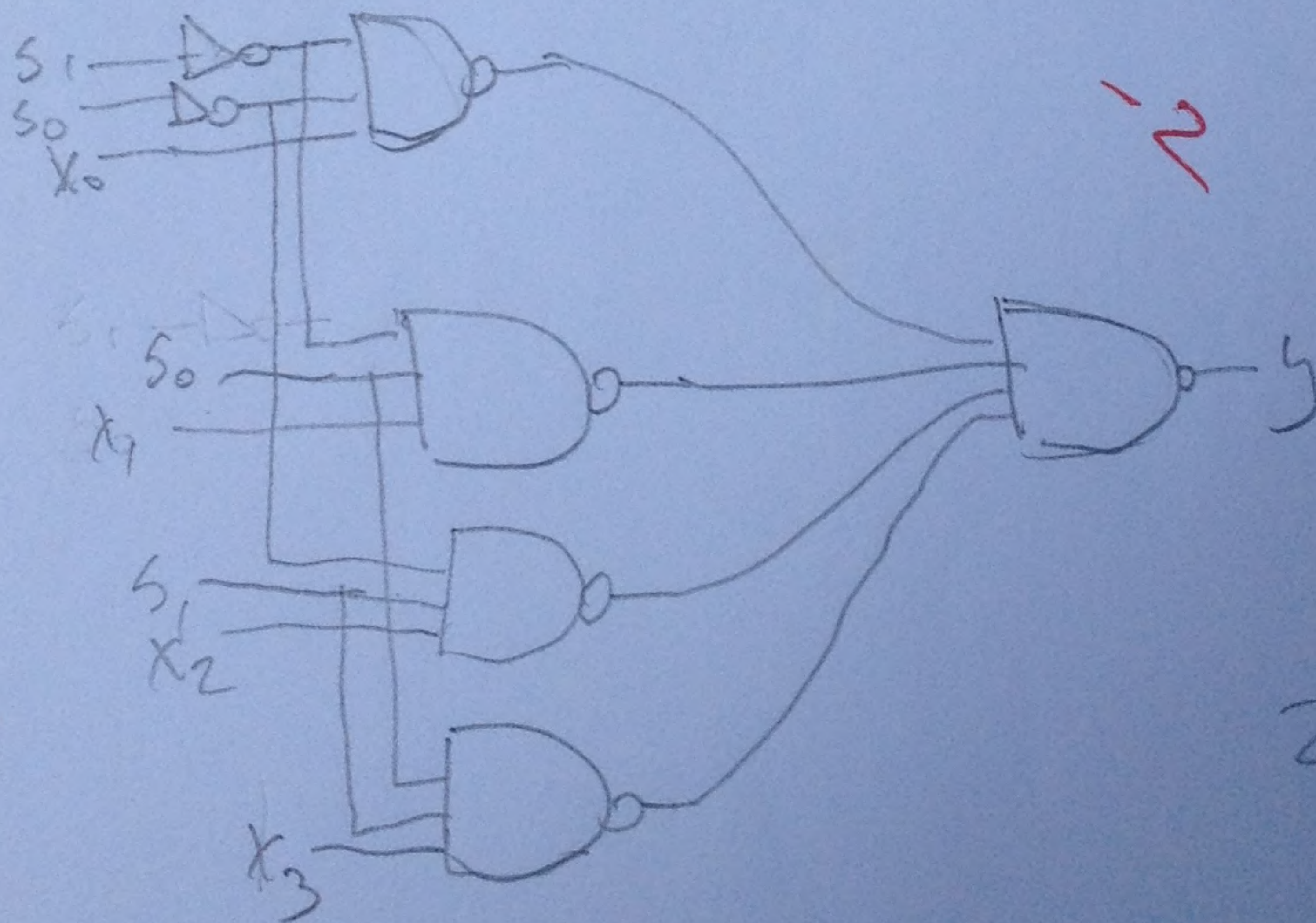POS: $s_1' s_0' x_0 + s_1' s_0 x_1 + s_1 s_0' x_2$
 $+ s_1 s_0 x_3$



~~5~~ 5 NAND gates = 20 transistors

2 3-input NAND gates = 12 transistors

24 transistors needed

Optional problem. (10 extra points) Implement MUX module using CMOS transmission gates TG, NOR and NOT gates. A transmission gate TG_i is controlled by signal C_i :

| C_i | TG_i |
|-------|--------|
| 0 | on |
| 1 | off |

Complete the following table defining the values of control variables C_i and the output y :

| s_1 | s_0 | C_0 | C_1 | C_2 | C_3 | y |
|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 1 | 0 | 0 | 0 | x_0 |
| 0 | 1 | 0 | 1 | 0 | 0 | x_1 |
| 1 | 0 | 0 | 0 | 1 | 0 | x_2 |
| 1 | 1 | 0 | 0 | 0 | 1 | x_3 |

Show switching expressions for C_i 's.

$$C_0 = s_1 \cdot s_0$$

$$C_1 = s_1 \cdot s_0'$$

$$C_2 = s_1 \cdot s_0'$$


$$C_3 = s_1 \cdot s_0$$

4-1

Show the final network. Label all inputs and outputs (external and internal). How many transistors are needed in total?

not
corret TC

+2

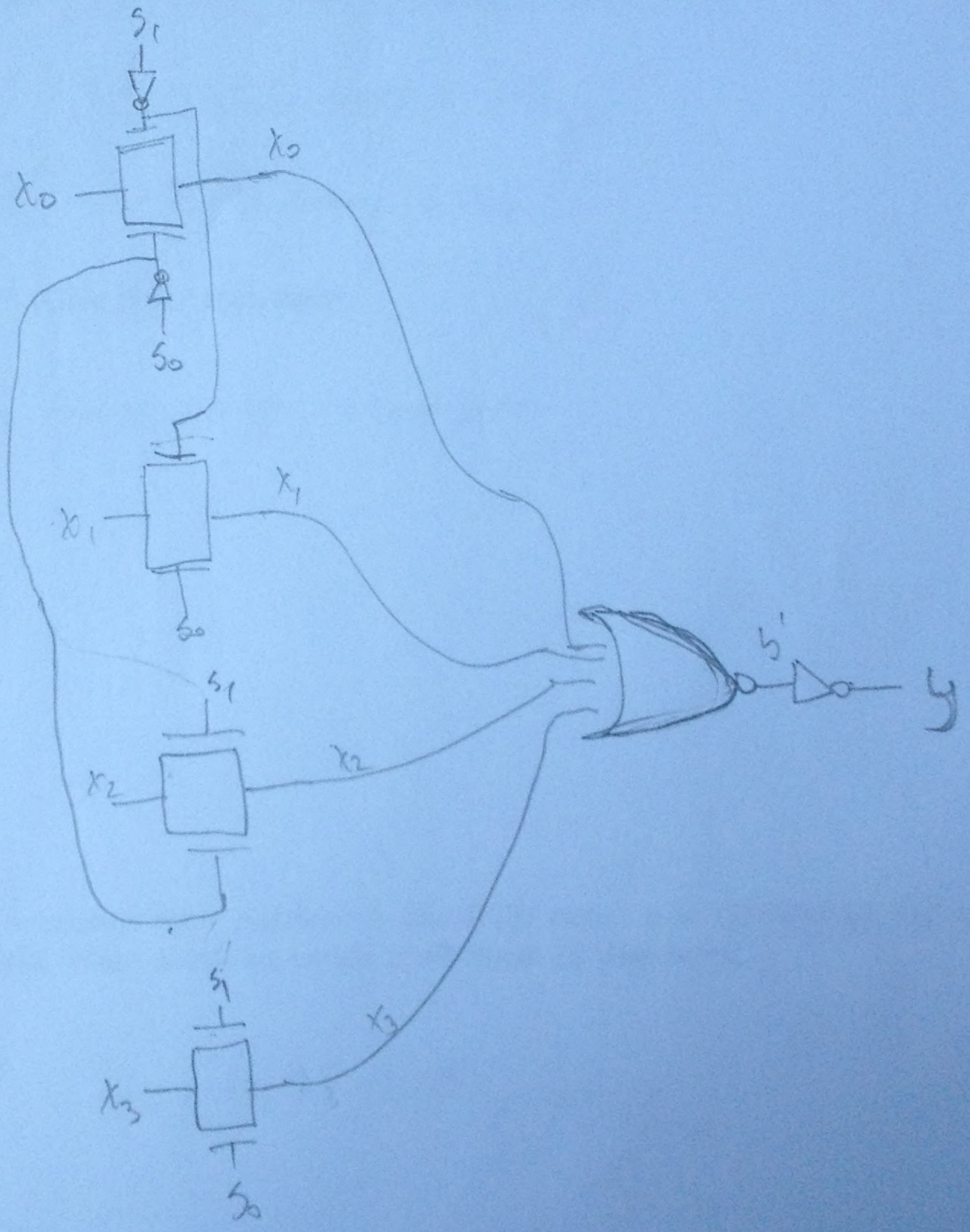

Problem 3 (10 points)

10

1. (5 points) A 8-bit vector represents a set of positive integers $\{0, \dots, N\}$. Which of the following coding alternatives

(a) BCD $10011001 = 99$, range = 100

(b) 2421 code (a decimal code) $11111111 = 99$ range = 100

(c) Excess-3 code (a decimal code) $11001100 = 99$ range = 100

(d) Octal $\begin{matrix} 2 & 1 & 0 & 2 & 1 \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ 111 & 111 & 111 & 111 & 111 \end{matrix} = 377_8 = 255$ range = 256

(e) Binary $11111111 = 2^8 - 1 = 255$, range = 256


provides the largest range? Why? (Give N for each case).



Octal and Binary since range is largest

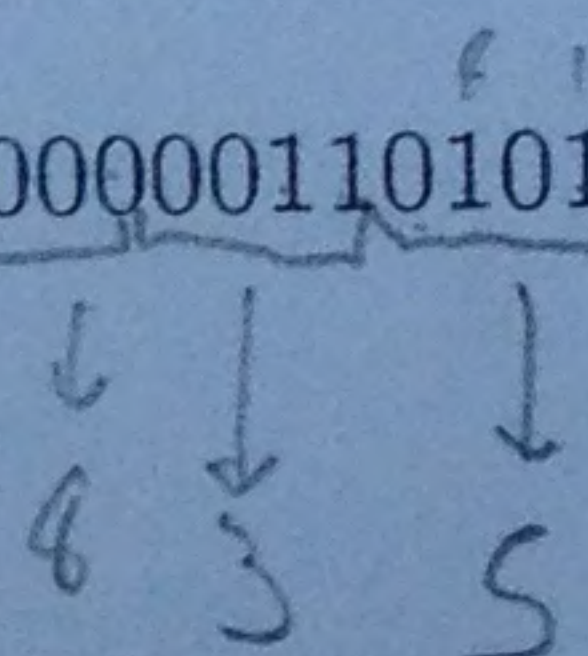2. (5 points)

a and b are 12-bit vectors that represent their numbers in the BCD code. $a = (100000110101)$ and the decimal of their sum $a + b$ is 1,800. What is the bit vector of b ? Show all your work.



$a = 435_{10}$

$b = 1800 - 435_{10} = 965_{10}$

$\begin{matrix} \downarrow & \downarrow & \downarrow \\ 100 & 10110 & 0101 \end{matrix} = b$




Problem 4 (10 points)

10

We would like to verify that the PLA implementation shown here implements the following switching functions:
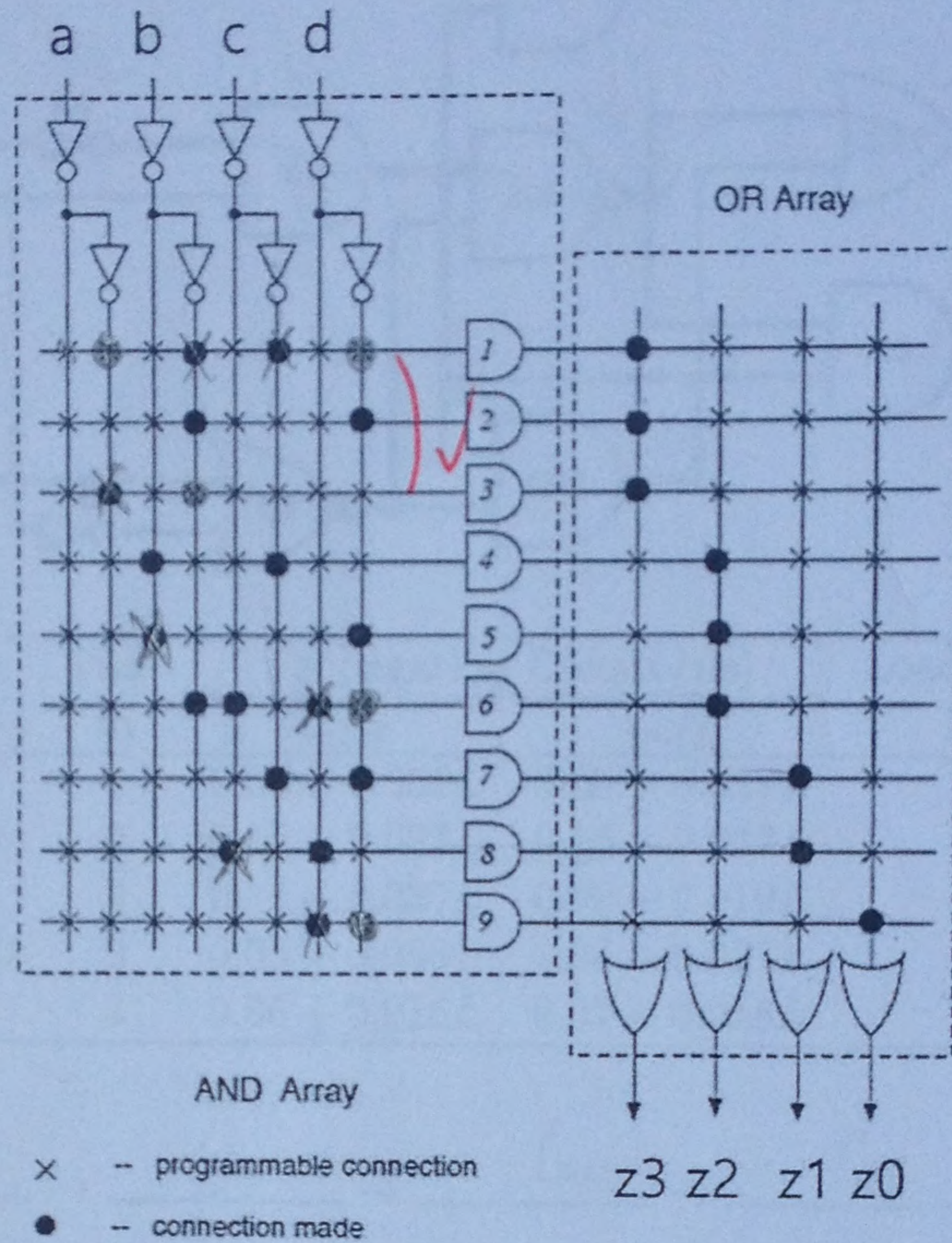
$$\begin{aligned} z_3 &= b + bd + ad \\ z_2 &= b'c + d + bc'd \\ z_1 &= cd + d' \\ z_0 &= d \end{aligned}$$



1. (6 points) Analyze the PLA shown above and show the output expressions.


$$\begin{aligned} z_0 &= d' \\ z_1 &= (d'c') + dc \\ z_2 &= (d'e'b) + (db') + (cb') \\ z_3 &= (a) + (db) + (bc) \end{aligned}$$

2. (4 points) Is the PLA implementation correct? If not, find errors and show the correct implementation (cross out wrong connections and insert correct ones)

Not correct

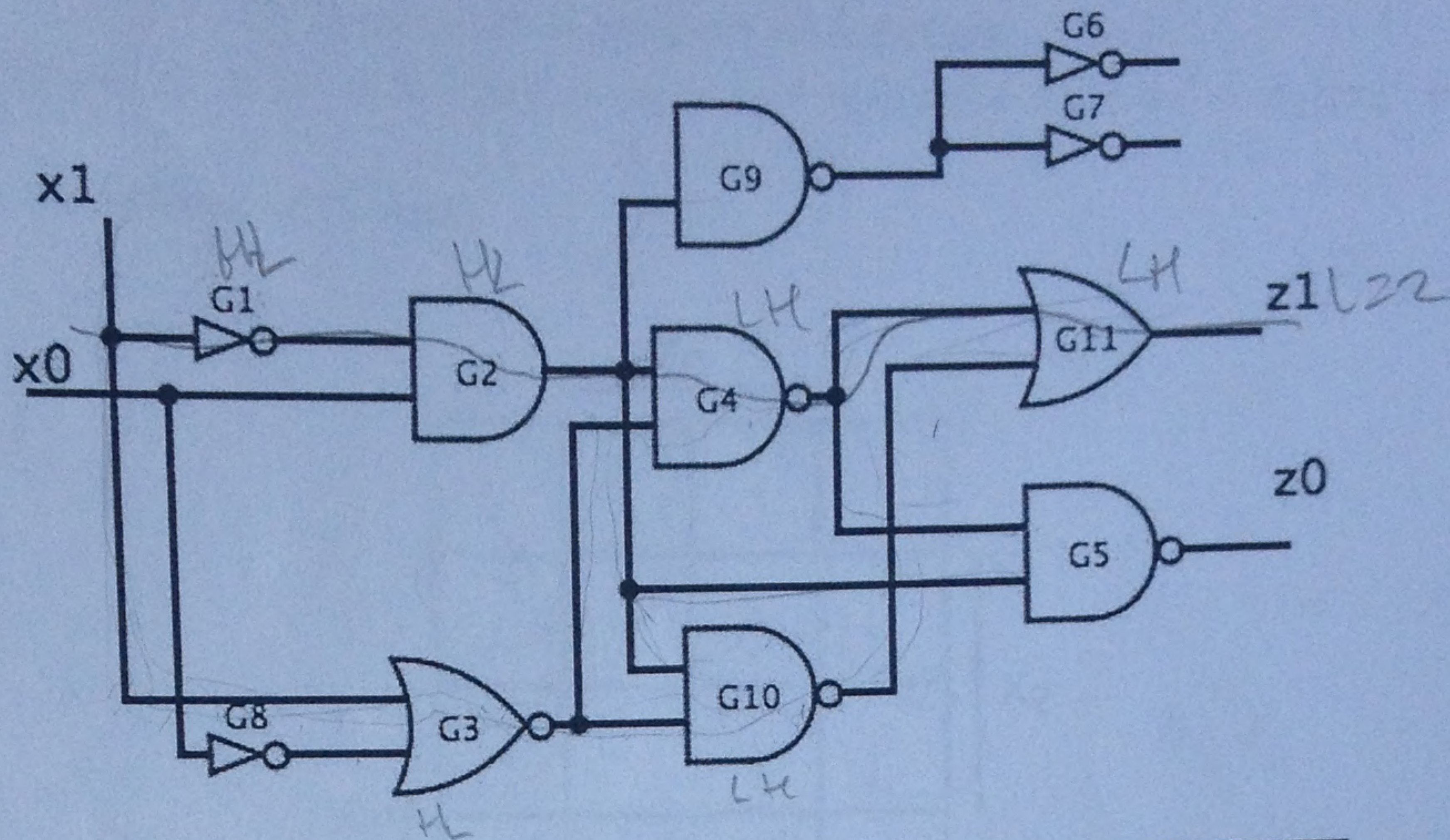Problem 5 (10 points)

Calculate the propagation delay $t_{pLH}(z1)$ when $x1$ changes. Assume that $z1$'s load value is 2. Fill in the blanks below with the appropriate values. You don't need to fill all the blanks.



| Gate Type | Fan-in | Propagation Delays (ns) | | Load Factor I |
|-----------|--------|-------------------------|-----------------|-----------------|
| | | t_{pLH} | t_{pHL} | |
| NOT | 1 | $0.02 + 0.038L$ | $0.05 + 0.017L$ | 1.0 |
| AND | 2 | $0.15 + 0.037L$ | $0.16 + 0.017L$ | 1.0 |
| OR | 2 | $0.12 + 0.037L$ | $0.20 + 0.019L$ | 1.0 |
| NAND | 2 | $0.05 + 0.038L$ | $0.08 + 0.027L$ | 1.0 |
| NOR | 2 | $0.06 + 0.075L$ | $0.07 + 0.016L$ | 1.0 |

Gate name: G1 → G2 → G4 → G11 → _____ → _____

Gate type: NOT-1 → AND-2 → NAND-2 → OR-2 → _____ → _____

LH / HL: HL → HL → LH → LH → _____ → _____

Output load L: 1 → 4 → 2 → 2 → _____ → _____

Prop. Delay: $0.05 + 0.017(1)$ → $0.16 + 0.017(4)$ → $0.05 + 0.038(2)$ → $0.12 + 0.037(2)$ → _____ → _____

Problem 6 (25 points)


For the switching function $f(x_3, x_2, x_1, x_0)$, we are given the information below for the dc-set and zero-set.

$(x_3 + x_2' + x_1 + x_0')(x_3 + x_2' + x_1' + x_0')(x_3' + x_2 + x_1 + x_0)(x_3' + x_2 + x_1' + x_0)(x_3' + x_2 + x_1' + x_0')$
 dc-set = (12, 13)
 zero-set = zero-set of function

Zero set (5, 7, 8, 10, 11)

1. (2 points) Fill out the following K-map.

5

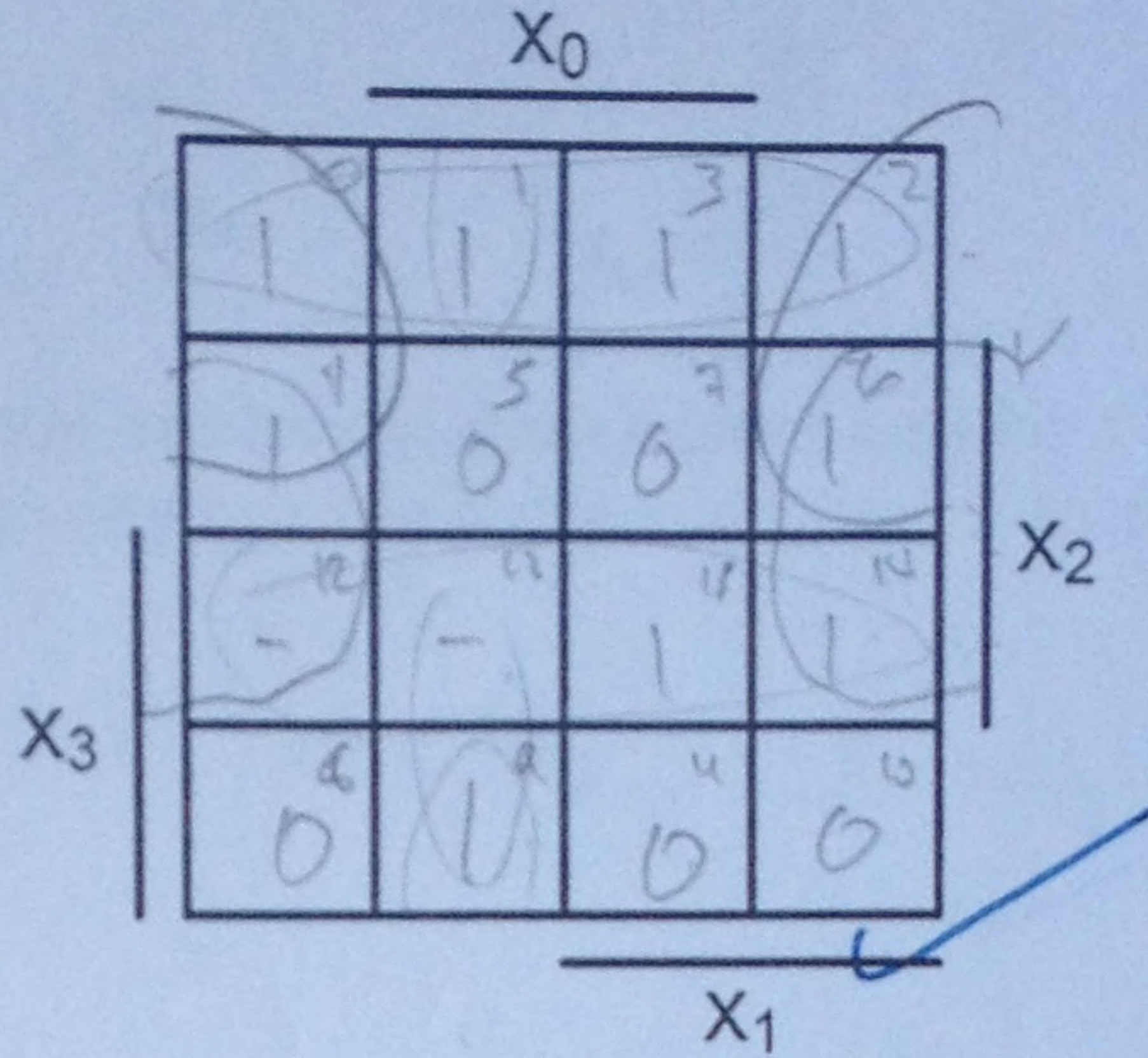

2. (3 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Do not circle implicants that are not prime.

3

- (a) x_3x_1
- (b) $x_3'x_2'$
- (c) $x_3'x_1$

- (d) $x_3'x_0'$
- (e) x_2x_0'
- (f) x_3x_2

- (g) $x_3x_2x_1$
- (h) $x_3'x_2'x_1'$
- (i) $x_2'x_1'x_0$

- (j) $x_3x_1'x_0$
- (k) $x_3'x_2x_1'x_0$
- (l) $x_3'x_2x_1x_0'$

not here

3. (3 points) Write down the complete set of essential prime implicants.

2

$x_3x_2, x_2'x_3', x_2x_0'$

4. (3 points) Write down the minimal sum of products expressions for f . If there are multiple forms of minimal sum of products expressions, you only need to write down one of them.

3

$x_3x_2 + x_2'x_3' + x_2x_0' + x_2'x_1'x_0$

(3 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Do not circle implicants that are not prime.


- (a) $(x_3' + x_2')$
- (d) $(x_3' + x_2 + x_1')$
- (g) $(x_3 + x_1' + x_0)$
- (j) $(x_3 + x_1' + x_0')$
- (b) $(x_3' + x_1')$
- (e) $(x_3' + x_1 + x_0')$
- (h) $(x_2' + x_1 + x_0')$
- (k) $(x_3 + x_2 + x_1 + x_0')$
- (c) $(x_3' + x_2 + x_0)$
- (f) $(x_3 + x_2' + x_0')$
- (i) $(x_3' + x_1 + x_0)$
- (l) $(x_3 + x_2' + x_1' + x_0)$

6. (3 points) Write down the complete set of essential prime implicants.

① $(x_2' + x_3 + x_0')$ $(x_1' + x_3 + x_2)$ $(x_3' + x_1 + x_0)$
 X x_1' X

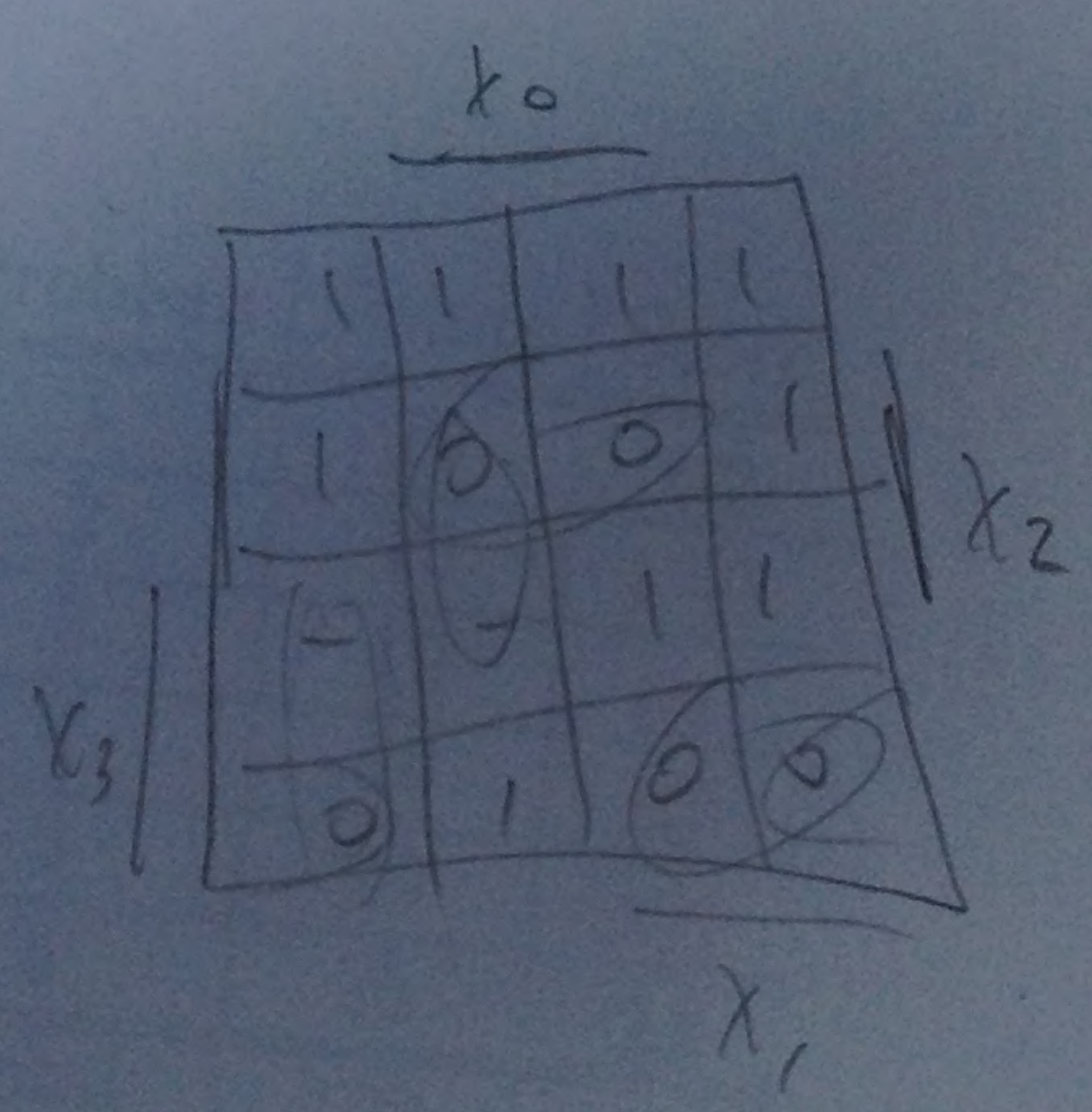7. (3 points) Write down the minimal product of sums expressions for f . If there are multiple forms of minimal product of sums expressions, you only need to write down one of them.

② $(x_2' + x_3 + x_0')$ $(x_1' + x_3 + x_2)$ $(x_3' + x_1 + x_0)$



- PIs
- $(x_0' + x_2 + x_3)$ ✓
 - $(x_0' + x_1 + x_2')$ ✓
 - $(x_3' + x_0 + x_1)$ ✓
 - $(x_3' + x_2 + x_0)$ ✓
 - $(x_1' + x_2 + x_3)$