

[CS M51A W13] SOLUTION TO QUIZ 1B

Date: 01/25/13

TA: Gabriel Pan (pansh@cs.ucla.edu)

Quiz Problems (50 points total)

Problem 1 (10 points)

The XNOR operation is defined as $x \odot y = xy + x'y'$ and the XOR operation is defined as $x \oplus y = x'y + xy'$. Show that $(x \odot y)' = x \oplus y$ using the postulates and theorems of Boolean algebra. **Do not use a table.**

Solution

$$\begin{aligned}(x \odot y)' &= (xy + x'y')' \\ &= (xy)'(x'y')' \\ &= (x' + y')(x + y) \\ &= (xx' + x'y + xy' + yy') \\ &= x'y + xy' \\ &= x \oplus y\end{aligned}$$

Problem 2 (25 points)

We are given the following switching function.

$$E_1(a, b, c, d) = bcd + a'b'd + bc + ac'd' + a'b'c' + ac'd + a'bcd'$$

1. (10 points) Simplify expression E_1 using the postulates of Boolean algebra.

Solution

$$\begin{aligned}E_1(a, b, c, d) &= bcd + a'b'd + bc + ac'd' + a'b'c' + ac'd + a'bcd' \\ &= bc(d + 1 + a'd') + a'b'd + ac'(d' + d) + a'b'c' \\ &= bc + a'b'd + ac' + a'b'c' \\ &= bc + a'b'd + c'(a + a'b') \\ &= bc + a'b'd + c'(a + b') \\ &= bc + a'b'd + ac' + b'c'\end{aligned}$$

2. (10 points) E_2 is given as the function below.

$$E_2(a, b, c, d) = E_1 + a'cd + ab$$

Given these two expressions, fill in the table below.

Solution

a	b	c	d	E_1	E_2
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1


3. (5 points) Write the switching function in the form specified below.

Solution From the table, we can write

$$E_1(x, y, z, w) = \sum m(0, 1, 3, 6, 7, 8, 9, 12, 13, 14, 15)$$

$$E_2(x, y, z, w) = \prod M(2, 4, 5, 10, 11)$$

Problem 3 (15 points)

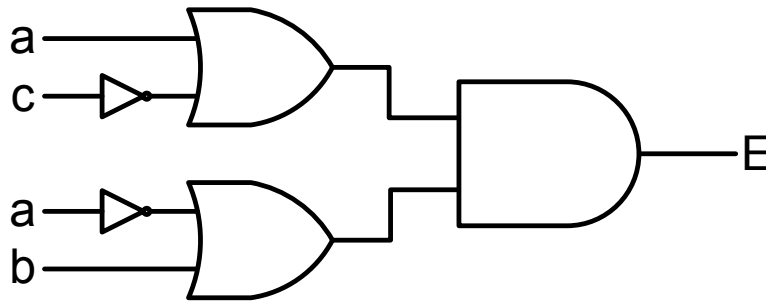

Given the above circuit:

1. (5 points) Obtain the most simplified sum of products form for $E(a, b, c)$.

Solution We first obtain the expression from the gate network, which is $E(a, b, c) = (a + c')(a' + b)$.

From here we can derive:

$$\begin{aligned} E(a, b, c) &= (a + c')(a' + b) \\ &= aa' + ab + a'c' + bc' \\ &= ab + a'c' + bc' \end{aligned}$$

2. (10 points) Obtain the product of maxterms form for $E(a, b, c)$.

Solution We first obtain the expression from the gate network, which is $E(a, b, c) = (a + c')(a' + b)$.

From here we can derive:

$$\begin{aligned} E(a, b, c) &= (a + c')(a' + b) \\ &= (a + c' + bb')(a' + b + cc') \\ &= (a + b + c')(a + b' + c')(a' + b + c)(a' + b + c') \\ &= M_1 \cdot M_3 \cdot M_4 \cdot M_5 \\ &= \prod M(1, 3, 4, 5) \end{aligned}$$