# [CS M51A W13] Solution to Quiz 3B

Date: 03/01/13

TA: Gabriel Pan (pansh@cs.ucla.edu)

## Quiz Problems (50 points total)

### Problem 1 (15 points)

Minimize the number of states of the system that correspond to the table shown below. Show the final minimized table. The input is x and the output is z.

	Inp	out
PS	x = 0	x = 1
A	E, 0	C, 1
B	A, 1	J, 0
C	D, 0	F, 0
D	J, 0	K, 1
E	A, 0	E, 1
F	A, 0	G, 1
G	J, 0	A, 0
H	A, 1	D, 0
Ι	K, 0	B, 1
J	D, 0	K, 1
K	I,0	B, 1
	NS	S,z

**Solution** Looking at the output values, we can write  $P_1 = (A, D, E, F, I, J, K)$  (output 0/1), (C, G) (output 0/0), (B, H) (output 1/0)

From here we move to:

			gr	oup	1			g	2	g	3
		D	$\mathbf{E}$	$\mathbf{F}$	Ι	J	Κ	C			Η
0	1	1	1	1	1	1	1	1	1 1	1	1
1	2	1	1	2	3	1	3	1	1	1	1
$P_2 = (A, F), (D, E, J), (I, K), (C, G), (B, H)$											
	ı		I			I	~			1	_
	g	1		g2		e e	<u>3</u>	g	4	g	5
									4 G		Η
0											Η
0 1									$\frac{4}{G}$		Η

	g1	g2	g	3	g4	g	5		6	g	7
	А	$\mathbf{F}$	D	J	Ε	Ι	Κ	$\mathbf{C}$	G	В	Η
0			3	3						1	
1			5	5		7	7	2	1	3	3
$P_4 =$	=(A)	), (F)	), (D	,J)	, (E),	(I,	K),	(C),	(G),	(B, I)	H)
	g1	g2	g	3	g4	e e	<u>5</u>	g6	g7	1	g8
	Α	$\mathbf{F}$	D	J	Е	Ι	Κ	$\mathbf{C}$	G	В	Η
0			3	3		5	5			1	1
1			5	5		8	8			3	3
•		g2 F	3	3		5				B 1	H 1

Now  $P_5 = P_4$  and no more reductions are possible. The minimal table is:

PS	x = 0	x = 1
G1	G4, 0	G6, 1
G2	G1, 0	G7, 1
G3	G3, 0	G5, 1
G4	G1, 0	G4, 1
G5	G5, 0	G8, 1
G6	G3, 0	G2, 0
G7	G3, 0	G1, 0
G8	G1, 1	G3, 0
	NS	S, z

#### Problem 2 (20 points)

Design a binary string detector using the state vector approach to cover all possible states, and deriving the minimum number of states afterwards. The detector takes a stream of binary bits as input, one bit at each clock. The output is 1 when it detects a string of 011, 100 or 110. The input signal is x(t), and the output signal is z(t).

1. (5 points) Fill in the empty slots in the state transition table.

#### Solution

PS	x = 0	x = 1
$S_{init}$	$S_0, 0$	$S_1, 0$
$S_0$	$S_{00}, 0$	$S_{01}, 0$
$S_1$	$S_{10}, 0$	$S_{11}, 0$
$S_{00}$	$S_{00}, 0$	$S_{01}, 0$
$S_{01}$	$S_{10}, 0$	$S_{11}, 1$
$S_{10}$	$S_{00}, 1$	$S_{01}, 0$
$S_{11}$	$S_{10}, 1$	$S_{11}, 0$
	NS	$\delta, z$

2. (15 points) Minimize the number of states in the transition table, and show the final minimized table. Use G1 to G7 for the minimized group names.

**Solution** Looking at the output of the previous table, we first get  $P_1$  as shown:

 $P_1 = (S_{init}, S_0, S_1, S_{00})$  (output 0/0),  $(S_{01})$  (output 0/1), and  $(S_{10}, S_{11})$  (output is 1/0).

		grou	р1	g2	groi	1р З	
	$S_{init}$	$S_0$	$S_1$	$S_{00}$	$S_{01}$	$S_{10}$	$S_{11}$
0	1	1	3	1		1	3
1	1	2	3	2		2	3

$P_2 = (S_{init}), (S_1), (S_0, S_{00}), (S_{01}), (S_{10}), (S_{$
--

	g1	g2	6	g3	g4	$g_{S}$	g6 C
	$S_{init}$	$S_1$	$S_0$	$S_{00}$	$S_{01}$	$S_{10}$	$S_{11}$
0			3	3			
1			4	4			

We can see that  $P_3$  will be the same as  $P_2$  and we stop here. By naming each group, we can write the following table.


PS	x = 0	x = 1
G1	G3, 0	G2, 0
G2	G5, 0	G6, 0
G3	G3, 0	G4, 0
G4	G5, 0	G6, 1
G5	G3, 1	G4, 0
G6	G5, 1	G6, 0
	NS	$\delta, z$

#### Problem 3 (15 points)

A sequential system has an input set  $I = \{a, b, c, d\}$  and an output set  $O = \{0, 1\}$ . The system tracks the number of occurrences of the string *cab* in x(0,t). It outputs 1 if the value is an odd number and 0 otherwise. Show the state diagram of the system. Use the minimum-number-of-states approach. (*Hint: You may need multiple instances of the same string detector.*)

For each state, clearly show the transition path for all variables in the input set I and the output values. Clearly identify the initial state.

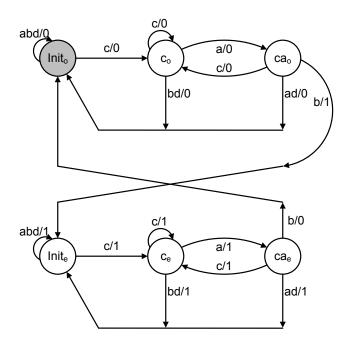**Solution** We need two separate instances of the string detector for *cab*, one for the even case and one for the odd case. Every time we encounter the string *cab*, we jump from one detector to the other as shown. The initial state is shaded in gray.



For a Moore machine, all states for the odd case output 1, all states for the even case output 0.