

# [CS M51A WINTER 12] SOLUTION TO QUIZ 4A

Date: 03/09/12

TAs: Neil Conos (conos@cs.ucla.edu), Gabriel Pan (pansh@cs.ucla.edu)

## Quiz Problems (50 points total)

### Problem 1 (10 points)

We wish to create an SR flip-flop using a T flip-flop. The transition table for the SR flip-flop is:

$PS = Q(t)$	$S(t)R(t)$			
	00	01	10	11
0	0	0	1	-
1	1	0	1	-
$NS = Q(t+1)$				

1. (3 points) Fill in the table below.

**Solution** From the given transition table, we can write:

$PS = Q(t)$	$S(t)R(t)$				$S(t)R(t)$			
	00	01	10	11	00	01	10	11
0	0	0	1	-	0	0	1	-
1	1	0	1	-	0	1	0	-
$NS = Q(t+1)$					$T$			


2. (7 points) Using the table, obtain the expression for  $T$  and draw the final circuit.

**Solution** From the completed table, we can get the following K-map:

		R			
		-----			
Q		0	0	-	1
		0	1	-	0
		-----			
				S	


and from this we get  $T = QR + Q'S$ .

The final circuit looks like:

 

 **Problem 2 (20 points)**

We would like to analyze the following sequential network. It has two input bits  $x_1$  and  $x_0$ , with a single output bit  $z$ .



- (12 points)** Write the minimal sum of product expressions for  $z$ ,  $y_1(t+1)$  and  $y_0(t+1)$ . Assume that a literal without a time label is equal to its value at time  $t$ , i. e.  $y_0$  is short for  $y_0(t)$ . To obtain the expressions for  $y_1(t+1)$  and  $y_0(t+1)$ , use the JK flip-flop characteristic expression shown here:

$$Q(t+1) = Q(t)K'(t) + Q'(t)J(t)$$

**Solution** From the given circuit, we can directly write the following:

$$\begin{aligned} z(t) &= y_1'y_0' \\ J_1(t) &= y_0'x_0' \\ K_1(t) &= y_0x_1 \\ J_0(t) &= y_1x_0' + y_1'x_1x_0 \\ K_0(t) &= y_1'x_0' \end{aligned}$$

Using the JK characteristic expression, we can derive:

$$\begin{aligned}
 y_1(t+1) &= y_1 K_1' + y_1' J_1 \\
 &= y_1 (y_0 x_1)' + y_1' (y_0' x_0') \\
 &= y_1 (y_0' + x_1') + y_1' y_0' x_0' \\
 &= y_1 y_0' + y_1 x_1' + y_1' y_0' x_0' \\
 &= y_0' (y_1 + y_1' x_0') + y_1 x_1' \\
 &= y_0' (y_1 + x_0') + y_1 x_1' \\
 &= y_1 y_0' + y_0' x_0' + y_1 x_1' \\
 y_0(t+1) &= y_0 K_0' + y_0' J_0 \\
 &= y_0 (y_1' x_0')' + y_0' (y_1 x_0' + y_1' x_1 x_0) \\
 &= y_0 (y_1 + x_0) + (y_1 y_0' x_0' + y_1' y_0' x_1 x_0) \\
 &= (y_1 y_0 + y_0 x_0) + (y_1 y_0' x_0' + y_1' y_0' x_1 x_0) \\
 &= y_1 (y_0 + y_0' x_0') + x_0 (y_0 + y_1' y_0' x_1) \\
 &= y_1 (y_0 + x_0') + x_0 (y_0 + y_1' x_1) \\
 &= y_1 y_0 + y_1 x_0' + y_0 x_0 + y_1' x_1 x_0 \\
 &= y_1 y_0 (x_0 + x_0') + y_1 x_0' + y_0 x_0 + y_1' x_1 x_0 \\
 &= y_1 y_0 x_0 + y_1 y_0 x_0' + y_1 x_0' + y_0 x_0 + y_1' x_1 x_0 \\
 &= (y_1 y_0 x_0 + y_0 x_0) + (y_1 y_0 x_0' + y_1 x_0') + y_1' x_1 x_0 \\
 &= y_0 x_0 + y_1 x_0' + y_1' x_1 x_0
 \end{aligned}$$

2. (8 points) Using the expressions, fill in the table below.

**Solution** From the expressions we can fill in the following:

<i>PS</i>	Input $x_1(t)x_0(t)$				Output
$y_1(t)y_0(t)$	00	01	10	11	$z$
00	10	00	10	01	1
01	00	01	00	01	0
10	11	10	11	10	0
11	11	11	01	01	0
	$y_1(t+1)y_0(t+1)$				
	<i>NS</i>				

The easiest approach to this is to find which locations each sum term turns to 1 and fill those with 1s, then any remaining slots are 0s. For example, from  $y_1 y_0'$  we can deduce that the whole row 10 is 1 for  $y_1(t+1)$ .

### Problem 3 (20 points)

1. (10 points) Given the following timing parameters, calculate the setup time, hold time and propagation delay of the sequential network given in problem 2. Assume that both inverted inputs and uninverted inputs are provided and there are no NOT gates present.

JK flip-flop characteristics:  $t_{su}(\text{cell}) = 0.8 \text{ ns}$ ,  $t_h(\text{cell}) = 2.7 \text{ ns}$ ,  $t_p(\text{cell}) = 1.8 \text{ ns}$

Gate characteristics:  $t_p(\text{AND2}) = t_p(\text{OR2}) = 3.5 \text{ ns}$ ,  $t_p(\text{AND3}) = 4.0 \text{ ns}$

**Solution** For  $d1^x$  and  $d1^y$ , in both cases the worst case path is through the 3-input AND gate.

$$d1^x = d1^y = t_p(\text{AND3}) + t_p(\text{OR2}) = 4.0 + 3.5 = 7.5(\text{ns})$$

Network setup time:

$$\begin{aligned}t_{su}(\text{net}) &= d1^x + t_{su}(\text{cell}) \\ &= 7.5 + 0.8 \\ &= 8.3 \text{ (ns)}\end{aligned}$$

Network hold time  $t_h(\text{net}) = t_h(\text{cell}) = 2.7 \text{ (ns)}$

Network propagation delay

$$\begin{aligned}t_p(\text{net}) &= t_p(\text{cell}) + d2 \\ &= t_p(\text{cell}) + t_p(\text{AND2}) \\ &= 1.8 + 3.5 = 5.3 \text{ (ns)}\end{aligned}$$

2. **(10 points)** If  $t_{in} = 5.5 \text{ ns}$  and  $t_{out} = 4.5 \text{ ns}$ , calculate the minimum clock period for this system.

**Solution** We evaluate the time periods required in relation to each possible signal path.

$$\begin{aligned}T_x &= t_{in} + d1^x + t_{su}(\text{cell}) = 5.5 + 7.5 + 0.8 = 13.8 \text{ (ns)} \\ T_y &= t_p(\text{cell}) + d1^y + t_{su}(\text{cell}) = 1.8 + 7.5 + 0.8 = 10.1 \text{ (ns)} \\ T_z &= t_p(\text{cell}) + d2 + t_{out} = 1.8 + 3.5 + 4.5 = 9.8 \text{ (ns)}\end{aligned}$$

Therefore the minimum clock period is:

$$\begin{aligned}T_{min} &= \max \{T_x, T_y, T_z\} \\ &= 13.8 \text{ (ns)}\end{aligned}$$