

Problem No. 1 (10 points)

5pts Part (a) An electric garage door opener *iLock* uses a small radio transmitter that sends a 5-bit sequence to a receiver inside the garage to open the door, and each receiver is supposed to respond to a different sequence. Suppose you live on a street with 40 houses, each using the same model of the opener.

2.5pts (a.1) How many houses must share a sequence with some other houses on the street?

Answer: 8 houses.

Show your work below for full credit:

$$2^5 = 32$$

$$40 - 32 = 8$$

2.5pts (a.2) Suppose a burglar Digi Hak wants to break into one specific garage using this type of opener. If he has a transmitter which can send different 5-bit sequences, at ~~least~~ ^{most} how many times he needs to try before he breaks into any particular garage?

Answer: 31

Show your work below for full credit:

$$2^5 - 1$$

5pts Part (b) Length can be measured by one 3-digit weighted mixed-radix number system (yards, feet, inches). The relationships between weights of each digit of this number system are: 1 yard = 3 feet, 1 foot = 12 inches. Assume that radix for the yard's digit is ten.

2.5pts (b.1) What is the largest number of inches that this number system can represent?

Answer: 359 inches.

2.5pts (b.2) How many inches are represented by the digit vector $X = (8, 2, 9)$?

Answer: 321 inches.

Show your work below for full credit:

$$(b.1) X_{max} = (9, 2, 11)$$

$$\Rightarrow X_{max} = 9 \times 3^2 + 2 \times 12 + 11 = \underline{359}$$

$$\text{OR: } X_{max} = 10 \times 3 \times 12 - 1 = \underline{359}$$

$$(b.2) X = 8 \times 3^2 + 2 \times 12 + 9 = 321$$

Problem No. 2 (10 points)

A high-tech startup *HotCom, Inc.* is operated by CEO *A*, CFO *B*, and two members of the Board of Directors, *C* and *D*.

To make a decision, *A* needs support from at least another board member, while *B* needs support from at least two other board members.

Part (a) *6 pts.*

Fill in the truth table of function *F* below. *F* = 1 if and only if a decision has been approved.

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Part (b) *4 pts.*

(b.1) Write the *minterm* expression for $F(A, B, C, D)$ in compact form:

2 pts.

$$F(A, B, C, D) = \sum m \{ \underline{7, 9, 10, 11, 12, 13, 14, 15} \}$$

(b.2) The switching expression for maxterm M_8 is:

2 pts.

$$M_8 = \underline{A' + B + C + D}$$

Problem No. 3 (10 points)

Your high school buddy BB Fred is interviewed for an internship position at a startup *Kookle Electronics*. One of his interview questions is the tabular minimization using the Quine-McCluskey algorithm for the following 4-input switching function:

$$f(a, b, c, d) = \sum m(4, 5, 6, 8, 9, 10, 13) + \sum d.c.(0, 7, 15)$$

BB Fred has completed the first step and the Prime Implicant Chart is shown below. You have to help him identify the essential prime implicants and then write the minimal AND-OR (sum-of-product) expression for $f(a, b, c, d)$.

Prime Implicant Chart

Prime Implicants	Minterms						
	4	5	6	8	9	10	13
0 - 00	X						
- 000				X			
100 -				X	X		
10 - 0				X		X	
1 - 01					X		X
01 - -	X	X	X				
- 1 - 1		X					X

Note: In the original image, the X's at (10, 8), (10, 10), (01, 6), and (01, 13) are circled. The prime implicants 10-0 and 01-- are labeled as essential (E).

4 pts Part (a) The essential prime-implicants in switching expressions are:

$ab'd', a'b$


6 pts Part (b) The minimal switching expression in AND-OR form is:

$f(a, b, c, d) =$ $ab'd' + a'b + ac'd$

Show all your work on the *prime implicant chart* above for full credit.

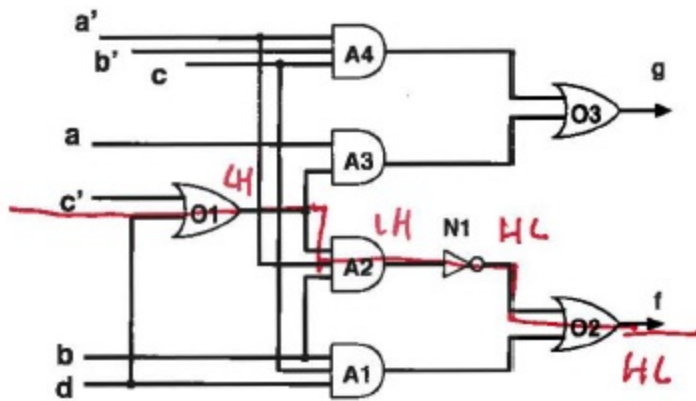Problem No. 4 (15 points)

Given the gate network below, answer the following questions:



3 pts. Part (a) Assuming that negated variables are available and that all gates have the same delays, identify the *critical path* of the network by listing its gates along the path, starting at the inputs:

O1 → A2 → N1 → O2

3 pts. Part (b) Assuming that load factors of all gates equal to 1 and that both outputs *f* and *g* have the output load value *L*, list the output load value of every gate in the *critical path* (e.g., A1: 1):

O1: 2 ; A2: 1 ; N1: 1 ; O2: L

4 pts. Part (c) Write the expression of the longest network propagation delay T_{pHL} in terms of delays of each gate (You do not need to compute the final result but the transition direction at each gate has to be indicated):


$T_{pHL} = T_{pHL}(O2) + T_{pHL}(N1) + T_{pLH}(A2) + T_{pLH}(O1)$

5 pts. Part (d) Assuming that negated variables are available, find the switching expression of the output *f* in two-level AND-OR (sum-of-product) form. It does not have to be minimal. Show your work below for full credit.

$f(a, b, c, d) = a + b' + cd' + bcd$, or $a + cd + cd' + b'$, or $a + b' + c$


Your work for Part (d):

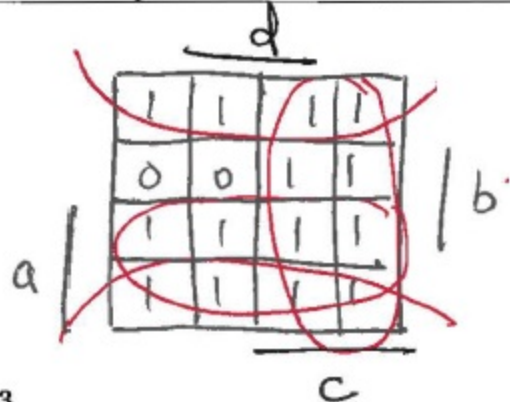all okay!
$$\begin{aligned} f &= (a'b(c'+d))' + bcd \\ &= a + b' + (c'+d)' + bcd \\ &= a + b' + cd' + bcd \\ &= a + cd + cd' + b' \\ &= a + c + b' \end{aligned}$$



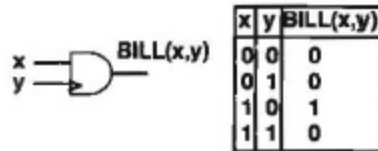Problem No. 5 (15 points) *Optional as bonus.*

Armed with a solid A in Spring 2014 CS M51A/EE M16 class, Elsa has easily landed a job as a digital system design engineer in *SuperLogic* after graduation. She is motivated to revolutionize the logic design and has invented a new type of logic gate, called *BILL* gates. Its symbol and truth table are given below.



8 pt

Part(a) Is the *BILL* gate a universal set?

Your answer: Yes.

Show all your work below for full credit.

① From the truth table:

$$BILL(x,y) = xy'$$

$$\therefore BILL(1,y) = y' \rightarrow \text{NOT gate}$$

② $BILL(x,y') = xy$

$$\therefore BILL(x, BILL(1,y)) = xy \rightarrow \text{AND gate}$$

\therefore Bill gates can implement {NOT, AND}, which is a universal set.

\therefore Bill gates are universal set.

(Continue on the next page)


(Continue from Problem No. 5)

^{7pts.} Part (b) If the answer in Part (a) is *yes*, draw a network that implements the sum of a 1-bit full adder using only *BILL* gates; If the answer is *no*, draw a network that implements the sum of a 1-bit full adder using *BILL* gates and any other types of gates as needed.


Show all your work below for full credit.

$$Sum = x \oplus y \oplus z.$$

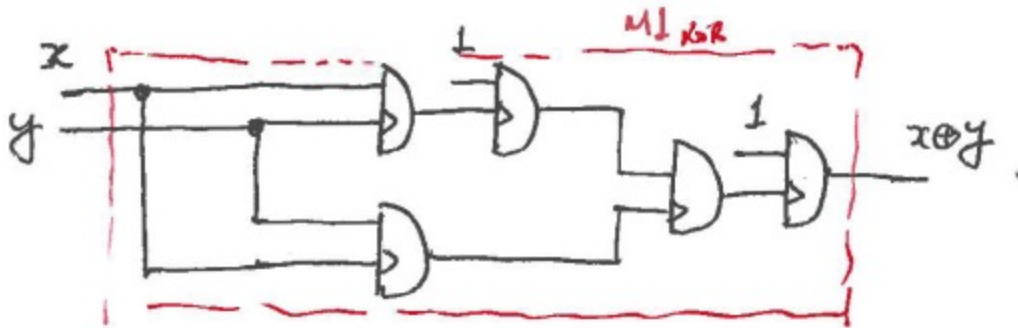an \oplus XOR gate is implemented with BILL gates as follows (ML)




\therefore Sum can be implemented as.

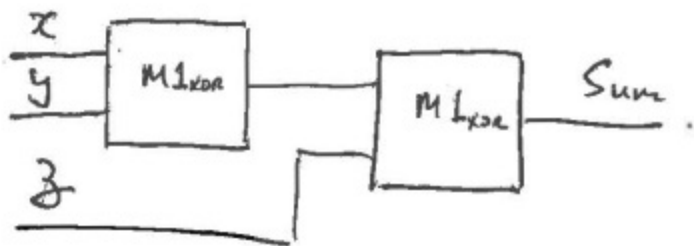

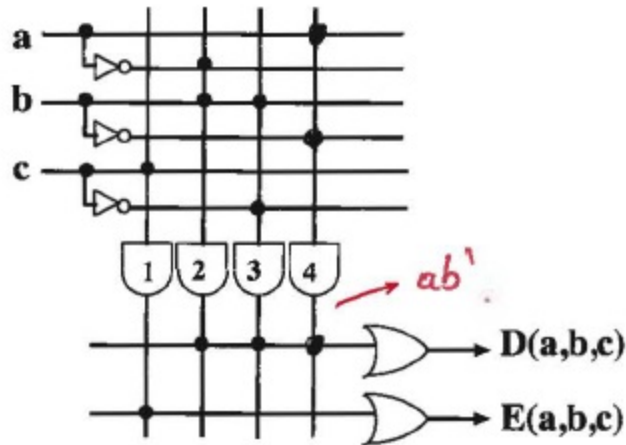Problem No. 6 (15 points)

A junior engineer Goofy is assigned to design a digital circuit using one PLA. The circuit converts a 3-bit 2's complement number abc into its 2-bit absolute value (unsigned integer) DE . He works out a minimal design and implements it on the PLA as shown below. Regrettably, he makes **ONE SINGLE MISTAKE** in the design. As a result, the circuit **DOES NOT** work correctly.



Your task is to help Goofy:

1. Debug the design and find the error. Show all your work in the provided space below.
2. Correct the error by adding and/or removing connections on the original PLA diagram above. Use a "X" for a connection removed and a heavy dot "•" for a connection added. Your correction **MUST BE MINIMAL**.

(Extra space available on the next page)

(Extra space for Problem No. 6)

5 pts Step 1: The truth table is:

	a	b	c	D	E
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	1	0
3	0	1	1	1	1
-4	1	0	0	-	-
3	1	0	1	1	1
	1	1	0	1	0
	1	1	1	0	1

→ can't be represented w/ 2-bits. → treated as don't care.

5 pts Step 2: Minimize using K-map.

	c	
a	0	1
	-	0

b

D

	c	
a	1	1
	-	1

b

E

$$\therefore D = a'b + bc' + ab' \quad E = c$$

5 pts Step 3: Compare Goofy's design from PLA implementation

$$D = a'b + bc'$$

$$E = c$$

∴ Goofy missed the term ab' . fixed as shown in PLA.

(End of Problem No. 6)

Problem No. 7 (15 points)

Fill in blanks in the following table by performing conversions and arithmetic operations in specified **binary number systems**. For one's complement and two's complement in parts (c) and (d), use **only** complementation and addition, and **indicate overflow if it occurs**. For part (e), use **only** range extension, shifting, complementation, and addition as needed, and **no** subtraction, multiplication, or division is allowed. Use provided space for all your work and **clearly LABEL** your steps and the final answer.

1 pt for each block.
 2 pts
 2 pts
 2 pts
 4 pts
 5 pts
 2.5 each.

Operations	Sign/Magnitude		1's Complement		2's Complement	
	Bit Vector	Signed Integer	Bit Vector	Signed Integer	Bit Vector	Signed Integer
Part (a): x	10100	-4	10100	-11	10100	N/A
Part (b): y	01011	+11	01011	N/A	01011	+11
Part (c): $s = x + y$	N/A	N/A	11111	-0	N/A	N/A
Part (d): $d = x - y$	11111	-15	N/A	N/A	overflow	
Part (e): $z = -\frac{3}{2}x + 7y$	N/A	N/A	N/A	N/A	1000000	-64

Show all your work below for full credit.

Part (a): x

SM: 0100 \rightarrow +4.
 10100 \rightarrow -4.
 1's C: 1 \rightarrow complemented form.
 10100 \rightarrow 01011 \rightarrow 11 \rightarrow -11

Part (b): y

SM: 01011 \rightarrow +11
 2's C: in true form \rightarrow +11

(Continue on the next page)

(Continue from Problem No. 7)

Part (c): $s = x + y$

$$\begin{array}{r}
 1'c. \quad 10100 \\
 + 01011 \\
 \hline
 11111 \\
 \downarrow \\
 -0.
 \end{array}$$

Part (d): $d = x - y$

$$\begin{array}{l}
 Sm: x - y = x + (-y) \\
 \begin{array}{r}
 10100 \\
 + 01011 \\
 \hline
 11111 \\
 \downarrow \\
 -15
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 2'c. \\
 10100 \\
 + 10100 \\
 \hline
 101000 \\
 \downarrow \\
 \text{overflow}
 \end{array}$$

(Continue on the next page)

(Continue from Problem No. 7)

Part (e): $z = -\frac{3}{2}x + 7y$

$$\overset{\textcircled{7}}{z} = -\left(x + \frac{x}{2}\right) + \overset{\textcircled{2}}{2^3}y + \overset{\textcircled{5}}{(-y)}$$

⑩ Range extension:

$$2^3y \rightarrow 5+3 = 8 \text{ bits.}$$

$$\therefore x = 11110100$$

$$y = 00001011$$

① $\frac{x}{2}: 1111010$

② $x + \frac{x}{2}: 11110100$

$$\begin{array}{r} \textcircled{1} \quad 1110110 \\ \leftarrow \text{carry} \end{array}$$

③ $-(x + \frac{x}{2}): 00010001$

$$\begin{array}{r} \underline{\hspace{1cm}} \\ 00010001 \end{array}$$

④ $2^3y: 01011000$

⑤ $-y: 11110100$

$$\begin{array}{r} \underline{\hspace{1cm}} \\ 11110101 \end{array}$$

⑥ $-\frac{3}{2}x + 2^3y: 01101010$

⑦ $\textcircled{1} \rightarrow 01011111$


← carry.

(End of Problem No. 7)

$$\therefore z = +\underline{95}$$

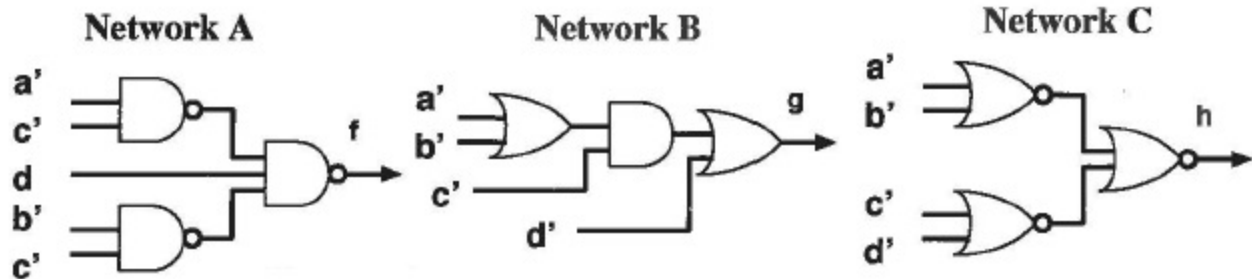Problem No. 8 (10 points)

Three gate networks A, B and C are given below. Tests have shown that two of them are *equivalent*, that is, they implement the same switching function. You are asked to identify the network that is not equivalent.



4 pts -
 Part (a) Describe in one sentence your approach.
 Answer: ① use boolean algebra + bubble logic. }
 ② use K-map } to compare.
 ③ use truth table

6 pts
 Part (b) The non-equivalent network is C.

Show all your work below for credit:

Method 1:

$$f = a'c' + d' + b'c'$$

$$g = (a' + b')c' + d' = a'c' + d' + b'c'$$

$$h = (a' + b')(c' + d') = a'c' + \underline{a'd'} + b'c' + \underline{b'd'}$$

⇒ Network C is different

(End of Midterm)