


15

**Problem 1 (20 points):**

Given the network below, find the critical path and calculate critical path delay. Assume the values of  $(x_3, x_2, x_1, x_0)$  are initially  $(1, 1, 1, 1)$  and they change to  $(0, 1, 0, 0)$  in the next clock cycle. Now, choose a gate on the critical path which maximally decreases overall delay when the gate decreases its delay by 20%. Finally, find the critical path in the new network and its length.

 $(1, 0) \quad (0, 1)$ 

Gate	Fan-in	$t_{PLH}$	$t_{PHL}$
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$

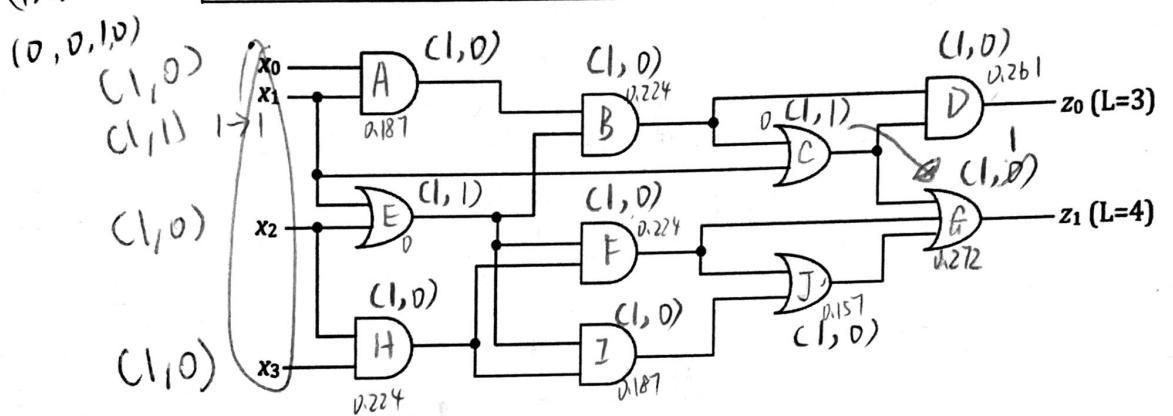 $(1, 1, 1, 1)$ 
 $(0, 0, 1, 0)$ 
 $(1, 0)$ 
 $(1, 1)$ 
 $(1, 0)$ 
 $(1, 0)$ 
 $x_0$ 
 $x_1$ 
 $x_2$ 
 $x_3$ 
**Gate**
**Fan-in**
 $(1, 0)$ 
 $(0, 1)$ 
**AND**
**2**
 $0.15 + 0.037L$ 
 $0.16 + 0.017L$ 
**AND**
**3**
 $0.20 + 0.038L$ 
 $0.18 + 0.018L$ 
**OR**
**2**
 $0.12 + 0.037L$ 
 $0.20 + 0.019L$ 
**OR**
**3**
 $0.12 + 0.038L$ 
 $0.34 + 0.022L$ 

*Before changing delay:*

$\text{Delay } (A, B, D) = 0.187 + 0.224 + 0.261 \times$

$\text{Same } (A, B, C, D)$

$\text{Delay } (A, B, C, G) = 0.187 + 0.224 + 0.272 = 0.683$

$\text{Same } (E, B, D)$

$\text{Delay } (E, B, C, D)$

$\text{Delay } (E, B, C, G) = 0.224 + 0.272 \times$

$\text{Delay } (E, F, G) = 0.224 + 0.272 \times$

$\text{Delay } (E, F, J, G) = 0.224 + 0.157 + 0.272 = 0.653$

$\text{Delay } (E, I, J, G) = 0.187 + 0.157 + 0.272 \times$

$\text{Delay } (H, F, J, G) = 0.224 + 0.224 + 0.157 + 0.272 = 0.877 \text{ ns.}$

$\text{Delay } (H, F, G) = 0.224 + 0.224 + 0.272 \times$

$\text{Delay } (H, I, J, G) = 0.224 + 0.187 + 0.157 + 0.272 \times$

Critical path : HFJ G, with time delay 0.877 ns

$t_{LH} =$

$A: 0.15 + 0.037 \cdot 1$

$B: t_{LH}$

$= 0.15 + 0.037 \cdot 2$

$= 0.224$

$C: t_{LL} = 0$

$D: 0.15 + 0.037 \cdot 3$

$= 0.261$

$E: t_{LH} = 0$

$F: t_{LH} = 0.15 + 0.037 \cdot 2$

$= 0.224$

$G: t_{LH} = 0.12 + 0.038 \cdot 4$

$= 0.272$

$H: t_{LH} = 0.15 + 0.037 \cdot 2$

$= 0.224$

$I: t_{LH} = 0.15 + 0.037 = 0.187$

$J: t_{LH} = 0.12 + 0.037$

$= 0.157$

**Problem 1 (Extra Page):**

Decrease  $f$  gate by 20%

$$\text{Delay}(G) = 0.272 \cdot (1-20\%) = 0.272 \cdot 0.8 = 0.2176 \text{ ns}$$

The other gates are the same.

same ( Delay (A,B, D) = 0.187 + 0.224 + 0.261 = 0.672 X

Delay (A, B, C, D)

Delay (A, B, C, G) = 0.187 + 0.224 + 0.2176 X

same ( Delay (E, B, D) = 0.224 + 0.261 X

Delay (E, B, C, D)

Delay (E, B, C, G) = 0.224 + 0.2176 X

Delay (E, F, G) = 0.224 + 0.2176 X

Delay (E, F, J, G) = 0.224 + 0.157 + 0.2176 X

Delay (E, J, J, G) = 0.187 + 0.157 + 0.2176 X

Delay (H, F, J, G) = 0.224 + 0.224 + 0.157 + 0.2176 = 0.8226 ns.

Delay (H, F, G) = 0.224 + 0.224 + 0.2176 X

Delay (H, I, J, G) = 0.224 + 0.187 + 0.157 + 0.2176 X

The Critical path in the new network is : H F J G with 0.8226 ns time delay

**Problem 2 (20 points):**

You are given the following Boolean function.


$$F(x_6, x_5, x_4, x_3, x_2, x_1, x_0) = x_6x_5x_4x_3 + x_6x_5'x_2 + x_6x_5'x_3'x_2' + x_6'x_1x_0 + x_6'x_5x_0'$$

Given the universal operation E as specified in the table, implement F using only the gates specified by E.


X	Y	E(X, Y)
0	0	1
0	1	1
1	0	0
1	1	1

$$E(x, y) = x' + y = (xy')'$$


$$\bar{x} \text{ NOT} = E(x, 0)$$

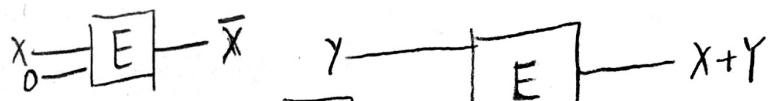
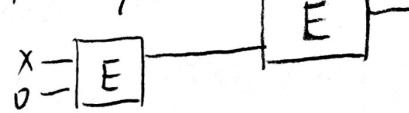
$$x+y \text{ OR} = E(x', y) = E(E(x, 0), y)$$



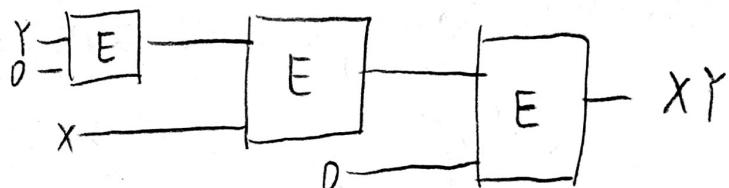
$$xy \text{ AND} = E(E(x, y'), 0) = E(E(x, E(y, 0)), 0)$$



$$\begin{aligned}
 F &= x_6x_5x_4x_3 + x_6x_5'x_2 + x_6x_5'x_3'x_2' + x_6'x_1x_0 + x_6'x_5x_0' \\
 &= E(\bar{E}(x_6x_5, E(x_4x_3, 0)), 0) + E(E(x_6x_2, E(x_5', 0)), 0) + E(\bar{E}(x_6', E(x_1x_0, 0)), 0) \\
 &\quad + E(E(x_6x_5', E(x_3'x_2', 0)), 0) + E(\bar{E}(x_6', E(x_5x_0, 0)), 0) \\
 &= E(E(E(E(x_6, E(x_5, 0)), 0), E(E(E(x_4, E(x_3, 0)), 0), 0)), 0) \\
 &\quad + E(E(E(E(x_6, E(x_2, 0)), 0), E(E(x_5, 0), 0)), 0) \\
 &\quad + E(E(E(E(x_6, E(E(x_5, 0), 0)), 0), E(E(x_3+x_2, 0), 0)), 0) \\
 &\quad + E(E(E(E(x_6, 0), E(E(E(x_1, E(x_0, 0)), 0), 0)), 0), 0) \\
 &\quad + E(E(E(E(x_6, 0), E(E(E(x_5, E(E(x_6, 0), 0)), 0), 0)), 0), 0)
 \end{aligned}$$

Problem 2 (Extra Page):

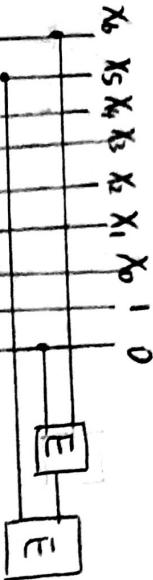

$$\begin{aligned} &= \cancel{E(E(E(E(X_6, E(X_5, D)), D), E(E(E(X_4, E(X_3, D)), D), D), D))} \\ &\quad + \cancel{E(E(E(E(X_6, E(X_2, D)), D), E(E(X_5, D), D)), D))} \\ &\quad + \cancel{E(E(E(E(X_6, E(E(X_5, D), D)), D), E(E(E(E(X_3, D), X_2), D), D), D), D))} \\ &\quad + \cancel{E(E(E(X_6, D), E(E(E(X_1, E(X_0, D)), D)), D)), D)} \\ &\quad + \cancel{E(E(E(X_6, D), E(E(E(X_5, E(E(X_0, D), D)), D), D)), D), D)} \end{aligned}$$




2D

**Problem 3 (20 points):**

For a K-map, M denotes the number of prime implicants of the K-map, and N denotes the number of essential prime implicants of the K-map. Draw a  $4 \times 4$  K-map that has the largest value of  $P = M - N$  among all the  $4 \times 4$  K-maps.

For example, in the following  $4 \times 4$  K-map,  $M=3$ ,  $N=2$ ,  $P=M-N=1$ .


	$x_0$		
$x_3$	0	0	0
	1	1	0
	1	1	1
	0	0	1

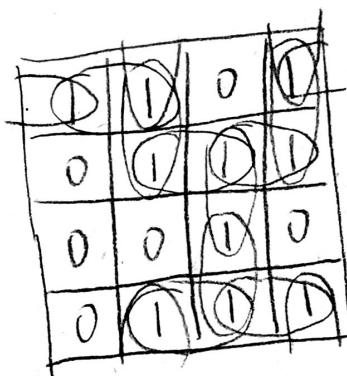

$$M=12$$

$$N=0$$

$$P = M - N = 12$$

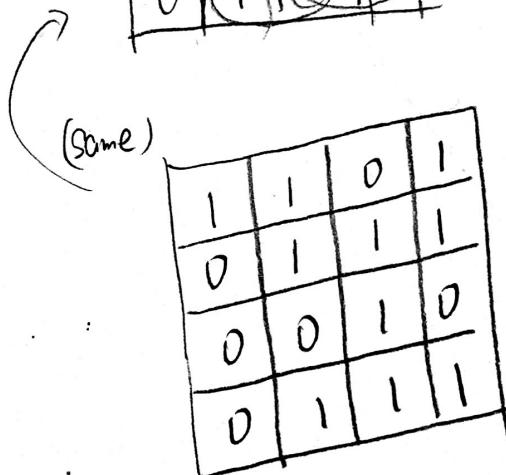

18 6

#### Problem 4 (20 points):

Given an input stream X, we want to recognize interchangably patterns A and B. We recognize A first, then B, followed by A again, then B again and so on.

For example,


1. Assume  $X = 01011010010101$ ,  $A=101$  and  $B=001$ .

We will first recognize A, then look for B. Please note that we ignore the second '101' (A) in X and we only search for B once we have found A. After finding B, we again search for A.

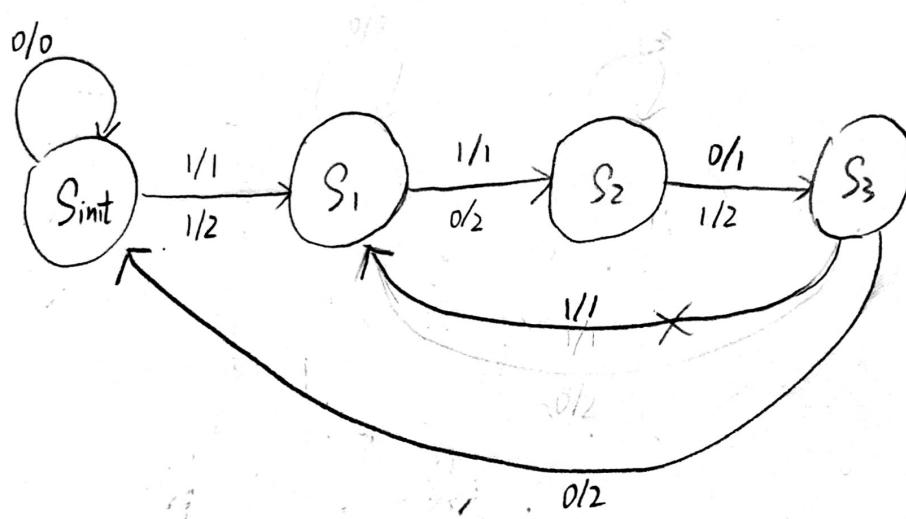2. Assume that we have  $X=1011$ ,  $A = 101$  and  $B=011$

We recognize A, but we do not recognize B as we only start looking for B once we have detected A. In other words, A and B do not overlap.

Now, you are given any input stream X. Design a finite state machine such that the system outputs 1 when it recognizes pattern  $A=1101$  and outputs 2 when it recognizes pattern  $B=1010$  after recognizing pattern A. In all other cases the machine should output 0. Show the state transition table and state transition diagram.



Needs 8 states.

11011 outputs 1 twice

<del>Input state</del>	0	1
$S_{init}$	$0 S_{init}$	$1 S_1$ $2 S_1$
$S_1$	$2 S_2$	$1 S_1$
$S_2$	$1 S_3$	$2 S_3$
$S_3$	$2 S_{init}$	$1 S_1$

**Problem 5 (20 points):**

Perform the following conversions:

~~X X X X  
8 4 2 1~~

a)  $(B2451)_{16} \rightarrow (x)_8$

b)  $(354)_7 \rightarrow (y)_5$

a)  $(B2451)_{16}$

= 0 1 0 | 1 1 0 0 | 1 0 | 0 1 0 0 | 0 1 | 0 1 0 0 1

= 2 6 2 2 | 2 1<sub>8</sub>

$X = 2622121$

b)  $(354)_7 = (3 \cdot 7^2 + 5 \cdot 7^1 + 4 \cdot 7^0)_{10}$

=  $(147 + 35 + 4)_{10}$

=  $186_{10}$

=  $1221_5$

$Y = 1221$

186 / 5      1  
37 / 5      2  
7 / 5      2  
1 / 5      1  
0

<b>Problem (Possible Points)</b>	<b>Points</b>
1(20)	15
2(20)	16 + 4.
3(20)	20.
4(20)	16
5(20)	70
Total (100)	27