

EE100 Midterm 2

Winter 2012

Solutions

Name

Signature

Student ID

Problem 1 (pts):

Problem 2 (pts):


Problem 3 (pts):

Problem 4 (pts):

Total (pts):

There are 9 pages total.

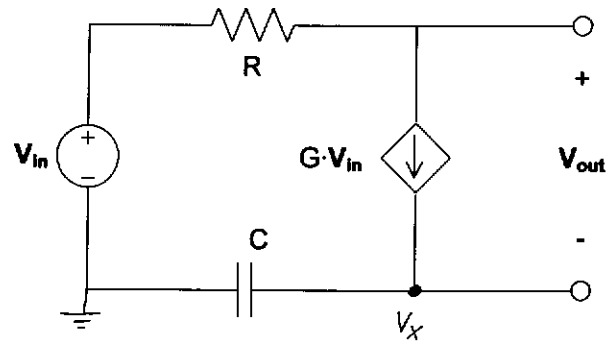1a) Find the transfer function $H(\omega) = V_{out}/V_{in}$ in terms of R , G , and ω for the circuit below.



$$\text{KCL: } G\tilde{V}_{in} = \frac{\tilde{V}_x}{1/j\omega C} = j\omega C\tilde{V}_x$$


$$\tilde{V}_x = \tilde{V}_{in} \frac{G}{j\omega C}$$

$$\begin{aligned} \text{KVL: } \tilde{V}_{in} &= G\tilde{V}_{in} \cdot R + \tilde{V}_{out} + \tilde{V}_x \\ &= GR\tilde{V}_{in} + \tilde{V}_{out} + \tilde{V}_{in} \frac{G}{j\omega C} \end{aligned}$$

$$\tilde{V}_{out} = \tilde{V}_{in} \left(1 - G \cdot R - \frac{G}{j\omega C} \right)$$

$$H(\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = 1 - G \cdot R - \frac{G}{j\omega C}$$

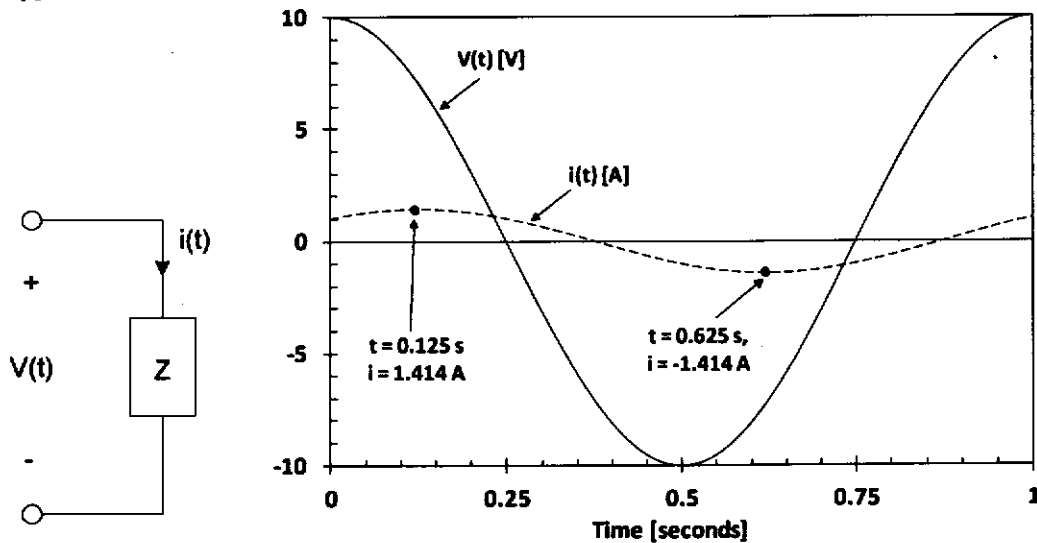1b) A certain two terminal load Z exhibits the following transient response when a sinusoidal voltage $V(t)$ is applied and the resulting current $i(t)$ is measured:



From the information given, reduce the load Z into its simplest possible configuration involving passive elements (i.e. resistors, inductors, capacitors).

$$v(t) = 10 \cos(2\pi t)$$

$$i(t) = \sqrt{2} \cos(2\pi t - 0.125 \cdot 360^\circ)$$

$$= \sqrt{2} \cos(2\pi t - 45^\circ)$$

$$\tilde{V} = 10 \angle 0^\circ$$


$$\tilde{I} = \sqrt{2} \angle -45^\circ$$

$$\frac{\tilde{V}}{\tilde{I}} = Z = \frac{10 \angle 0^\circ}{\sqrt{2} \angle -45^\circ} = 7.07 \angle 45^\circ = 5 + 5j = R + jX$$


Since the reactance is positive (current lags voltage), it is inductive in nature. We can model the total impedance by a resistor and inductor in series:

$$Z = R + j\omega L = 5 + 5j$$
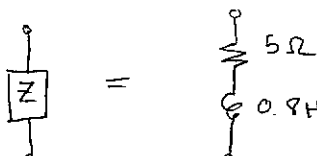
$$\boxed{\begin{matrix} R = 5 \Omega \\ L = \frac{5}{2\pi} = 0.8 \text{ H} \end{matrix}}$$



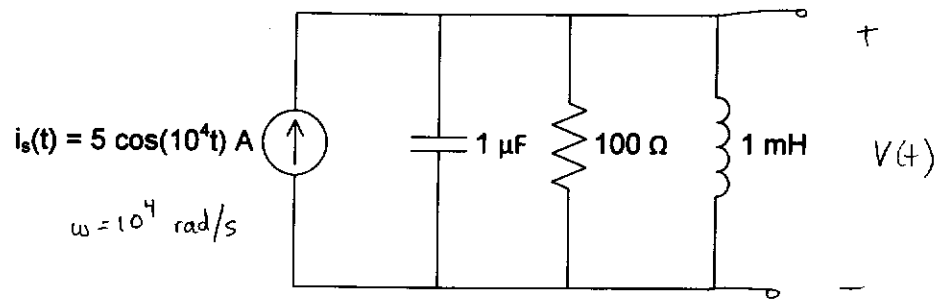2a) Find the average power, reactive power, and apparent power delivered by the current source in the circuit below.



$$Z = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$

$$= \frac{1}{0.01 + j(0.01 - 0.1)} = \frac{1}{0.01 - 0.09j}$$

$$= \frac{1}{0.09055 \angle -83.66^\circ} = 11.04 \angle 83.66^\circ$$

$$\tilde{I}_s = 5 \angle 0^\circ = \overbrace{3.536 \sqrt{2}}^{I_{\text{rms}}} \angle 0^\circ$$


$$\tilde{V} = \tilde{I}_s Z = 5 \angle 0^\circ \cdot 11.04 \angle 83.66^\circ = 55.22 \angle 83.66^\circ = \underbrace{39.05 \sqrt{2}}_{V_{\text{rms}}} \angle 83.66^\circ$$

$$\text{App. power} = V_{\text{rms}} I_{\text{rms}} = 39.05 (3.536) = 138.1 \text{ [VA]}$$

$$P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos \theta = 138.1 \cos(83.66^\circ) = 15.25 \text{ [W]}$$


$$Q = V_{\text{rms}} I_{\text{rms}} \sin \theta = 138.1 \sin(83.66^\circ) = 137.25 \text{ [VAR]}$$

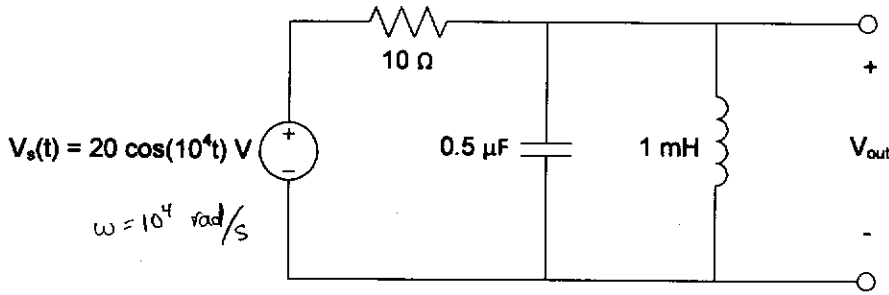2b) Find and draw the Thevenin and Norton equivalent circuits as seen from the port V_{out} in the circuit below.



$$Z_C = \frac{-j}{\omega C} = -200j \Omega$$


$$Z_L = j\omega L = 10j \Omega$$

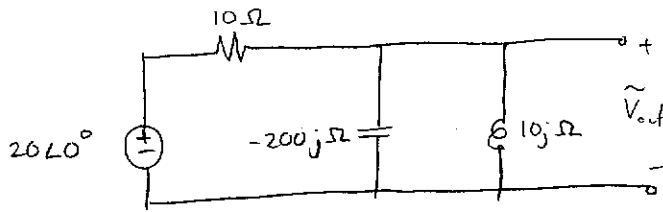


$$\begin{aligned} \tilde{V}_{out} &= 20 \cdot \frac{-200j \parallel 10j}{10 + (-200j \parallel 10j)} \\ &= 20 \cdot \frac{10.53j}{10 + 10.53j} \\ &= \frac{210.53 \angle 90^\circ}{14.52 \angle +46.48^\circ} \end{aligned}$$

$$-200j \parallel 10j = \frac{-2000j^2}{-190j} = 10.53j$$
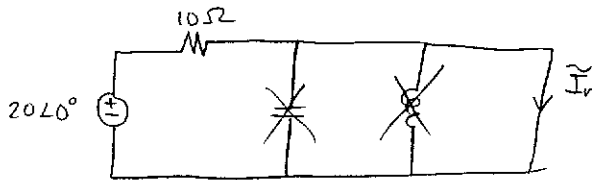
$$\tilde{V}_T = 14.5 \angle 43.52^\circ \text{ [V]}$$



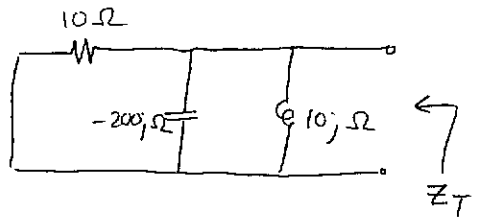
$$\tilde{I}_n = \frac{20}{10} = 2 \angle 0^\circ \text{ [A]}$$




$$\begin{aligned} Z_T &= 10 \parallel -200j \parallel 10j \\ &= 10 \parallel 10.53j \\ &= \frac{105.3j}{10 + 10.53j} = \frac{105.3 \angle 90^\circ}{14.52 \angle 46.48^\circ} \end{aligned}$$
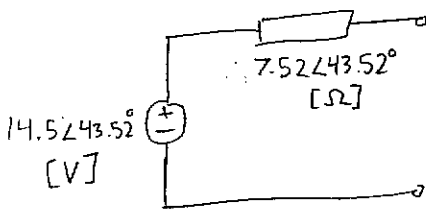
$$Z_T = 7.25 \angle 43.52^\circ \text{ [\Omega]}$$



Thevenin

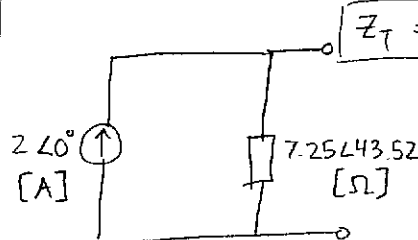


Norton

3a) Find the transfer functions in terms of R_1 , R_2 , and C .

$$H_1(\omega) = \frac{I_{R_2}}{I_{IN}}(\omega)$$
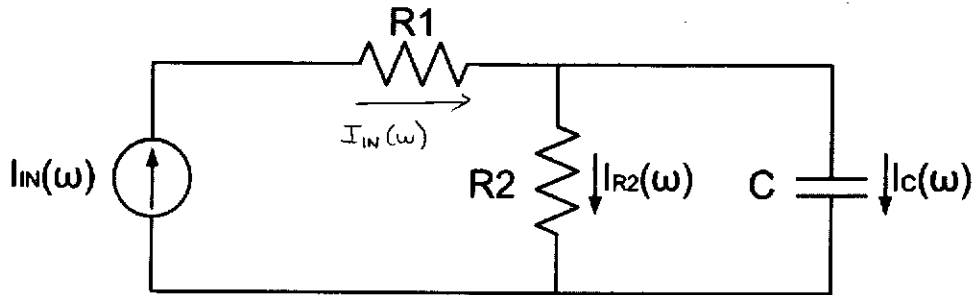
$$H_2(\omega) = \frac{I_C}{I_{IN}}(\omega)$$



$$\tilde{I}_{R_2} = \tilde{I}_{IN} \frac{Z_C}{R_2 + Z_C} = \tilde{I}_{IN} \frac{1/j\omega C}{R_2 + 1/j\omega C} = \tilde{I}_{IN} \frac{1}{1 + j\omega R_2 C}$$

$$H_1(\omega) = \frac{\tilde{I}_{R_2}}{\tilde{I}_{IN}} = \frac{1}{1 + j\omega R_2 C} \quad \leftarrow \text{LPF}$$

$$\tilde{I}_C = \tilde{I}_{IN} \frac{R_2}{R_2 + Z_C} = \tilde{I}_{IN} \frac{R_2}{R_2 + 1/j\omega C} = \tilde{I}_{IN} \frac{j\omega R_2 C}{1 + j\omega R_2 C}$$



$$H_2(\omega) = \frac{\tilde{I}_C}{\tilde{I}_{IN}} = \frac{j\omega R_2 C}{1 + j\omega R_2 C} \quad \leftarrow \text{HPF}$$

For $R_1 = 1 \text{ k}\Omega$
 $R_2 = 10 \text{ k}\Omega$
 $C = 1 \mu\text{F}$



$$R_2 C = 10^4 \cdot 10^{-6} = 10^{-2}$$

$$\frac{1}{R_2 C} = 100 \text{ rad/s}$$

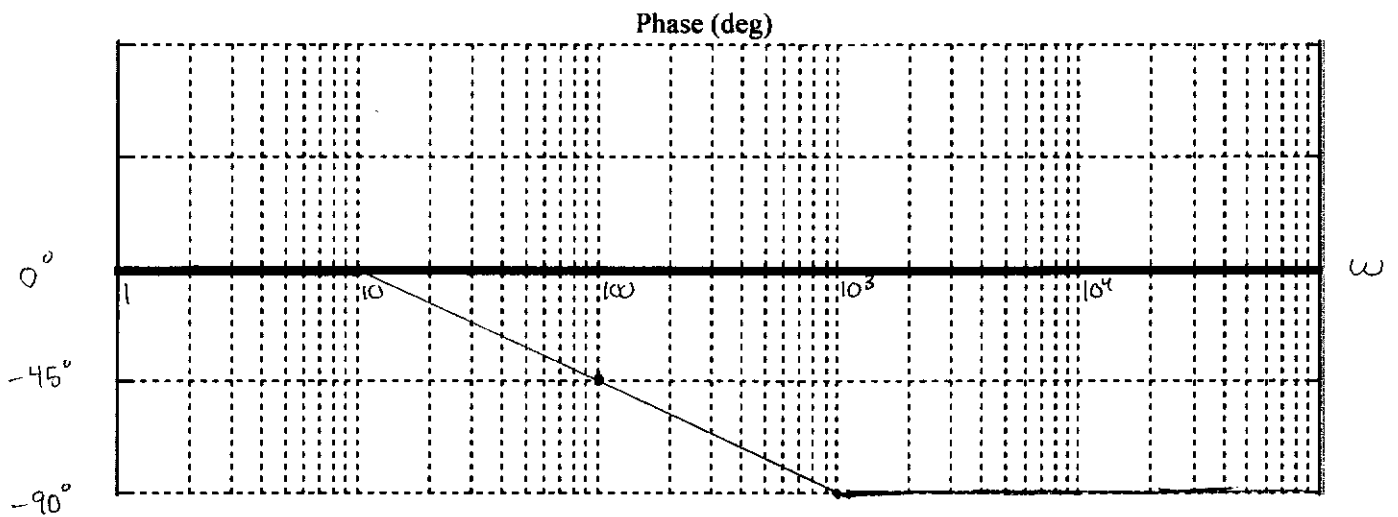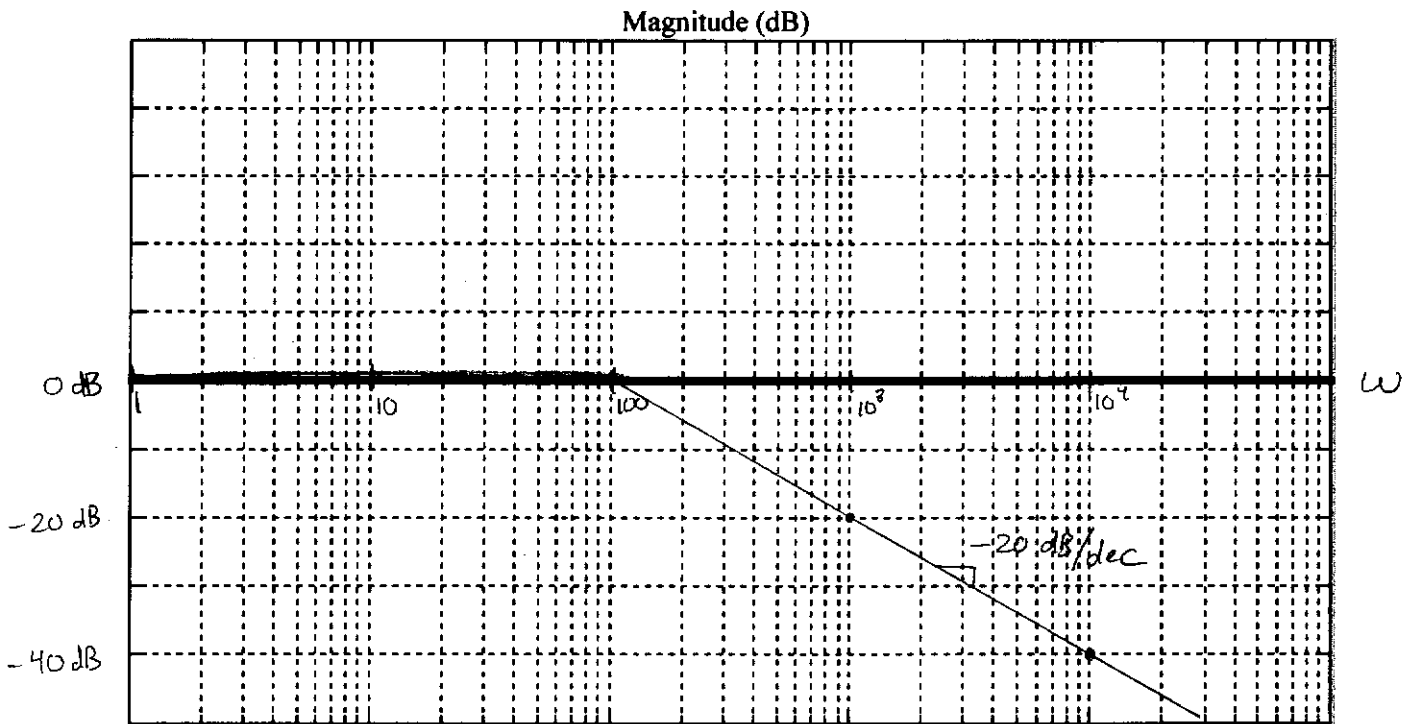
3b) Plot the magnitude and phase using Bode plots of $H_1(\omega) = I_{R2}/I_{IN}(\omega)$.
 Accurately depict and label the key features.
 Assume $R_1 = 1\text{K}\Omega$, $R_2 = 10\text{K}\Omega$ and $C = 1\ \mu\text{F}$.



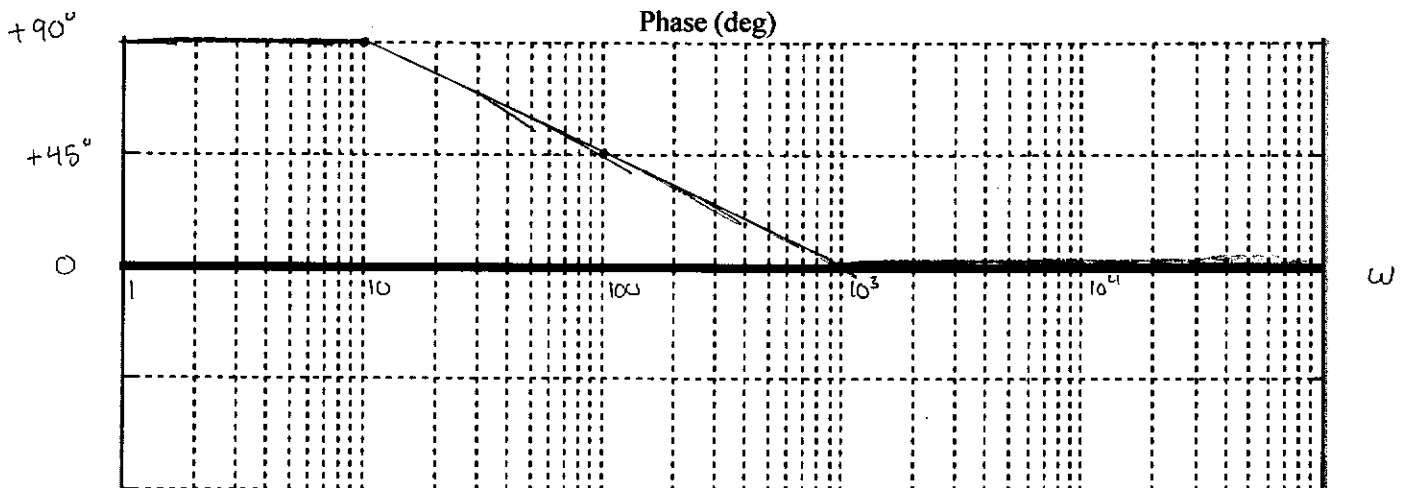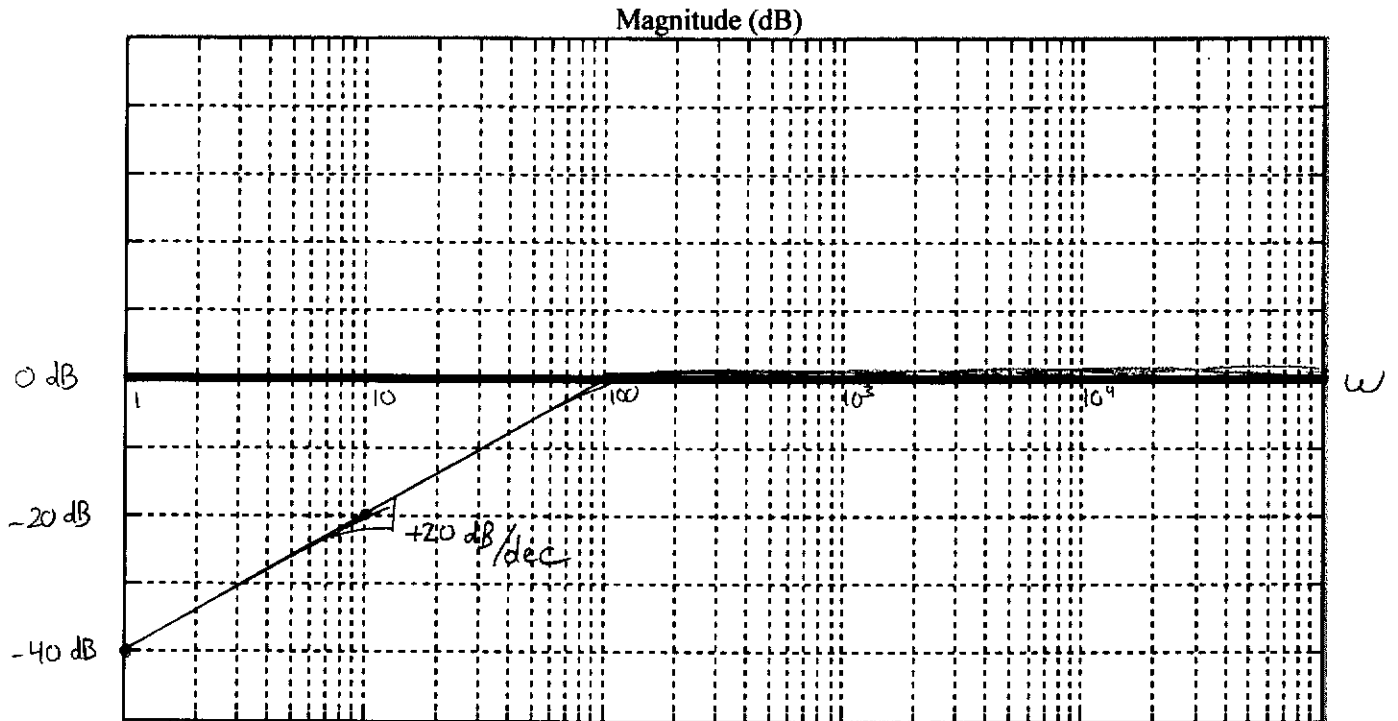3c) Plot the magnitude and phase using Bode plots of $H_2(\omega) = I_C/I_{IN}(\omega)$.
 Accurately depict and label the key features.
 Assume $R_1 = 1\text{K}\Omega$, $R_2 = 10\text{K}\Omega$ and $C = 1\ \mu\text{F}$.





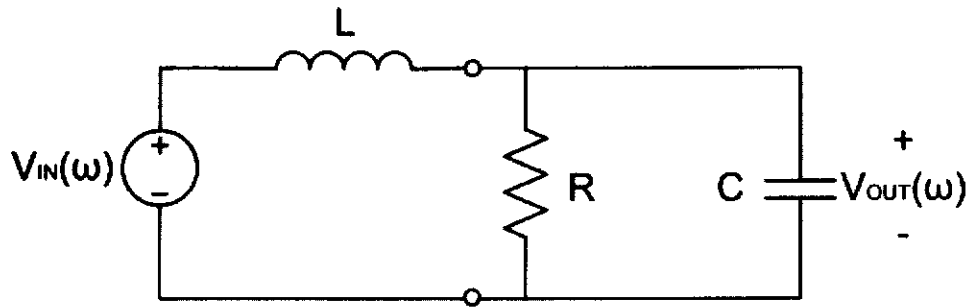4a) Consider the circuit below. Given reasonable component values, what type of filter do we have? Low pass, high pass, band pass, band reject, etc.



Very low frequencies

Very high frequencies

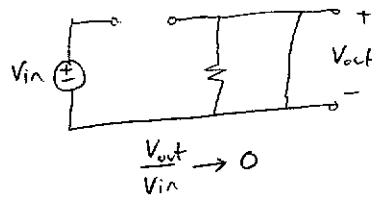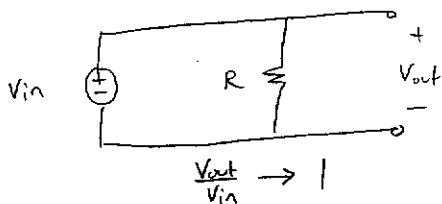

This represents a low pass filter.

4b) Find the resonant frequency of this circuit. Leave your answer in terms of R, L, and C.

$$\begin{aligned}
 Z &= j\omega L + \frac{1}{\frac{1}{R} + j\omega C} = j\omega L + \frac{R}{1 + j\omega RC} \\
 &= j\omega L + \frac{R(1 - j\omega RC)}{1 + (\omega RC)^2} = \frac{R}{1 + (\omega RC)^2} + j \left[\omega L - \frac{\omega R^2 C}{1 + (\omega RC)^2} \right] \\
 & \qquad \qquad \qquad = 0 \text{ at } \omega = \omega_0
 \end{aligned}$$


$$\omega_0 L = \frac{\omega_0 R^2 C}{1 + (\omega_0 RC)^2}$$

$$1 + (\omega_0 RC)^2 = \frac{R^2 C}{L}$$

$$\omega_0^2 = \left(\frac{R^2 C}{L} - 1 \right) \frac{1}{(RC)^2} = \frac{1}{LC} - \frac{1}{(RC)^2}$$

$$\boxed{\omega_0 = \sqrt{\frac{1}{LC} - \frac{1}{(RC)^2}}}$$

4b)

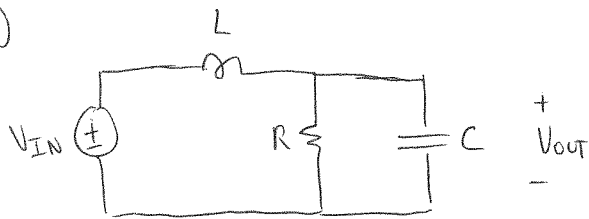

Alternate solution

Text mentions ω_0 occurs near the maximum of $|H(\omega)|$

This is only true with a large enough Q . However, full credit is still awarded if you followed this approach.

$$\frac{V_{out}}{V_{in}} = H(\omega) = \frac{\left(\frac{1}{R} + j\omega C\right)^{-1}}{\left(\frac{1}{R} + j\omega C\right)^{-1} + j\omega L} = \frac{1}{1 + (j\omega L)\left(\frac{1}{R} + j\omega C\right)} = \frac{1}{1 - \omega^2 LC + j\omega \frac{L}{R}}$$

$$|H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + \left(\omega \frac{L}{R}\right)^2}} = \left(1 + \omega^4 L^2 C^2 - 2\omega^2 LC + \omega^2 \frac{L^2}{R^2}\right)^{-1/2}$$

$$\frac{d}{d\omega} |H(\omega)| = \frac{4\omega^3 L^2 C^2 - 4\omega LC + 2\omega \frac{L^2}{R^2}}{(\dots)^{3/2}}$$

Assume ω_0 occurs when $\frac{d}{d\omega} |H(\omega)| = 0$

$$4\omega^3 L^2 C^2 - 4\omega LC + 2\omega \frac{L^2}{R^2} = 0$$

$$\omega^2 L^2 C^2 = LC - \frac{1}{2} \frac{L^2}{R^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{1}{2} \frac{1}{R^2 C^2}} = \omega_0$$