

Solution to 1

Lossless line $R' = 0$, $G' = 0$ and $\alpha = 0$

$$\begin{cases} Z_0 = R_0 = \sqrt{L'/C'} \\ \beta = \omega \sqrt{L'C'} \end{cases}$$

divide $Z_0/\beta = \frac{R_0}{\beta} = \frac{1}{\omega C'}$

$$C' = \frac{\beta}{R_0 \omega} = \frac{3}{2\pi \times 100^8 (70)} = 68.2 \text{ pF/m}$$

$$\begin{aligned} L' &= R_0^2 C' = (70)^2 (68.2 \times 10^{-12}) \\ &= 334.2 \text{ nH/m} \end{aligned}$$

5 points.

Solution to 2. (1) $Z_L = \frac{Z_L}{Z_0} = \frac{40 + j30}{100} = 0.4 + j0.3 = r_L + jx_L$

(2) locate Z_L on Smith chart

Draw the SWR circle

Then y_L is opposite to Z_L on SWR circle.

$$y_L = g_L + jb_L = 1.6 - j1.2.$$

Alternatively $y_L = \frac{Z_0}{Z_L} = \frac{100}{40 + j30} \times \text{by c.c.}$
 $= 1.6 - j1.2.$

(3) Draw $g=1$ circle.

The SWR circle intersects the $g=1$ circle at points

A $y_{\#A} = 1 - j1.04 \pm 0.02$

B $y_{\#B} = 1 + j1.04 \pm 0.02$

so the shunt impedance must be

A $y = +1.04$
 B $y = -1.04$

(4) Thus the required shunt admittance is

$$Y_s = Y_0 y_s = \pm j1.04 \left(\frac{1}{100} \right) = \pm j10.4 \text{ mS.}$$


Both are possible values.

Problem 2

stub l2

The Complete Smith Chart

Black Magic Design

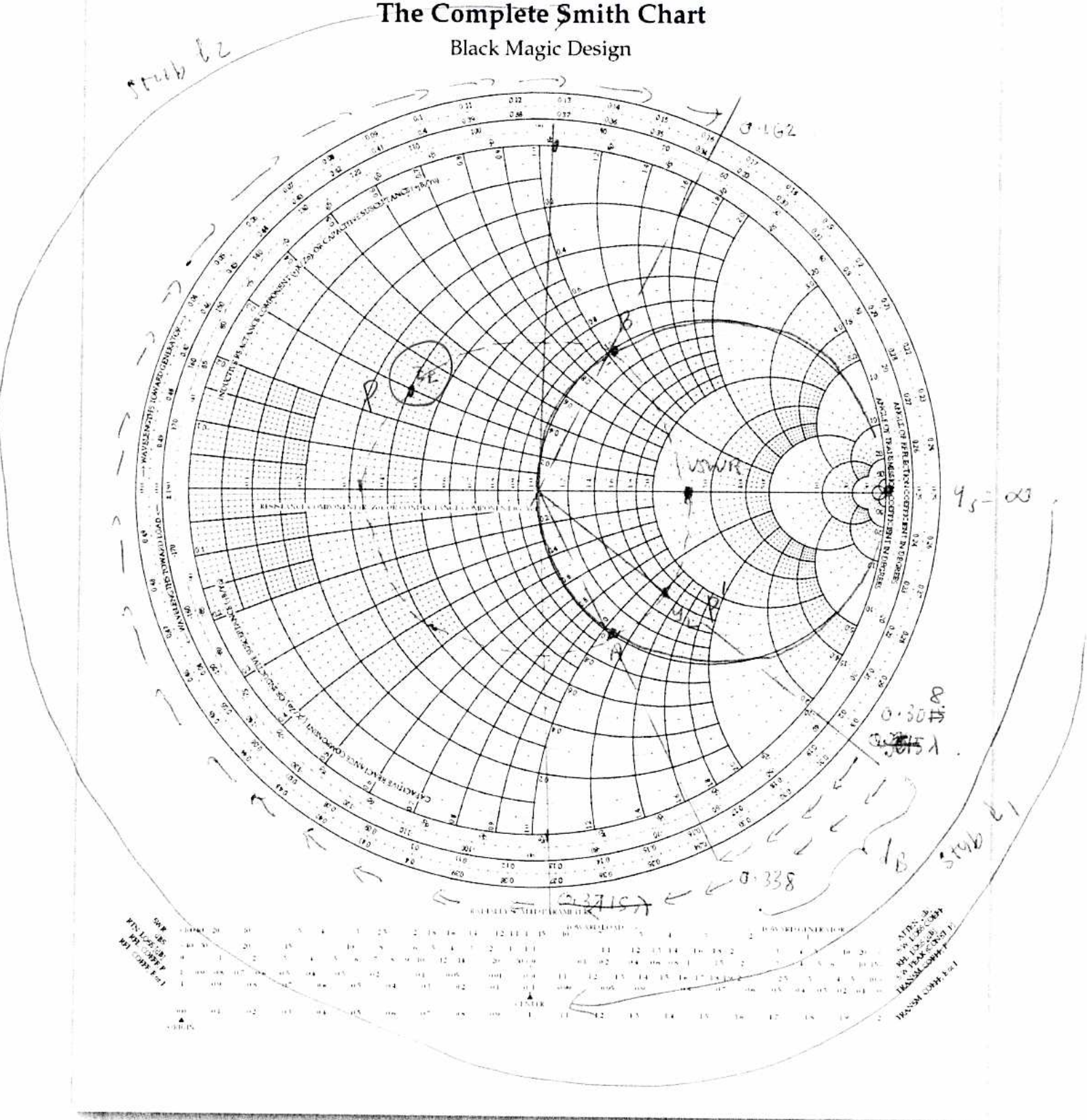

SWR
 1.00 1.50 2.00 3.00 4.00 5.00 6.00 7.00 8.00 9.00 10.00 15.00 20.00 30.00 40.00 50.00 60.00 70.00 80.00 90.00 100.00

0.0005

0.3715

0.338

0.308

0.308


0.3715

ATTEN: dB
 0.1 0.2 0.3 0.4 0.5 0.6 0.7 0.8 0.9 1.0 1.2 1.5 2.0 2.5 3.0 4.0 5.0 6.0 7.0 8.0 10.0 15.0 20.0 30.0 40.0 50.0 60.0 70.0 80.0 90.0 100.0

stub l1

Solukon r3.

i)

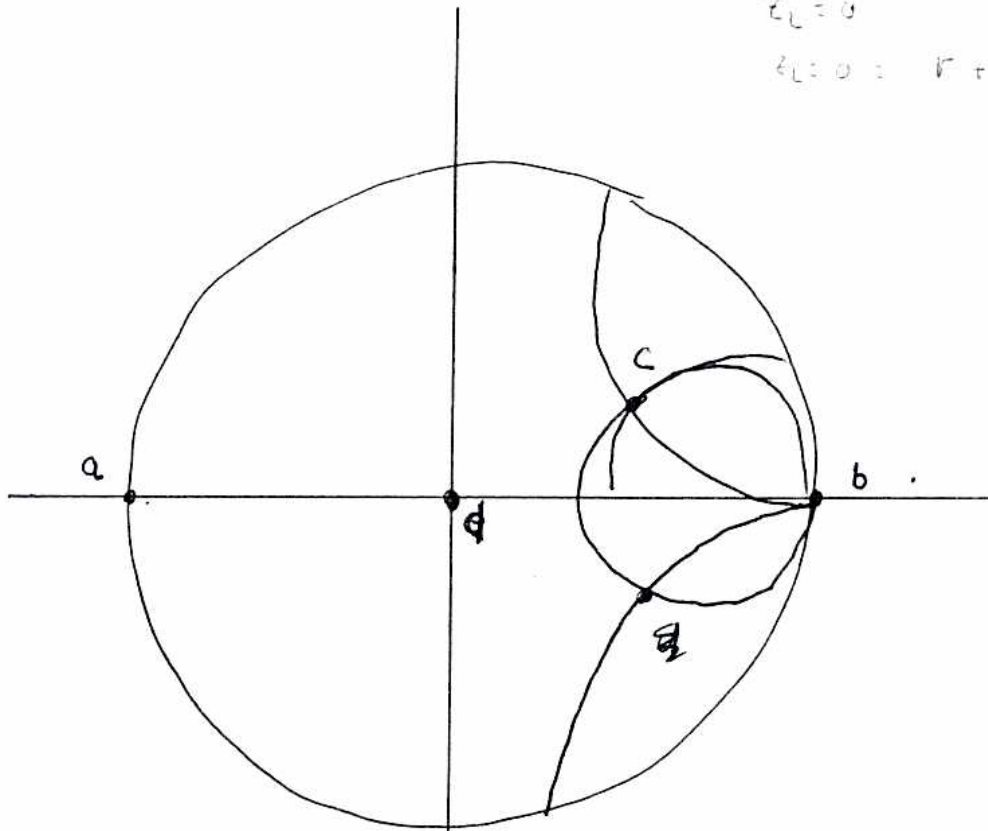

$Z_L = 0$
 $\Gamma_L = 0 = V + jX$

- a = 1
- b = 1
- c = 1
- d = 1


ii)

a) $0.61 e^{-j 30^\circ}$

b) 4.3

c) $Z_{in} = 22.5 + j 45 \Omega$ ($6.25 + j 47 \Omega$)

d) 0.208λ
 0.21λ

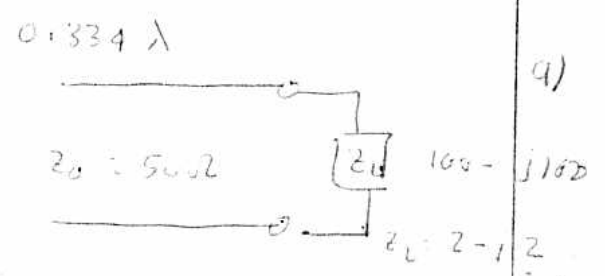

- a) 3
- b) 2
- c) 3
- d) 3

OK well


Solution to 4.

$$f\lambda = v_p \quad \text{and} \quad v_p = c/\epsilon_r^{1/2}$$

$$v_p = \frac{3 \times 10^8}{\sqrt{3.62}} = 1.58 \times 10^8 \text{ m/s}$$


$$\lambda = v_p / f = \frac{1.58 \times 10^8}{400 \times 10^6} = 39.4 \text{ cm}$$

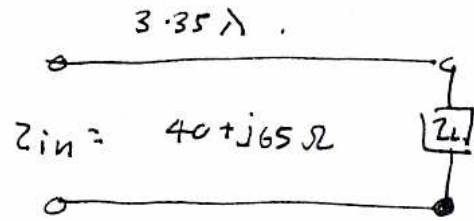but $l = 1.32 \text{ m}$
 $l/\lambda = 3.35 \lambda$



$1/2$ wavelength towards the generator is $\times 2$ 360°
 $3 \lambda = 6$ times round
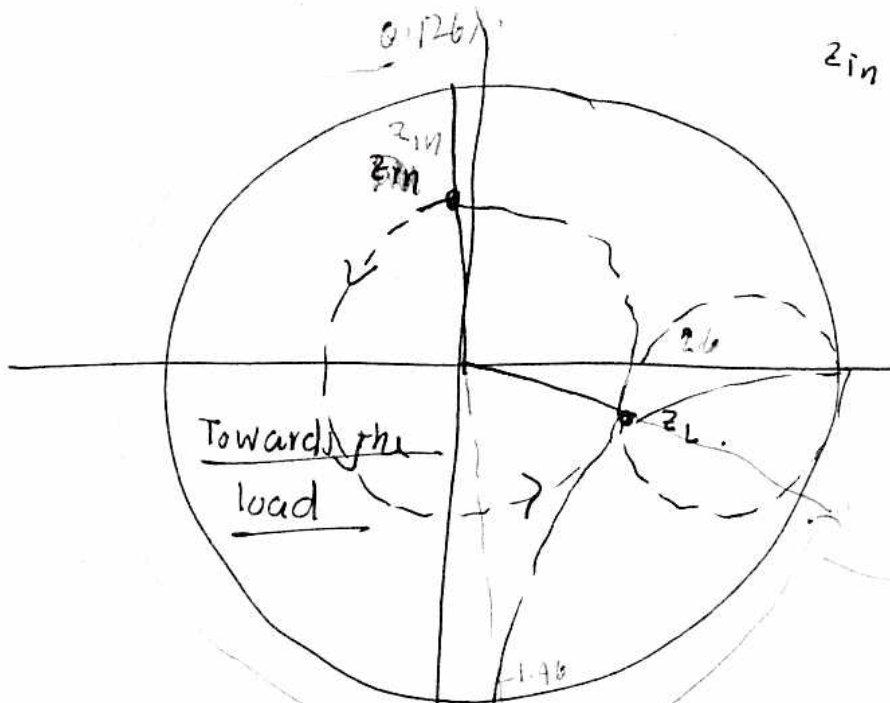
$$0.35 \lambda = 2 \times 0.35 \times 360^\circ = 2 \times 126^\circ = 252^\circ \text{ anticlockwise from } Z_{in}$$



$$Z_{in} = \frac{40 + j65}{75} = 0.53 + j0.86$$

Now move a distance 0.35λ toward the load

This corresponds to $Z_L = 2.6 - j1.46$

$$Z_1 = Z_0 Z_L = 194 - j109 \Omega$$

2/24/17/104

The Complete Smith Chart

Black Magic Design


move 0.125λ
toward the
load

0.35 -
0.126

0.224

0.5 -
0.128

0.374

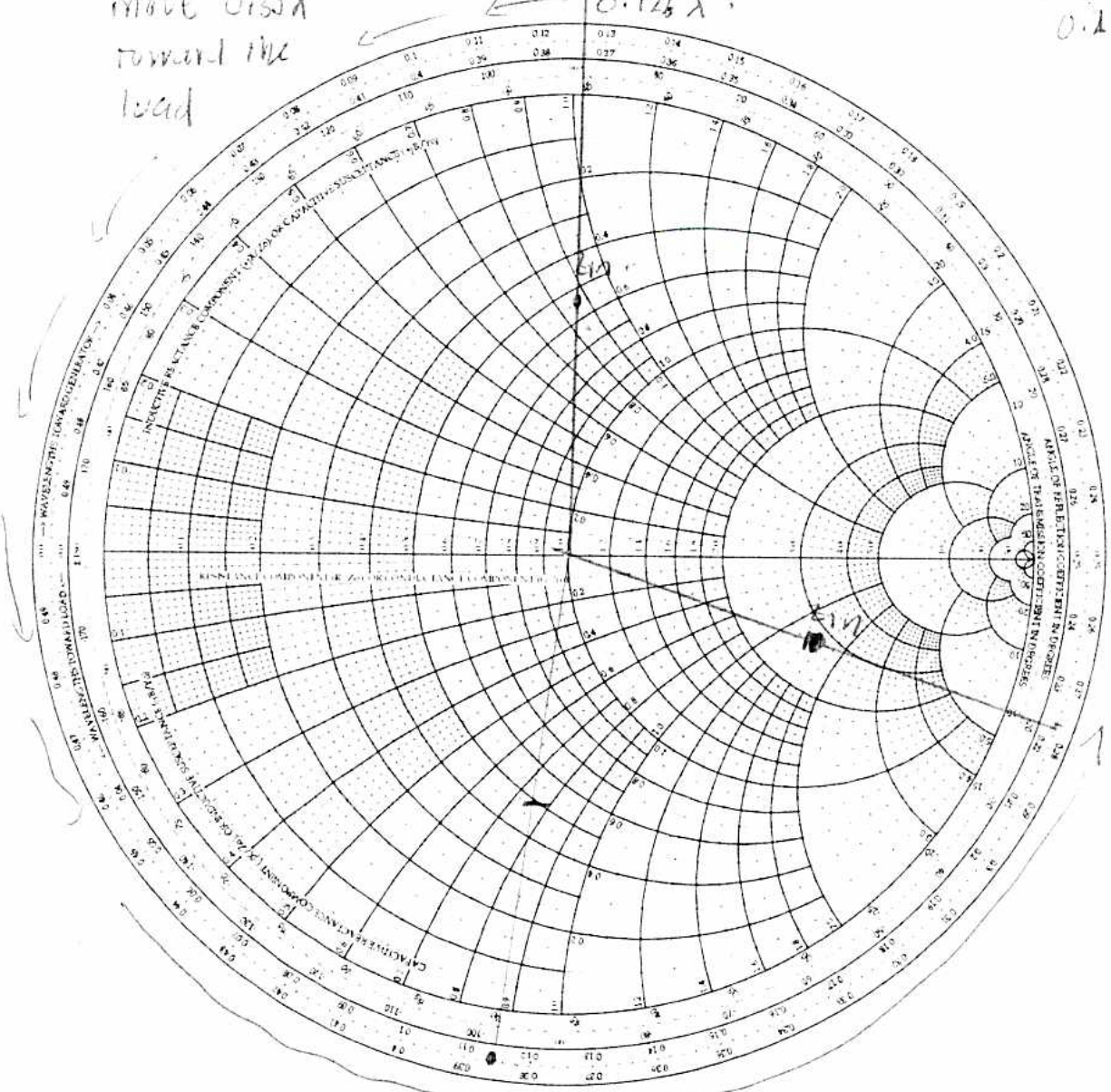

SWR

| | | | | | | | | | | | | | | | | | | | | | | |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| 1.0 | 1.2 | 1.5 | 2.0 | 3.0 | 4.0 | 5.0 | 6.0 | 7.0 | 8.0 | 9.0 | 10 | 12 | 15 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | 90 | 100 |
| 0.0 | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | 1.0 | 1.1 | 1.2 | 1.3 | 1.4 | 1.5 | 1.6 | 1.7 | 1.8 | 1.9 | 2.0 | 2.2 | 2.5 |

REFLECTION COEFFICIENT

| | | | | | | | | | | | | | | | | | | | | | | |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| 0.0 | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | 1.0 | 1.1 | 1.2 | 1.3 | 1.4 | 1.5 | 1.6 | 1.7 | 1.8 | 1.9 | 2.0 | 2.2 | 2.5 |
| 0.0 | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | 1.0 | 1.1 | 1.2 | 1.3 | 1.4 | 1.5 | 1.6 | 1.7 | 1.8 | 1.9 | 2.0 | 2.2 | 2.5 |

ATTEN. DB

| | | | | | | | | | | | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|-----|
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 12 | 15 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | 90 | 100 |
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 12 | 15 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | 90 | 100 |

TRANSM. LOSS COEFF. (dB)

| | | | | | | | | | | | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|-----|
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 12 | 15 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | 90 | 100 |
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 12 | 15 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | 90 | 100 |

uhm 25



What are the boundary conditions for the tangential and the normal component of the electric field intensity and the electric flux density between two dissimilar dielectrics with ϵ_{R1} and ϵ_{R2} .

$$E_{t1} = E_{t2} \quad \frac{D_{n1}}{D_{n2}} = \frac{\epsilon_{R1}}{\epsilon_{R2}}$$

$$D_{n1} = D_{n2}$$

$$\epsilon_{R1} E_{n1} = \epsilon_{R2} E_{n2}$$

2
2

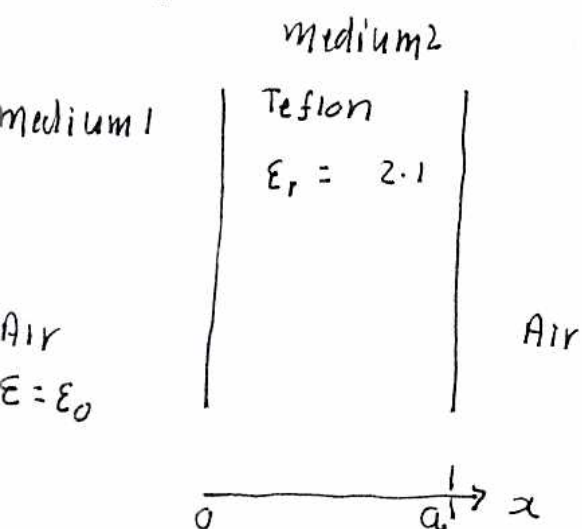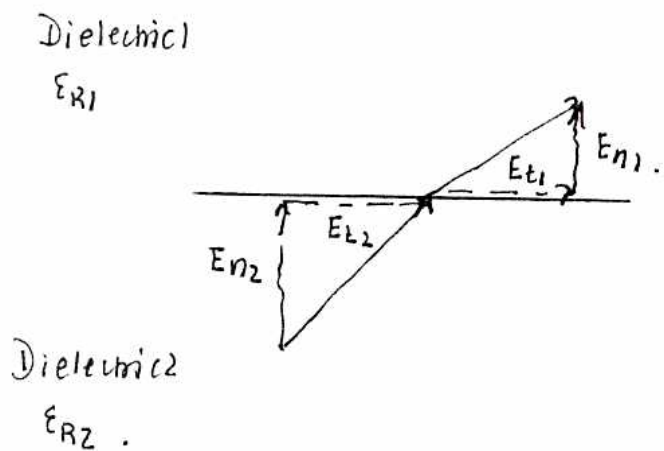

A slab of teflon thickness a and $\epsilon_r = 2.1$ is immersed in a uniform external field $\hat{x} E_0$

Use the dielectric boundary conditions to calculate the electric field E_i , inside the teflon, the polarization flux density \underline{P} and the electric flux density D_i inside the teflon. (Assume ρ_s , the surface charge density is zero).

$$D_{n1} = \epsilon_0 E_{n1} = \epsilon_0 E_0 = D_{n2} = \epsilon_0 \epsilon_r E_{in}$$

$$D_{n_2} = \epsilon_0 E_{in} + P_{in} \quad |$$

$$P_{in} = D_{n_2} - \epsilon_0 E_{in}$$

$$= \epsilon_0 (E_{i_0} - E_{in})$$

$$= 0.524 \epsilon_0 E_0 \quad |$$

$$D_i = D_0 = \epsilon_0 E_0 \quad \checkmark \quad |$$