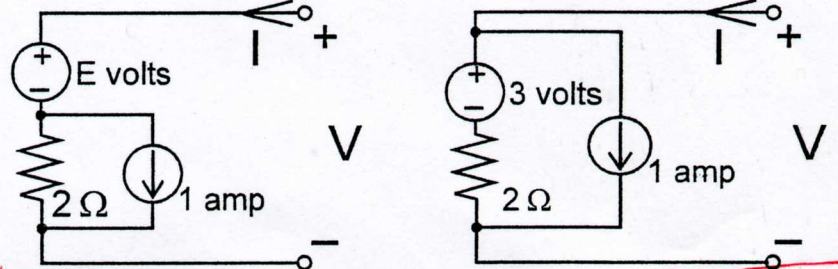



MID-TERM EXAMINATION

Do all work in this examination packet. There are four questions. Each counts 25 points. Good luck!

1A. (5 points) Find the value of E for which the two one-ports shown to the right have the same V vs. I relations.



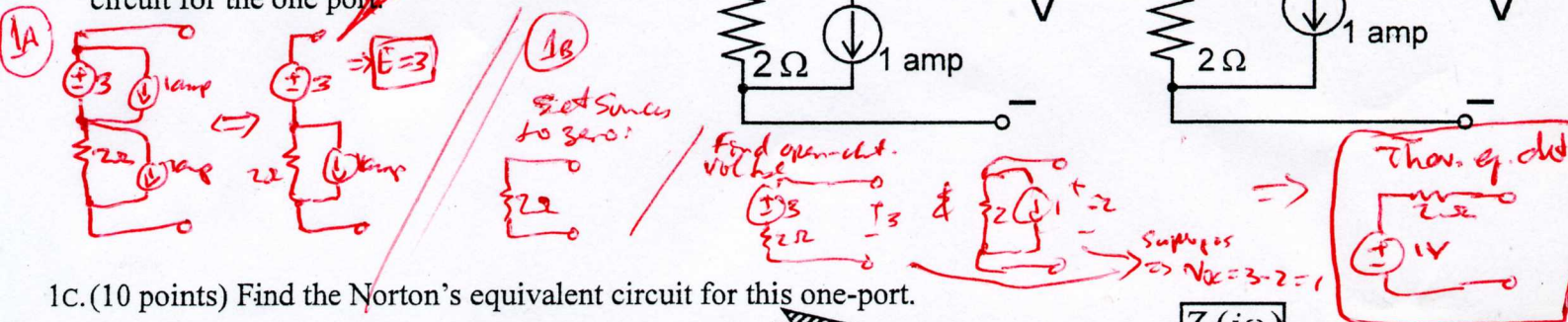1B. (5 points) Find the Thevenin's equivalent circuit for the one port.




1C. (10 points) Find the Norton's equivalent circuit for this one-port.


Set $I_1 = 0$ & $V_2 = 0$ to get Z_{Norton} :



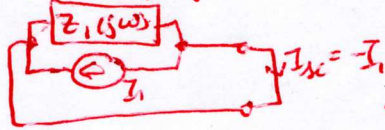
Use Superposition to get I_{Norton} : 1) Turn on I_1 only ($V_2 = 0$)



2) Turn on V_2 only ($I_1 = 0$)

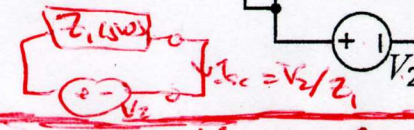

So: $I_{sc} = \frac{V_2}{Z_1} - I_1$


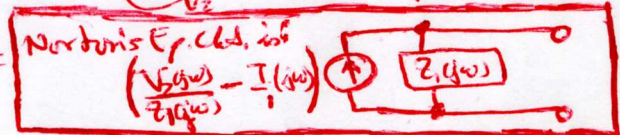


1D. (5 points) Network N contains only linear resistors. Determine the value of R.

	(1)	(2)	(3)	(4)
V	-2R	20	2	12
I	2	5	-1	-3

	(1)	(2)	(3)	(4)
V	6	-100	5	-16
I	-7	-30	-5/2	4

leave ports (3) & (4) inside

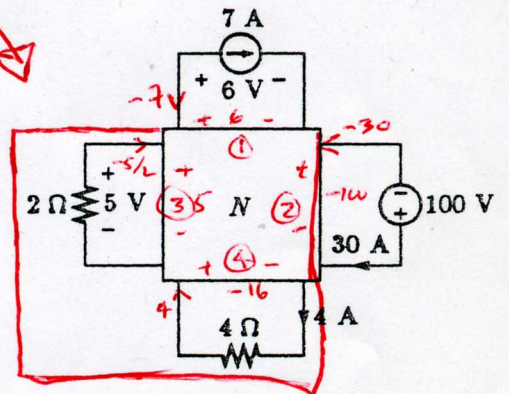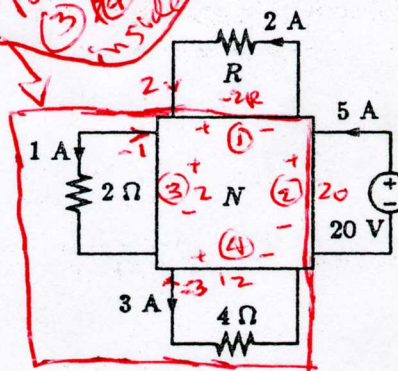



$$\begin{matrix} \vec{V} \times \vec{I} \\ (-7)(-2R) = 600 & \begin{matrix} -5 & 48 \\ -5 & 48 \end{matrix} \\ \vec{V} \times \vec{I} \\ 12 & -500 \end{matrix}$$

Ports (3) & (4) are unnecessary!

$$(1A)R - 600 = 12 - 500 \Rightarrow 14R = 112 \Rightarrow R = \frac{112}{14} = 8$$

R=8

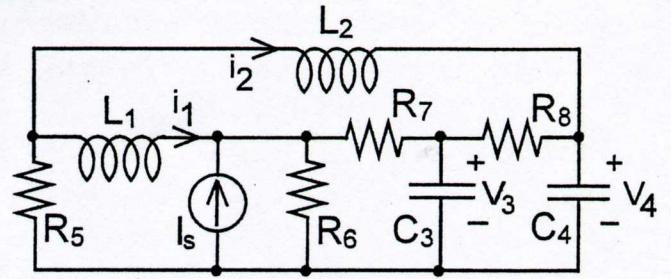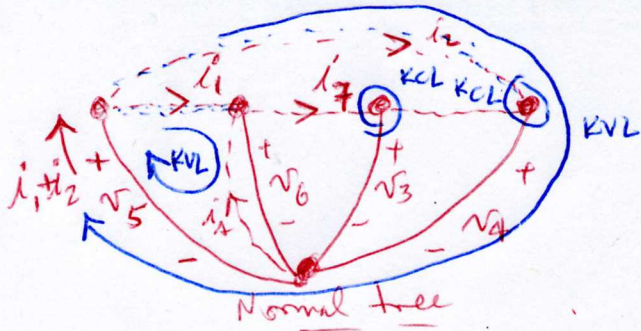2. (25 points) Write state equations for this circuit.



$$\begin{aligned} L_1 \frac{di_1}{dt} &= -R_5(i_1+i_2) - v_6 \\ L_2 \frac{di_2}{dt} &= -R_5(i_1+i_2) - v_4 \\ C_3 \frac{dv_3}{dt} &= i_7 + \frac{1}{R_8}(v_4-v_3) \\ C_4 \frac{dv_4}{dt} &= i_2 + \frac{1}{R_8}(v_3-v_4) \end{aligned}$$

We (just) need to express v_6 & i_7 in terms of the state variables (v_3, v_4, i_1, i_2).

One more KCL:

$$i_7 + \frac{1}{R_6}v_6 = i_1 + i_s \quad (A)$$

One more KVL:

$$i_7 R_7 + v_3 = v_6 \quad (B)$$

Substituting v_6 from (B) into (A) gives:

$$i_7 + \frac{R_7}{R_6}i_7 + \frac{1}{R_6}v_3 = i_1 + i_s$$

$$\Rightarrow i_7 = \left(\frac{R_6}{R_6+R_7}i_1 - \frac{1}{R_6+R_7}v_3 + \frac{R_6}{R_6+R_7}i_s \right) \quad (C)$$

Then, putting (C) into (B) gives:

$$v_6 = v_3 + \frac{R_6 R_7}{R_6+R_7}i_1 - \frac{R_7}{R_6+R_7}v_3 + \frac{R_6 R_7}{R_6+R_7}i_s = \left(\frac{R_6}{R_6+R_7}v_3 + \frac{R_6 R_7}{R_6+R_7}i_1 + \frac{R_6 R_7}{R_6+R_7}i_s \right)$$


$$\begin{cases} L_1 \frac{di_1}{dt} = -R_5 i_1 - R_5 i_2 - \frac{R_6}{R_6+R_7}v_3 - \frac{R_6 R_7}{R_6+R_7}i_1 - \frac{R_6 R_7}{R_6+R_7}i_s \\ L_2 \frac{di_2}{dt} = -R_5 i_1 - R_5 i_2 - v_4 \\ C_3 \frac{dv_3}{dt} = \frac{R_6}{R_6+R_7}i_1 - \frac{1}{R_6+R_7}v_3 - \frac{1}{R_8}v_3 + \frac{1}{R_8}v_4 + \frac{R_6}{R_6+R_7}i_s \\ C_4 \frac{dv_4}{dt} = i_2 + \frac{1}{R_8}v_3 - \frac{1}{R_8}v_4 \end{cases}$$

$$\frac{d}{dt} \begin{pmatrix} i_1 \\ i_2 \\ v_3 \\ v_4 \end{pmatrix} = \begin{bmatrix} -\frac{(R_5+R_6||R_7)}{L_1} & -\frac{R_5}{L_1} & -\frac{R_6}{L_1(R_6+R_7)} & 0 \\ -\frac{R_5}{L_2} & -\frac{R_5}{L_2} & 0 & -\frac{1}{C_3} \left(\frac{1}{R_6+R_7} + \frac{1}{R_8} \right) \\ \frac{R_6}{C_3(R_6+R_7)} & 0 & \frac{1}{C_3 R_8} & -\frac{1}{C_3 R_8} \\ 0 & \frac{1}{C_4} & -\frac{1}{C_4 R_8} & 0 \end{bmatrix} \begin{pmatrix} i_1 \\ i_2 \\ v_3 \\ v_4 \end{pmatrix} + \begin{pmatrix} -\frac{R_6||R_7}{L_1} \\ 0 \\ \frac{R_6}{C_3(R_6+R_7)} \\ 0 \end{pmatrix} i_s$$

3A. (5 points) This circuit is in the sinusoidal steady state. Find the voltage (phasor) V_{AB} (i.e., $V_A - V_B$).

Notice that the inductor jX_L is irrelevant because no current flows through it!

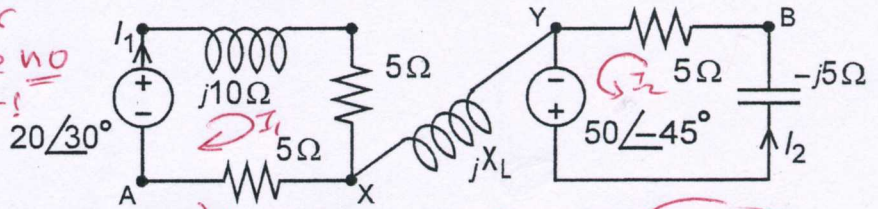Thus, its $\frac{di}{dt} = 0 \Rightarrow V_{XY} = 0$



Now, $20\angle 30^\circ = (10 + j10)I_1 \Rightarrow I_1 = \frac{20\angle 30^\circ}{10\sqrt{2}\angle 45^\circ} = \frac{2}{\sqrt{2}}\angle -15^\circ = \sqrt{2}\angle -15^\circ$

Also, $50\angle 45^\circ = I_2(5 - j5) \Rightarrow I_2 = \frac{50\angle 45^\circ}{5\sqrt{2}\angle -45^\circ} = \frac{10}{\sqrt{2}}$

And $V_{AB} = (V_A - V_X) + (V_X - V_Y) + (V_Y - V_B) = (-5I_1) + 0 + (-5I_2) = -5(I_1 + I_2) = -5\left(\frac{10}{\sqrt{2}} + \sqrt{2}\angle -15^\circ\right)$
 $= -\left(\frac{50}{\sqrt{2}} + 5\sqrt{2}[\cos 15^\circ - j\sin 15^\circ]\right) = -(35.3553 + 6.8301 - j1.8301) = -42.1855 + j1.8301$

$V_{AB} = 42.225\angle +177.52^\circ$

3B. (20 points)

a) In this circuit, calculate the complex power supplied by each source.

b) Calculate the total complex power absorbed by the circuit elements. (Hence, verify the part a answer.)

a) Writing mesh equations:

$3I_1 + j4(I_1 - I_2) = 10\angle 0^\circ$

and $j4(I_2 - I_1) - j2I_2 + 2I_1 = 0$

$(3 + j4)I_1 - j4I_2 = 10$

$(2 - j4)I_1 + j2I_2 = 0$

Adding twice 2nd row to 1st row $\Rightarrow (7 - j4)I_1 = 10 \Rightarrow I_1 = \frac{10}{7 - j4}$

$= \frac{10(7 + j4)}{49 + 16} = \frac{70 + j40}{65} = \frac{14 + j8}{13}$. That is $I_1 = \frac{14 + j8}{13} = 1.240\angle 29.7^\circ A$

\therefore From 2nd mesh eqn: $j2I_2 = -(2 - j4)I_1 \Rightarrow I_2 = \frac{-(2 - j4)}{j2} I_1 = \frac{j4 - 2}{j2} I_1 = (2 + j)I_1$

$\therefore I_2 = (2 + j)(14 + j8)/13 = (28 + j14 + j16 - 8)/13 \Rightarrow I_2 = \frac{20 + j30}{13} = 2.774\angle 56.31^\circ A$

Complex Power Supplied by V_1 source:

$S_1 = \frac{1}{2} V_1 I_1^* = \frac{1}{2} (10\angle 0^\circ) (1.240\angle -29.7^\circ) = \frac{1}{2} 12.40\angle -29.7^\circ = 5.383 - j3.077 VA$

Complex Power Supplied by controlled source:

$S_2 = \frac{1}{2} (V_2) (-I_2^*) = -\frac{1}{2} 2I_1 I_2^* = -(1.240\angle 29.7^\circ) (2.774\angle -56.31^\circ) = -3.440\angle -26.565^\circ = -3.077 + j1.538 VA$

b) $P_{3\Omega} = \frac{1}{2} |I_1|^2 \times 3 = 2.308 W$

$Q_{j4\Omega} = \frac{1}{2} (j |I_1 - I_2|^2 \times 4) = j6.154 VAR$

$Q_{-j2\Omega} = \frac{1}{2} (-j |I_2|^2 \times 2) = -j7.692 VAR$

and, from (a): $S_1 + S_2 = 2.306 - 1.539 VA \approx 2.308 - j1.538 VA$

Complex power absorbed is:

$S = 2.308 + j6.154 - j7.692$

$= 2.308 - j1.538 VA$

7.692
-6.154
TSB

Answer to (b)

Answer to (a)

4. (25 points)

In this circuit, find the complex phasors: (a) I_2 , (b) I_1 , and (c) I_R .(a) Writing voltage/current relations for the coupled coils:

$$\hat{V}_1 = \hat{I}_1(j\omega(0.1)) + \hat{I}_2(j\omega(0.01)) \quad (1)$$

$$\hat{V}_2 = \hat{I}_2(j\omega(0.001)) + \hat{I}_1(j\omega(0.01))$$

Using KVL in the secondary loop:

$$0 = \hat{I}_2(5 + j\omega(0.001)) + \hat{I}_1(j\omega(0.01)) \quad (2)$$

$$\hat{V}_1 = 500 \hat{I}_R \quad (3)$$

$$\hat{I}_1 + \hat{I}_R = 4 \angle 0^\circ \text{ mA} = 0.004 \angle 0^\circ \text{ A} \quad (4)$$

$$\Rightarrow \hat{I}_R = 0.004 - \hat{I}_1 \quad (5) \quad \leftarrow \text{Amps}$$

Putting (5) into (3) gives \hat{V}_1 as a function of \hat{I}_1 :

$$\hat{V}_1 = 500(0.004 - \hat{I}_1) = 2 - 500 \hat{I}_1 \quad (6)$$

Substituting \hat{V}_1 in (1) by using (6): $2 - 500 \hat{I}_1 = j\omega(0.1) \hat{I}_1 + j\omega(0.01) \hat{I}_2$

$$\Rightarrow \hat{I}_1 = [2 - \hat{I}_2(j\omega(0.01))] / [500 + (0.1)j\omega] \quad (7)$$

Substituting for \hat{I}_1 in (2), using (7):

$$0 = (5 + j\omega(0.001)) \hat{I}_2 + j\omega(0.01) (2 - j\omega(0.01) \hat{I}_2) / [500 + j\omega(0.1)] \Rightarrow \hat{I}_2 = \frac{-j\omega(0.02)}{2500 + j\omega}$$

Since the current source is $4 \cos \omega t = 4 \cos 5000t$, we have $\omega = 5000$

$$\therefore \hat{I}_2 = \frac{-j100}{2500 + j5000} = \frac{-j}{25 + j50} = \frac{1 \angle -90^\circ}{56.1 \angle 63.43^\circ} = \boxed{17.9 \angle -153.4^\circ \text{ mA}}$$

$$(b) \text{ Putting } \hat{I}_2 \text{ into (2): } 0 = \hat{I}_2(5 + j5) + j50 \hat{I}_1 \Rightarrow \hat{I}_1 = \frac{-(5 + j5) \hat{I}_2}{j50}$$

$$\Rightarrow \hat{I}_1 = \left(\frac{8}{25 + j50} \right) \left(\frac{5 + j5}{j50} \right) = \frac{-5 + j5}{-2500 + j1250} = \frac{-1 + j1}{-500 + j250} = \frac{\sqrt{2} \angle 135^\circ}{(250) \angle -26.6^\circ}$$

$$= \frac{\sqrt{2} \angle 135^\circ}{(250) \sqrt{5} \angle -26.6^\circ} = \boxed{2.53 \angle -18.4^\circ \text{ mA}}$$

$$(c) \text{ Putting } \hat{I}_1 \text{ into (5): } \hat{I}_R = (4 - 2.53 \angle -18.4^\circ) \text{ mA}$$

$$= 4 - 2.53 \cos(18.4^\circ) + j2.53 \sin(18.4^\circ)$$

$$= 1.6 + j0.8 = \boxed{1.79 \angle 26.6^\circ \text{ mA}}$$

