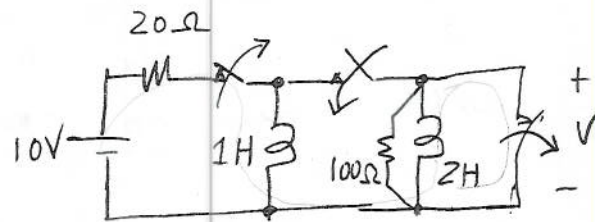


[10]

1. The circuit shown is at equilibrium for a long time. At  $t=0$ , the switches are thrown as indicated.




- (a) What is  $v(t=0_+)$ ? (b) How much energy is eventually dissipated in the resistor (as  $t \rightarrow \infty$ )?

Part A: At steady-state ( $t < 0$ ):

Current will flow through the inductor and completely bypass the  $100\ \Omega$  resistor and  $2H$  inductor since:



- Inductors act as short circuits at steady state when DC voltages are applied
- Current always flow through the path of least resistance

Steady-state ( $t < 0$ ):

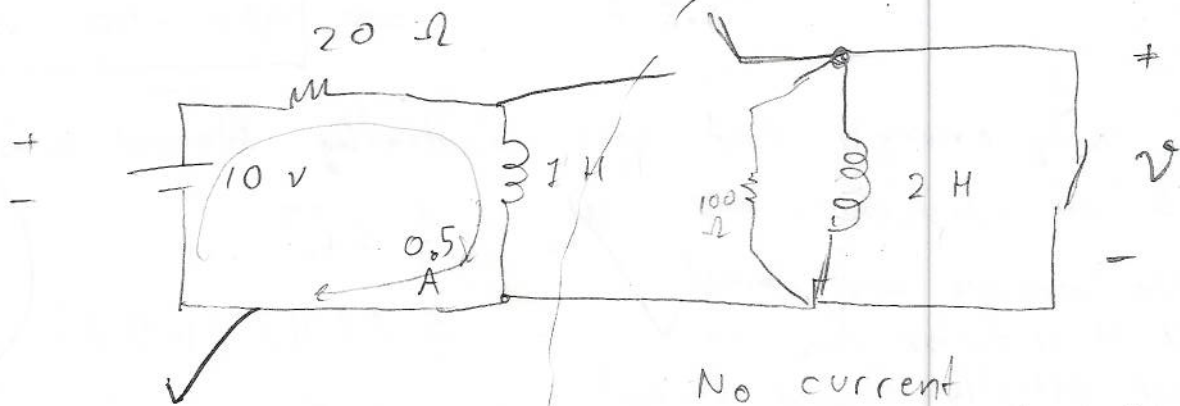

No current enters this dotted region of network

2.  
[15]

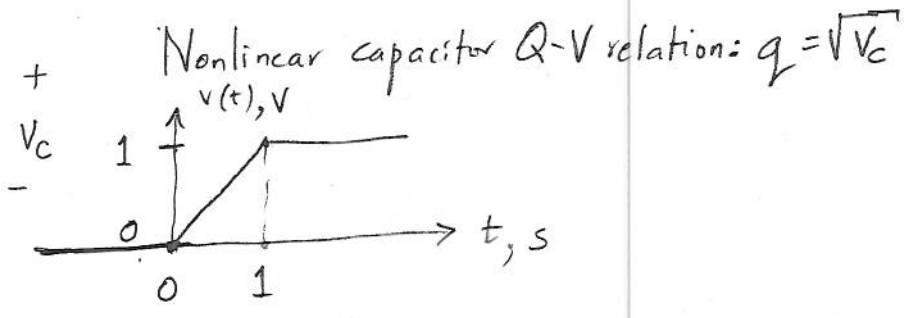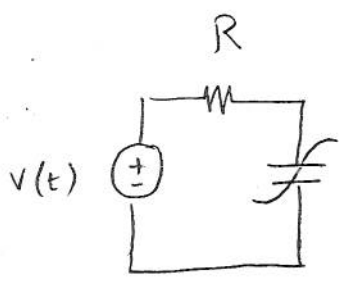

As  $t \rightarrow \infty$ , (a) What is  $V_c$ ?  
 (b) How much energy is stored in the capacitor?

Part A: As  $t \rightarrow \infty$ , which implies steady-state, the capacitor will be fully charged, and no current will run through the circuit any longer.  $\Rightarrow i(t) = 0, V_R(t) = 0$

$$\Rightarrow \lim_{t \rightarrow \infty} V_c(t) = \lim_{t \rightarrow \infty} v(t) = 1$$

$$\Rightarrow \boxed{\text{As } t \rightarrow \infty, V_c(t) = 1 \text{ V}}$$

Part B:

$$i(t) = \frac{dq}{dt} = \frac{1}{2} \left( \frac{1}{\sqrt{V_c}} \right) \cdot \frac{dV_c}{dt}$$

$$\Rightarrow p(t) = i(t) \cdot v(t) = \frac{1}{2} V_c(t)^{1/2} \frac{dV_c}{dt}$$

Energy stored in capacitor

$$= \int_{-\infty}^{+\infty} p(t) dt = \frac{1}{2} \int_{-\infty}^{+\infty} V_c(t)^{1/2} dV_c$$


(Assuming that  $V_c(t)$  at  $t = -\infty = 0$ , which means that capacitor was uncharged)

$$= \frac{1}{2} \cdot \frac{2}{3} \cdot \left( V_c(t)^{3/2} \Big|_{t=-\infty}^{t=+\infty} \right) = \frac{1}{3} (1 - 0) = \frac{1}{3} \text{ J}$$

$\Rightarrow$  Energy stored =  $\frac{1}{3}$  J

15

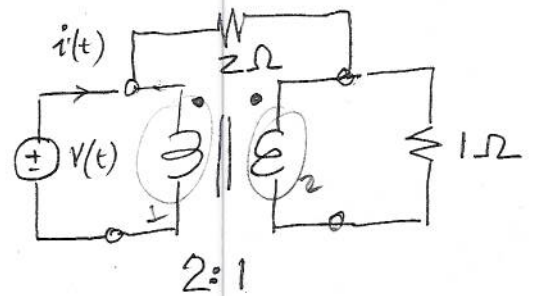3. This circuit uses an ideal transformer with a 2:1 turns ratio. (The two coils share a common flux, and their self inductance  $\rightarrow \infty$ ).



The voltage source  $v(t)$  perceives a resistance  $R = \frac{v(t)}{i(t)}$ .  
What is  $R$ ?

For an ideal transformer,  $\phi$  is the same through each turn of the coils.

$\Rightarrow$

$$\frac{v_1}{N_1} = \frac{d\phi}{dt}$$


$$\frac{v_2}{N_2} = \frac{d\phi}{dt}$$

$$\Rightarrow \frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$\Rightarrow \frac{v_1(t)}{v_2(t)} = \frac{N_1}{N_2} = \frac{2}{1}$$

$$\Rightarrow v_1(t) = 2v_2(t)$$
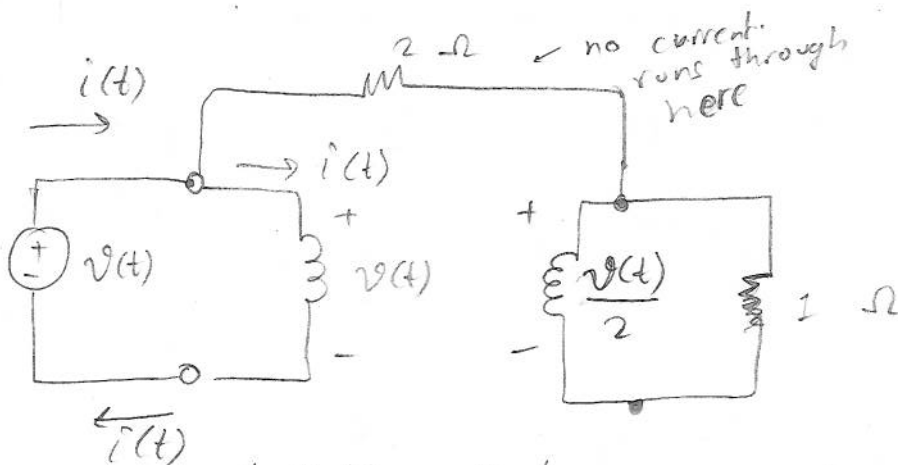
$$v \cdot i = \frac{v \cdot v}{R \cdot v}$$





$$i(t) \cdot v(t) = 1 \Omega \cdot i_2(t)$$

Notice that the voltage source  $v(t)$  has current  $i(t)$  entering/leaving it.  $\Rightarrow$


No current enters/leaves the  $2 \Omega$  resistor.

★ Now, we use energy considerations to find a relationship between  $i(t)$  and  $v(t)$ .  
(next page)


4. Find  $V_x$  and  $i_x$   
[20]

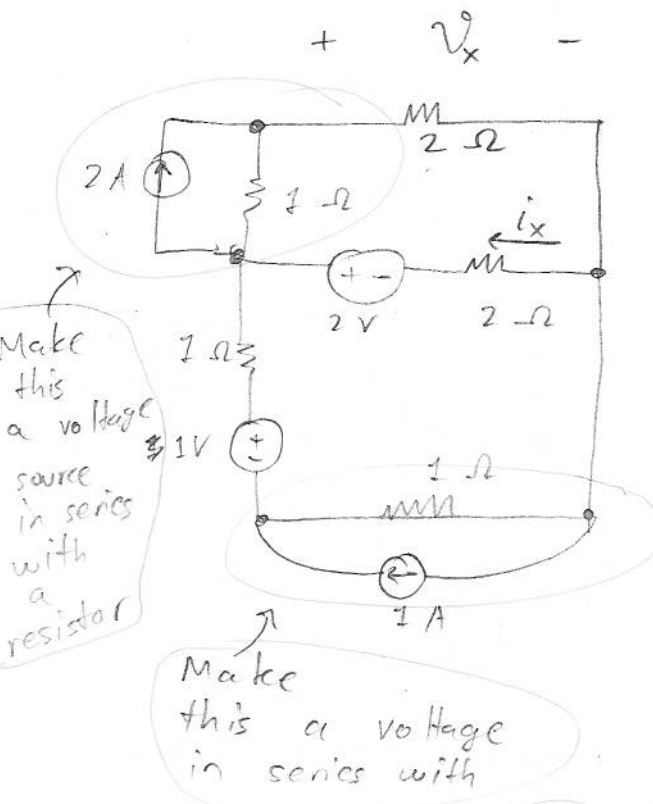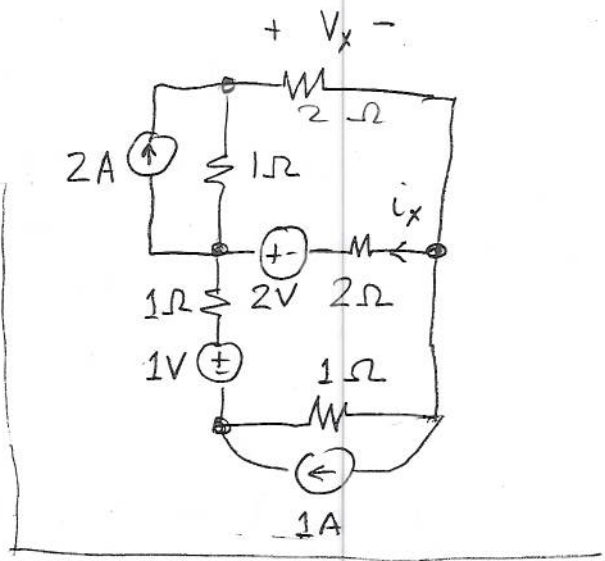

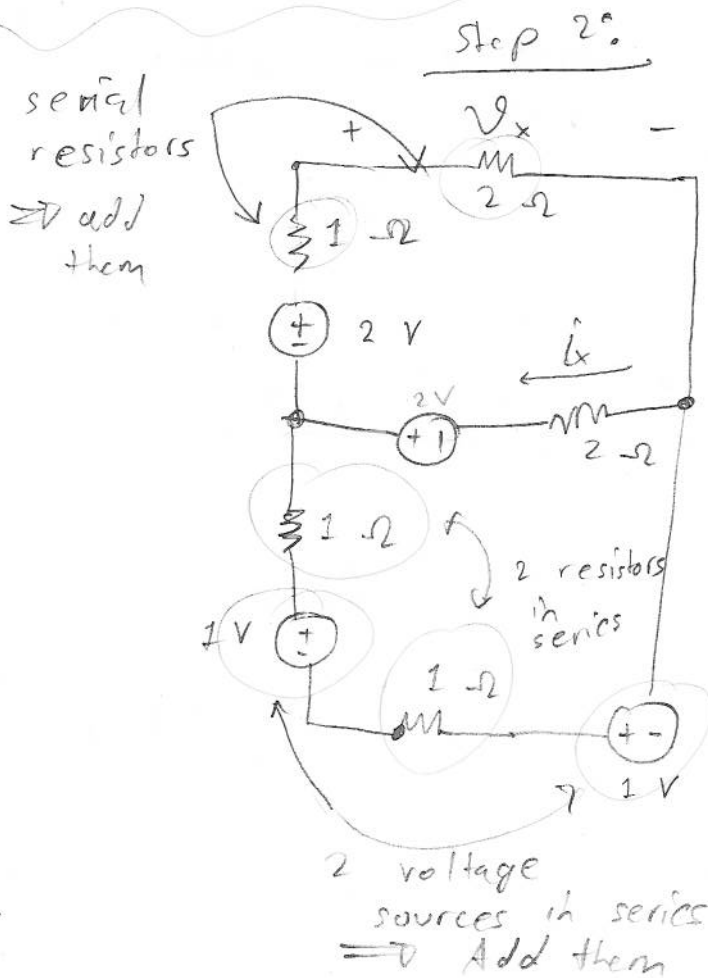★ We can use source transformations to greatly simplify the circuit.



⇒ We can now simplify loop 2:

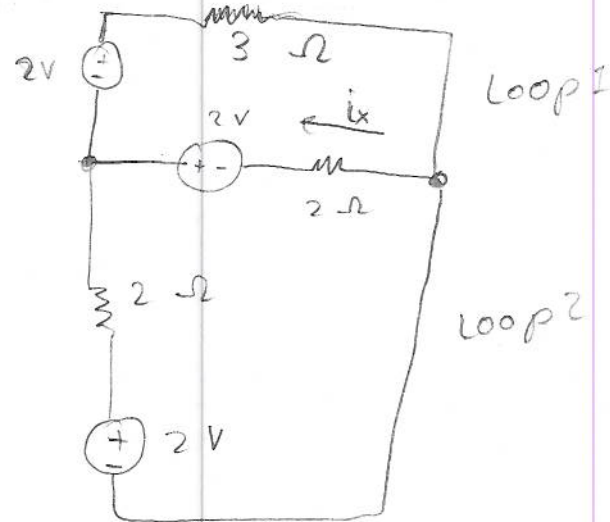


Notice that once we solve for current  $i_x$  in loop 1.

next page

To solve for  $v_x$ , look at Loop 1

at step 2:

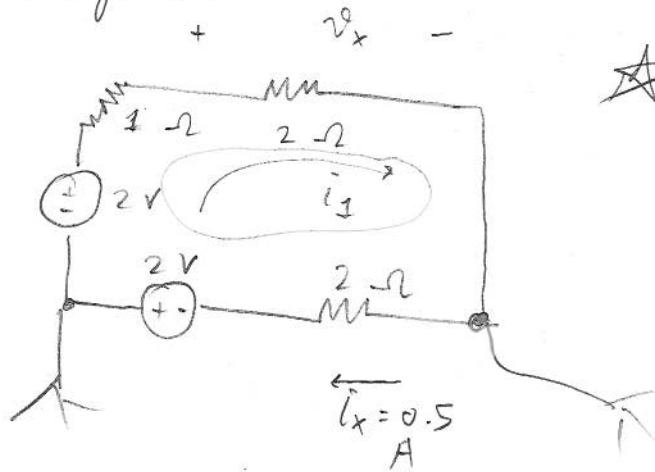

★ Use KVL to solve for  $i_1$ , then we know  $v_x = (2\ \Omega) \cdot i_1$  (we already know  $i_x = 0.5\ \text{A}$ )

KVL:

$$-2\left(\frac{1}{2}\right) + 2 + 2 - i_1 - 2i_1 = 0$$

$\Rightarrow$

$$-1 + 2 + 2 - 3i_1 = 0 \Rightarrow 3i_1 = 3$$

$$\Rightarrow i_1 = 1\ \text{A}$$

20  $\Rightarrow$

$$v_x = +(2\ \Omega) \cdot i_1$$

$$= 2\ \Omega \times 1\ \text{A}$$

$$v_x = +2\ \text{V}$$

$\Rightarrow$

$$i_x = +0.5\ \text{A}$$

$$v_x = +2\ \text{V}$$

with given polarities and directions