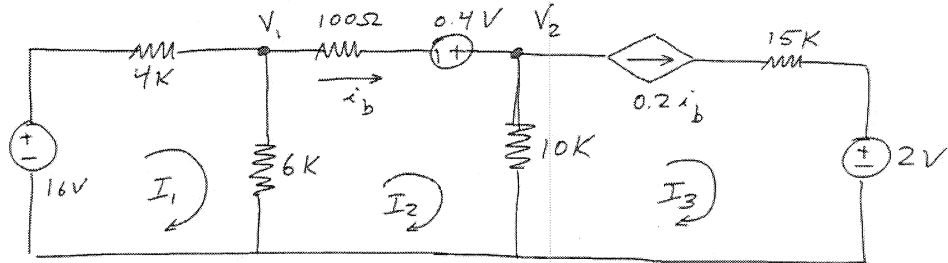


Problem 1.

10 pts

For the circuit given below, write, but do not solve, the equations for both the Mesh Current Method and the node Voltage Method.



$$I_1: -16 + 4k(I_1) + 6k(I_1 - I_2) = 0$$

$$10kI_1 - 6kI_2 = 16$$

$$I_2: 100I_2 - .4 + 10k(I_2 - I_3) + 6k(I_2 - I_1) = 0$$

$$-6kI_1 + 16,100I_2 - 10kI_3 = 0.4$$

$$I_3: \cancel{15k(0.2I_3) + 2 + 10k(I_3 - I_2) = 0} \quad I_3 = 0.2i_b = 0.2I_2$$

$$\cancel{2kI_2 - (I_2)(10k) + 10kI_3 = -2}$$

$$\cancel{-7kI_2 + 10kI_3 = -2}$$

$$V_1: \frac{V_1 - 16}{4k} + \frac{V_1}{6k} + \frac{V_1 - V_2 + 0.4}{100} = 0$$

$$125V_1 - 120V_2 = 0$$

$$V_2: \frac{V_2 - .4 - V_1}{100} + \frac{V_2}{10k} + 0.2i_b = 0$$


$$i_b = \frac{V_1 - V_2 + .4}{100} \rightarrow .2i_b = \frac{V_1 - V_2 + .4}{500}$$

$$-80V_1 + 81V_2 = 32$$

10 pts

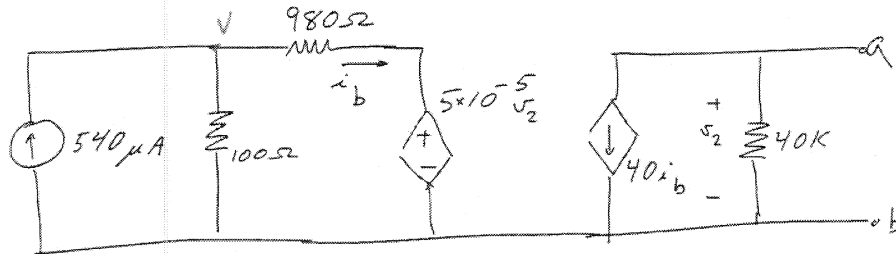Problem 2.

Find both the Norton and the Thevenin equivalent circuits with respect to the terminals *ab*.



$$V_{oc} = 40k(-40i_b) = V_2$$

$$-540\mu A + \frac{V}{100} + i_b = 0$$

$$i_b = \frac{V - (5 \times 10^{-5})(40k)(-40i_b)}{980}$$

$$980i_b = V + 80i_b$$

$$900i_b = V$$

$$i_b = \frac{V}{900}$$

$$-540\mu A + \frac{V}{100} + \frac{V}{900} = 0$$

$$V = .0486$$

$$i_b = \frac{V}{900} = 54\mu A$$

$$V_{oc} = V_{TH} = (40k)(-40)(54\mu A) = -86.4V$$


$$I_{sc} = -40i_b$$

$$i_b = \frac{(540\mu A) \left(\frac{100}{980+100} \right)}{1} = 50\mu A$$


$$I_{sc} = -2mA$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{86.4}{.002} = 43,200 \Omega$$

Thevenin:

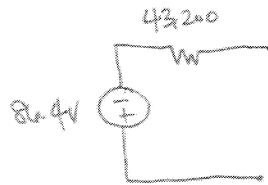

Norton:

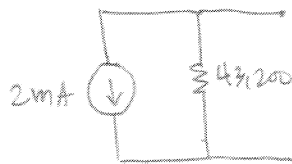

10 pts


Problem 3.

For the circuit shown below R_o is varied until it absorbs the maximum power from the circuit

7 pts (a) Find R_o

3 pts (b) Find the maximum power being transferred to R_o .

V_{Test} Method:

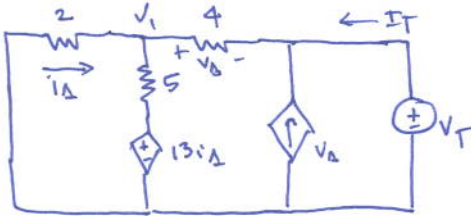

$$\frac{v_1}{2} + \frac{v_1 - 13i_\Delta}{5} + \frac{v_1 - v_T}{4} = 0$$

$$i_\Delta = -\frac{v_1}{2}$$

$$\frac{v_1}{2} + \frac{v_1 - 13(-v_1/2)}{5} + \frac{v_1 - v_T}{4} = 0$$

$$\frac{v_1}{2} + \frac{v_1}{5} + \frac{13v_1}{10} + \frac{v_1}{4} = \frac{v_T}{4}$$

$$\frac{9v_1}{4} = \frac{v_T}{4}$$

$$v_1 = \frac{v_T}{9}$$


$$v_\Delta = \frac{v_T}{9} - v_T = -\frac{8v_T}{9}$$

$$I_T = -v_\Delta + \frac{v_T - v_T/9}{4}$$

$$I_T = \frac{8v_T}{9} + \frac{2v_T}{9}$$

$$I_T = \frac{10v_T}{9}$$
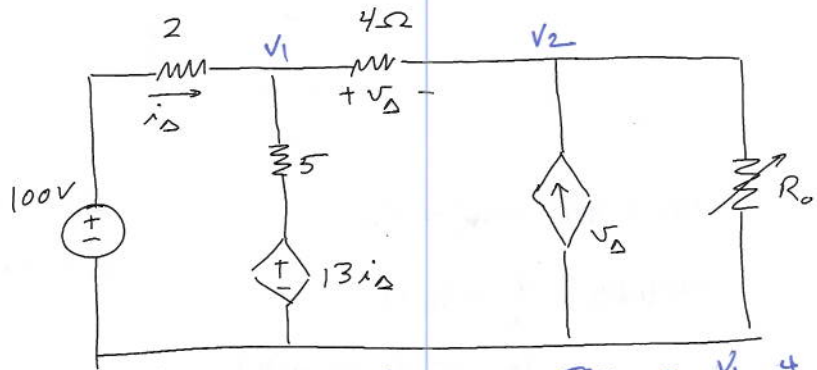
$$\frac{v_T}{I_T} = .9\Omega = R_{TH} = R_o$$



Alt: Voc, another option

$$\frac{v_1 - 100}{2} + \frac{v_1 - 13i_\Delta}{5} + \frac{v_1 - v_2}{4} = 0$$

$$i_\Delta = \frac{100 - v_1}{2}$$

$$\textcircled{1} \frac{v_1 - 100}{2} + \frac{v_1 - 13(\frac{100 - v_1}{2})}{5} + \frac{v_1 - v_2}{4} = 0$$

$$\frac{v_2 - v_1}{4} - v_\Delta = 0$$



$$v_\Delta = v_1 - v_2$$

$$\frac{v_2 - v_1}{4} - v_1 + v_2 = 0$$

$$\textcircled{2} 5v_2 = 5v_1 \rightarrow v_1 = v_2$$

$$\frac{v_2 - 100}{2} + \frac{v_2 - 13(\frac{100 - v_2}{2})}{5} + 0 = 0$$

$$v_2 = 90V = V_{TH}$$

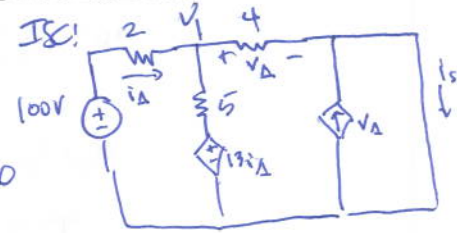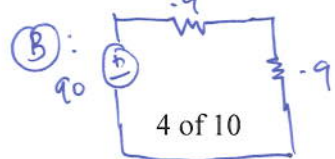

$$\frac{v_1 - 100}{2} + \frac{v_1 - 13i_\Delta}{5} + \frac{v_1}{4} = 0$$

$$i_\Delta = \frac{100 - v_1}{2}$$

$$v_1 = 80V$$

$$v_\Delta = 80V$$

$$I_{sc} = \frac{v_1}{4} + v_\Delta = 20 + 80$$

$$= 100A$$







$$R_{TH} = \frac{V_{oc}}{I_{sc}} = .9\Omega$$

$$P_{transferred} = \frac{V_o^2}{R} = \frac{(45)^2}{.9} = 2250W$$

10 pts

Problem 4.

Find i_o .

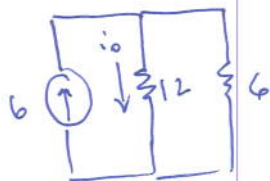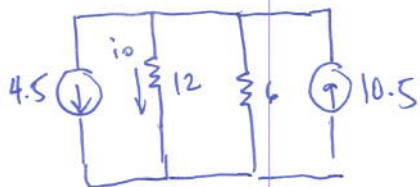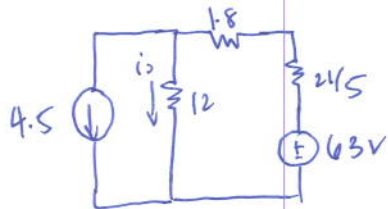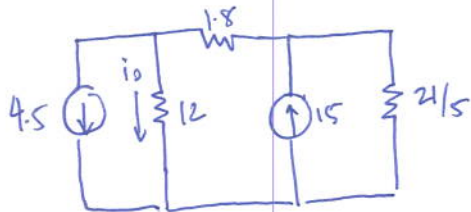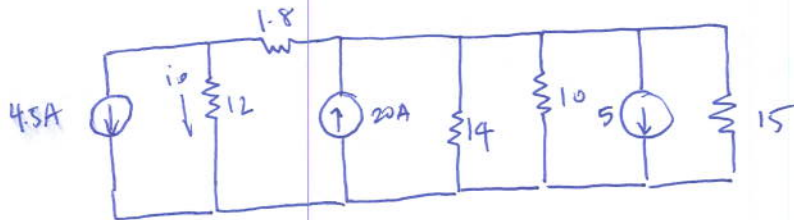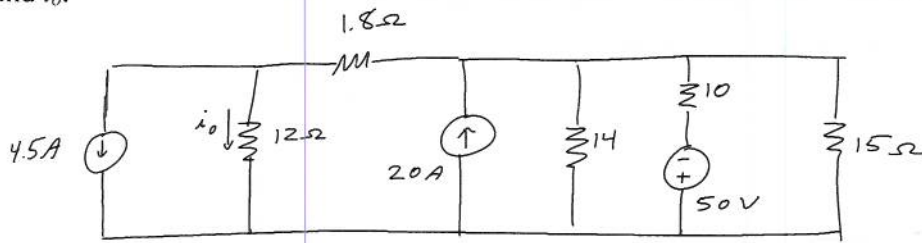

$$i_o = \frac{6(6)}{18} = \underline{2A}$$



10 pts

Problem 5.

Assume a **real Op-Amp** operating in the linear region. With

$R_{in} = 110K$; $R_o = 0 K$; $A = 1000$

Calculate v_o/v_g .

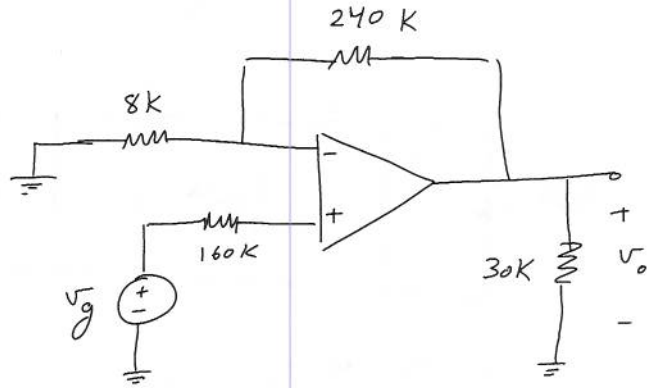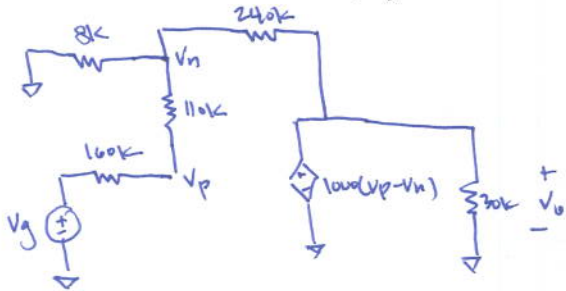

$$\textcircled{1} \frac{v_n - v_g}{240k} + \frac{v_n}{8k} + \frac{v_n - v_o}{240k} = 0$$

$$\textcircled{2} v_o = 1000(v_p - v_n) \quad \text{Solve for } v_n$$

$$\textcircled{3} v_p = v_g - 160k \left(\frac{v_g - v_n}{240k} \right) \quad \text{plug in } v_n$$

$$v_n = v_g - \frac{27v_o}{11000}$$

$$\frac{31v_g}{240k} = \frac{11861v_o}{2.64 \times 10^9}$$

$$\frac{v_o}{v_g} = 28.75$$

10 pts

Problem 6.


Assuming ideal Op-Amps

5 pts

a) Find i_a

5 pts

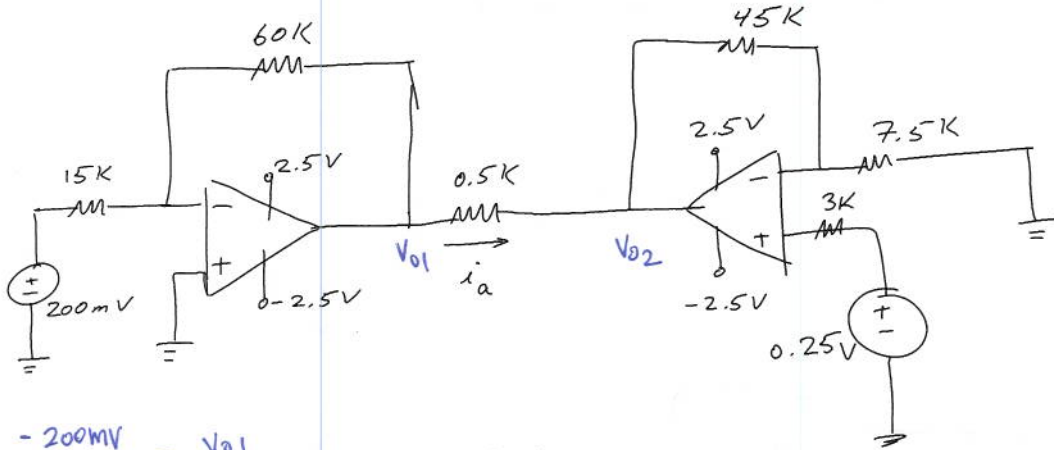b) For what value of the left source is $i_a = 0$?



$$\frac{-200\text{mV}}{15\text{k}} - \frac{V_{01}}{60\text{k}} = 0$$

$$V_{01} = -0.8\text{V}$$

$$\frac{0.25 - V_{02}}{45\text{k}} + \frac{0.25}{7.5\text{k}} = 0$$

$$V_{02} = 1.75\text{V}$$

$$A. \quad i_a = \frac{V_{01} - V_{02}}{500} = \frac{-0.8 - 1.75}{500} = \underline{-5.1\text{mA}}$$

$$B. \quad V_{01} = 1.75$$

$$\frac{-x}{15\text{k}} - \frac{1.75}{60\text{k}} = 0$$

$$V_s = -0.4375\text{V}$$

10 pts

Problem 7.The two series connected capacitors are connected to the terminals of a black box at $t=0$.The resulting current $i(t) = 900e^{-2500t} \mu\text{A}$

5 pts



a) Find $v_o(t)$ for $t \geq 0$;

2 pts

b) How much energy was initially stored in C_1 and C_2 ?

3 pts

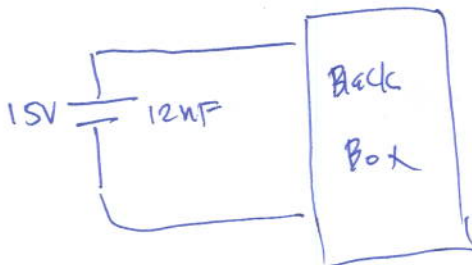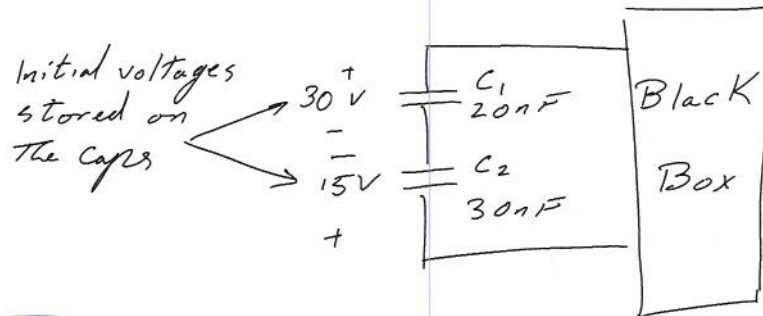c) What is the equivalent resistance of the black box?



$$v(t) = \frac{1}{C} \int_0^t i dt + v(t_0)$$

$$= \frac{1}{12\text{nF}} \int_0^t 900e^{-2500t} dt + 15$$

$$= -30e^{-2500t} + 15 + 30$$

$$v(t) = 45 - 30e^{-2500t} \text{ V}$$

A. $v_o(t) = 45 - 30e^{-2500t}$

B. $W_{\text{cap}} = \frac{1}{2} C v^2$

$$C_1 = \frac{1}{2} (20\text{nF}) (30)^2 = 9 \mu\text{J}$$

$$C_2 = \frac{1}{2} (30\text{nF}) (15)^2 = 3.375 \mu\text{J}$$

C. $\frac{1}{C_{\text{eq}} R_{\text{eq}}} = 2500$


$$C_{\text{eq}} = 12 \text{ nF}$$

$$R_{\text{eq}} = \underline{33,333.3 \Omega}$$

10 pts

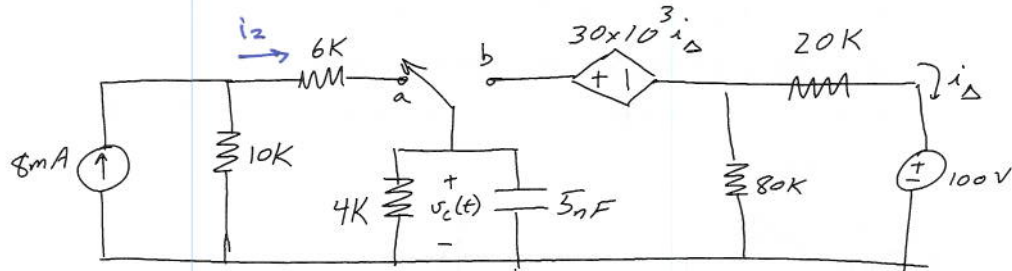
Problem 8.

The switch has been at location a for a long time. At $t=0$, the switch moves to b. find $v_o(t)$ for $t \geq 0$;



$$V_o(0) = \frac{(8mA)(10k)}{10k + 10k} = i_2 = 4mA$$

$$V_o(0) = (4mA)(4k) = 16V$$

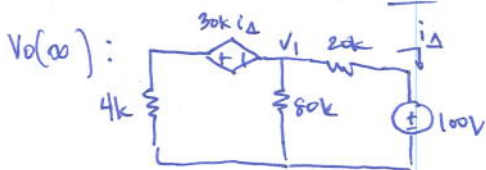

$$\frac{v_1 + (90k)(i_D)}{4k} + \frac{v_1}{80k} + \frac{v_1 - 100}{20k} = 0$$


$$i_D = \frac{v_1 - 100}{20k}$$

$$v_1 = 61.81V$$

$$i_D = -1.9mA$$


$$\begin{aligned} V_o(\infty) &= 61.81 + 30k(i_D) \\ &= 61.81 - 57.27 \\ &= \underline{4.55V} \end{aligned}$$

$$C = 5nF$$

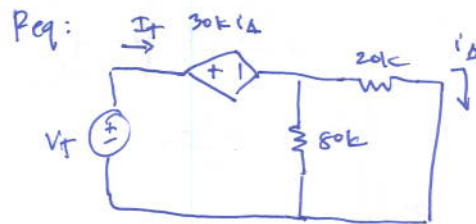

$$i_D = \frac{I_T(80k)}{100k} = 0.8 I_T$$

$$80k || 20k = 16k$$

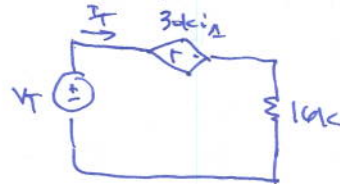

$$V_T = 30k(0.8 I_T) + 16k I_T$$

$$R_{TH} = \frac{V_T}{I_T} = 40k\Omega$$

$$R_{eq} = 4k || 40k = 3636.36\Omega$$

$$\frac{1}{RC} = 55000$$

$$V(t) = V_f + (v_i - v_f)e^{-t/\tau}$$

$$= 4.55 + (16 - 4.55)e^{-55000t}$$

$$V(t) = 4.55 + 11.45e^{-55000t} V$$

10 pts

Problem 9.


There is no energy stored on the capacitors at the instant the two switches are closed

5 pts a) Express $v_o(t)$ as a function of v_a , v_b , R , and C .

5 pts b) How long will it take to saturate the amplifier if

$R=40K$ $C=25\text{ nF}$ $v_a=10\text{ mV}$ $v_b=60\text{ mV}$
 $V_{cc}=12V$

7.91

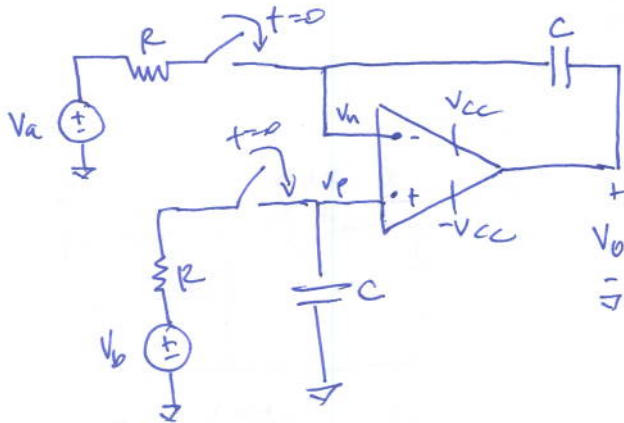

A. $V_p:$

$$C \frac{dv_p}{dt} + \frac{v_p - v_b}{R} = 0$$

$$\frac{dv_p}{dt} + \frac{v_p}{RC} = \frac{v_b}{RC}$$

$v_n:$

$$\frac{v_n - v_a}{R} + C \frac{d(v_n - v_o)}{dt} = 0$$

$$\frac{dv_o}{dt} = \frac{dv_n}{dt} + \frac{v_n}{RC} - \frac{v_a}{RC}$$

$v_n = v_p$

$$\frac{dv_n}{dt} + \frac{v_n}{RC} = \frac{dv_p}{dt} + \frac{v_p}{RC} = \frac{v_b}{RC}$$

$$\frac{dv_o}{dt} = \frac{v_b}{RC} - \frac{v_a}{RC} = \frac{1}{RC} (v_b - v_a)$$

$$v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy$$

B.
$$v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dx$$

$$RC = (40K)(25nF) = 1ms$$

$$v_b - v_a = 60mV - 10mV = 50mV$$

$$v_o = \frac{50mV}{1ms} \int_0^t dx$$

$$v_o = 50t$$

$$50 t_{sat} = 12$$

$$t_{sat} = \frac{12}{50} = 0.24s$$