

UCLA  
 Department of Electrical Engineering  
**EE10 – Spring 2010**  
**Midterm**  
 April 28<sup>th</sup>, 2010

1. Exam is closed book. You are allowed **one 8 ½ x 11” double-sided cheat sheets**.
2. Calculators are allowed.
3. Show the intermediate steps leading to your final solution for each problem.
4. **There will be no partial credit for work done correctly using a wrong answer from a previous part of a question. For example, if part a) is wrong and part b) depends on part a), then part b) will be wrong. Therefore, be very careful and double check your work!**
5. You can use both sides of the sheets to answer questions.
6. Write your final answers in the BOX and use correct units for your answers.


Problem	Maximum Score	Your Score	Comments
1. a)	2		
1. b)	2		
1. c)	2		
1. d)	2		
1. e)	2		
2. a)	4		
2. b)	3		
2. c)	3		
3. a)	7		
3. b)	7		
3. c)	6		
4.	10		
	Total: 50		
		Total	

NAME:

UID:

1. The current  $i_o$  in the circuit is 2A.

[10 pts]

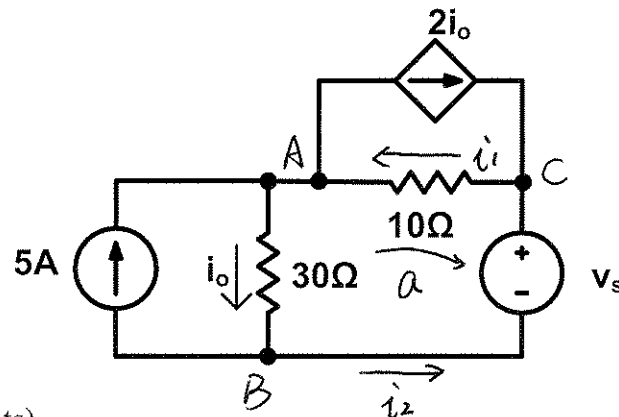

a) Calculate  $v_s$  (2 pts)

$$\text{KCL for node A: } i_o + 2i_o - i_i - 5 = 0$$

$$\Rightarrow i_i = i_o + 2i_o - 5 = 2\text{A} + 4\text{A} - 5\text{A} = 1\text{A}$$

$$\text{KVL for path a: } -30\Omega \cdot i_o - 10\Omega \cdot i_i + v_s = 0$$

$$\Rightarrow v_s = 30\Omega \cdot 2\text{A} + 10\Omega \cdot 1\text{A} = 70\text{V}$$

$$v_s = 70\text{V}$$

b) Calculate the power of the *independent VOLTAGE* source and circle if it is *absorbed* OR *delivered*. (2 pts)

$$\text{KCL for node B: } 5 + i_2 - i_o = 0$$

$$\Rightarrow i_2 = i_o - 5 = 2\text{A} - 5\text{A} = -3\text{A}$$

$$P_{v_s} = -i_2 \cdot v_s = -(-3\text{A})(70\text{V}) = 210\text{W}$$

$$\text{Power (absorbed, delivered) = 210W}$$

c) Calculate the power of the *independent CURRENT* source and circle if it is *absorbed* OR *delivered*. (2 pts)

$$P_{5A} = -5A \cdot V_{AB} = -5A \cdot (30\Omega \cdot 2A) = -300W$$

$$\text{Power (absorbed, delivered)} = 300W$$

d) Calculate the power of the *CONTROLLED current* source and circle if it is *absorbed* OR *delivered*. (2 pts)

$$P_{2i_0} = 2i_0 \cdot V_{AC} = 4A \cdot (-1A \cdot 10\Omega) = -40W$$

$$\text{Power (absorbed, delivered)} = 40W$$

e) Calculate the total power dissipated in the *two resistors*. (2 pts)

$$P_{30\Omega} = i_0^2 \cdot 30\Omega = (2A)^2 \cdot 30\Omega = 120W$$


$$P_{10\Omega} = i_1^2 \cdot 10\Omega = (1A)^2 \cdot 10\Omega = 10W$$

$$P_{\text{resistors}} = P_{30\Omega} + P_{10\Omega} = 130W$$

$$\text{Total power} = 130W$$

2. Find a)  $i_1$ , b)  $i_2$  and c)  $v_o$  in the circuit.

[10 pts]

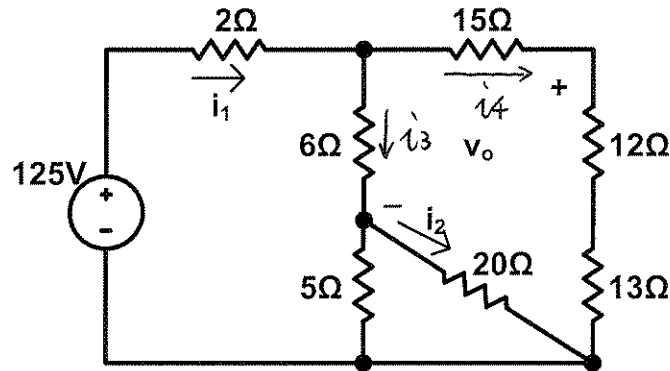

$$i_1 = \frac{125V}{2\Omega + (6\Omega + 5\Omega \parallel 12\Omega) \parallel (15\Omega + 12\Omega + 13\Omega)} = \frac{125V}{2\Omega + 10\Omega \parallel 140\Omega} = 12.5A$$

$$i_3 = \frac{15\Omega + 12\Omega + 13\Omega}{6\Omega + 5\Omega \parallel 12\Omega + 15\Omega + 12\Omega + 13\Omega} \cdot i_1 = 0.8 \cdot 12.5A = 10A$$

$$i_2 = \frac{5\Omega}{5\Omega + 20\Omega} \cdot i_3 = 0.2 \cdot 10A = 2A$$


$$i_4 = i_1 - i_3 = 12.5A - 10A = 2.5A$$

$$V_o = 6\Omega \cdot i_3 - 15\Omega \cdot i_4 = 6\Omega \cdot 10A - 15\Omega \cdot 2.5A = 22.5V$$

a) $i_1 =$	12.5A
b) $i_2 =$	2A
c) $v_o =$	22.5V

## 3. Node-voltage &amp; mesh-current method

[20 pts]

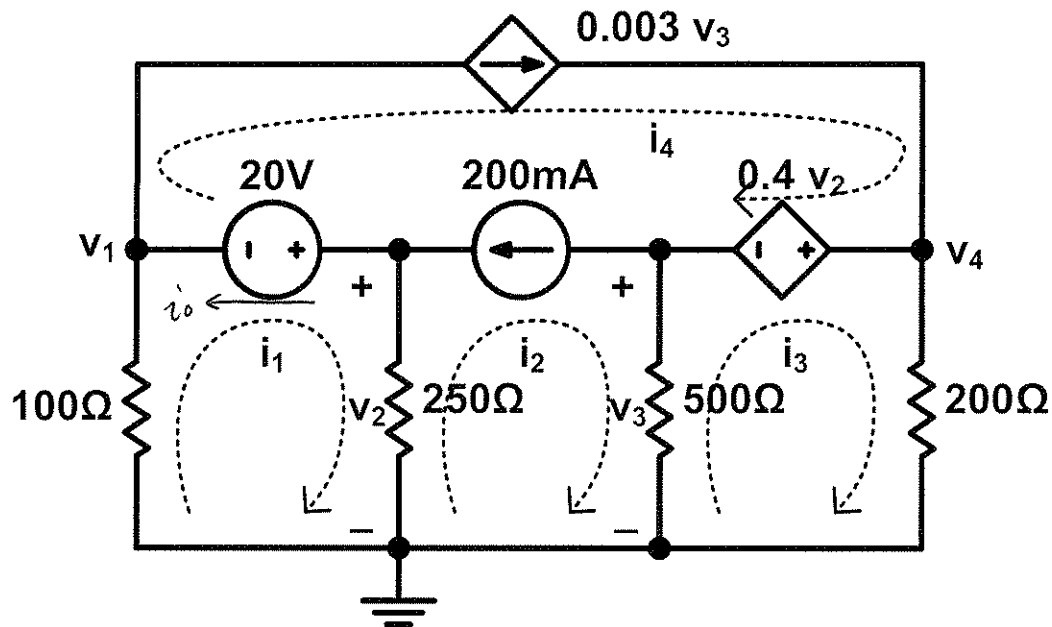

a) Make equations to find  $v_1$ ,  $v_2$ ,  $v_3$  and  $v_4$  using the node-voltage method. Use the reference node and the notation in the circuit. (7 pts)

$$\frac{V_1}{100} + \frac{V_2}{250} + 0.003V_3 - 0.2 = 0$$

$$V_1 + 20 = V_2$$

$$\frac{V_4}{200} + \frac{V_3}{500} - 0.003V_3 + 0.2 = 0$$

$$V_3 + 0.4V_2 = V_4$$

$$\text{EQN1: } 0.01V_1 + 0.004V_2 + 0.003V_3 = 0.2$$

$$\text{EQN2: } V_1 - V_2 = -20$$

$$\text{EQN3: } -0.001V_3 + 0.005V_4 = -0.2$$

$$\text{EQN4: } 0.4V_2 + V_3 - V_4 = 0$$

b) Make equations to find  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  using the mesh-current method. Use the notation in the circuit. (7 pts)

$$100i_1 - 20 + 250(i_1 - i_2) = 0 \quad (1)$$

$$i_2 - i_4 = -0.2 \quad (2)$$

$$500(i_3 - i_2) - 0.4V_2 + 200i_3 = 0 \quad (3)$$

$$i_4 = 0.003V_3 \quad (4)$$

$$V_2 = 250(i_1 - i_2) \quad \text{substitute} \quad (3)$$

$$V_3 = 500(i_2 - i_3) \quad \text{substitute} \quad (4)$$

EQN1:	$350i_1 - 250i_2 = 20$
EQN2:	$i_2 - i_4 = -0.2$
EQN3:	$-100i_1 - 400i_2 + 700i_3 = 0$
EQN4:	$1.5i_2 - 1.5i_3 - i_4 = 0$

c) Find power absorbed by 20V source by solving equations from a) or b). (6 pts)

Solving equations from (a)

$$V_1 = 24V \quad V_2 = 44V \quad V_3 = -72V \quad V_4 = -54.4V$$

$$i_0 + \frac{V_2}{250} - 0.2 = 0 \Rightarrow i_0 = 0.2 - \frac{V_2}{250} = 24mA$$

$$P_{20V} = (20V)(24mA) = 480mW$$

Solving equations from (b),  $i_1 = -0.24A$   $i_2 = -0.416A$   $i_3 = -0.272A$


Power absorbed = 480mW
------------------------

$$i_4 = -0.216A$$


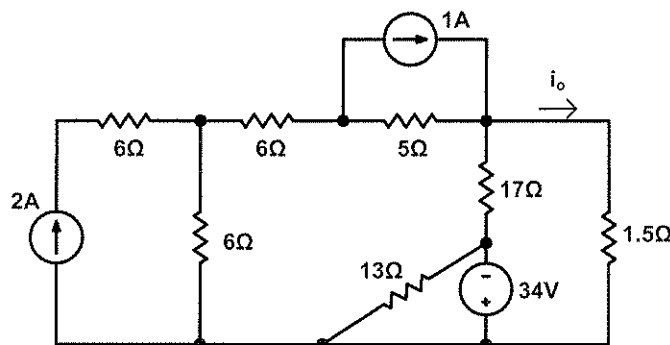
4. Source transformation

[10 pts]



Use a series of source transformation to find the current  $i_o$  in the circuit.



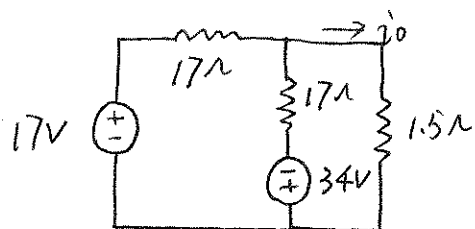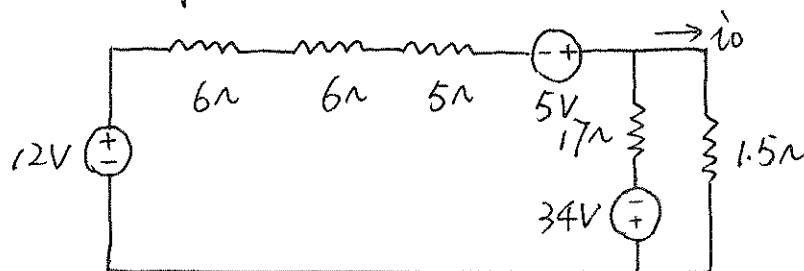Remove  $6\Omega$  and  $13\Omega$  resistors first. then apply a source transformation to each current source yields



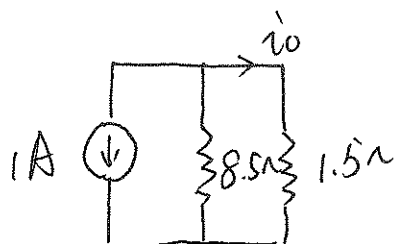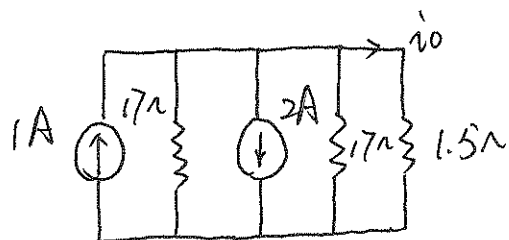Apply source transformation on voltage sources



$$i_o = -\frac{8.5}{8.5+1.5} \cdot 1A = -0.85A$$

$$i_o = -0.85A$$