

Total of 3 questions, 100 minutes.


P1 (30)	28
P2 (30)	30
P3 (40)	40
Total (100)	98

$$0 \leq k = \frac{M}{\sqrt{L_1 L_2}} \leq 1$$

$$M \leq \sqrt{L_1 L_2}$$

$$M^2 \leq L_1 L_2$$

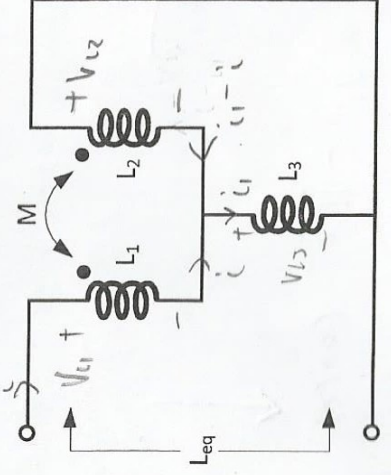- For the circuit shown below,
  - Find the equivalent inductance,  $L_{eq}$ .
  - Show that  $L_{eq}$  is always positive.



$$i + i_1 = i_2 \quad V_{eq}$$

$$a) \begin{cases} V_{L1} = L_1 \frac{di}{dt} + M \frac{d(i-i)}{dt} \\ V_{L2} = L_2 \frac{d(i-i)}{dt} + M \frac{di}{dt} = -L_2 \frac{d(i-i)}{dt} \end{cases}$$

$$L_2 \frac{di}{dt} - L_2 \frac{d(i-i)}{dt} + M \frac{di}{dt} = L_3 \frac{d(i-i)}{dt}$$

$$(L_2 - M) \frac{di}{dt} = (L_3 + L_2) \frac{d(i-i)}{dt}$$

$$\frac{d(i-i)}{dt} = \frac{L_2 - M}{L_3 + L_2} \frac{di}{dt}$$

$$V_{eq} = L_{eq} \frac{di}{dt} = V_{L1} + V_{L3}$$

$$= L_1 \frac{di}{dt} + M \frac{d(i-i)}{dt} + L_3 \frac{di}{dt}$$

$$= (L_1 - M) \frac{di}{dt} + (M + L_3) \frac{d(i-i)}{dt}$$

$$L_{eq} \frac{di}{dt} = (L_1 - M) \frac{di}{dt} + (M + L_3) \left( \frac{L_2 - M}{L_3 + L_2} \right) \frac{di}{dt}$$

$$L_{eq} = \frac{(L_1 - M)(L_2 + L_3) + (L_3 + M)(L_2 - M)}{L_2 + L_3}$$

$$L_{eq} = \frac{L_1 L_2 + L_1 L_3 - L_2 M - L_3 M + L_2 L_3 - L_3 M + L_2 M - M^2}{L_2 + L_3}$$

$$L_{eq} = \frac{L_1 L_2 + L_2 L_3 + L_1 L_3 - 2 L_3 M - M^2}{L_2 + L_3}$$

$L_1 L_3$ , and  $L_2 + L_3$  are all positive because inductances are positive. We know that  $0 \leq M^2 \leq L_1 L_2$  from the definition of the coupling factor  $[0 \leq M \leq \sqrt{L_1 L_2}]$

simply leave:

$$L_{eq} = L_1 + \frac{L_2 L_3}{L_2 + L_3} - \left( \frac{M^2 + 2ML_3}{L_2 + L_3} \right) > 0$$

$$L_1 + \frac{L_2 L_3}{L_2 + L_3} > \frac{M^2 + 2ML_3}{L_2 + L_3}$$

$$L_1 L_2 + L_1 L_3 + L_2 L_3 > M^2 + 2ML_3$$

$$L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2 > M^2 + 2ML_3 + L_3^2$$

$$L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2 > (M + L_3)^2$$

$$-\sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2} < M + L_3$$

$$< \sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2}$$

$$-L_3 - \sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2} < M < \sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2} - L_3$$

$$M < \sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2} - L_3$$

$$-(L_3 + \sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2}) < M < \sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2} - L_3$$

$$\sqrt{L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2} - \sqrt{L_3^2} > 0$$

see back side for an analysis of inequality

$$L_{eq} = L_1 + \frac{L_2 L_3}{L_2 + L_3} - \left( \frac{M^2 + 2L_3 M}{L_2 + L_3} \right) > 0$$

$\downarrow$   
 (i) because  $M$  is defined to be  $M > -\sqrt{l_1 l_2}$ , the left side of the inequality holds true. The other factors than  $\sqrt{l_1 l_2}$  on the left only make the quantity increasingly negative. Therefore, the left side of the inequality holds true, as  $M$  will always be greater than  $-l_3 - \sqrt{l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2}$

$\downarrow$   
 (ii) The factors  $\sqrt{l_3^2}$  and  $-\sqrt{l_3^2}$  cancel out in their effect on the right side of the inequality. Effectively, we want to prove that  $M < \sqrt{l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2} - \sqrt{l_3^2}$  given that  $M < +\sqrt{l_1 l_2}$ . So, we need to prove that

$$\sqrt{l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2} - \sqrt{l_3^2} \geq \sqrt{l_1 l_2}$$

$$l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2 - 2\sqrt{l_1 l_2 l_3^2 + l_2 l_3^3 + l_1 l_3^3 + l_3^4} + l_3^2 \geq l_1 l_2$$

$$l_2 l_3 + l_1 l_3 + l_3^2 - 2\sqrt{l_1 l_2 l_3^2 + l_2 l_3^3 + l_1 l_3^3 + l_3^4} + l_3^2 \geq 0$$

The contribution to this inequality from  $l_1$  &  $l_2$  is insignificant, because the leftmost term will always exceed the center one in terms of  $l_1$  &  $l_2$ 's contributions, due to the power of each term ( $l_1$  vs.  $l_2$ ). Therefore, because the contributions of  $l_3$  cancel out, we can say that  $M < \sqrt{l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2} - \sqrt{l_3^2}$ .







$$0 \leq M \leq \sqrt{l_1 l_2}$$

Hence,  $\sqrt{l_1 l_2} \leq M \leq \sqrt{l_1 l_2}$  lies within the range of  $-l_3 - \sqrt{l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2} < M < \sqrt{l_1 l_2 + l_2 l_3 + l_1 l_3 + l_3^2} - \sqrt{l_3^2}$ , so we have proven that  $low > 0$

$$P_R = \frac{2}{36}$$


$$P_R = \frac{1}{18} \text{ W}$$

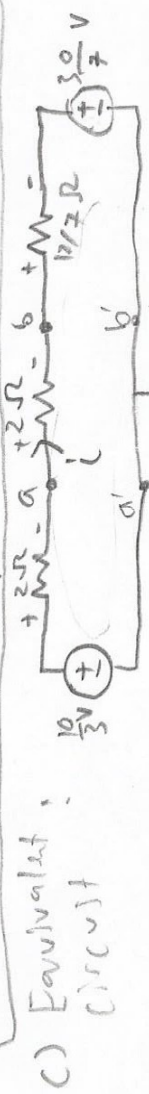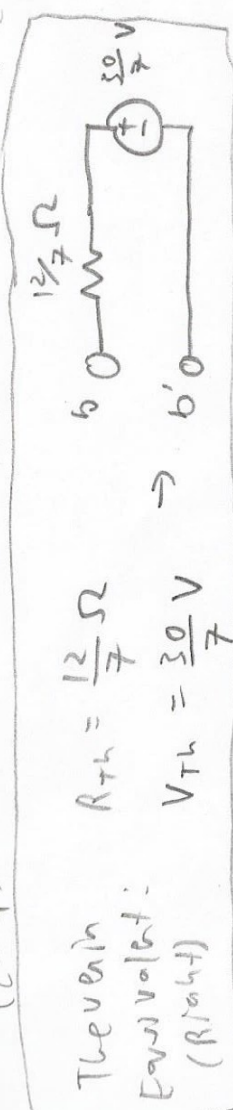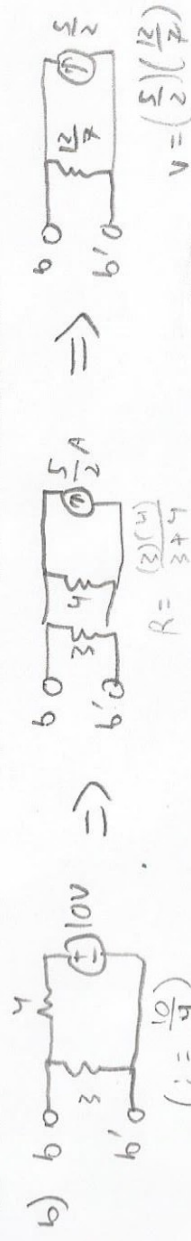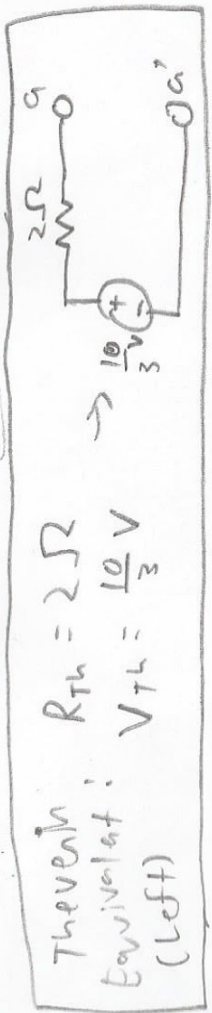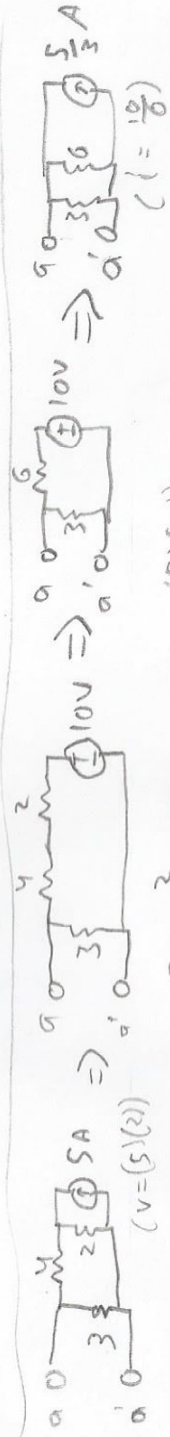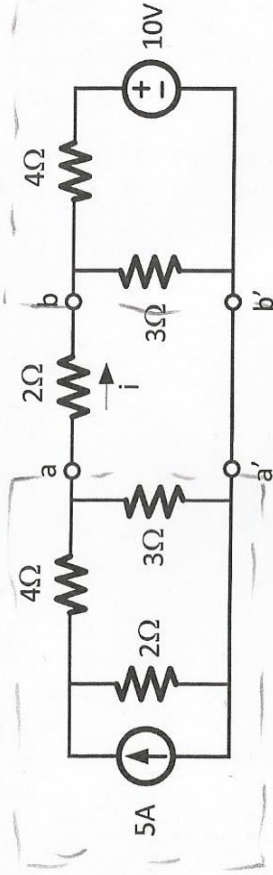2. In the circuit below,
- Find the Thevenin equivalent at left side of  $a - a'$  nodes.
  - Find the Thevenin equivalent at the right side of  $b - b'$  nodes
  - Find the current  $i$  by constructing an equivalent circuit using part a and b Thevenin circuits.
  - Calculate the power dissipated in the middle  $2\Omega$  resistor.  $P_R = i^2 R = 2i^2$




KVL:  $0 = \frac{10}{3} - (2)(i) - (\frac{12}{7})(i) - \frac{30}{7} = \frac{70 - 90}{21} - (\frac{28 + 12}{7})i = -(\frac{20}{21} + \frac{40}{7})i$   
 $\frac{40}{7}i = -\frac{20}{21} \rightarrow i = -\frac{1}{6} \text{ A}$  (see top for R.d)

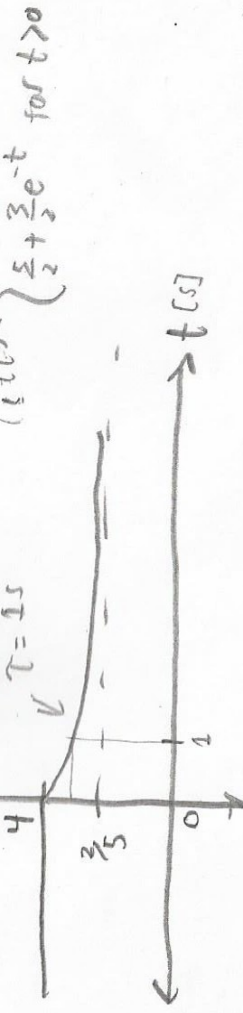check:  
 $V_b = \frac{3}{7}(10)$   
 $V_b = \frac{30}{7}$   
 $V_a = \frac{3}{7}(10)$   
 $V_a = \frac{30}{7}$   
 $V_R = V_a - V_b = \frac{30}{7} - \frac{30}{7} = 0$



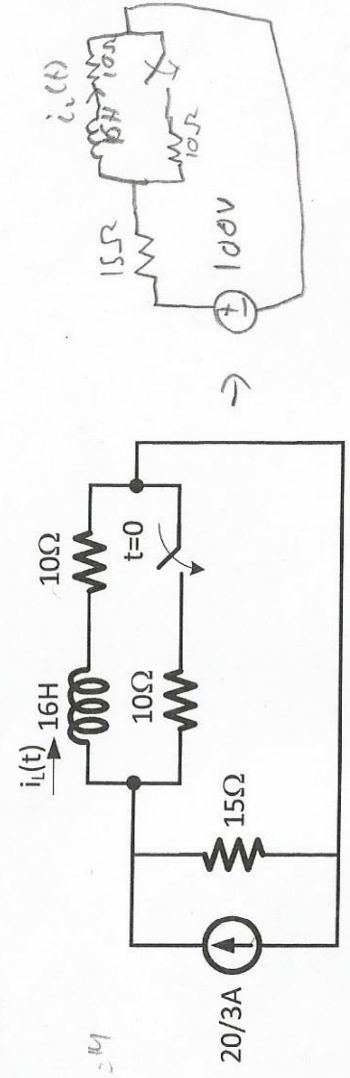
3. The circuit below has been idle for a long time (switch is open). At  $t = 0$ , the switch is closed.

- Find the inductor current right before and after the switch is closed ( $i_L(0^-)$ ), and  $i_L(0^+)$ .
- Find and plot  $i_L(t)$ .



$$\frac{15}{25} \cdot \frac{20}{3} = \frac{5}{3} \cdot \frac{4}{1} = \frac{4}{3} \text{ A}$$

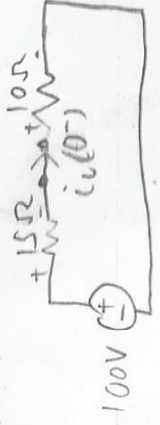a) Steady state:  $t = 0^-$ , inductor is shorted...



$$KVL: 100 - 15[i_L(0^-)] - 10[i_L(0^-)] = 0$$


$$100 = 25[i_L(0^-)]$$

$$i_L(0^-) = 4 \text{ A}$$

Because there is no impulse/infinite current when the switch is closed, we have  $i_L(0^+) = i_L(0^-) = 4 \text{ A}$

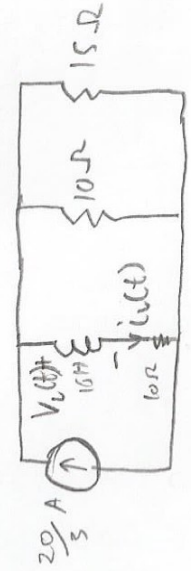b)  $t = 0^+$ : inductor has full charge... acts as a current source

$$V_L(t) = L \frac{di_L(t)}{dt} \rightarrow i_L(t) = \frac{1}{L} \int V_L dt$$




$$R = \frac{10 \times 15}{10 + 15} = \frac{150}{25} = \frac{30}{5} = 6 \Omega$$



$$i_L(t) = (I_F + (i_L(0) - I_F))e^{-t/\tau}$$

$$i_L(t) = \frac{5}{2} + (4 - \frac{5}{2})e^{-t/\tau}$$
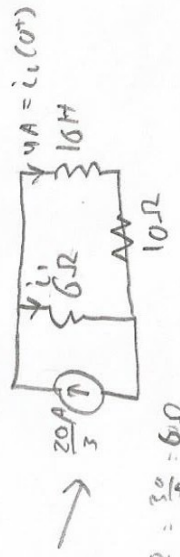
$$i_L(t) = \frac{5}{2} + \frac{3}{2}e^{-t}$$



$$\tau = \frac{L}{R} = \frac{10 \text{ H}}{16 \Omega} = \frac{1}{1.6} = \frac{5}{8} \text{ s}$$

$$i_L(0^+) = i_L = 4 \text{ A}$$

$$i_L(\infty) = i_F = \frac{5}{2} \text{ A}$$

$$i_L(t) = \begin{cases} 4 & \text{for } t < 0 \\ \frac{5}{2} + \frac{3}{2}e^{-t} & \text{for } t > 0 \end{cases}$$

\* See top of page for graph