

Name: \_\_\_\_\_


UID: \_\_\_\_\_

Total of 2 questions.


- Open notes but no calculator, internet, CCLE, ...
- Submit your PDF no later than 11:50AM to CCLE as <Last\_First\_UID>

<b>P1 (44)</b>	
<b>P2 (56)</b>	
<b>Total (100)</b>	

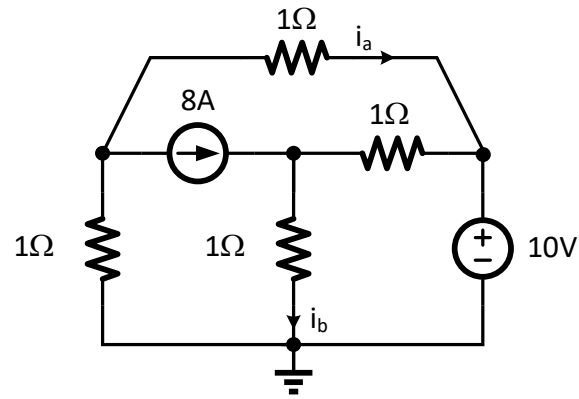1. Shown below is an LTI network comprising resistors and independent sources.
  - a. (14) Using the node voltage analysis, find the currents  $i_a$  and  $i_b$ . Take the datum node as shown.
  - b. (20) Redo part a using superposition.
  - c. (10) Calculate the power delivered by each of the independent sources.




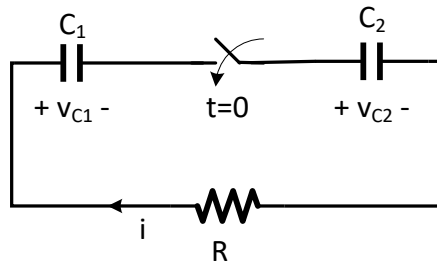2. The circuit below has been idle for a long time. Capacitor  $C_1$  has an initial voltage of  $12V$ , while capacitor  $C_2$  has no initial charge. The switch is closed at  $t = 0$ .  $C_1 = 6F$ ,  $C_2 = 3F$ , and  $R = \frac{1}{2}\Omega$ .
- (4) Calculate the resistor current right after the switch closure ( $i(0^+)$ ).
  - (18) Find and plot the resistor current ( $i(t)$ ) for  $t \geq 0$ .
  - (28) Find the capacitors voltages ( $v_{C1}(t)$  and  $v_{C2}(t)$ ) for  $t \geq 0$ .
  - (6) What is the final voltage of the capacitors (at  $t = \infty$ )?



10 H Midterm

Achintya Padmal

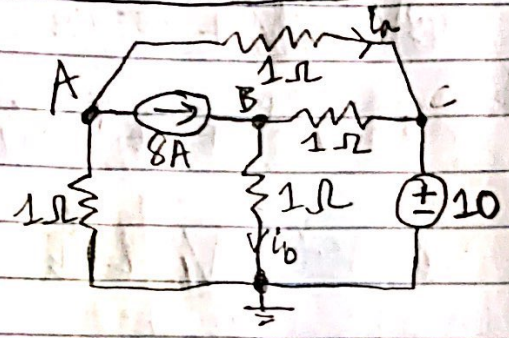

NVA


a) @A:  $8 + \frac{V_A - 0}{1} + i_a = 0$   
 @B:  $-8 + i_b + \frac{V_B - 10}{1} = 0$

$i_a = V_A - 8 = \frac{V_A - 10}{1}$   
 $-2V_A = -18 \quad V_A = 9$   
 $i_a = -1 - 8 = -9A = 9A$   
 $i_b = -V_B + 18 = V_B$   
 $18 = 2V_B \quad V_B = 9$

**$i_b = 9A$**


b) Superposition

i) Short voltage source

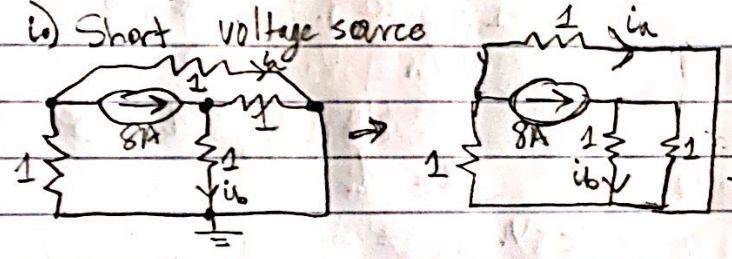


Current divider

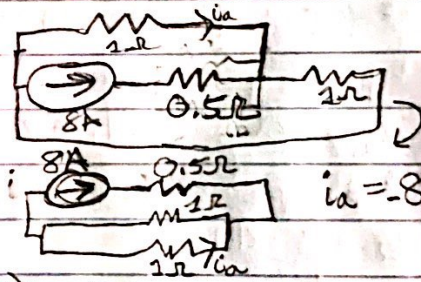$i_b = 8A \left( \frac{1\Omega}{1\Omega + 1\Omega} \right) = 4A$



$i_a = -8A \left( \frac{1\Omega}{1\Omega + 1\Omega} \right) = -4A$

ii) Open current source

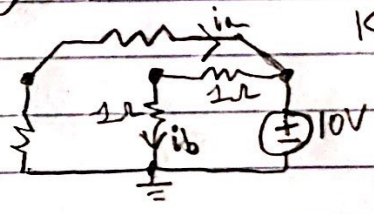


KVL<sub>B</sub>:  $10 - i_b(1) - i_b(1) = 0$   
 $10 - 2i_b = 0 \quad i_b = 5A$   
 KVL<sub>A</sub>:  $10 + i_a(1) + i_a(1) = 0$   
 $10 + 2i_a = 0 \quad i_a = -5A$

$i_a = i_{a1} + i_{a2} = -4A + (-5A) = -9A = i_a$   
 $i_b = i_{b1} + i_{b2} = 4A + 5A = 9A = i_b$

c)  $V_{is} = |V_A - V_B| = 8$

$P_{is} = V_{is}(i_s) = (8V)(8A) = 64W$

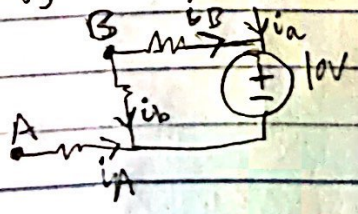
$i_{vs} = i_b + i_A - i_a - i_B = i_b + \frac{V_A}{1} - i_a - \frac{V_B}{1} = 9 + 1 - (-9) - 9 = 10A$



$P_{vs} = V_s(i_{vs}) = (10V)(10A) = 100W$



$$Q = CV$$

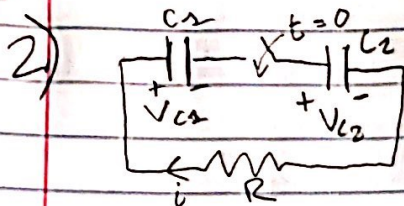

$$V_{c1}(0^-) = 12V \quad Q_{c2}(0^-) = 0$$

$$C_1 = 6F \quad C_2 = 3F \quad R = \frac{1}{2}\Omega$$

a) KVL:  $V_{c1}(0^+) + V_{c2}(0^+) - i(0^+)R = 0$

no impulse current  $\rightarrow V_{c1}(0^-) + V_{c2}(0^-) - i(0^-)R = 0$

$$12V + \frac{0C}{3F} = 40 \times \frac{1}{2}\Omega$$


$$i(0^-) = 24A$$

b) @  $t \rightarrow \infty$ , capacitors reach steady state as  $OC$  dca  $i_{c1} = i_{c2} = 0$

$$i_F = 0 \quad Q_{c2} = 24A \times 3F = 72C$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{6(3)}{9} = 2F$$
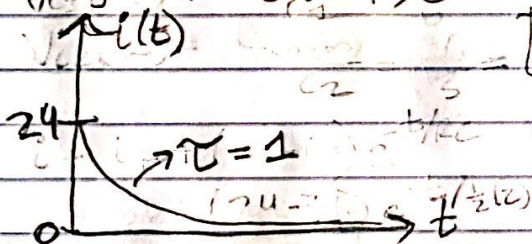
$$i(t) = i_F + (i_i - i_F)e^{-t/RC} = 0 + (24 - 0)e^{-t/(1/2)(2)}$$



$$i(t) = 24e^{-t}$$

$$V_{c1} + V_{c2} - iR = 0$$

$$i = C_1 \frac{dV_1}{dt} = C_2 \frac{dV_2}{dt}$$

$$c) V_{c1} = \frac{1}{C_1} \int_0^t i(\tau) d\tau = \frac{1}{6} \int_0^t 24e^{-\tau} d\tau = 4(-e^{-\tau}) \Big|_0^t$$

$$= -4e^{-t} + 4 + C$$

$$d) V_{c1}(0) = 12 = -4e^{-0} + 4 + C \quad C = 12$$

$$V_{c1}(t) = -4e^{-t} + 16$$

$$V_{c2} = \frac{1}{C_2} \int_0^t i(\tau) d\tau = \frac{1}{3} \int_0^t 24e^{-\tau} d\tau = 8(-e^{-\tau}) \Big|_0^t$$

$$V_{c2}(0) = 0 = -8e^{-0} + 8 + C \quad C = 0$$

$$V_{c2}(t) = -8e^{-t} + 8$$

e)  $V_{c1}(\infty) + V_{c2}(\infty) = 0 \quad V_{c2}(\infty) = -V_{c1}(\infty)$

$$Q_{c1}(0) - Q_{c1}(\infty) = Q_{c2}(\infty)$$

$$C_1 V_{c1}(0) - C_1 V_{c1}(\infty) = C_2 V_{c2}(\infty)$$

$$6(12) - 6V_{c1}(\infty) = 3V_{c2}(\infty)$$

$$3V_{c1}(\infty) = 72$$

$$V_{c1}(\infty) = 24V$$

$$V_{c1}(\infty) = 24V$$

$$V_{c2}(\infty) = -24V$$