

Name: _____


UID: _____

Total of 2 questions.


- Open notes but no calculator, internet, CCLE, ...
- Submit your PDF no later than 11:50AM to CCLE as <Last_First_UID>

P1 (44)	
P2 (56)	
Total (100)	

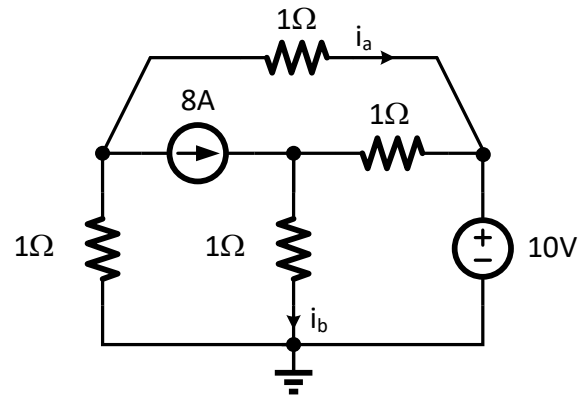1. Shown below is an LTI network comprising resistors and independent sources.
 - a. (14) Using the node voltage analysis, find the currents i_a and i_b . Take the datum node as shown.
 - b. (20) Redo part a using superposition.
 - c. (10) Calculate the power delivered by each of the independent sources.



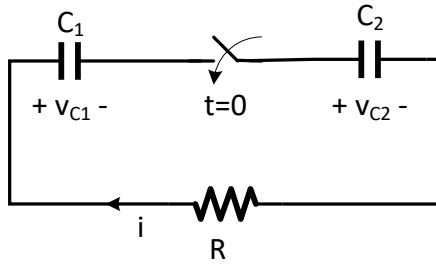
2. The circuit below has been idle for a long time. Capacitor C_1 has an initial voltage of $12V$, while capacitor C_2 has no initial charge. The switch is closed at $t = 0$. $C_1 = 6F$, $C_2 = 3F$, and $R = \frac{1}{2}\Omega$.
- (4) Calculate the resistor current right after the switch closure ($i(0^+)$).
 - (18) Find and plot the resistor current ($i(t)$) for $t \geq 0$.
 - (28) Find the capacitors voltages ($v_{C1}(t)$ and $v_{C2}(t)$) for $t \geq 0$.
 - (6) What is the final voltage of the capacitors (at $t = \infty$)?



This got 100%

ECE 10H Midterm

Blake Lazare
705310999

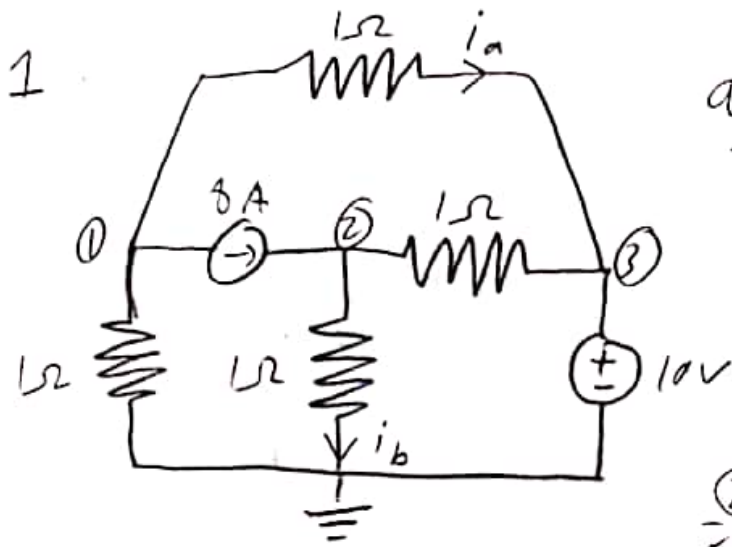

$$a) 0 = 8A + i_a + \frac{V_1 - 0V}{1\Omega} \quad (1)$$

$$0 = -8A + \frac{V_2 - 0V}{1\Omega} + \frac{V_2 - V_3}{1\Omega} \quad (2)$$

$$V_3 = 0V + 10V = 10V$$

$$\Rightarrow 0 = -8A + \frac{V_2}{1\Omega} + \frac{V_2 - 10V}{1\Omega}$$

$$\Rightarrow 0 = -8V + V_2 + V_2 - 10V \Rightarrow 18V = 2V_2 \Rightarrow V_2 = 9V$$

$$i_b = \frac{V_2 - 0V}{1\Omega} = \frac{9V - 0V}{1\Omega} = 9A$$



$$i_a = \frac{V_1 - V_3}{1\Omega} \quad (1) \Rightarrow 0 = 8A + \frac{V_1 - V_3}{1\Omega} + \frac{V_1}{1\Omega}$$

$$V_3 = 10V \Rightarrow 0 = 8A + \frac{V_1 - 10V}{1\Omega} + \frac{V_1}{1\Omega}$$

$$\Rightarrow -8V = V_1 - 10V + V_1 \Rightarrow 2V = 2V_1 \Rightarrow V_1 = 1V$$

$$i_a = \frac{V_1 - V_3}{1\Omega} = \frac{1V - 10V}{1\Omega} = \frac{-9V}{1\Omega} = -9A$$

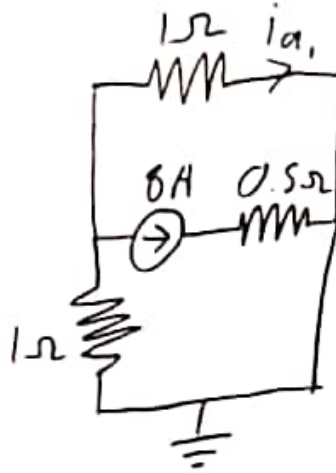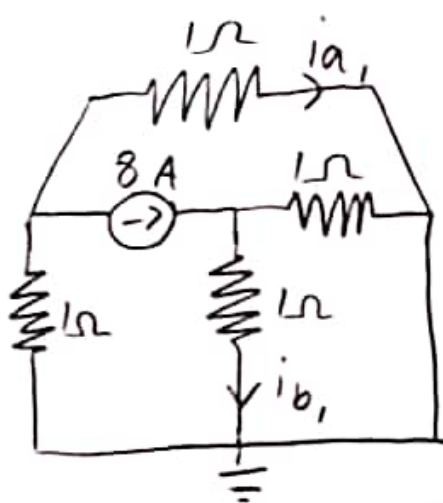1. b) by super position, do 2 cases with 1 source each





The 8A gets split between 60 branches, each with 1Ω of resistance.

By symmetry these branches each get 4A

$$\Rightarrow i_{b1} = 4A$$

Apply the same logic to find i_{a1}
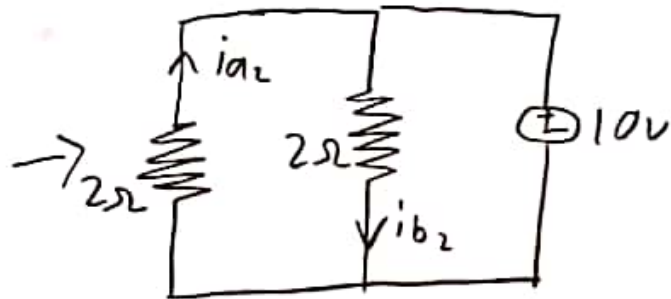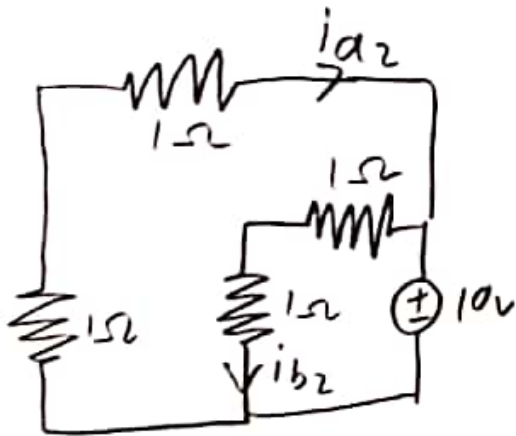
$$i_{a1} = -4A \text{ (direction opposite)}$$



$$\Rightarrow i_{a2} = -\frac{10V}{2\Omega} = -5A$$

$$i_{b2} = \frac{10V}{2\Omega} = 5A$$

$$i_a = i_{a1} + i_{a2} = -4A - 5A = -9A$$

$$i_b = i_{b1} + i_{b2} = 4A + 5A = 9A$$

match ✓

$$1. c) V_{\text{current source}} = V_2 - V_1 = 9\text{V} - 1\text{V} = 8\text{V}$$

$$P = IV = 8\text{A} \cdot 8\text{V} = 64\text{W}$$

Current source delivers 64W of power

$$I_{\text{voltage source}} = I_{V_S}$$

$$\text{by KCL, } 0 = -i_a - I_{V_S} + \frac{10\text{V} - V_2}{1\Omega}$$

$$\Rightarrow 0 = -(-9\text{A}) - I_{V_S} + \frac{10\text{V} - 9\text{V}}{1\Omega} \Rightarrow 0 = 9\text{A} - I_{V_S} + \frac{1\text{V}}{1\Omega}$$

$$\Rightarrow I_{V_S} = 9\text{A} + 1\text{A} = 10\text{A}$$

$$P = I_{V_S} V_{V_S} = 10\text{A} \cdot 10\text{V} = 100\text{W}$$


voltage source delivers 100W of power

check if valid: power used by all resistors

$$P = \sum I^2 R = (9\text{A})^2 \cdot 1\Omega + (9\text{A})^2 \cdot 1\Omega + (1\text{A})^2 \cdot 1\Omega + (1\text{A})^2 \cdot 1\Omega \\ = 164\text{W}$$

$$P_{CS} + P_{VS} = 64\text{W} + 100\text{W} = 164\text{W} \text{ match } \checkmark$$

2.

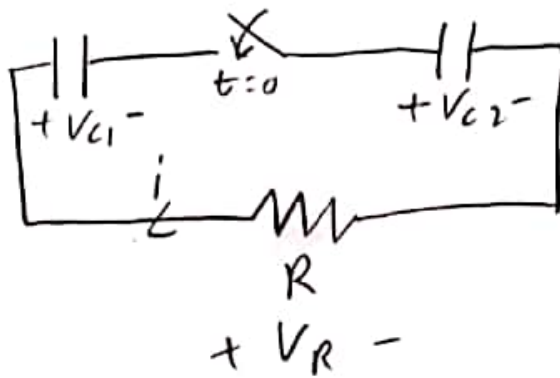

$$V_{C1}(0^-) = 12V$$

$$V_{C2}(0^-) = 0V$$

$$C_1 = 6F \quad C_2 = 3F$$

$$R = \frac{1}{2} \Omega$$

a) at $t=0^+$, C_2 has no voltage drop across it and therefore acts like a short connection. C_1 , however, has 12V across it and acts as a voltage source.

$$\Rightarrow V_R(0^+) = 12V \Rightarrow \boxed{i(0^+) = \frac{-V_R(0^+)}{R} = \frac{-12V}{\frac{1}{2}\Omega} = -24A}$$

negative sign from direction of current

$$b) V_R = V_{C1} + V_{C2}$$

$$V_{C1} = 12V + \frac{1}{C_1} \int_0^t i(\tau) d\tau \quad V_{C2} = 0 + \frac{1}{C_2} \int_0^t i(\tau) d\tau$$

$$\Rightarrow V_R = 12V + \frac{1}{C_1} \int_0^t i(\tau) d\tau + \frac{1}{C_2} \int_0^t i(\tau) d\tau$$

$$\Rightarrow -Ri = 12V + \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int_0^t i(\tau) d\tau$$

$$\Rightarrow -\frac{1}{2}\Omega i = 12V + \left(\frac{1}{6F} + \frac{1}{3F}\right) \int_0^t i(\tau) d\tau$$

$$\Rightarrow i = -24V - \frac{6\Omega}{6F} \int_0^t i(\tau) d\tau$$

continued

2. b) continued

$$\Rightarrow \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int_0^t i(\tau) d\tau = -12V - Ri$$

$$\Rightarrow \int_0^t i(\tau) d\tau = \frac{-Ri}{\left(\frac{1}{C_1} + \frac{1}{C_2}\right)} - \frac{12V}{\left(\frac{1}{C_1} + \frac{1}{C_2}\right)}$$

offset for
evaluating
at 0

take derivative of both sides

$$i(t) = \frac{-R}{\frac{1}{C_1} + \frac{1}{C_2}} \frac{di}{dt} \Rightarrow i = A e^{\frac{-(\frac{1}{C_1} + \frac{1}{C_2})t}{R}}$$


$$\text{let } \tau = \frac{R}{\frac{1}{C_1} + \frac{1}{C_2}}$$

know $i(0^+) = -24A$

$$\Rightarrow i(0) = -24A = A e^{-\frac{0}{\tau}} \Rightarrow A = -24A$$

$$\tau = \frac{R}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{\frac{1}{2} \Omega}{\frac{1}{6F} + \frac{1}{3F}} = \frac{\frac{6}{2}}{3} s = 1s$$
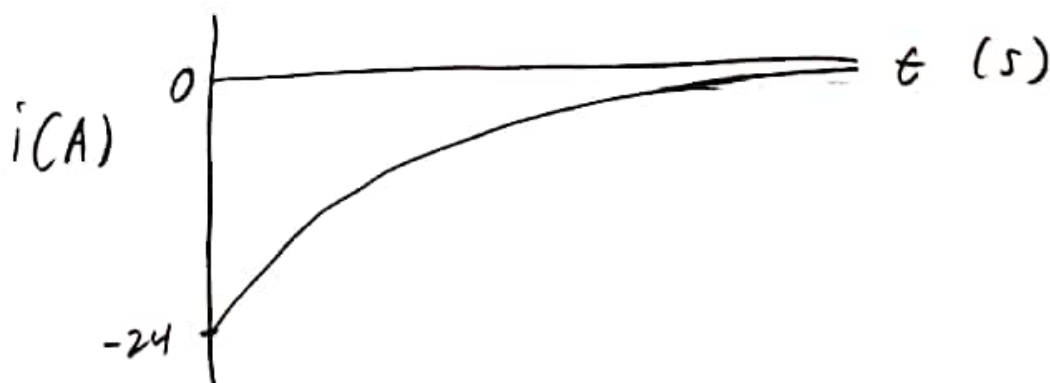
$$\Rightarrow \boxed{i = -24A e^{-t \cdot \frac{1}{s}}}$$



ECE 10H Midterm

c) previously shown

$$V_{C_1} = 12v + \frac{1}{6F} \int_0^t i(\tau) d\tau \quad V_{C_2} = \frac{1}{3F} \int_0^t i(\tau) d\tau$$

$$\Rightarrow V_{C_1} = 12v + \frac{1}{6F} \int_0^t -24A e^{-\tau \cdot \frac{1}{5}} d\tau$$

$$= 12v + \frac{24A}{6F} \left(e^{-\tau \cdot \frac{1}{5}} \right) \Big|_0^t = 12v + 4v \left(e^{-t \cdot \frac{1}{5}} - 1 \right)$$

$$V_{C_1} = 8v + 4v e^{-t \cdot \frac{1}{5}}$$

$$V_{C_2} = \frac{1}{3F} \int_0^t -24A e^{-\tau \cdot \frac{1}{5}} d\tau = \frac{24A}{3F} \left(e^{-\tau \cdot \frac{1}{5}} \right) \Big|_0^t$$

$$V_{C_2} = 8v \left(e^{-t \cdot \frac{1}{5}} - 1 \right)$$

$$\begin{aligned} 2. d) \lim_{t \rightarrow \infty} V_{C_1}(t) &= \lim_{t \rightarrow \infty} (8V + 4V e^{-t \cdot \frac{1}{3}}) \\ &= 8V + 4V \cdot 0 = 8V \end{aligned}$$

$$\begin{aligned} \lim_{t \rightarrow \infty} V_{C_2}(t) &= \lim_{t \rightarrow \infty} (8V (e^{-t \cdot \frac{1}{3}} - 1)) \\ &= 8V(0 - 1) = -8V \end{aligned}$$

This makes sense as there should be zero current at $t = \infty$, so the capacitor voltages should cancel