

ECE10

Midterm Exam


Winter 2018




Total of 3 questions, 100 minutes.

P1 (30)	30
P2 (30)	30
P3 (40)	40
Total (100)	

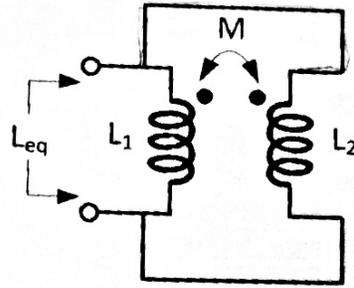1. Find the equivalent inductance of the circuit below. $L_1 = 5H$, $L_2 = 2H$, and $M = 3H$.



set up

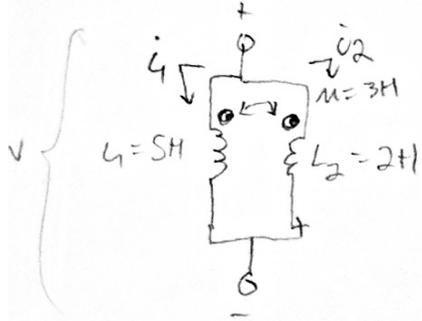

$$V = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \quad (1)$$

$$V = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt} \quad (2)$$

Inductance matrix $L = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} = \begin{bmatrix} 5 & 3 \\ 3 & 2 \end{bmatrix}$

$$V = L \frac{di(t)}{dt}$$

$$V = L_{eq} \left[\frac{di_1(t)}{dt} + \frac{di_2(t)}{dt} \right] \quad (3)$$

$$L_{eq} = L_{eq1} \parallel L_{eq2} =$$

solving:

$$(1) = (2) \quad 5i_1' + 3i_2' = 2i_2' + 3i_1'$$

$$2i_1' = -i_2'$$

$$i_1' = -\frac{1}{2}i_2' \rightarrow \text{substitute in } V = 5\left(-\frac{1}{2}i_2'\right) + 3(i_2')$$

$$V = \frac{1}{2}i_2' + 3\left(-\frac{1}{2}i_2'\right)$$

substitute into

$$(3) \quad V = L_{eq} \left[-\frac{1}{2}i_2' + i_2' \right]$$

$$(3) \quad \frac{1}{2}i_2' = L_{eq} \left[\frac{1}{2}i_2' \right]$$

$$\Rightarrow L_{eq} = 1H$$

+30


$$L_{eq1} = \frac{V}{i_1'} = L_1 + M = 8H$$

$$L_{eq2} = \frac{V}{i_2'} = L_2 + M = 5H$$

$$L_{eq} = \frac{1}{\frac{1}{8} + \frac{1}{5}} = \frac{40}{13}$$

* Had trouble solving the algebra but the inductance matrix and equations are at the top if this is wrong

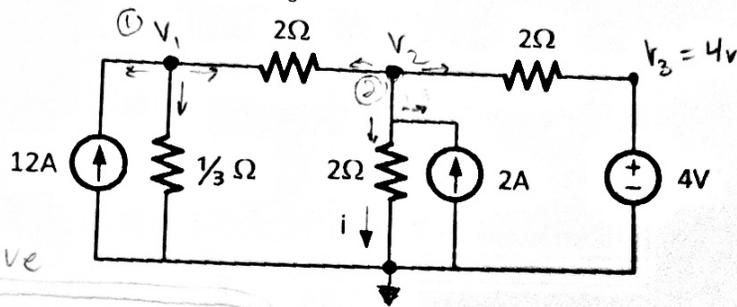2. In the circuit below, using node analysis,
 a. Find the current i .
 b. Find the power dissipated in the $\frac{1}{3}\Omega$ resistor.



(a)

Nodal Equations needed to solve

$$\textcircled{1} \quad -12 + \frac{V_1}{\frac{1}{3}} + \frac{V_1 - V_2}{2} = 0$$

$$\textcircled{2} \quad -2 + \frac{V_2}{2} + \frac{V_2 - 4}{2} + \frac{V_2 - V_1}{2} = 0$$

Algebra:

simplify

$$\textcircled{1} \quad -12 + 3V_1 + \frac{V_1 - V_2}{2} = 0$$

$$\textcircled{2} \quad -2 + \frac{1}{2}V_2 + \frac{1}{2}V_2 - 2 + \frac{1}{2}V_2 - \frac{1}{2}V_1 = 0$$

$$-4 + \frac{3}{2}V_2 - \frac{1}{2}V_1 = 0$$

Solving:

$$\textcircled{1} \quad 2 \times (3V_1 + \frac{V_1 - V_2}{2}) = 12 \times 2$$

$$6V_1 + V_1 - V_2 = 24$$

$$7V_1 - 24 = V_2$$

$$\textcircled{2} \quad -4 + 1.5V_2 - \frac{1}{2}V_1 = 0$$

$$\textcircled{1} \quad -12 + 0.5V_2 + 3.5V_1 = 0$$

$$-16 + V_2 + 3V_1 = 0$$

$$V_2 = 16 - 3V_1$$

$$16 - 3V_1 = 7V_1 - 24$$

$$40 = 10V_1$$

$$\boxed{V_1 = 4V}$$


$$\Rightarrow \boxed{V_2 = 4V}$$

$$\textcircled{b} \quad P_{\frac{1}{3}\Omega} = iV = \frac{V^2}{R} = i^2 R$$

$$P = \frac{V^2}{\frac{1}{3}} = \frac{4^2}{\frac{1}{3}} = 48W$$


+30

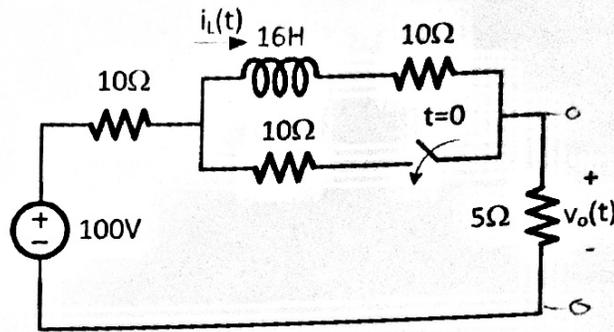3. The circuit below has been idle for a long time (switch is open). At $t = 0$, the switch is closed.
- Find the inductor current right before and after the switch is closed ($i_L(0^-)$, and $i_L(0^+)$).
 - Find v_o right before and after the switch is closed ($v_o(0^-)$, and $v_o(0^+)$).
 - Find and plot $v_o(t)$.



(a)

$t = 0^-$:

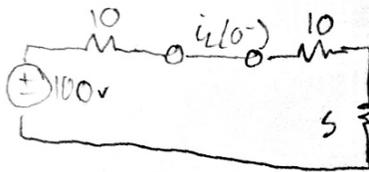


$$i_L(0^-) = \frac{100\text{V}}{25\Omega} = 4\text{A}$$

$$i_L(0^+) = i_L(0^-) = 4\text{A}$$

$$V_o(0^-) = i_L(0^-) \cdot 5 = 20\text{V}$$

(b)

$t = 0^+$:

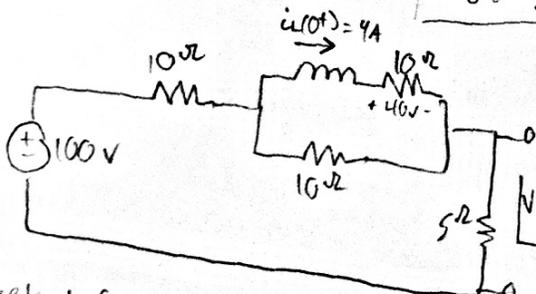

$$V_o(0^+) = 28\text{V}$$

$$V_L = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \int \frac{V_L}{L} dt$$

see next sheet before all work below

found on next sheet

(c) $t > 0$

from next sheet $i_L(t) = 2.5 + 1.5e^{-t}$ A, $V_L(t) = -24e^{-t}$ volts



$$KVL: 100\text{V} = 10 \cdot i_o(t) - 24e^{-t} + (2.5 + 1.5e^{-t}) \cdot 10 + 5 \cdot i_o(t)$$

$$V_o(t) = i_o(t) \cdot 5 = \left[\frac{100 + 24e^{-t} - (2.5 + 1.5e^{-t}) \cdot 10}{15} \right] \cdot 5$$


+26

$$V_o(t) = \left[100 + 9e^{-t} - 25 \right] \frac{1}{3}$$


$$V_o(t) = 25 + 3e^{-t} \text{ volts}$$

Plotted

$t=0^+$

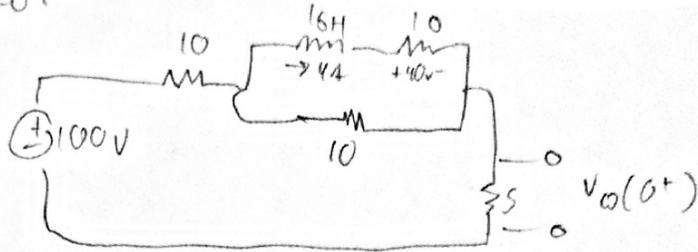

$t=\infty$

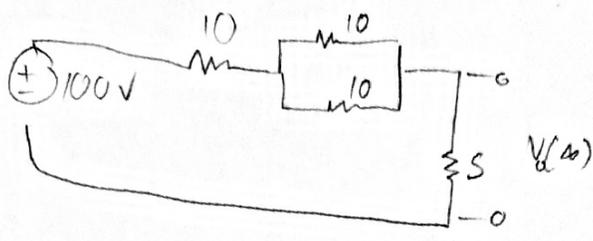

$$V_o(\infty) = \frac{10 + 5 + 5}{10 + 5 + 5} 100v = 25v$$

find the current and voltage in the inductor first.

$$i_L(0^+) = 4A$$

$$i_L(\infty) = \frac{V_{o(\infty)}}{10\Omega} = \frac{25v}{10\Omega} = 2.5A$$

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty))e^{-t/\tau}$$


$$= 2.5 + (4 - 2.5)e^{-t/\tau}$$

$$= 2.5 + 1.5e^{-t/\tau} A$$

$$V_L(t) = L \frac{di_L(t)}{dt} = (-1.5e^{-t/\tau}) \left(\frac{1}{\tau}\right) (16H)$$

$$V_L(t) = -24e^{-t} \text{ volts}$$

$$V_L(0^+) = -24v$$

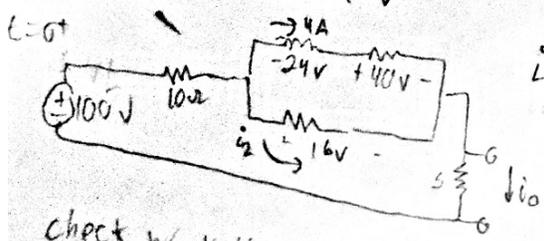



$$i_2 = \frac{16v}{10\Omega} = 1.6A$$

$$i_o = i_2 + i_L(0^+) = 5.6A$$

$$V_o(0^+) = 5\Omega \cdot 5.6A = 28v$$


check w/ voltage divider
 $(100 - 16) \cdot \frac{1}{3} = 28v$

Req for inductor

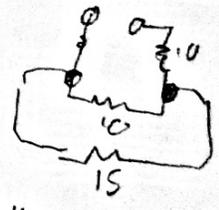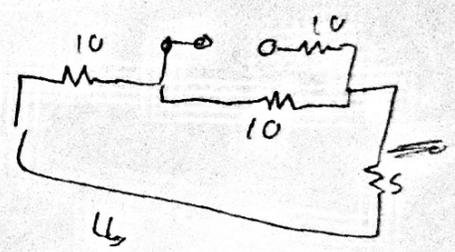

$$10 \parallel 15 + 10 = 16\Omega$$
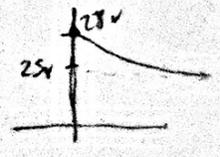
$$\tau = L/R = \frac{16}{16} = 1 \text{ second}$$



7 $V_o(t) =$