

UCLA

Department of Electrical Engineering

EE10 Final

Instructor: Prof. Gupta

Spring 2011

June 8th, 2011

1. Exam is closed book. You are allowed **one 8 ½ x 11” double-sided cheat sheet.**
2. Calculators are allowed.
3. **Cross out everything that you don't want me to see. Points will be deducted for everything wrong!**
4. **Do NOT use Laplace Transforms to solve any problems.**

Name:

*Solution*

Student ID:


Student on Left:

Student on Right:

Student in Front:

Problem	Maximum Score	Your Score
1	10	
2	10	
3	11	
4	9	
5	10	
Total	50	

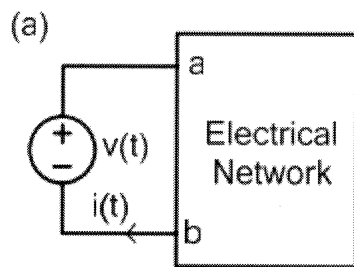**Q1. (a) (5 points)** Figure (a) shows a voltage source  $v(t)$ , applied to a linear electrical network that potentially contains independent and dependent sources, resistances, inductances, and capacitances. Figure (b) shows steady state measurements obtained for the set-up shown in Figure (a). Determine the Thevenin equivalent circuit for the electrical network from these measurements.



(b)

$v(t)$ in Volts	$i(t)$ in Amps
$\sin(10^3 t)$	0
$\cos(10^3 t)$	$(\sqrt{2})\cos(10^3 t + 45^\circ)$


$i(t) = 0$  gives open circuit voltage  $V_{th} = \sin 10^3 t$

given Thevenin equivalent, current  $i(t) = \frac{V(t) - V_{th}(t)}{Z_{th}}$

when  $v(t) = \cos 10^3 t$   $i(t) = \sqrt{2} \cos(10^3 t + 45^\circ)$

$$V_m = 1 \quad V_{thm} = e^{-j90^\circ} \quad I_m = \sqrt{2} e^{j45^\circ}$$

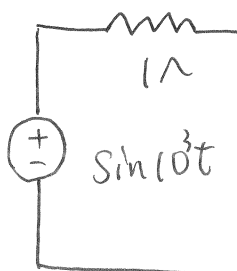
$$\text{Therefore } Z_{th} = \frac{V_m - V_{thm}}{I_m} = \frac{1 + j}{\sqrt{2} e^{j45^\circ}} = 1$$




$$V_{th} = \sin 10^3 t$$

$$Z_{th} = 1 \Omega$$

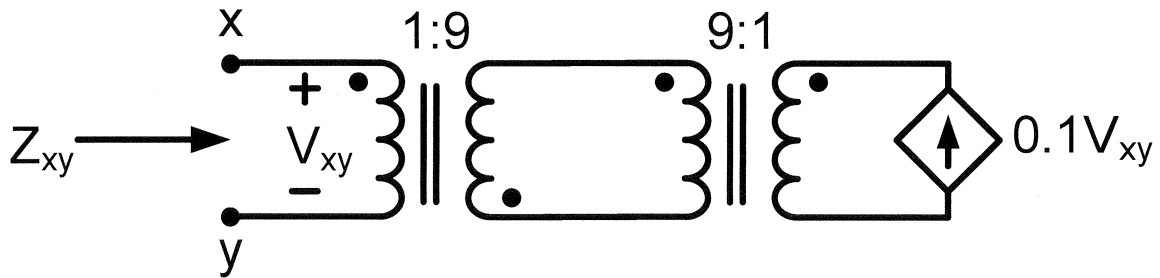(b) (5 points) Determine the impedance,  $Z_{xy}$ , looking into the terminals x and y. Assume the transformers are ideal.



Apply test source  $V_T$

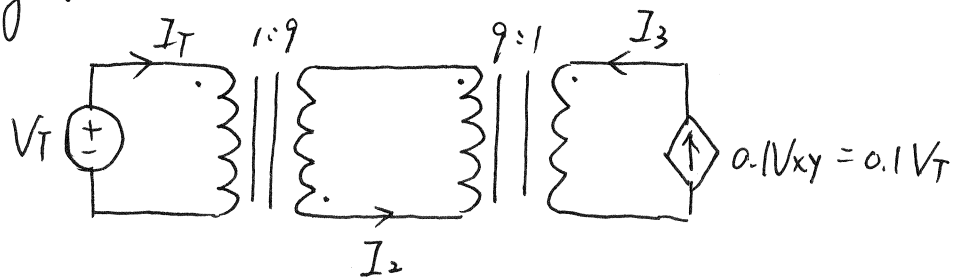

According to the ideal transformer


$$I_2 = \frac{1}{9} I_1 \quad I_3 = 9 I_2 = \frac{1}{9} I_1 \cdot 9 = I_1$$

And  $I_3 = 0.1V_{xy} = 0.1V_T = I_1$  then


$$Z_{xy} = \frac{V_T}{I_1} = \frac{V_T}{0.1V_T} = 10\Omega$$

$Z_{xy} = 10\Omega$

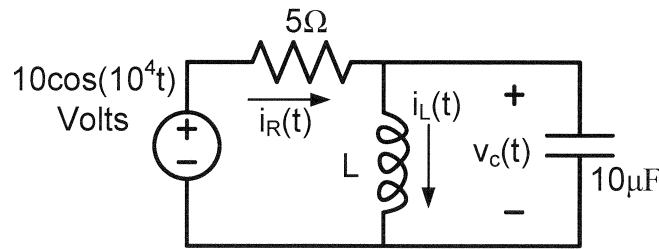**Q2. (a) (3 points)** Draw the phasor domain representation for the circuit shown in the figure.


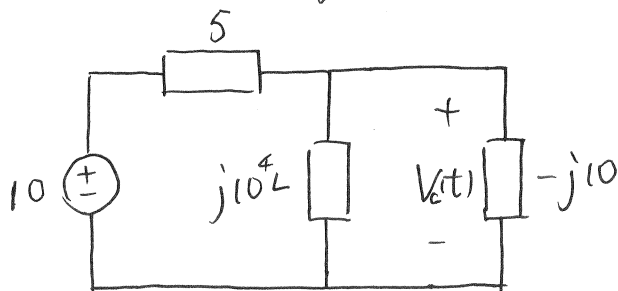
$$\omega = 10^4 \quad \frac{1}{j\omega C} = -j10$$



**(b) (3 points)** Determine the value of the inductance  $L$ , such that the steady state component of  $v_C(t)$  is in phase with the voltage source ?

$$Z_{LC} = \frac{+j(10^4 L)(-j10)}{j10^4 L - j10} = -\frac{j(10^5 L)}{10^4 L - 10} = -j \frac{10^5 L}{10^4 L - 10}$$



$$V_C = \frac{Z_{LC}}{Z_R + Z_{LC}} \cdot 10 = \frac{10}{1 + Z_R/Z_{LC}} = \frac{10}{1 + 5 \frac{10^4 L - 10}{-j10^5 L}} = \frac{10}{1 + j5 \frac{10^4 L - 10}{10^5 L}} = A e^{j\varphi}$$

where  $\tan\varphi = 5 \frac{10^4 L - 10}{10^5 L}$   $V_C$  in phase with voltage source

$$\varphi = 0 \quad \text{therefore } 10^4 L - 10 = 0 \Rightarrow L = 1 \text{ mH}$$

$L = 1 \text{ mH}$

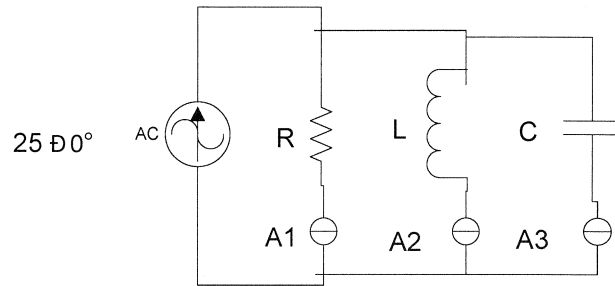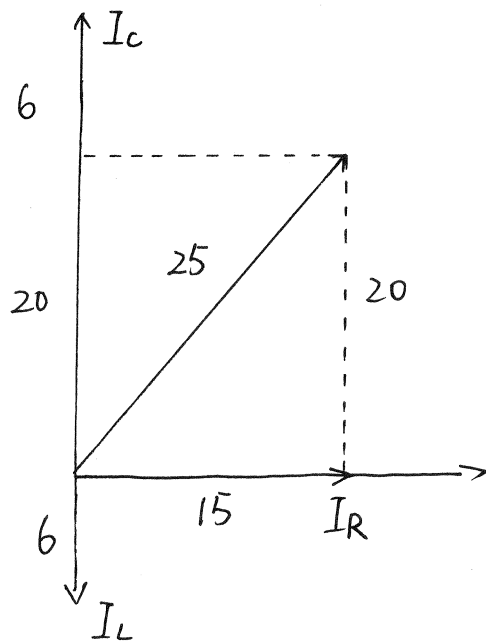(c) (4 points) A1, A2, A3 are three ammeters which read just the magnitudes of the currents. A1 and A2 read 15A and 6A respectively. What does A3 read? Solve the problem graphically.



$$I_C = 20 + 6 = 26$$

$$|I_C + I_R + I_L| = 25 \quad \text{then} \quad (A_3 - A_2)^2 + A_1^2 = 25^2$$

$$A_1 = 15 \quad A_2 = 6 \Rightarrow A_3 - A_2 = \pm 20 \Rightarrow A_3 = 26 \quad \text{or} \quad -14$$

Since  $I_C$  and  $I_L$  are in different direction, the  $A_3, A_2$  have the same sign. therefore  $A_3 = 26$



**A3 reads 26V**

**Q3.** Consider the circuit with the following elements:


$V_{S1} = 16 \text{ V}$ ;  $V_{S2} = -12 \text{ V}$  (notice the **negative sign!**);  $R_1 = 20 \Omega$ ;  $R_2 = 60 \Omega$ ;  $R_3 = 5 \Omega$ ;  $R_4 = 6 \Omega$ ;  $R_5 = 6 \Omega$ ;  $R_6 = 7 \Omega$ ;  $L = 150 \text{ mH}$ ;  $R_L = 20 \Omega$

Assume DC steady-state conditions at  $t < 0$ .

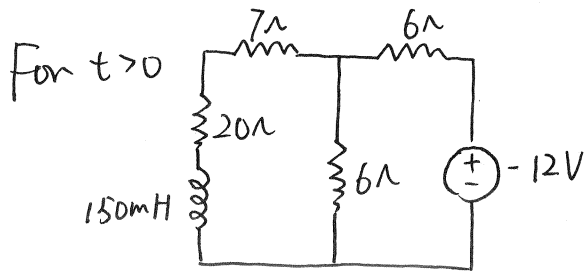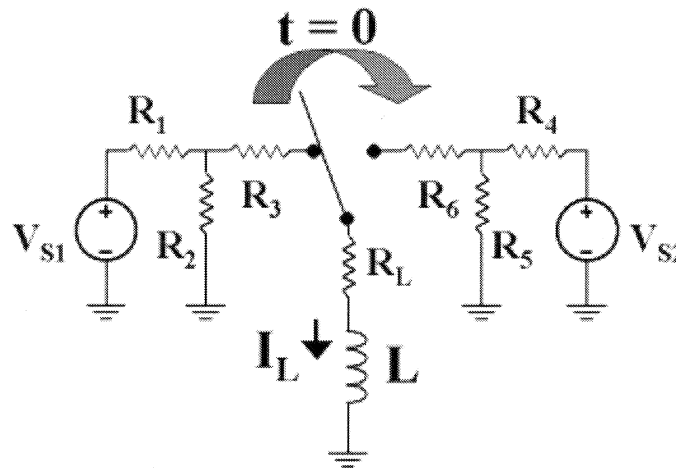**(a) (5 points)** Write and solve the differential equation for the inductor current  $i_L$  as a function of time at  $t > 0$ .



apply source transformation

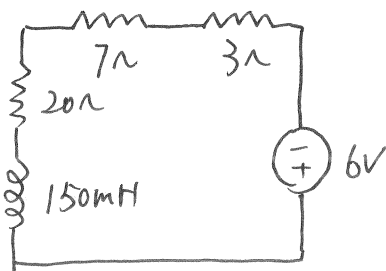


KVL:  $i_L \cdot 30 + 150\text{mH} \frac{di_L}{dt} + 6 = 0$

solving 1st order differential equations

$$i_L' = -0.2 \quad i_L = K e^{-200t}$$

$$i_L(t) = i_L + i_L' = K e^{-200t} - 0.2$$

For  $t < 0$  find steady state

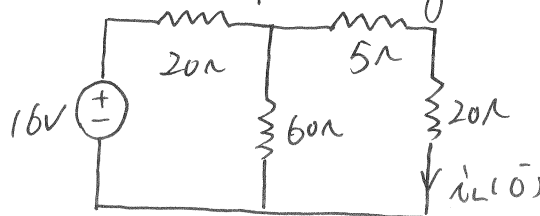

$$i_L(0^-) = \frac{16}{20+60} \cdot \frac{60}{60+25} = 0.3 \text{ A} = i_L(0^+)$$

$$i_L(0^+) = K - 0.2 = 0.3 \Rightarrow K = 0.5$$

$$i_L(t) = 0.5 e^{-200t} - 0.2$$

**( $t > 0$ )**

**(b) (3 points)** Determine the range of resistances  $R_6$  to ensure the time constant  $\tau < 1$  msec.

$$\tau = \frac{L}{R_{\text{total}}} = \frac{0.15}{23 + R_6} < 10^{-3}$$

$$\text{then } (23 + R_6) > 0.15 \times 10^3 = 150 \Rightarrow R_6 > 127 \Omega$$

$$R_6 > 127 \Omega$$

**(c) (3 points)** A second order circuit shows an underdamped natural response  $i(t) = \exp(-t)\cos(2t + \pi/3)$ . What is the characteristic equation for this circuit?

$$\text{From natural response } s_{1,2} = -1 \pm j2$$


$$\text{then } (s+1)^2 = -4 \Rightarrow s^2 + 2s + 5 = 0$$

$$\text{Characteristic equation: } s^2 + 2s + 5 = 0$$

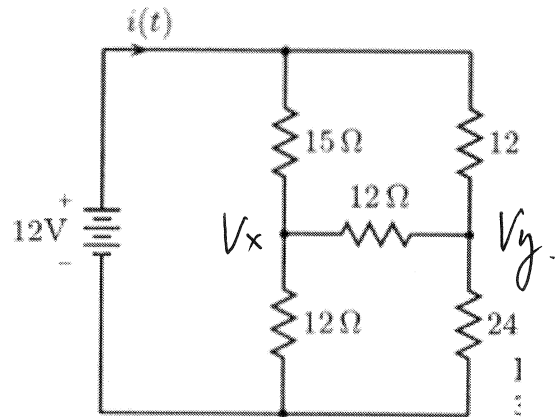**Q4. (a) (5 points)** Compute the power supplied by the battery in the circuit below.

Apply node method

$$\begin{cases} \frac{V_x - 12}{15} + \frac{V_x - V_y}{12} + \frac{V_x}{12} = 0 \\ \frac{V_y - 12}{12} + \frac{V_y - V_x}{12} + \frac{V_y}{24} = 0 \end{cases}$$



Solving for  $V_x, V_y$

$$\begin{cases} V_x = 6V \\ V_y = 7.2V \end{cases}$$


So  $i(t) = \frac{12 - 6}{15} + \frac{12 - 7.2}{12} = 0.8A$

power supplied by 12V:  $p = 12V \times 0.8A = 9.6W$


**Power supplied by 12V: 9.6W**



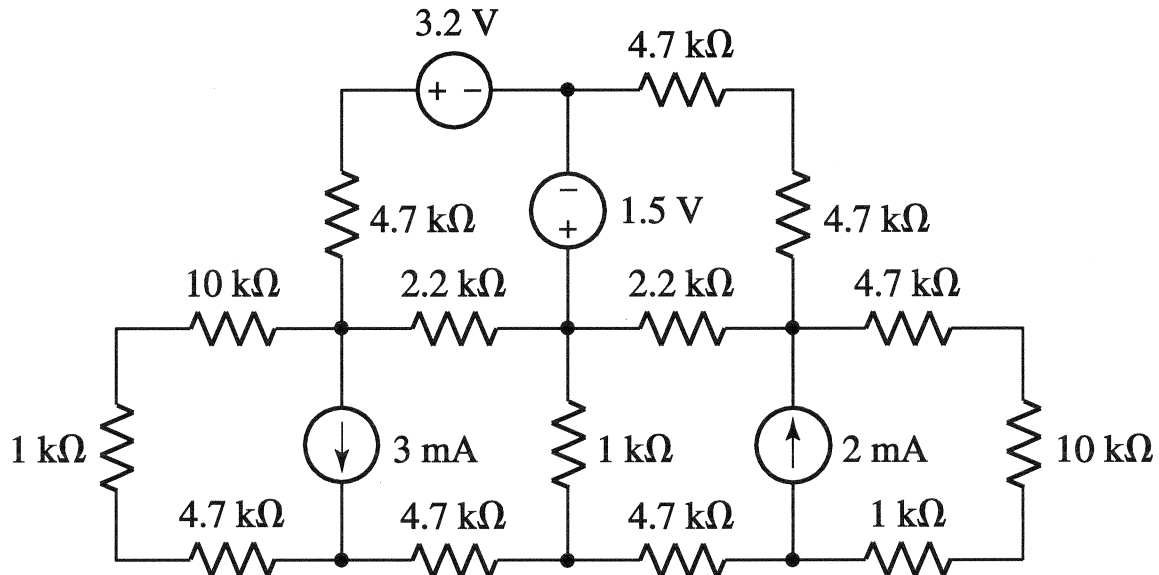(b) (4 points) Write the loop equation in matrix form for the circuit below. Make any simplifications to the circuit needed to do that. Clearly label the currents. You don't need to solve the equations.



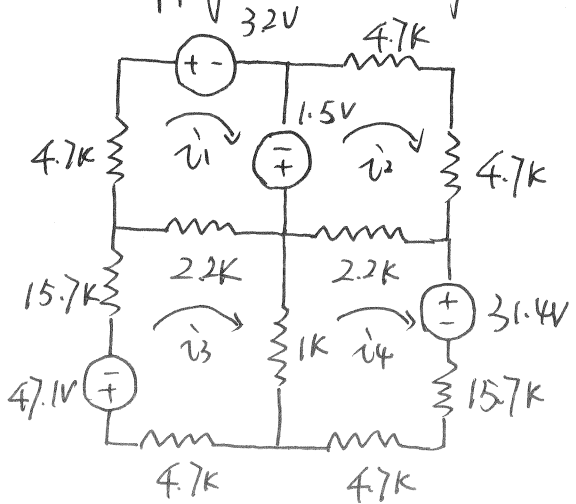Apply source transformation first, then write loop equation




$$\begin{bmatrix} 6.9k & 0 & -2.2k & 0 \\ 0 & 11.6k & 0 & -2.2k \\ -2.2k & 0 & 23.6k & -1k \\ 0 & -2.2k & -1k & 23.6k \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} -1.7 \\ -1.5 \\ -47.1 \\ -31.4 \end{bmatrix}$$

**Q5. (a) (3 points)** you were taught that superposition works for RLC circuits. So to find out the loop current in the adjacent circuit, you remove  $V_1$  calculate current and then remove  $V_2$  and calculate current and then add them up to find total current as follows:

$$I_1 = (V_2 + V_3)/R; I_2 = (V_1 + V_3)/R$$

$$I = I_1 + I_2 \text{ (by superposition)} = (V_1 + V_2 + 2V_3)/R$$

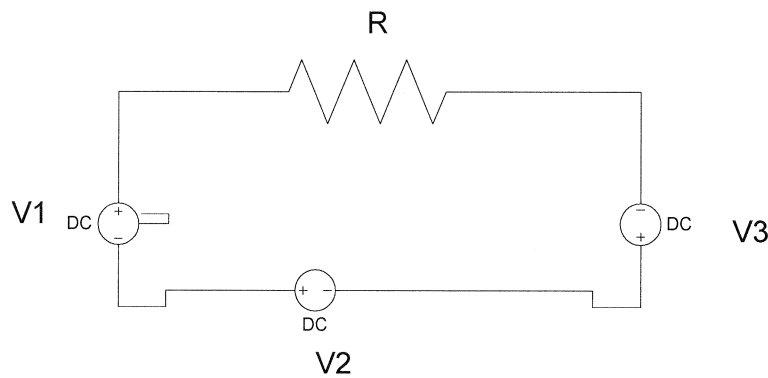But for this simple circuit, you know  $I$  should be  $(V_1 + V_2 + V_3)/R$ . Now you are confused and start cursing your professor who told you that RLC circuit is linear and superposition works. What went wrong here?



For superposition, we should find response for one source at



a time  $I_1 = \frac{V_1}{R}$   $I_2 = \frac{V_2}{R}$   $I_3 = \frac{V_3}{R}$

$$I = I_1 + I_2 + I_3 = \frac{V_1 + V_2 + V_3}{R} \text{ (by superposition)}$$

In the wrong set up of problem,  $V_3$  has been active twice. which leads to wrong answer

**(b) (4 points)** What is the Thevenin equivalent for the following circuit? The network N has v-i relationship of  $v_n(t) = 3i_n(t) + 7$ . What is the Thevenin equivalent if you remove  $v_s(t)$ ?


$v(t) = v_s(t)$  Thevenin equivalent

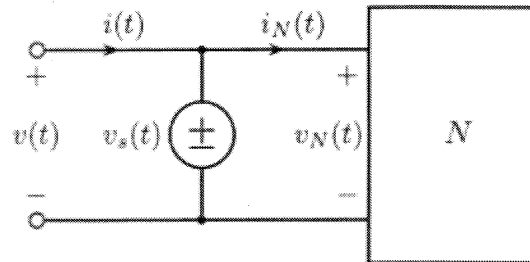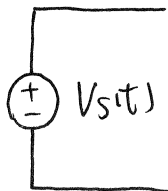

After removing  $v_s(t)$ .  $v(t) = 3i(t) + 7$

open circuit  $i(t) = 0$   $V_{th} = 7V$  short-circuit  $0 = 3i(t) + 7$

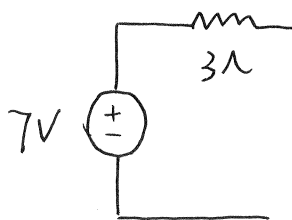$i(t) = -\frac{7}{3}$  However  $i_{sc} = -i(t) = \frac{7}{3}$   $R_{th} = \frac{7V}{7/3A} = 3\Omega$



**(c) (3 points)** You design a "special" capacitor for which  $Q = CV^{1.5}$ . What is the energy stored in it when the voltage across it is  $V$  (in terms of  $C$  and  $V$ )?

$$q = cV^{1.5}$$

$$W_c = \int_0^V v dq = \int_0^V v c 1.5 v^{0.5} dv = 1.5c \int_0^V v^{1.5} dv$$

$$= 1.5c \frac{1}{1.5+1} v^{2.5} \Big|_0^V$$

$$= 0.6cV^{2.5}$$

$$W_c = 0.6cV^{2.5}$$