

EE10 Final

Department of Electrical Engineering, UCLA

Summer 2017

Instructor: Prof. Gupta

1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. Do NOT use Laplace Transforms to solve any problems.
4. No points will be given without proper explanations

Name:

Student ID:

Student on Left:

Student on Right:

Student in Front:


Time: 135 minutes

Problem	Maximum Score	Your Score
1	12	
2	8	
3	12	
4	8	
Total	40	

**Q1. 12 points (2+2+2+6)**

For the circuit below, the 15A current source has been operating for a long time and suddenly jumps in value to 22A at  $t=0$ . Find  $v_s$  when:

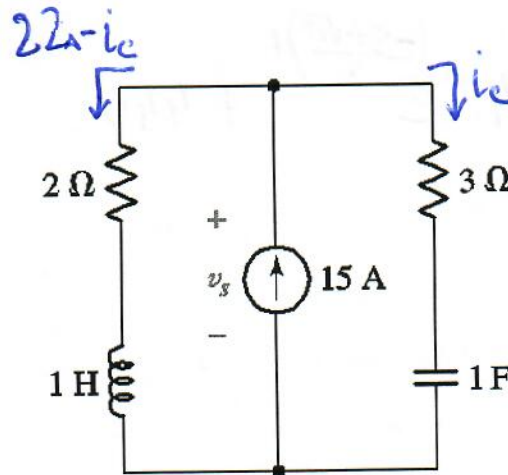- a)  $t=0^-$
- b)  $t=0^+$
- c)  $t=\infty$
- d)  $t=4s$



a)  $V_s(0^-) = 2\Omega \cdot 15A = \boxed{30V}$

b)  $V_s(0^+) = 7A \cdot 3\Omega + V_c(0^+) = 21V + \overbrace{V_c(0^-)}^{=30V} = \boxed{51V}$

c)  $V_s(t \rightarrow \infty) = 2\Omega \cdot 22A = \boxed{44V}$

d) 
$$i_c 3\Omega + \frac{1}{C} \int_{0^+}^t i_c dt + V_c(0^+) = (22A - i_c) 2\Omega + L \frac{d}{dt} (22A - i_c)$$

$$-14A + i_c 5\Omega + \frac{1}{1F} \int_{0^+}^t i_c dt = -1H \frac{d}{dt} i_c \rightarrow i_c'' + 5i_c' + i_c = 0$$

$s^2 + 5s + 1 = 0 \rightarrow \frac{-5 \pm \sqrt{25-4}}{2} = \frac{-5 \pm \sqrt{21}}{2} \rightarrow$  overdamped system.

$$V_s(t) = A e^{\frac{-5+\sqrt{21}}{2}t} + B e^{\frac{(-5-\sqrt{21})}{2}t} + \underbrace{V_s(\infty)}_{=44V} = A e^{\frac{(-5+\sqrt{21})}{2}t} + B e^{\frac{(-5-\sqrt{21})}{2}t} + 44V$$

$V_s(0^+) = A + B + 44V = 51V \rightarrow A + B = 7V$

$$V_s'(0^+) = -\left(\frac{5+\sqrt{21}}{2}\right)A + \left(\frac{-5+\sqrt{21}}{2}\right)B = \underbrace{V_s'(0^+) - 15A \cdot 2\Omega}_{=7A}$$

$$V_s' = i_c' 3\Omega + \frac{i_c}{1F} = \frac{-3\Omega}{1H} V_L + \frac{i_c}{1F} \rightarrow V_s'(0^+) = -3 \overbrace{V_L(0^+)}^{=31V-30V} + \overbrace{i_c(0^+)}^{=7} = -3(1V) + 7 = -5 \frac{V}{sec}$$

$$V_L = L \frac{d}{dt} (22A - i_c) \rightarrow i_c' = -\frac{V_L}{L}$$

$$A+B=7V$$

$$-\left(\frac{s+\sqrt{21}}{2}\right)A + \left(\frac{-s+\sqrt{21}}{2}\right)B = -56 \frac{V}{sec}$$


$$\begin{bmatrix} 1 & 1 \\ -\left(\frac{s+\sqrt{21}}{2}\right) & \frac{-s+\sqrt{21}}{2} \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} 7 \\ -56 \end{bmatrix} \rightarrow \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} 11.90 \\ -4.9 \end{bmatrix}$$

$$V_s(t) = 11.9e^{-\left(\frac{s+\sqrt{21}}{2}\right)t} - 4.9e^{\left(\frac{-s+\sqrt{21}}{2}\right)t} + 44V$$

$$V_s(t=4sec) \approx 41.874V$$

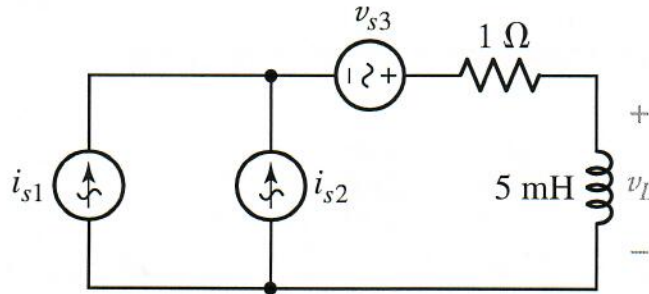**Q2. (8 points)**

In the circuit below,  $i_{s1} = 2 \cos(200t)$  A,  $i_{s2} = 1 \cos(100t)$  A, and  $v_{s3} = 2 \sin(200t)$  V. Find  $v_L(t)$ .




$$v_L(t) = L \frac{d}{dt} (i_{s1} + i_{s2}) = 5 \text{ mH} [-400 \sin(200t) - 100 \sin(100t)]$$

$$v_L(t) = -2 \text{ V} \sin(200t) - \frac{1}{2} \text{ V} \sin(100t)$$

**Q3(5 + 5 + 2 = 12points)**

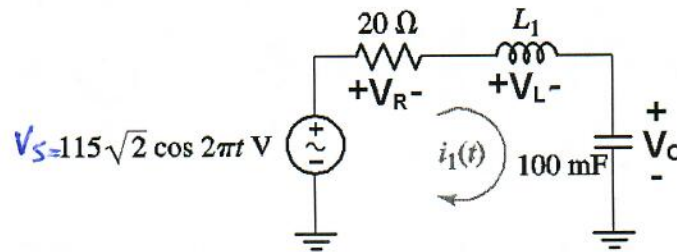- a) Design a combination of inductors, resistors, and capacitors that has an admittance of  $4\angle -10^\circ$  nS at  $\omega = 50$  rad/s.
- b) In the circuit below  $i_1(t) = 8.132 \cos(2\pi t)$  A. What is the inductance of  $L_1$ ?



c) Draw a phasor diagram showing  $I$ ,  $V_R$ ,  $V_C$ .

a)  $Y(\omega) = 4 \times 10^{-9} \angle -10^\circ \rightarrow Z(\omega) = \frac{10^9}{4} \angle 10^\circ \rightarrow$  inductive impedance.


$Z(\omega) = R + jL\omega = \sqrt{R^2 + (L\omega)^2} \angle \tan^{-1}\left(\frac{L\omega}{R}\right)$

$$\left\{ \begin{array}{l} R^2 + (L\omega)^2 = \frac{10^{18}}{16} \\ \frac{L\omega}{R} = \tan(10^\circ) \end{array} \right\} \rightarrow \begin{array}{l} L \approx 868 \text{ KH} \\ R \approx 246.2 \text{ M}\Omega \end{array}$$

b)  $V_s$  and  $i_1$  are in phase  $\rightarrow -X_L = X_C \rightarrow \omega L = \frac{1}{\omega C} \rightarrow L = \frac{1}{\omega^2 C} \approx 253.3 \text{ mH}$



c)  $V_C = 8.132 \angle 0^\circ \cdot \frac{1}{j\omega C}$

$V_C = 12.94 \angle -90^\circ$

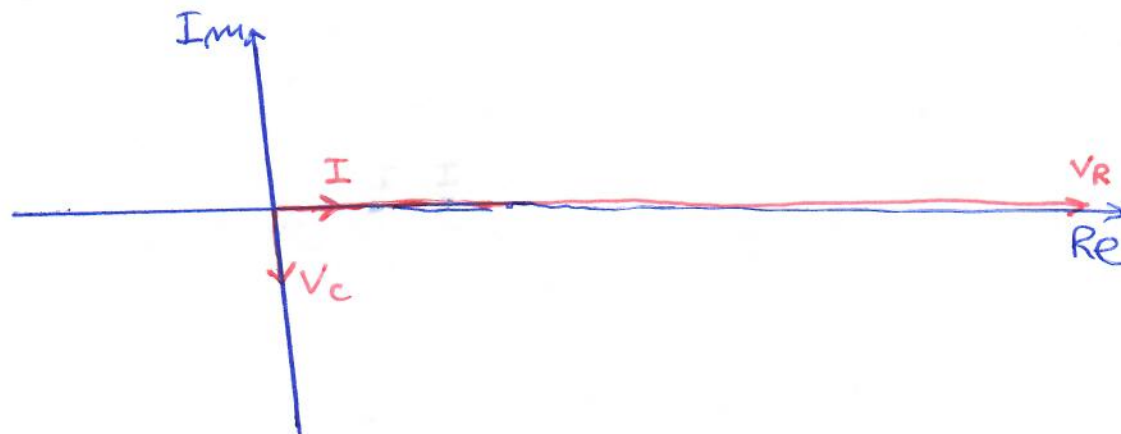

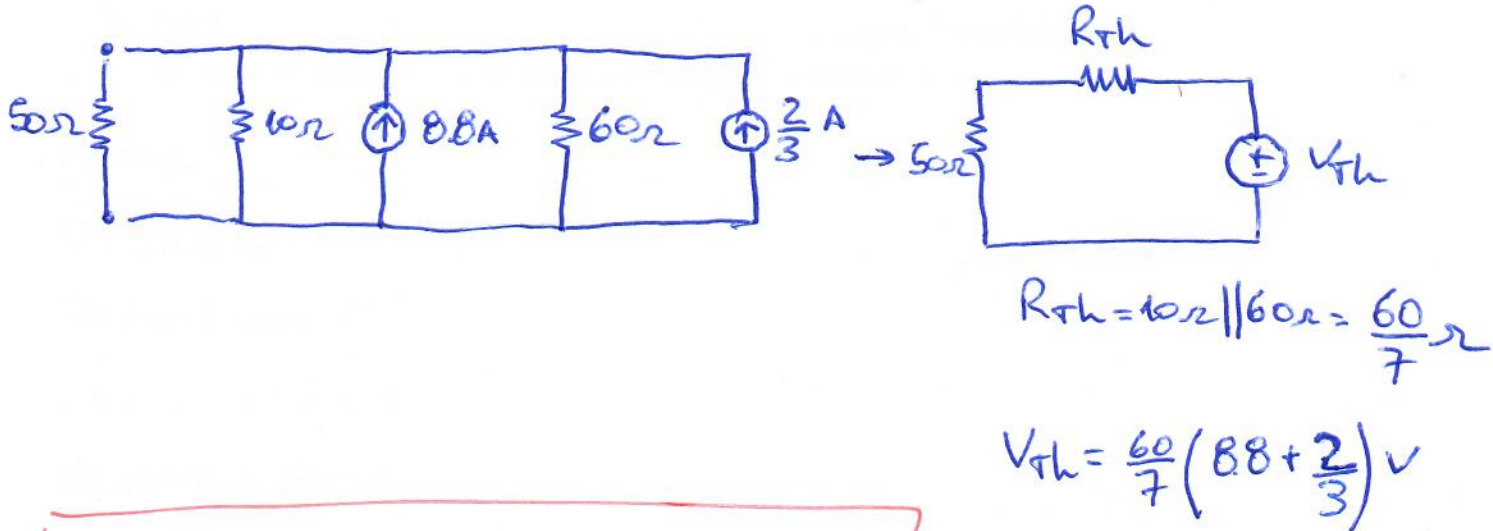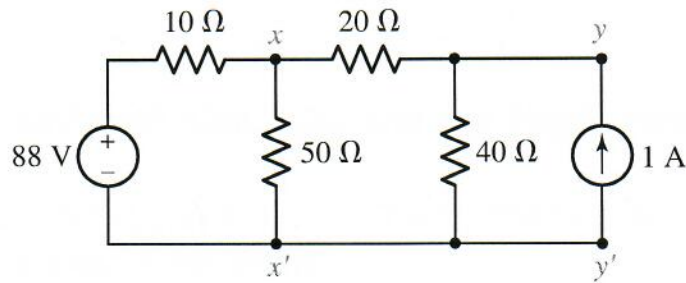Q4. (8 points)

Find the power consumed by resistor between x and x' using Thevenin equivalent.



$$P_{50\Omega} = \left( V_{Th} \frac{50\Omega}{50\Omega + R_{Th}} \right)^2 \frac{1}{50\Omega} \approx 95.96 \text{ W}$$