

ECE10 Midterm I

Department of Electrical Engineering, UCLA

Spring 2019

Instructor: Prof. Gupta

1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. No points will be given without proper explanations
4. Time allotted: 75 minutes

Name:  
 Student  
 Student  
 Student  
 Student




Problem	Maximum Score	Your Score
1	8	8
2	4	4
3	8	8
4	10	10
Total	30	30

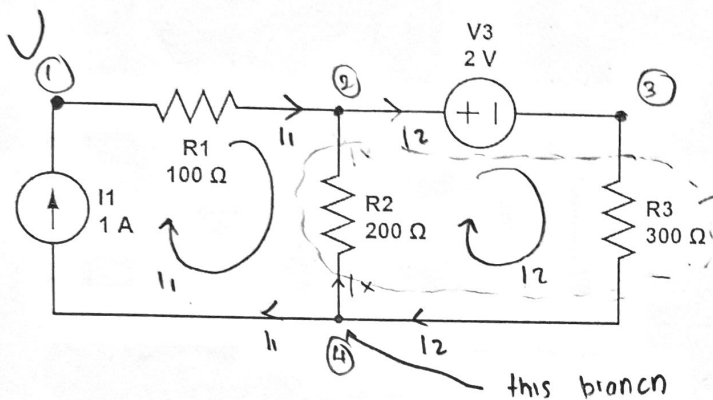
**Q1. (2+2+2+2 = 8 points)**

For this circuit, please answer the following questions:


- How many nodes and how many branches?
- Please draw the equivalent graph after killing the independent sources.
- Please draw ONE spanning tree for the graph.
- Write the KVL equations based on the cut-set. Clearly mark which branch is the loop current flowing in.




Finding  $i_a$

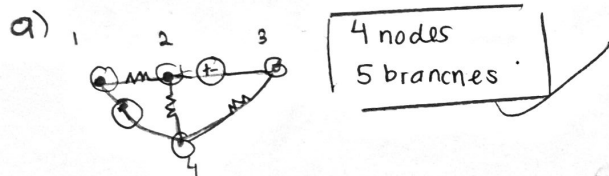

(b) Killing all independent sources

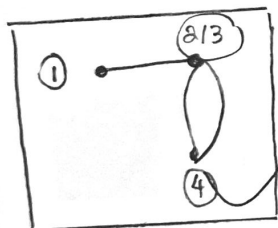


(c) Spanning Tree

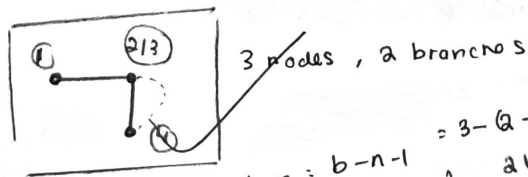

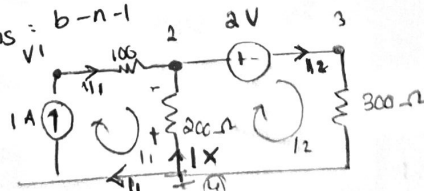(d) 1 chord

minimum KVL equations =  $b - n + 1 = 5 - 4 + 1 = 2$



KVL equation between loop

$$-12(300) - (i_2 - i_1)200 - 2 = 0 \quad \text{--- (1)}$$

$$(v_1 - v_0) = -i_1(100) = -(i_2 - i_1)(200)$$

$$v_1 = (i_1 - i_2)(200) + i_1(100)$$

$$v_1 = 200i_1 + 100i_1 - 200i_2$$

$$v_1 = 300i_1 - 200i_2$$

$$i_x + i_1 = i_2$$

$$i_x = i_2 - i_1$$

$$i_1 = A$$


Second KVL equation

$$(1300i_1 - 200i_2) - (100i_1) + (i_2 - i_1)(200) = 0 \quad \text{--- (2)}$$

$$\text{or } v_1 - i_1(100) + (i_2 - i_1)(200) = 0$$

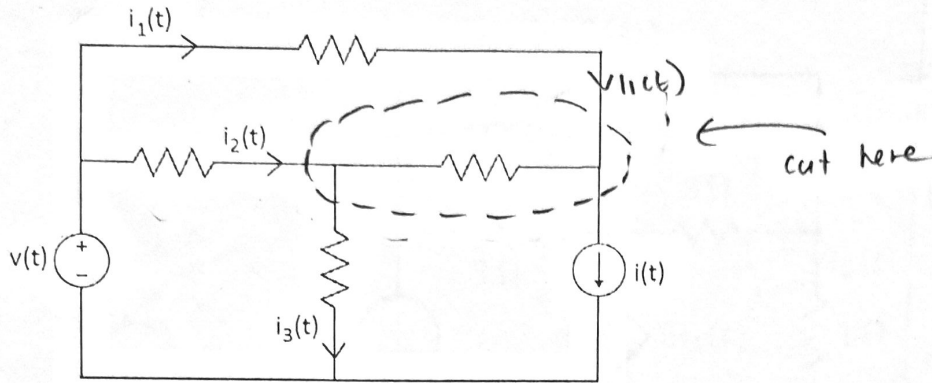Q2. (4 points)

Draw the cutset relating  $i_1$ ,  $i_2$ ,  $i_3$  and write exactly ONE KCL equation corresponding to the cutset.



our cutset










by supernodal analysis,

$$i_1(t) + i_2(t) = i_3(t) + i(t)$$



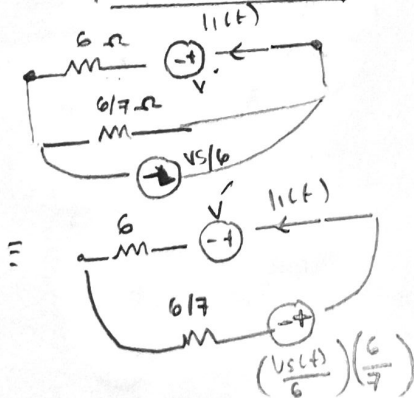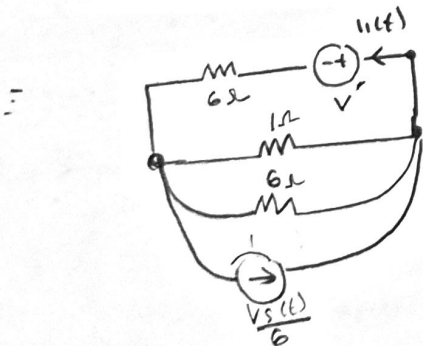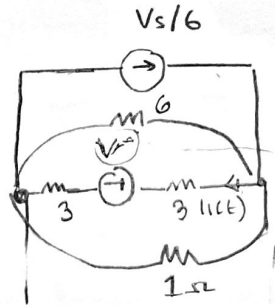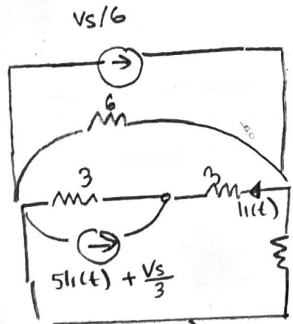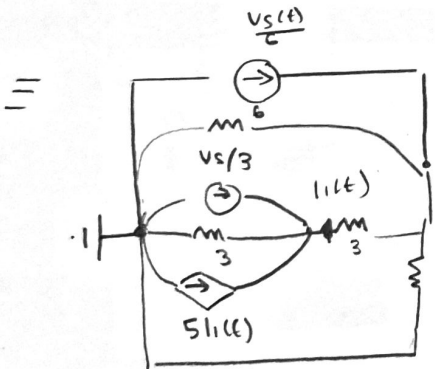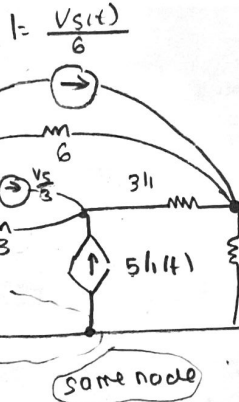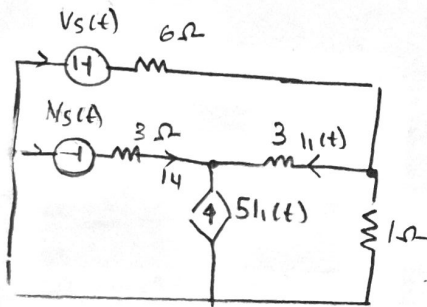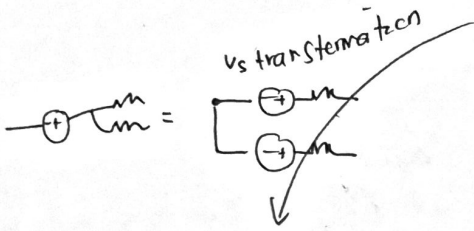
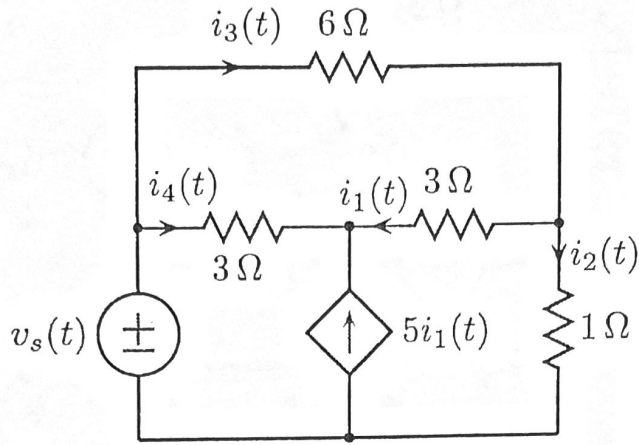
Q3. 8 points

Find  $i_1$  in terms of  $v_s$  using source transformations.



$$v' = (5i_1(t) + \frac{v_s}{3}) \cdot 3$$

$$v' = 15i_1(t) + v_s$$

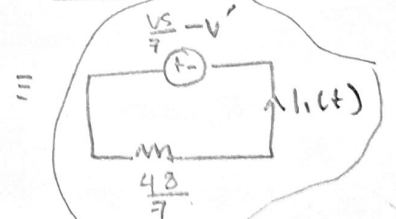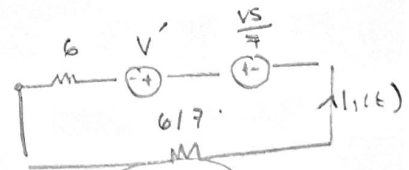

answer at top

$$v' = 15i_1(t) + v_s$$

$$\frac{v_s}{7} - (15i_1 + v_s) = i_1(t) \frac{48}{7}$$

$$-\frac{6}{7}v_s = i_1(t) \left[ \frac{48}{7} + 15 \right]$$

$$\frac{153}{7}i_1(t) = -\frac{6}{7}v_s$$

$$i_1(t) = -\frac{2}{51}v_s \text{ A}$$



Answer  $\uparrow$

$$\text{or } i_1(t) = -0.0392v_s \text{ A}$$



Q4. 10 points

Find the thevenin equivalent of the circuit below at the two nodes on the right using superposition.

Zero-out voltage source  
 $\Rightarrow$  becomes a short circuit

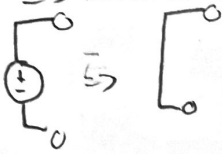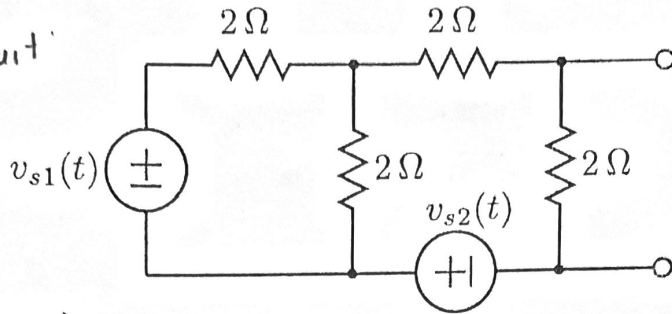Superposition: zero out  $v_{s1}(t)$


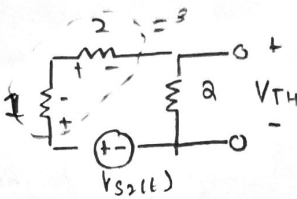
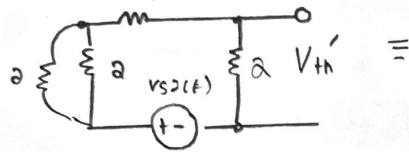


using voltage divider equation

$$V_{TH}' = \frac{2}{2+2+1} v_{s2}(t)$$

$$V_{TH}' = \frac{2}{5} v_{s2}(t)$$



Zero-out  $v_{s2}(t)$

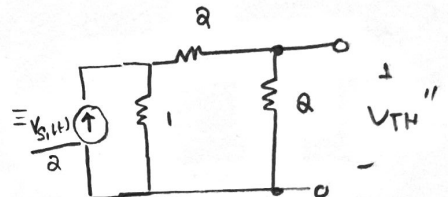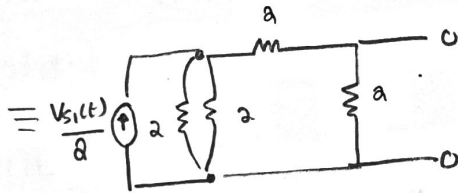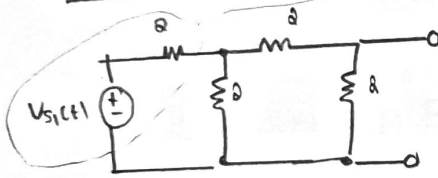

by voltage divider equation

$$V_{TH}'' = \frac{2}{2+2+1} \left( \frac{v_{s1}(t)}{2} \right)$$


$$V_{TH}'' = \frac{1}{5} v_{s1}(t)$$

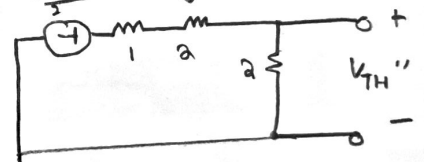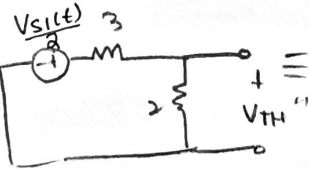

by superposition, we get:



$$V_{TH} = V_{TH}' + V_{TH}'' = 0.4 v_{s2}(t) + 0.2 v_{s1}(t)$$

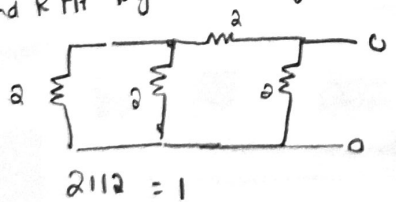Find  $R_{TH}$  by disabling all indep sources




$$2 \parallel 2 \parallel 2 = 1$$

$$R_{TH} = 1.2 \Omega$$

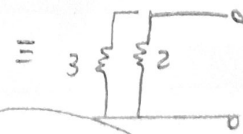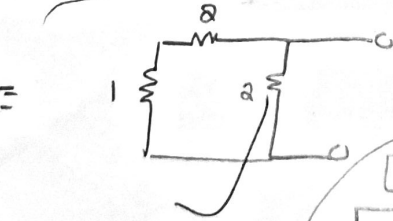

$$\begin{aligned} 3 \parallel 2 \\ = \frac{3 \cdot 2}{3+2} = \frac{6}{5} \end{aligned}$$

$\therefore$  Thevenin equivalence

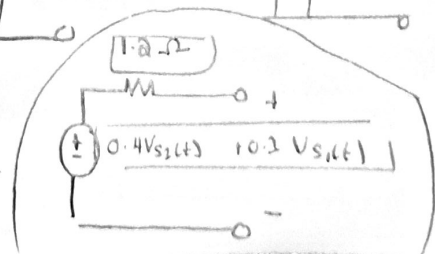

← answer