
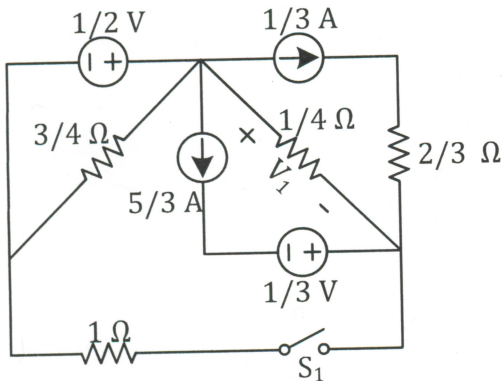


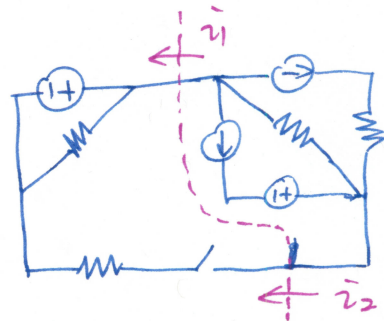**Question 1 (6 points)**

Use source transformation to solve the following question, what is the voltage  $V_1$  when switch  $S_1$  is open?



⇒




The above dashed line goes through a cutset.  $i_1 + i_2 = 0$


Since  $i_2 = 0$ ,  $i_1 = 0$  as well.

⇓

Simplified Circuit:

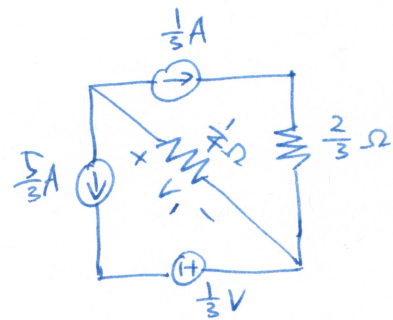

⇐

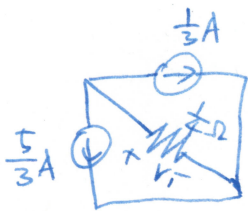

$$-V_1 = \left(\frac{1}{3} + \frac{5}{3}\right) \times \frac{1}{4} = \frac{1}{2} V$$

$$V_1 = -\frac{1}{2} V$$

**Question 2 (4 + 3 points)**

- (a) You solved some circuit using loop method and after an hour of calculations, you wrote down the matrix equations corresponding to it but unfortunately you spilled coffee on the piece of paper. As a result only part of the equations is visible:


$$\begin{bmatrix} v1 \\ v2 \\ v3 \\ v4 \end{bmatrix} = \begin{bmatrix} 1 & -3 & -8 & -2 \\ -3 & 4 & -1 & -7 \\ -8 & -1 & 9 & -5 \\ -2 & -7 & -5 & 2 \end{bmatrix} \begin{bmatrix} i1 \\ i2 \\ i3 \\ i4 \end{bmatrix}$$

What do you need to assume to fill in the remaining entries in the matrix? In this case, fill in the remaining entries.


( { Diagonal values are positive  
Non-diagonal values are non-positive  
matrix is symmetric )

We need to assume that there is no dependent sources in the circuit.

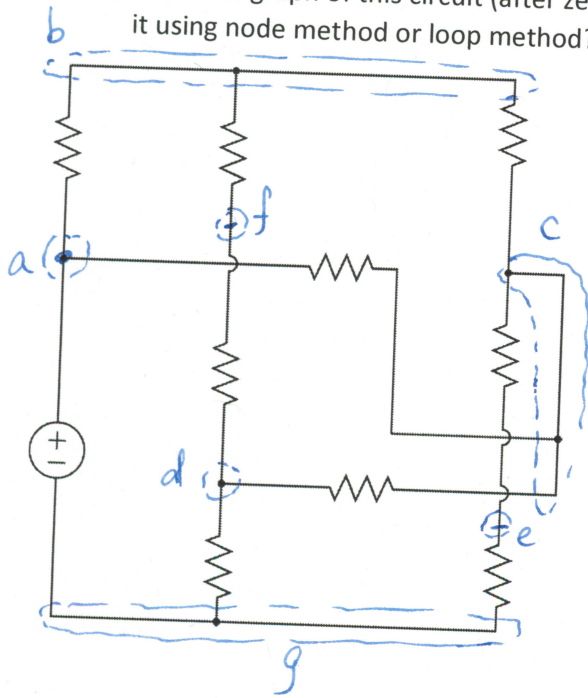(b) Draw the graph of this circuit (after zeroing the voltage source). Will it be better to solve it using node method or loop method?




Without zeroing voltage source

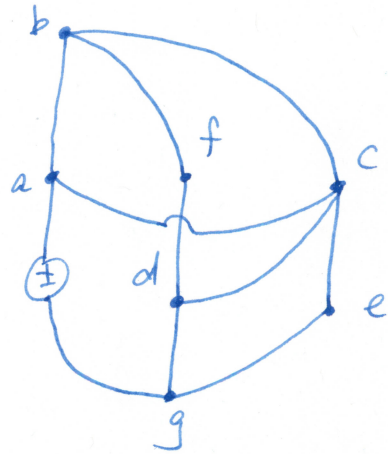

⇓

After zeroing the voltage source  
(combine "a" and "g")

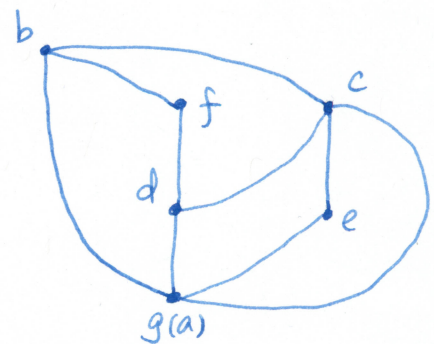There are 6 nodes  $\Rightarrow$  5 independent node voltages  
4 loops  $\Rightarrow$  4 independent loop currents




⇓

It's better to use loop method.

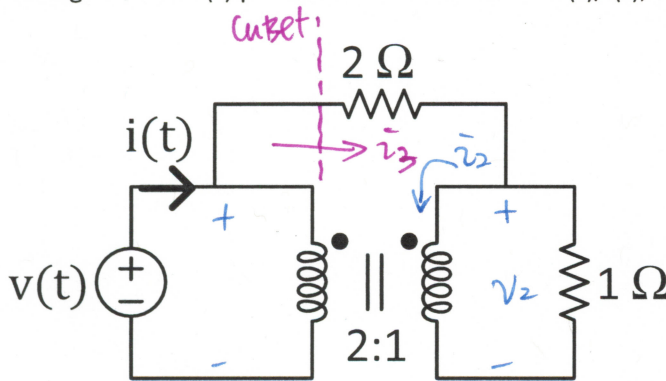Question 3 (6 points)

The voltage source  $v(t)$  perceives a resistance  $R = v(t)/i(t)$ , when  $v(t) = 5\cos(2t)$ ,  $R = ?$



Total current through cutset = 0

$$\Rightarrow i_3 = 0$$

$v(t) = 5\cos(2t)$  means that it's an AC voltage, and that the transformer is working normally.

Equations for ideal transformer:

$$\begin{cases} \frac{v}{2} = \frac{v_2}{1} \\ i \times 2 + i_2 \times 1 = 0 \end{cases}$$

We also know that:


$$-i_2 \times (1\Omega) = v_2$$

Therefore:

$$v = 2v_2 = -2i_2 = 2 \times (2i) = 4i$$

$$R = \frac{v}{i} = \boxed{4\Omega}$$

Question 4 (3 + 4 + 4 points)

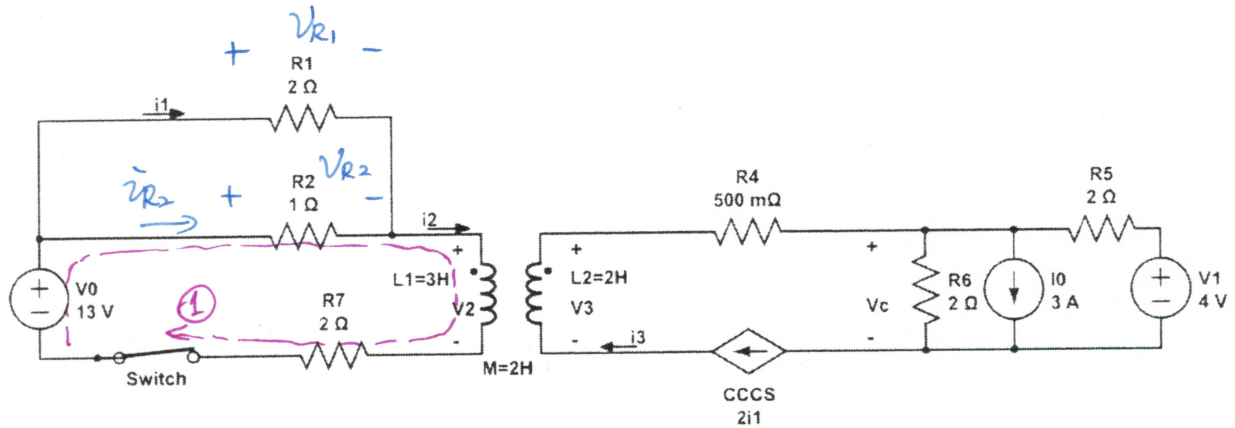

- Please represent  $V_2$  and  $V_3$  in term of  $i_2$ ,  $i_3$ ,  $L_1$ ,  $L_2$  and  $M$ .
- At time  $t = t_0$ ,  $i_1 = 1A$ . Please find the voltage  $V_2$  and current  $i_2$  at time  $t = t_0$ .
- At the same time  $t = t_0$ , calculate the voltage  $V_3$  and the voltage  $V_c$  at time  $t = t_0$ .

$$(a) \begin{cases} V_2 = L_1 \frac{di_2}{dt} - M \frac{di_3}{dt} \\ V_3 = M \frac{di_2}{dt} - L_2 \frac{di_3}{dt} \end{cases}$$

$$(b) \quad V_{R1} = \dot{i}_1 \times 2 = 2\dot{i}_1, \quad V_{R1} = V_{R2} \Rightarrow \dot{i}_{R2} = \frac{V_{R2}}{1} = 2\dot{i}_1$$

$$\dot{i}_2 = \dot{i}_1 + \dot{i}_{R2} = \dot{i}_1 + 2\dot{i}_1 = \underline{\underline{3\dot{i}_1}} = \underline{\underline{3A}}$$

$$\text{KVL on loop } \textcircled{1}: \quad 13 - \dot{i}_1 \times 2 - V_2 - \dot{i}_2 \times 2 = 0 \Rightarrow V_2 = \underline{\underline{5V}}$$

$$(c) \quad \text{Plug in values for equations in part (a):} \quad \dot{i}_2 = 3\dot{i}_1, \quad \dot{i}_3 = 2\dot{i}_1$$

$$5 = L_1 \frac{di_2}{dt} - M \frac{di_3}{dt} = 3 \times 3 \frac{di_1}{dt} - 2 \times 2 \frac{di_1}{dt} = 5 \frac{di_1}{dt} \Rightarrow \frac{di_1}{dt} = 1$$

$$V_3 = 2 \times 3 \frac{di_1}{dt} - 2 \times 2 \frac{di_1}{dt} = 2 \frac{di_1}{dt} = \underline{\underline{2V}}$$

To find  $V_c$ , apply source transformation on  $V_1$  and  $R_5$ :

