
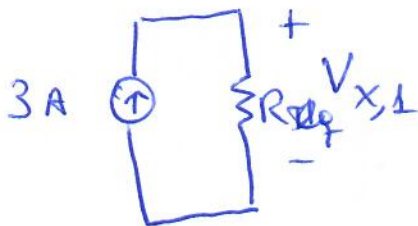
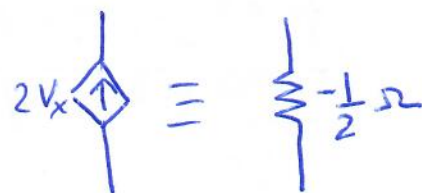
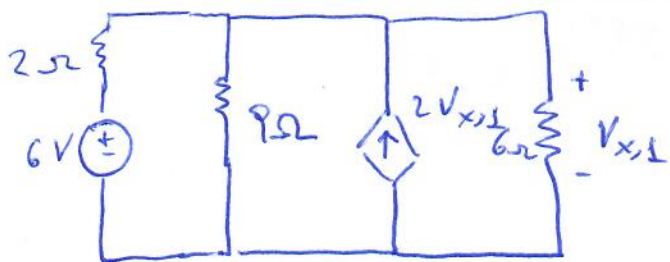


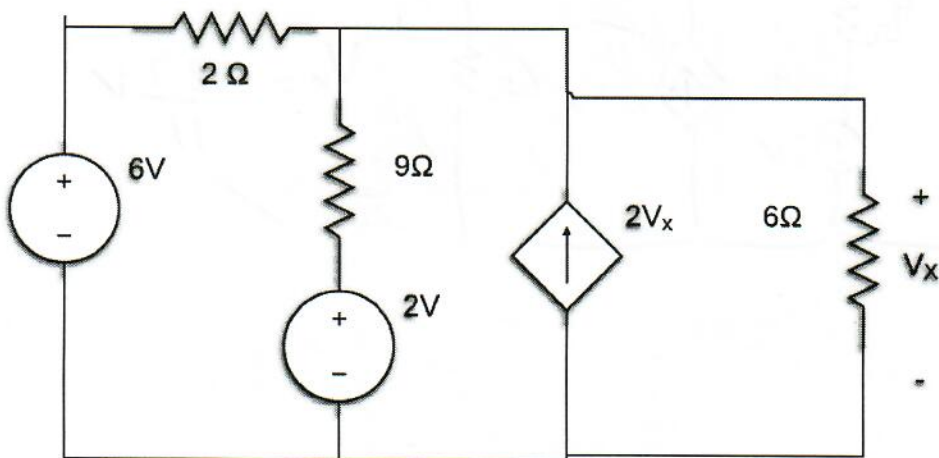Q1. Find V_x by superposition in the circuit below. (8points)





$$R_{eq} = 2\Omega \parallel 9\Omega \parallel \frac{1}{2}\Omega \parallel 6\Omega$$

$$= \left(\frac{1}{2} + \frac{1}{9} + 2 + \frac{1}{6} \right)^{-1}$$

$$V_{x,1} = 3A \left(\frac{-27\Omega}{33} \right) = \underline{\underline{-\frac{27}{11}V}}$$
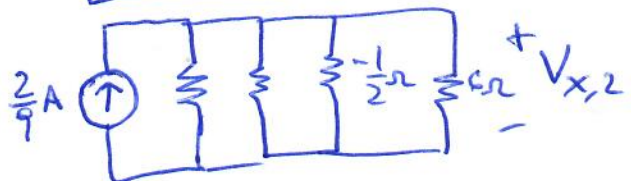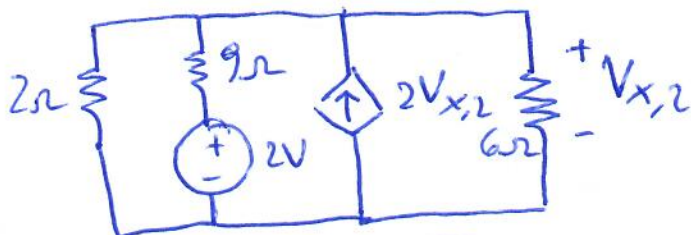
$$= \left(\frac{27 + 6 + 9 - 108}{54} \right)^{-1}$$




$$V_{x,2} = \frac{2}{9}A \left(\frac{-27\Omega}{33} \right) = \underline{\underline{-\frac{2}{11}V}}$$

$$= -\frac{27}{33}\Omega$$

$$V_x = V_{x,1} + V_{x,2}$$


$$V_x = \underline{\underline{-\frac{29}{11}V}}$$

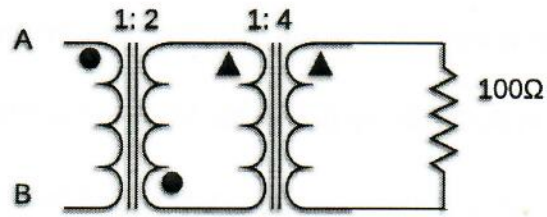Q2. Find the Thevenin Equivalent between A and B. (8 points)







$$i = \frac{100 \cdot 8V}{100\Omega} = \frac{2V}{25\Omega}$$
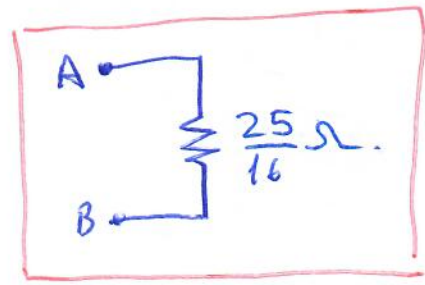
$$I = 8i = 8 \cdot \frac{8V}{100\Omega} \rightarrow V = I \cdot \frac{100\Omega}{64} = R_{eq}$$



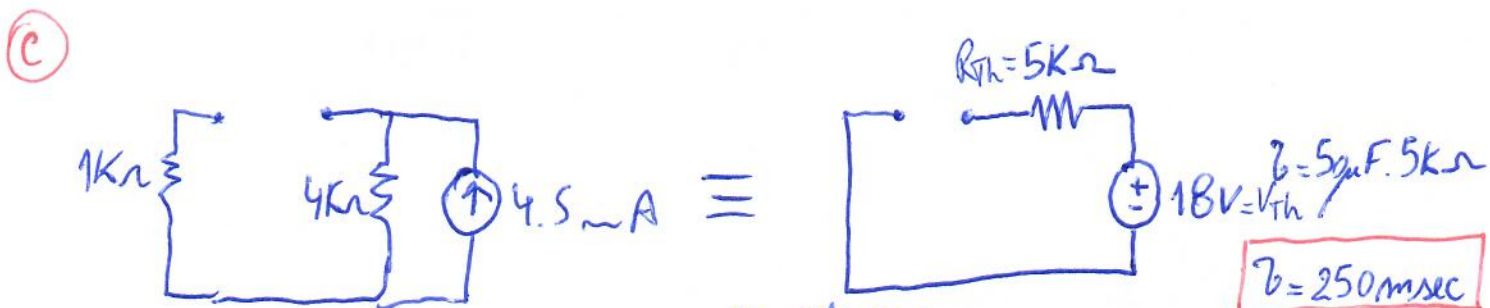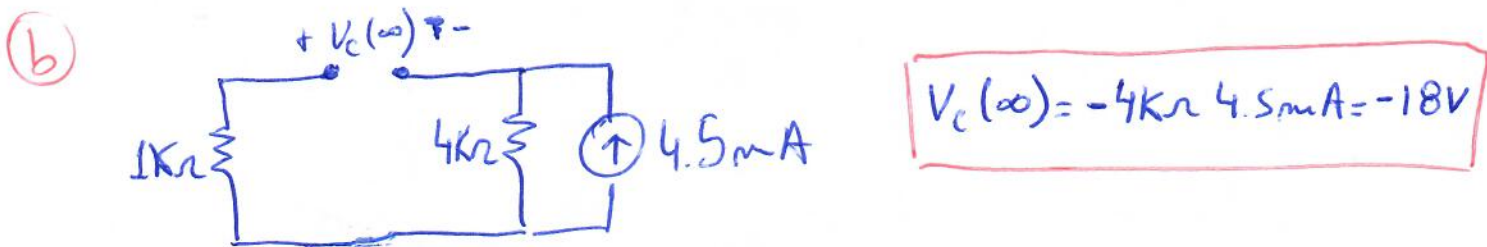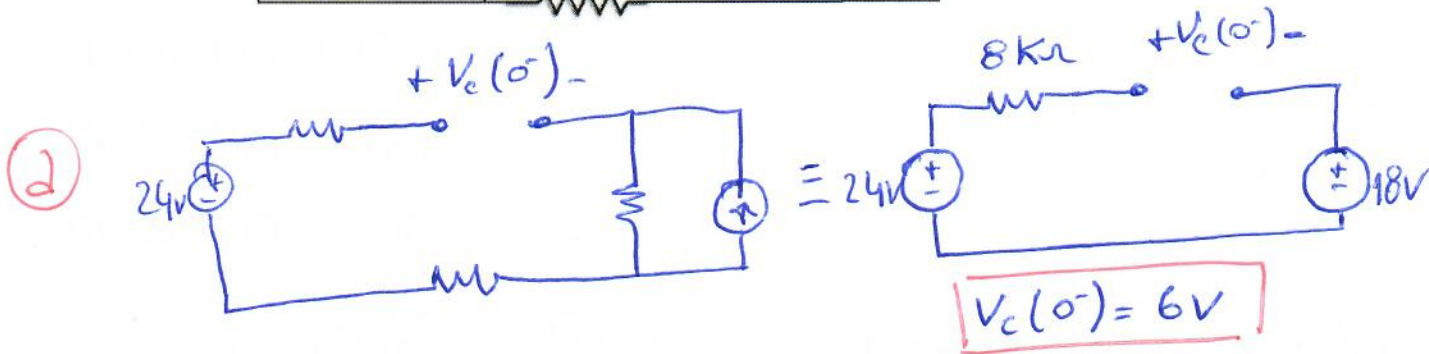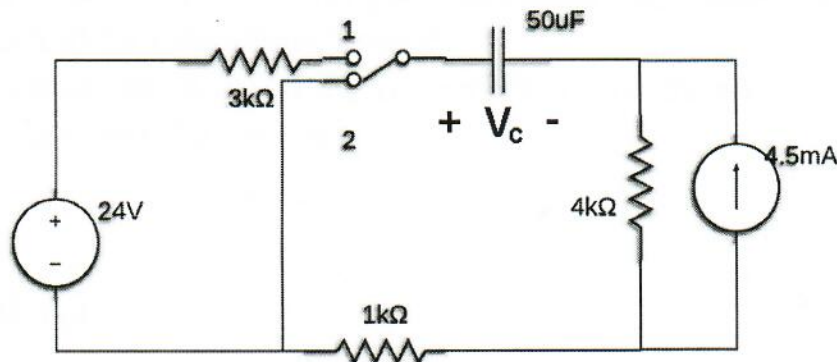Q3. In the circuit below, the switch was moved from position 1 to position 2 at $t=0$. It had been in position 1 for a very long time before then. (14 points)

- Draw the equivalent circuit at $t=0^-$ and use it to find the initial condition $V_c(0^+)$. (4 points)
- Draw the final condition $t \rightarrow \infty$ circuit to find out the final condition $V_c(\infty)$. (3 points)
- Use Thevenin equivalent to find out the time constant of the circuit for $t > 0$. (4 points)
- Now find $V_c(t)$ for $t > 0$. (3 points)



(d) The voltage across the capacitor for $t > 0$ is given by:

$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)]e^{-t/\tau}$$

In this case $V_c(0^+) = V_c(0^-) = 6V$

$$V_c(t) = -18V + 24Ve^{-\frac{t}{2.5 \times 10^{-3} sec}} \quad t > 0$$