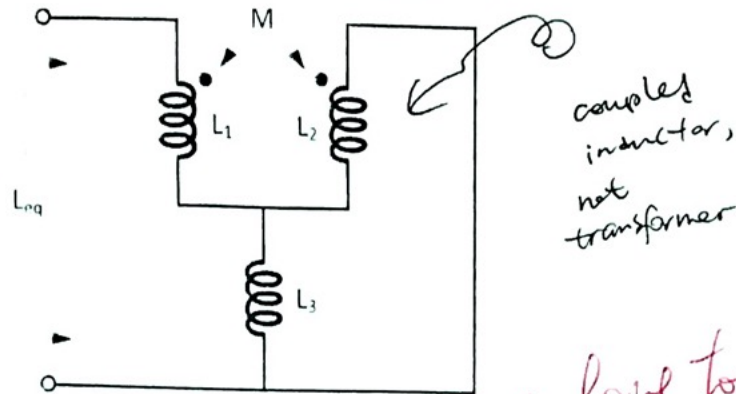


Name: Xiashe YangUID: 504640737Discussion: 1A FridayTotal of 3 questions, 90 minutes.Only a calculator, a pencil, a ruler and an eraser allowed

P1	4
P2	27
P3	37
Total	68

1. (30 points) Find the equivalent inductance of the circuit below.



you have to define it!

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{cases}$$


$$L_1 // L_3 = \frac{1}{\frac{1}{L_1} + \frac{1}{L_3}} = \frac{L_1 L_3}{L_1 + L_3}$$

$$L_2 // L_3 = \frac{1}{\frac{1}{L_2} + \frac{1}{L_3}} = \frac{L_2 L_3}{L_2 + L_3}$$

$$\begin{aligned} \frac{di_1}{dt} &= \left(v_1 - M \frac{di_2}{dt} \right) \frac{1}{L_1} \\ &= \left[v_1 - M \left(v_2 - M \frac{di_1}{dt} \right) \frac{1}{L_2} \right] \frac{1}{L_1} \\ &= \left[v_1 - \frac{M v_2}{L_2} + \frac{M^2}{L_2} \frac{di_1}{dt} \right] \frac{1}{L_1} \\ \frac{di_1}{dt} &= \left(v_1 - M \frac{di_2}{dt} \right) \frac{1}{L_1} \end{aligned}$$

$$\begin{aligned} \frac{di_2}{dt} &= \frac{v_1 L_2 - M v_2}{M^2 L_1} \\ K_{12} &= \frac{M}{L_1 L_2} \end{aligned}$$



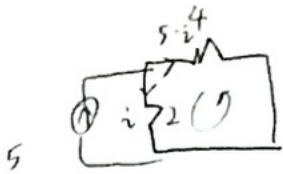
$$\begin{aligned} \frac{di_1}{dt} &= \left(\frac{v_1}{L_1} - \frac{M v_2}{L_1 L_2} \right) \frac{L_1 L_2}{M^2 L_1 - L_1 L_2} \\ &= \frac{v_1 L_2}{M^2 L_1 L_2} - \frac{M v_2}{M^2 L_1 L_2} \end{aligned}$$



$$\begin{aligned}
 -2i + 4(5-i) &= 0 \\
 -2i + 20 - 4i &= 0 \\
 20 &= 6i \\
 i &= \frac{10}{3}
 \end{aligned}$$

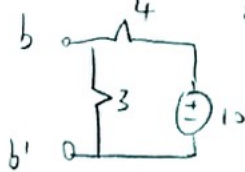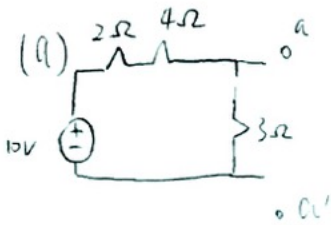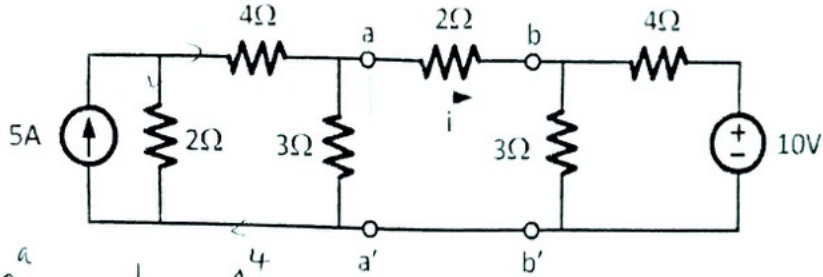2. (30 points) In the circuit below,

- Find the current i by finding the Thevenin equivalent at $a - a'$ and $b - b'$ nodes.
- Calculate the power dissipated in the middle 2Ω resistor.




(b) $P = UI$

$= I^2 R$


$= (\frac{10}{6})^2 \times 2$

$= \boxed{\frac{1}{18}} \text{ W} - 3$

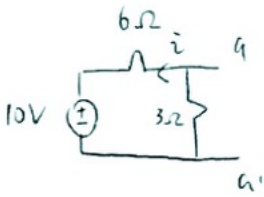




$\bar{i} = \frac{10V}{6\Omega + 3\Omega} = \frac{10}{9}$

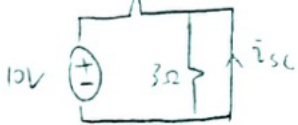$V_{oc} = \bar{i} \cdot 3\Omega = \frac{10}{3} \text{ V}$




$\bar{i}_{sc} = \frac{10V}{6\Omega} = \frac{5}{3} \text{ A}$

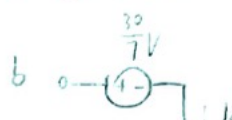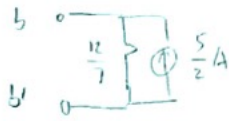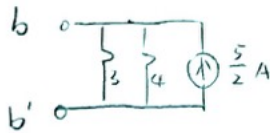$R_{th} = \frac{V_{oc}}{\bar{i}_{sc}} = \frac{\frac{10}{3}}{\frac{5}{3}} = 2\Omega$




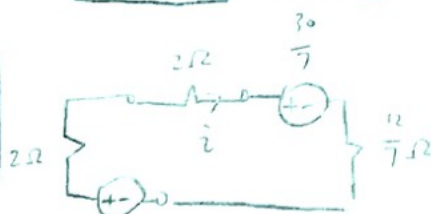$V_{th} = \frac{30}{7} \text{ V}$ $R_{th} = \frac{12}{7} \Omega$




$$\begin{aligned}
 -2 \cdot \bar{i} - \frac{30}{7} - \frac{12}{7} \cdot \bar{i} + \frac{12}{7} - 2\bar{i} &= 0 \\
 -\frac{20}{7} &= \frac{40}{7} \bar{i}
 \end{aligned}$$



$\bar{i} = -\frac{1}{6} \text{ A}$

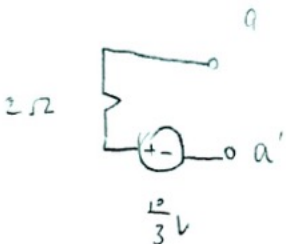

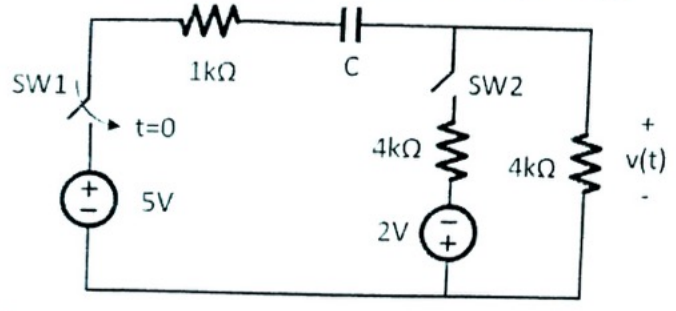$C = 500 \text{ pF}$ $V_C(0^-) = 0 \text{ V}$
 3. (40 points) In the following circuit, switch SW1 closes at $t = 0$, and switch SW2 closes when $v(t)$ reaches 2V. Calculate and plot $v(t)$.



$t=0 \sim v(t) = 2 \text{ V}$

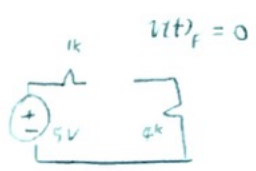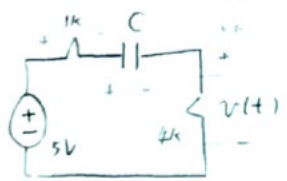

$V_C(0^-) = 0$



$V_C(0^+) = 0$



$v(t)_i = 5 \text{ V} \times \frac{4}{4+1} = 4 \text{ V}$

$\tau = R_{eq} C = 5 \text{ k} \cdot 500 \times 10^{-12}$

$$v(t) = 4 e^{-\frac{t}{5000 \times 10^{-12} \times 5000}}$$
 ($t=0 \sim v(t) = 2 \text{ V}$)

$v(t) = 2$


$4 e^{-\frac{t}{2.5 \times 10^{-6}}} = 2$

$-\frac{t}{2.5 \times 10^{-6}} = \ln \frac{1}{2}$

$t = 1.73 \times 10^{-6} \text{ s}$

$t > v(t) = 2$

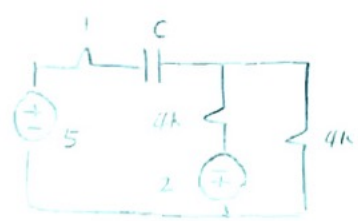$t > 1.73 \times 10^{-6} \text{ s} = t_1$



$V_{C1} = \frac{2}{2+1} \times 2 = 1 \text{ V}$



No jump.

$V_C(t_1^+) = V_C(t_1^-)$

$v_C(5^+) = 0 = v_C(t_1^-)$

$v_C(t) = 5 - 5e^{-\frac{t}{\tau}}$

$v_C(t) = V_C = 5 \text{ V}$

$v_C(t) = 5(1 - e^{-\frac{t}{5 \times 10^{-6}}})$


$v_C(t_1^+) = v_C(t_1^-)$

$= v_C(1.73 \times 10^{-6})$

$= 5 \times (1 - e^{-\frac{1.73 \times 10^{-6}}{5 \times 10^{-6}}})$

$= 2.5 \text{ V}$

$v(t)_i :$

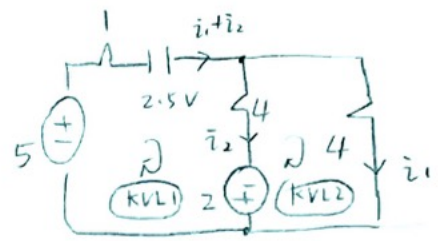

$-2.5 - 4i_2 + 2 + 5 - i_1 - i_2 = 0$ (KVL1)

$-2 + i_1 \times 4 - 4i_2 = 0$ (KVL2)

$4.5 - 5i_2 - i_1 = 0$

$i_2 - i_1 = \frac{1}{2}$

$i_2 = i_1 + \frac{1}{2}$

$4.5 - 5(i_1 + \frac{1}{2}) - i_1 = 0$

$4.5 - 5i_1 - 2.5 - i_1 = 0$


$i_1 = \frac{2}{6} = \frac{1}{3}$

$v(t)_i = i_1 \cdot 4 = \frac{4}{3} \text{ V}$ ✓


$v(t) = 1 + (\frac{4}{3} - 1) e^{-\frac{t}{\tau}}$

$\tau = C \cdot R_{eq}$

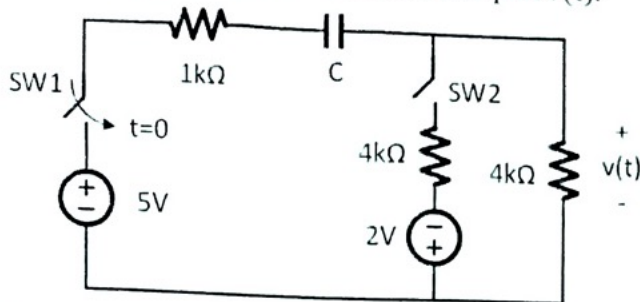3. (40 points) In the following circuit, switch SW1 closes at $t = 0$, and switch SW2 closes when $v(t)$ reaches 2V. Calculate and plot $v(t)$.




$t=0 \sim v(t) = 2V$

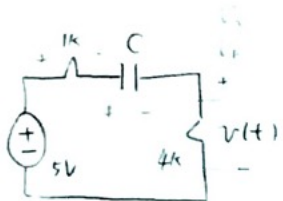

$t > v(t) = 2$

$t > 1.73 \times 10^{-6} s = t_1$

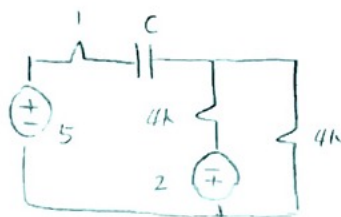

$v(t)_F = \frac{6}{4+4} \times 2 = 1V$



No jump.

$v_c(t_1^+) = v_c(t_1^-)$

$v_c(0^+) = 0 = v_c(t_1^-)$

$v_c(t) = 5 - 5e^{-\frac{t}{\tau}}$

$v_c(t) = v_c = 5V$

$v_c(t) = 5(1 - e^{-\frac{t}{5 \times 10^{-6}}})$


$v_c(t_1^+) = v_c(t_1^-)$

$= v_c(1.73 \times 10^{-6})$

$= 5 \times (1 - e^{-\frac{1.73 \times 10^{-6}}{5 \times 10^{-6}}})$

$= 2.5V$

$v(t)_i :$

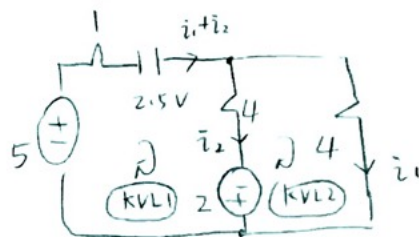

$-2.5 - 4i_2 + 2 + 5 - i_1 - i_2 = 0$ (KVL1)

$-2 + i_1 \times 4 - 4i_2 = 0$ (KVL2)

$4.5 - 5i_2 - i_1 = 0$

$i_2 - i_1 = \frac{1}{2}$

$i_2 = i_1 + \frac{1}{2}$

$4.5 - 5(i_1 + \frac{1}{2}) - i_1 = 0$

$4.5 - 5i_1 - 2.5 - i_1 = 0$


$i_1 = \frac{2}{6} = \frac{1}{3}$

$v(t)_i = i_1 \cdot 4 = \frac{4}{3} V$ ✓

$v(t) = 1 + (\frac{4}{3} - 1)e^{-\frac{t}{\tau}}$

$\tau = C \cdot R_{eq}$

$v(t)_F = 0$

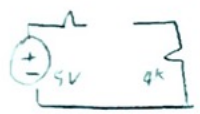

$v_c(0^-) = 0$



$\therefore v_c(0^+) = 0$



$v(t)_i = 5V \times \frac{4}{4+1} = 4V$

$\tau = R_{eq} C = 5k \cdot 500 \times 10^{-12}$

$v(t) = 4e^{-\frac{t}{5000 \times 10^{-12} + 2 \times 500}}$
 ($t=0 \sim v(t) = 2V$)

$v(t) = 2$

$4e^{-\frac{t}{2.5 \times 10^{-6}}} = 2$


$-\frac{t}{2.5 \times 10^{-6}} = \ln \frac{1}{2}$

$t = 1.73 \times 10^{-6} s$

Req: when all sources are turned off


$$\frac{1}{\frac{1}{4} + \frac{1}{4}}$$

15

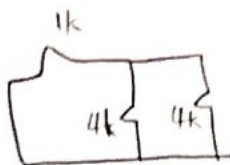

$$R_{eq} = 4k \parallel 4k + 1k = 3k$$
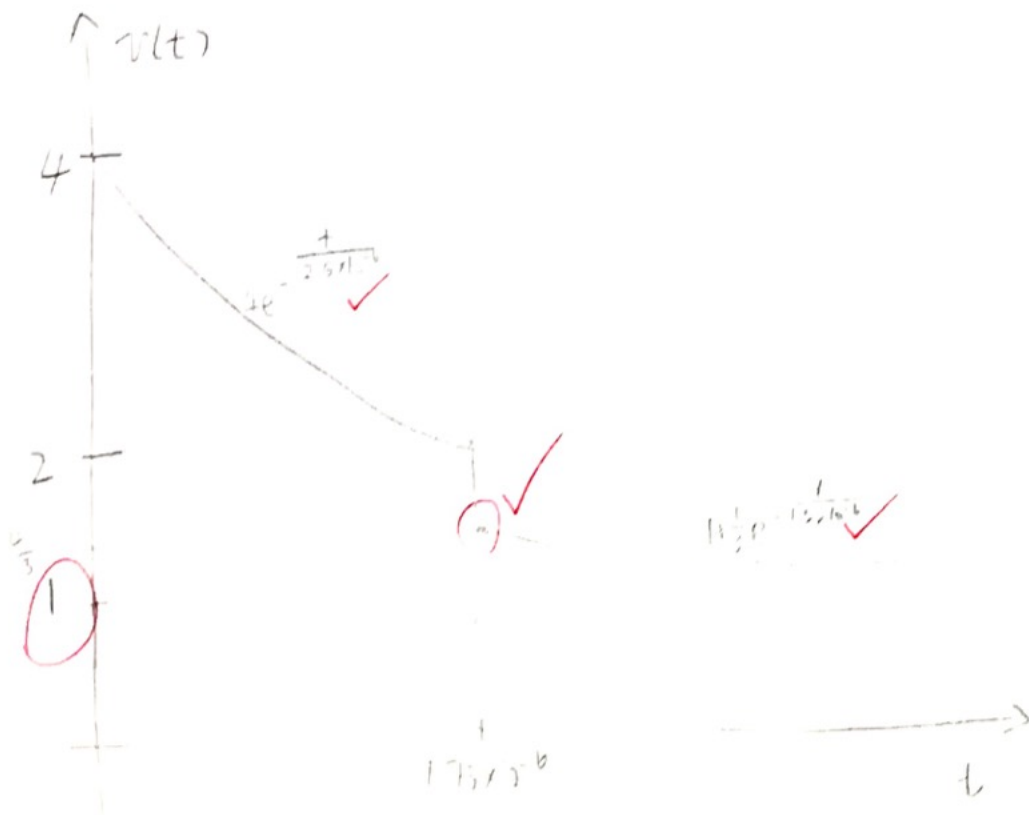
$$v(t) = 1 + \frac{1}{3} e^{-\frac{t}{5 \times 10^{-6} \times 3000}} \text{ V } (t > 1.73 \times 10^{-6} \text{ s})$$



$$v(t) = \begin{cases} 4e^{-\frac{t}{2.5 \times 10^{-6}}} \text{ V } (0 < t < 1.73 \times 10^{-6}) \\ 1 + \frac{1}{3} e^{-\frac{t}{1.5 \times 10^{-6}}} \text{ V } (t > 1.73 \times 10^{-6}) \end{cases}$$