

ECE 10, Winter 2020, Final Examination – March 20, 2020

Instructions: This exam booklet consists of exam problems, blank sheets for the solutions, reference sheets with mathematical identities, and additional blank sheets. Please follow these instructions while answering your exam:

- 1. Write your name and student identification number below.**
- 2. You have 3 hours to finish your exam.**
- 3. Write your solutions in the provided blank sheets after each problem.**
- 4. The sheets marked “Scratch...” will NOT be graded. These sheets are provided for your rough calculations only.**
- 5. Write your solutions clearly. You may box in your final answer. Illegible solutions will NOT be graded.**
- 6. Be brief.**
- 7. Open text, notes, homework and homework solutions.**
- 8. Calculators are allowed.**

NAME: _____

STUDENT ID: _____

TA SECTION: _____

Problem	Score
#1	/5
#2	/15
#3	/35
#4	/20
#5	/25
Total	/100

Problem 1: Refer to Figure 1. Note that Z represents impedance while Y represents admittance. For each of the following statements indicate whether it is true or false. Circle the appropriate response. Give reasons. **Be very brief; no more two sentences for each response.**

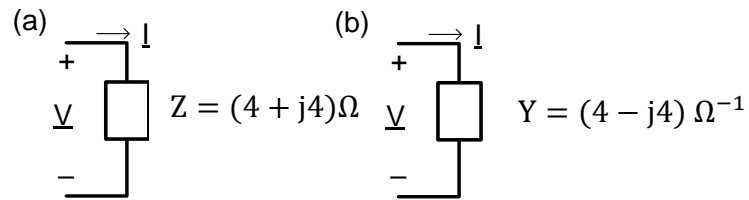


Figure 1

a. In Figure 1(a), the voltage V lags the current, I , by 45 degrees.

True False

b. In Figure 1(b), the voltage V lags the current, I , by 45 degrees.

True False

(2 + 3 = 5 points)

(1 page max allowed)

Solution:

Problem 2: Consider the circuit shown in Figure 2.

(a) What is the impedance looking into 1-1', in sinusoidal steady state, at an angular frequency of 1 rad/s?

(b) Determine the angular frequency, ω , for which the network looking into 1-1' is purely resistive. What is the value of this purely resistive impedance?

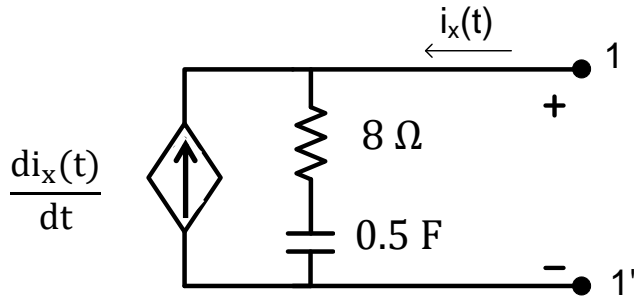


Figure 2

(5 + 10 = 15 points)

(2 pages max allowed)

Solution:

Problem 3: Refer to the circuit schematic shown in Figure 3.

- Obtain the phasor domain representation for the circuit shown in the figure.
- Solve for the phasors of $i_B(t)$ and $i_L(t)$ i.e. \underline{I}_B , and \underline{I}_L . Express your numerical phasor answers in polar form (i.e. in $re^{j\theta}$ form). You are free to use any analysis method of your choice.
- Draw a complex plane “phasor” diagram showing \underline{V}_A , \underline{I}_L , \underline{V}_L , and \underline{V}_s . Indicate the angles and magnitudes of these phasors on the diagram.
- Determine the sinusoidal steady state expression for $v_A(t)$. Does it lead or lag $v_s(t)$? By how many degrees?
- What is the impedance, Z , seen by the source, $v_s(t)$ i.e. the impedance seen looking into the dashed box in the figure? Is it resistive, inductive, or capacitive?

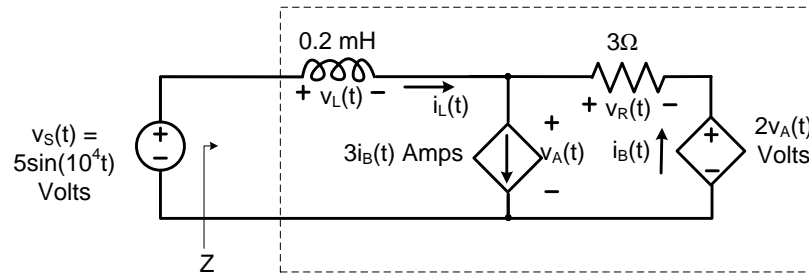


Figure 3

(5 + 8 + 10 + 7 + 5 = 35 points)

(3 pages max allowed)

Solution:

Problem 4: Refer to Figure 4 for this problem. What is the Norton's equivalent circuit for sinusoidal steady state operation?

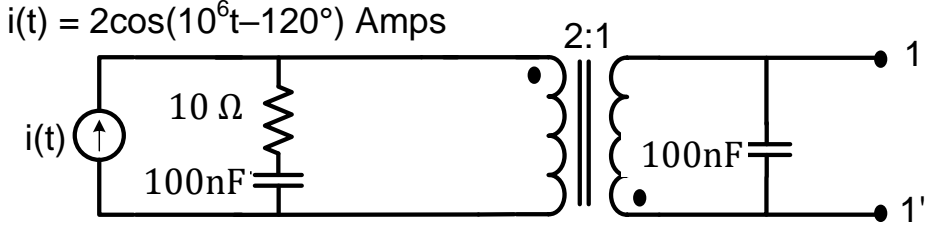


Figure 4

(10 + 10 = 20 points)
(3 pages max allowed)
Solution:

Problem 5: Refer to Figure 5 for this problem. Both switches changed from position 1 to position 2 at time $t = 0$, after the circuits having achieving steady state. Use $V_B = 4V$, $R = 200\Omega$, $R_L = 400\Omega$, $C_1 = 2mF$, $C_2 = 4mF$, and $V_S(t) = 4\cos(2.5t)$ Volts unless stated otherwise.

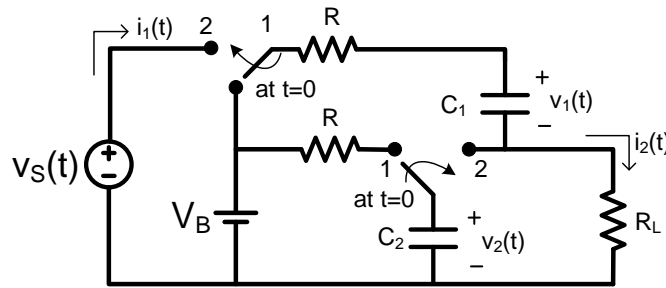


Figure 5

- Determine the values of $v_1(t)$ and $v_2(t)$ just before $t = 0$.
- Determine the values of $i_1(t)$ and $i_2(t)$ just after $t = 0$.
- Using $i_1(t)$ and $i_2(t)$ as your unknowns, write down the time-domain mesh current equations for this circuit for $t \geq 0$.
- Determine the values of $\left. \frac{dv_2}{dt} \right|_{t=0+}$, $\left. \frac{di_2}{dt} \right|_{t=0+}$, and $\left. \frac{d^2i_2}{dt^2} \right|_{t=0+}$.

(4 + 6 + 6 + 9 = 25 points)

(3 pages max allowed)

Solution:

Reference Sheet #1

Trigonometric Identities:

$$\sin A = \cos(A - 90^\circ) = \cos(A - \pi/2)$$

$$\cos A = \sin(A + 90^\circ) = \sin(A + \pi/2)$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(A \pm B) = \cos A \cos B \pm \sin A \sin B$$

$$\cos A + \cos B = 2 \cos((A+B)/2) \cos((A-B)/2)$$

$$\cos A - \cos B = -2 \sin((A+B)/2) \sin((A-B)/2)$$

$$\sin A + \sin B = 2 \sin((A+B)/2) \cos((A-B)/2)$$

$$\sin A - \sin B = 2 \cos((A+B)/2) \sin((A-B)/2)$$

$$\cos 2A = 2 \cos^2 A - 1 = \cos^2 A - \sin^2 A = 1 - 2 \sin^2 A$$

$$\sin 2A = 2 \sin A \cos A$$

$$\cos 3A = 4 \cos^3 A - 3 \cos A$$

$$\sin 3A = 3 \sin A - 4 \sin^3 A$$

$$a \cos A + b \sin A = \sqrt{a^2 + b^2} \cos(A - \tan^{-1}(b/a))$$

Complex Arithmetic:

$$\operatorname{Re}\{z_1 \pm z_2\} = \operatorname{Re}\{z_1\} \pm \operatorname{Re}\{z_2\}$$

$$\operatorname{Im}\{z_1 \pm z_2\} = \operatorname{Im}\{z_1\} \pm \operatorname{Im}\{z_2\}$$

$$\operatorname{Re}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Re}\{z_2\} - \operatorname{Im}\{z_1\} \operatorname{Im}\{z_2\}$$

$$\operatorname{Im}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Im}\{z_2\} + \operatorname{Im}\{z_1\} \operatorname{Re}\{z_2\}$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$x + jy = r e^{j\theta} \text{ where } r = \sqrt{x^2 + y^2}, \theta = \tan^{-1}(y/x)$$

$$r e^{j\theta} = x + jy \text{ where } x = r \cos \theta, y = r \sin \theta$$

$$|z_1 z_2| = |z_1| |z_2|, \text{ angle}(z_1 z_2) = \text{angle}(z_1) + \text{angle}(z_2)$$

$$|1/z| = 1/|z|, \text{ angle}(1/z) = -\text{angle}(z)$$

$$(x + jy)^* = x - jy, \text{ angle}(z^*) = -\text{angle}(z)$$

Quadratic Equations:

$$\text{The roots of } ax^2 + bx + c = 0 \text{ are } x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

SCRATCH (Will NOT Be Graded)

SCRATCH (Will NOT Be Graded)