

Problem 1: Consider the circuit shown in Figure 1.

- Draw a graph for this circuit.
- Identify (draw) a tree that does **not** include the branches C_2 and R . Choose it such that you have the minimum number of equations to solve.
- Use mesh current method to write the equations for this circuit. Make sure that $i_C(t)$ and $i_R(t)$ are two of the unknowns. Assume that no energy is stored in any of the inductors or capacitors.


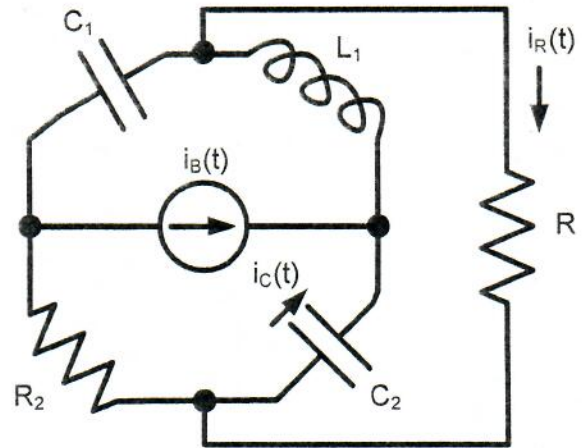


Figure 1.


(5 + 10 + 10 = 25 points)

Solution:

(a)

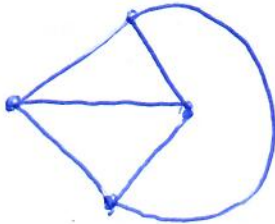

(b)

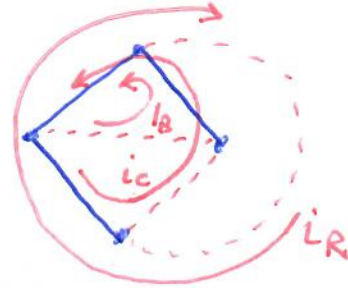

(c)

$$i_R(t)R + [i_R(t) - i_C(t)]R_2 + \frac{1}{C_1} \int_0^t (i_R(t) - i_C(t) - i_B(t)) dt = 0$$

$$\frac{1}{C_2} \int_0^t i_C(t) dt + L_1 \frac{d}{dt} [i_C(t) + i_B(t)] + \frac{1}{C_1} \int_0^t (i_C(t) + i_B(t) - i_R(t)) dt + [i_C(t) - i_R(t)]R_2 = 0$$

Problem 2: Refer to Figure 2 for this problem. Calculate the Norton's equivalent of this network looking into the terminals 1-1'. Use any method of your choice.

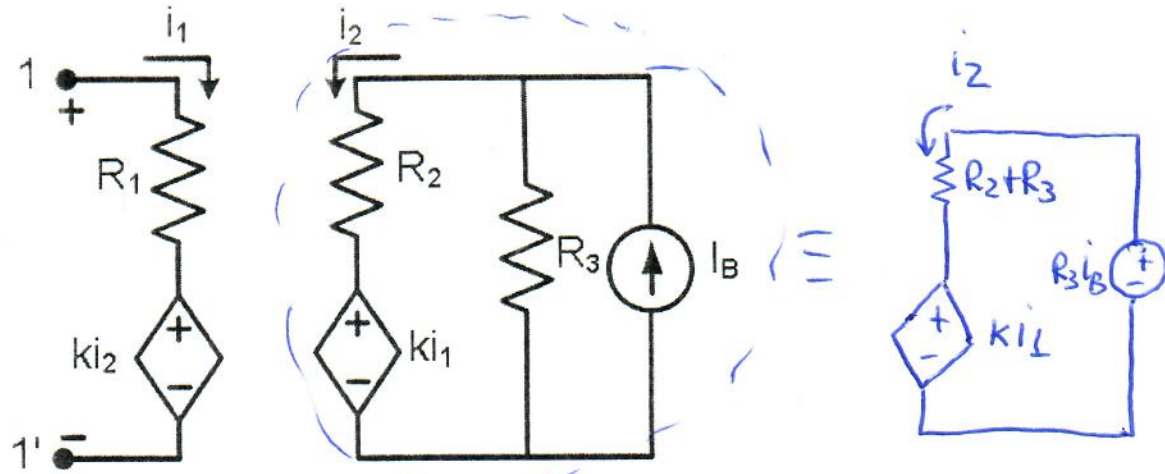


Figure 2.

(20 + 20 = 40 points)

Solution:

For V_{oc} :

$$i_1 = 0 \rightarrow V_{oc} = K i_2 \quad i_2 = \frac{I_B R_3}{R_2 + R_3}$$

$$V_{oc} = \frac{K I_B R_3}{R_2 + R_3}$$

For I_{sc} :




$$I_{sc} = -i_1 = \frac{K i_2}{R_1}$$

$$i_2 = \frac{K I_{sc} + R_3 I_B}{R_2 + R_3}$$

$$\rightarrow R_1 (R_2 + R_3) I_{sc} = K (K I_{sc} + I_B R_3) \rightarrow I_{sc} = \frac{K I_B R_3}{R_1 (R_2 + R_3) - K^2}$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = R_1 - \frac{K^2}{R_2 + R_3}$$

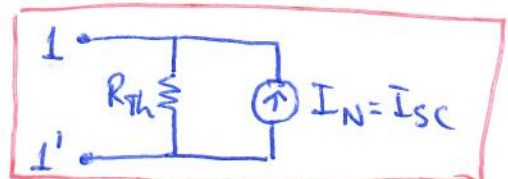


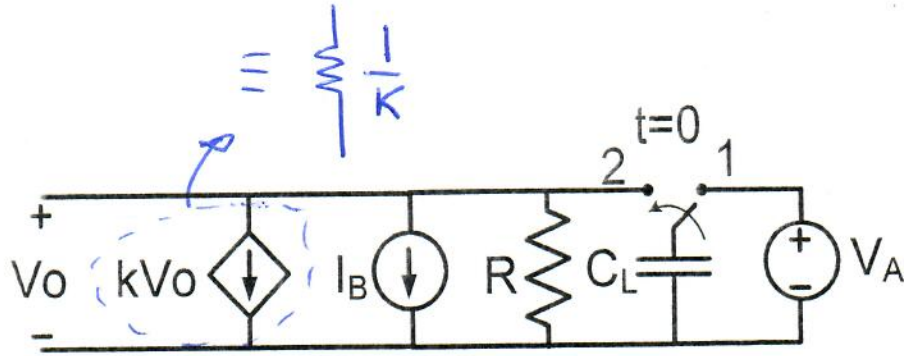


Figure 3

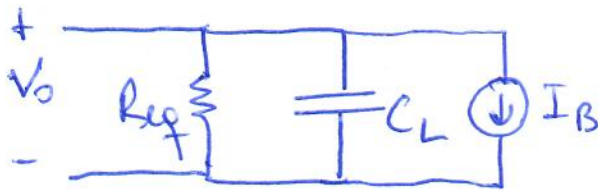Problem 3: Refer to Figure 3 for this problem. Find $V_o(t)$ for all $t \geq 0$.
(35 points)

Solution: For $t > 0$:

$$R_{eq} = \frac{1}{K} \parallel R = \frac{R}{1+RK}$$



1st order circuit \rightarrow so: $V_o(t) = A + B e^{-t/\tau}$

$$\left. \begin{aligned} V_o(0^+) &= V_A & V_o(0^+) &= A + B e^{-0} = A + B \\ V_o(\infty) &= -I_B R_{eq} & V_o(\infty) &= A + B e^{-\infty} = A \end{aligned} \right\} \rightarrow$$

$$\begin{aligned} A &= -I_B R_{eq} \\ A + B &= V_A \rightarrow B = V_A + I_B R_{eq} \end{aligned}$$

$$\tau = R_{eq} C_L = \frac{R C_L}{1+RK}$$

$$\rightarrow V_o(t) = -\frac{I_B R}{1+RK} + \left(V_A + \frac{I_B R}{1+RK} \right) e^{-t/\tau}$$

$$\tau = \frac{R C_L}{1+RK}$$