

Solution to midterm 1

Problem 1: Derive the Thevenin's equivalent of the circuit shown in Figure 1.



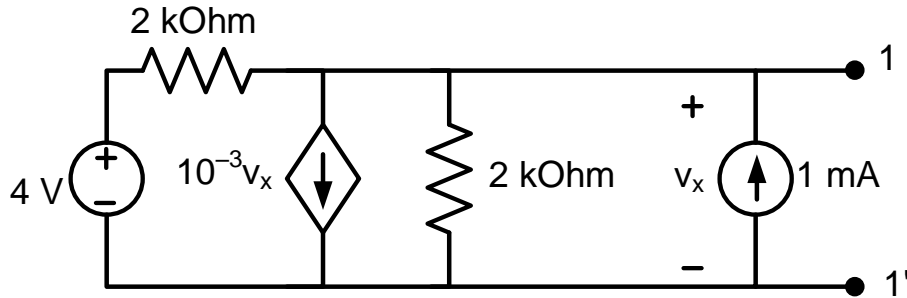


Figure 1

Solution 1: source transformation

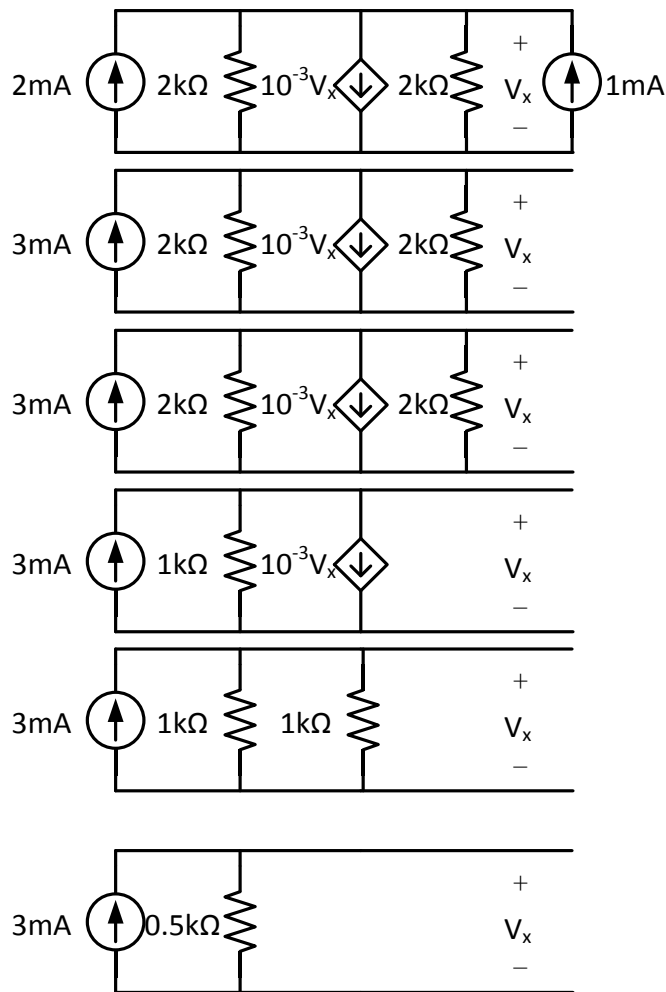


$$(i=10^{-3}V_x, v=V_x, v/i=10^3\Omega)$$

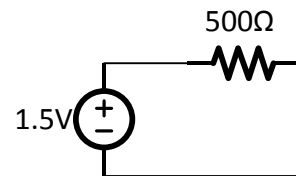

Solution 2:

1. Calculate open circuit voltage V_{oc}

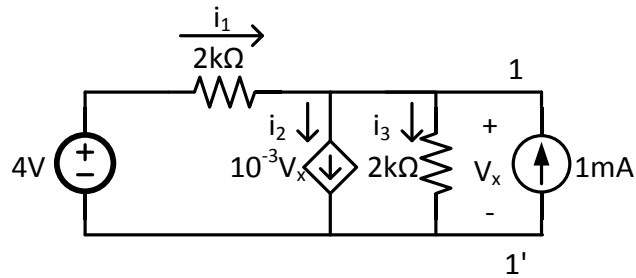


$i_1 - i_2 - i_3 + 1\text{mA} = 0$ (KCL at node 1)

$$\frac{(4V - V_x)}{2k\Omega} - 10^{-3}V_x - \frac{V_x}{2k\Omega} + 1\text{mA} = 0$$

We get $V_x = 1.5V$, $V_{TH} = V_{oc} = V_x = 1.5V$

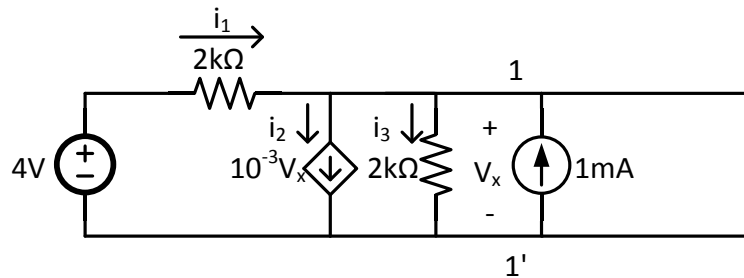2. Calculate short circuit current I_{sc}



$$V_x = 0$$


$i_1 - i_2 - i_3 + 1\text{mA} - I_{sc} = 0$ (KCL at node 1)

No current flows through dependent source and $2k\Omega$ resistor on the right. So $i_3 = 0$, $i_2 = 0$.

$$i_1 = 4V / 2k\Omega = 2\text{mA}$$

$$I_{sc} = i_1 + 1\text{mA} = 3\text{mA}$$

3. $R_{TH} = \frac{V_{oc}}{I_{sc}} = 500\Omega$

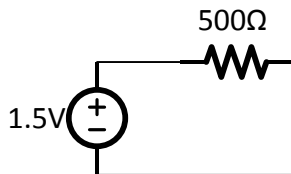

Problem 2: Determine the current $i_A(t)$ in the circuit shown in Figure 2 using superposition.


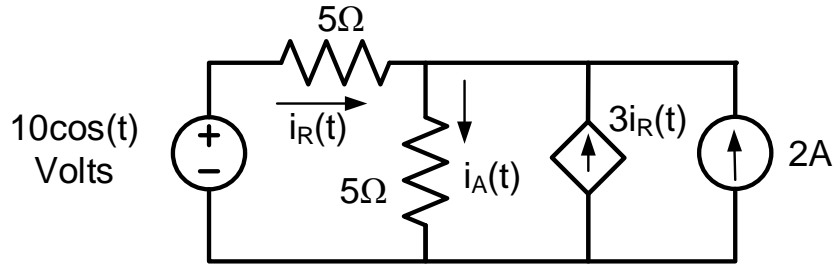



Figure 2

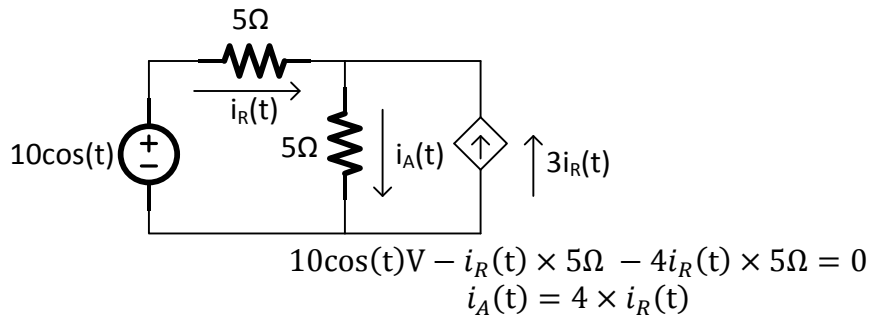1. Replace 2A current source with open circuit



We get $i_A(t) = 1.6\cos(t)$

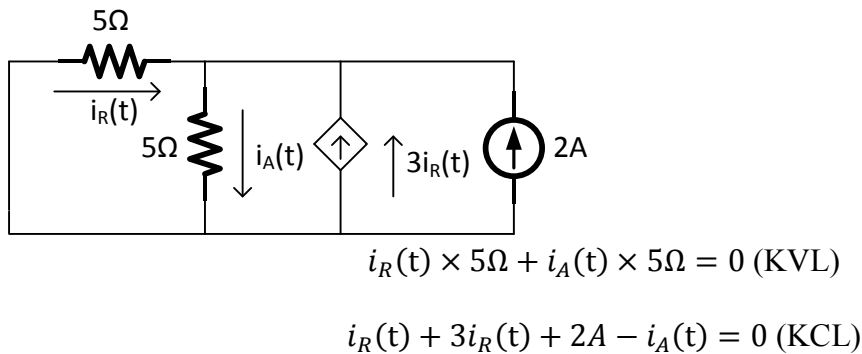2. Replace 10cos(t) voltage source with short circuit



We get $i_A(t)=0.4A$

3. By adding to responses, we get $i_A(t)=0.4+1.6 \cos(t)$ (A)

Problem 3: Consider a capacitor whose capacitance C changes with the potential difference, V , applied across it in the following manner:

$$C = C(V) = C_0 + C_1V$$

where $C_0 = 10\text{F}$ and $C_1 = 2\text{F/V}$ respectively. This capacitor was charged from 2V to 4V . Calculate the amount of work done in doing so?

$$\text{Work} = \int_2^4 V dQ = \int_2^4 V \cdot C(V) dV = \int_2^4 V \cdot (C_0 + C_1V) dV = \frac{1}{2} C_0 (4^2 - 2^2) + \frac{1}{3} C_1 (4^3 - 2^3) = 97.33\text{J}$$