

Problem 1: Consider the circuit shown in Figure 1.

- Draw a graph for this circuit.
- Identify (draw) a spanning tree that does **not** include the branches R_8 and V_B .
- For loop current method identify a minimum set of loop currents and mark your chosen set of chord currents on the circuit diagram.
- Mark the currents in every branch in terms of your chosen unknowns.
- Write the loop (KVL) equation for a loop that includes V_B .


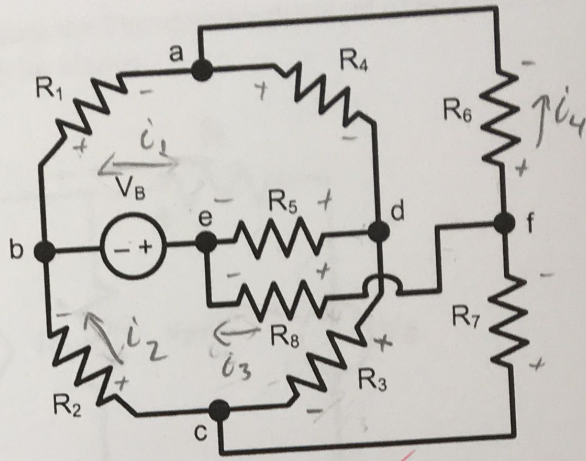
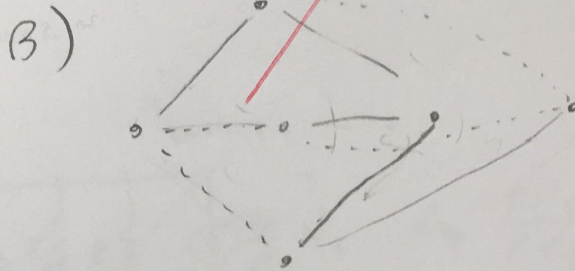


Figure 1.

(5 + 5 + 5 + 5 + 5 = 25 points)

Solution:

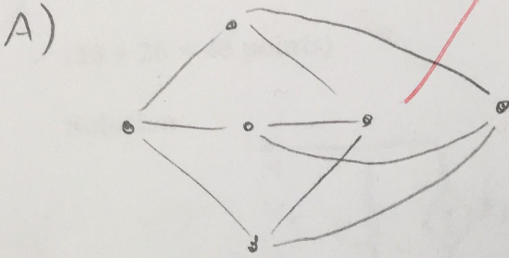


C) 4 loop currents: i_1, i_2, i_3, i_4 marked with i_1, i_2, i_3 and i_4 and with dashed line

D) Current Through:

- $R_1: i_1 + i_2$
- $R_2: i_2$
- $R_3: i_2 + i_3 + i_4$
- $R_4: i_1 + i_2 + i_4$
- $R_5: i_1 - i_3$
- $R_6: i_4$
- $R_7: i_3 + i_4$
- $R_8: i_3$
- $V_B: i_1$

in which directions -2

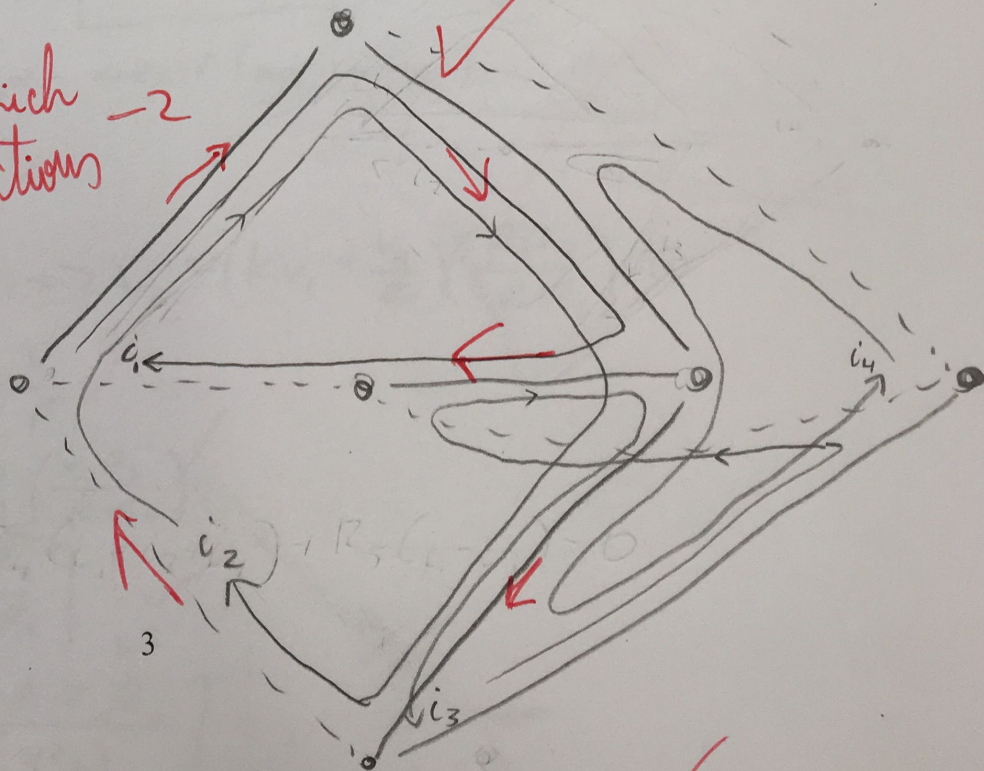

E) $V_B + R_1(i_1 + i_2) + R_4(i_1 + i_2 + i_4) + R_5(i_1 - i_3) = 0$

E) $V_B + R_1(i_1 + i_2) + R_4(i_1 + i_2 + i_4) + R_5(i_1 - i_3) = 0$ (loop i_1)

Problem 2: Refer to Figure 2 for this problem. Calculate the Thevenin's equivalent of this network looking into the terminals 1-1'. Use any method of your choice.


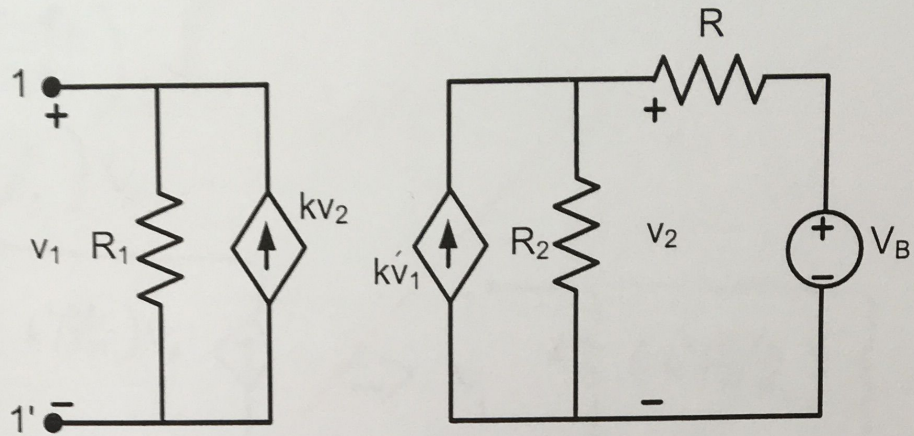


Figure 2.

(20 + 20 = 40 points)

Solution:

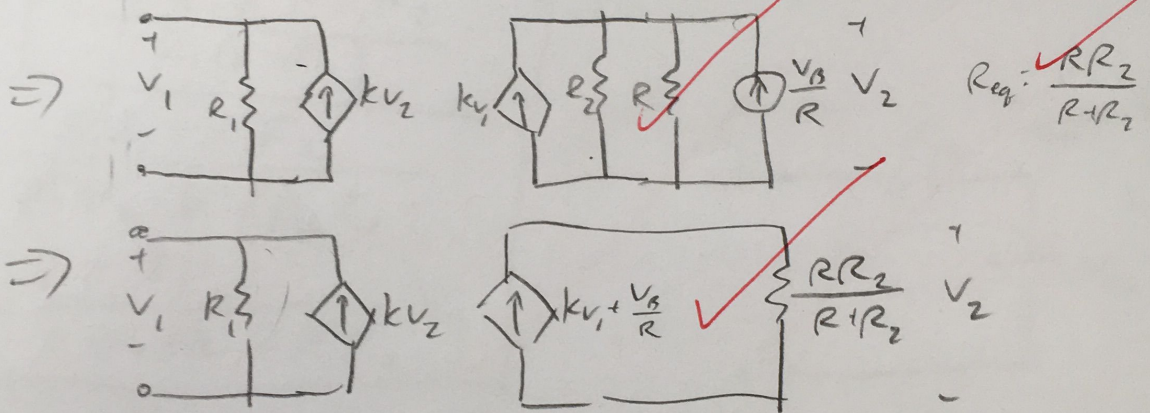

Set terminals 1-1' to open circuit (no current).

$$KCL \begin{cases} kv_2 = \frac{v_1}{R_1} \quad \textcircled{1} \\ kv_1 + \frac{v_B}{R} = v_2 \left(\frac{RR_2}{R+R_2} \right)^{-1} \Rightarrow v_2 = \left(kv_1 + \frac{v_B}{R} \right) \left(\frac{RR_2}{R+R_2} \right) \quad \textcircled{2} \end{cases}$$

$$\text{plug } \textcircled{2} \rightarrow \textcircled{1} \quad k \left(kv_1 + \frac{v_B}{R} \right) \left(\frac{RR_2}{R+R_2} \right) = \frac{v_1}{R_1}$$





$$\frac{v_1}{R_1} - k^2 v_1 \frac{RR_2}{R+R_2} = k \frac{v_B}{R} \left(\frac{RR_2}{R+R_2} \right)$$

$$V_{th} = V_{oc} = v_1 = \frac{k v_B R_2}{R+R_2} \left[\frac{1}{R_1} - k^2 \frac{RR_2}{R+R_2} \right]^{-1}$$

$$V_{th} = \frac{k v_B R_2}{R+R_2} \left[\frac{R+R_2 - k^2 R R_1 R_2}{R_1 (R+R_2)} \right]^{-1}$$



$$V_{th} = \frac{k R_1 R_2 v_B}{R+R_2 - k^2 R R_1 R_2}$$

Set independent sources to 0

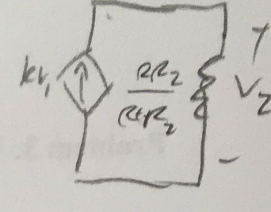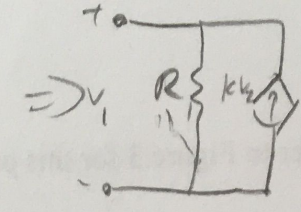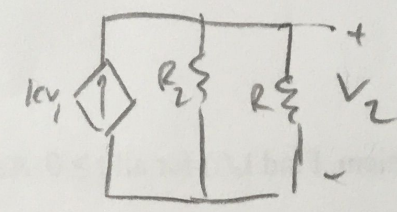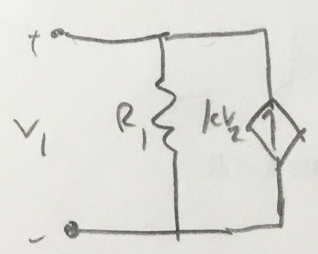

$$KCL \sum kv_1 = v_2 \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$
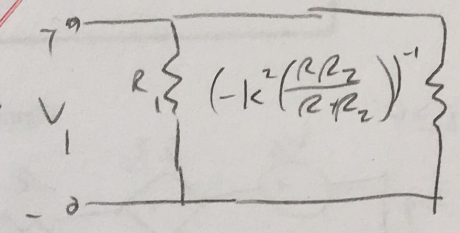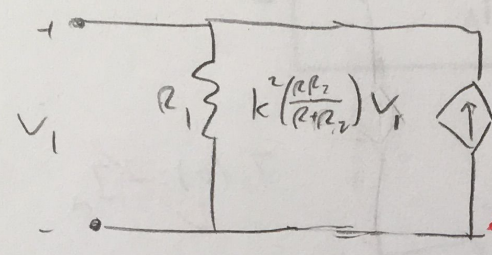
$$v_2 = k \left(\frac{R_1 R_2}{R_1 + R_2} \right) v_1$$




$$R_{th} = \left[\frac{1}{R_1} - \frac{k^2 R_1 R_2}{R_1 + R_2} \right]^{-1}$$


$$= \left[\frac{R_1 + R_2 - k^2 R_1 R_2}{R_1 (R_1 + R_2)} \right]^{-1}$$

$$R_{th} = \frac{R_1 R_2 + R_1 R_2}{R_1 + R_2 - k^2 R_1 R_2}$$

$$V_{th} = \frac{k R_1 R_2}{R_1 + R_2 - k^2 R_1 R_2} v_3$$

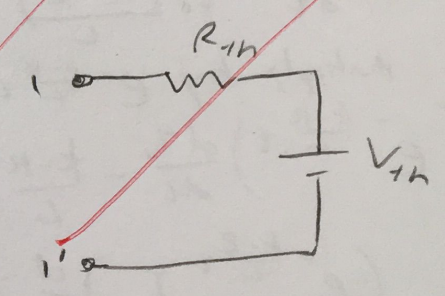

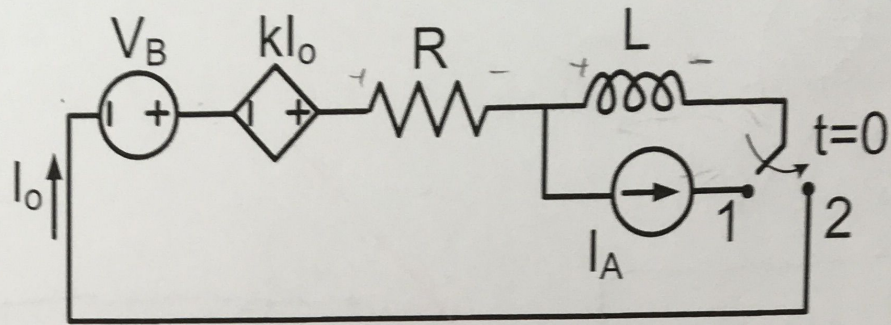Problem 3: Refer to Figure 3 for this problem. Find $I_o(t)$ for all $t \geq 0$. Assume $k < R$.



(35 points)

Solution:

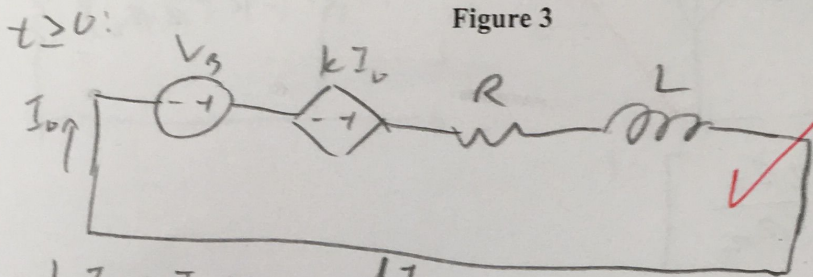


Figure 3

$I_o(0) = -I_A$

$$-V_B - kI_o + I_o R + L \frac{dI_o}{dt} = 0$$

$$L \frac{dI_o}{dt} - I_o (k - R) = V_B$$

Multiply by $e^{-\frac{k-R}{L}t}$

$$\left(e^{-\frac{k-R}{L}t} \right) \frac{dI_o}{dt} - \frac{k-R}{L} e^{-\frac{k-R}{L}t} I_o = \frac{V_B}{L} e^{-\frac{k-R}{L}t}$$

$$\left(e^{-\frac{k-R}{L}t} I_o \right) \frac{d}{dt} = \frac{V_B}{L} e^{-\frac{k-R}{L}t}$$

$$e^{-\frac{k-R}{L}t} I_o = \frac{V_B}{L} \left(-\frac{k-R}{L} \right)^{-1} e^{-\frac{k-R}{L}t} + C$$

$$I_o = \frac{-V_B}{k-R} + C e^{\frac{k-R}{L}t}$$

$$I_o(0) = \frac{-V_B}{R-k} + C e^{\frac{k-R}{L}(0)} = -I_A$$

$$C = -I_A - \frac{V_B}{R-k}$$

$$I_o(t) = \frac{V_B}{R-k} - \left(I_A + \frac{V_B}{R-k} \right) e^{-\frac{R-k}{L}t}$$

$t \geq 0$