

$$\begin{aligned} P_1: P &= i \cdot v \\ &= \frac{dQ}{dt} \cdot v \\ &= \frac{d(vC)}{dt} \cdot v \\ &= \left(C \frac{dv}{dt} + v \frac{dc}{dt} \right) v \end{aligned}$$

$$P dt = (6v - av^2) dv + v^2 d(6 - av)$$


$$W = \int_2^4 (6v - av^2) dv + \int_2^4 (-av^2) dv$$

$$= \left(\frac{1}{2} 6v^2 - \frac{2}{3} av^3 \right) \Big|_2^4$$

$$= \frac{136}{3} \text{ J}$$

P2: find V_{oc} : leave part II' open $\Rightarrow V_x = 0 \Rightarrow V_{oc} = 2 \times 10^3 \times 10^{-3} V_x = 9 V$

find R_{TH} : apply test V_T, I_T

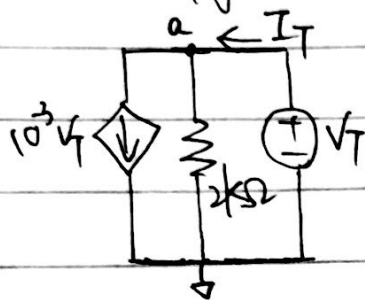


KCL @ node a: $I_T = 10^3 V_T + \frac{V_T}{2 \times 10^3}$

$$I_T = \frac{3}{2000} V_T$$

$$R_{TH} = \frac{V_T}{I_T} = \frac{2000}{3} \Omega$$

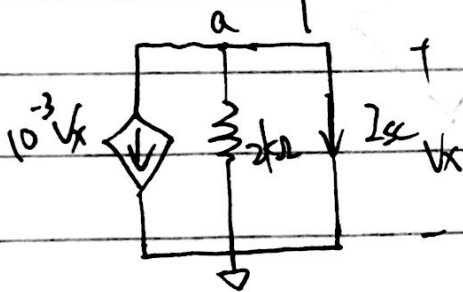
find I_{sc} : leave part II' short $\Rightarrow V_x = 0$








KCL @ node a:

$$I_{sc} = -10^3 V_x - \frac{V_x}{2 \times 10^3} = 0 A$$

Norton's equivalent circuit:

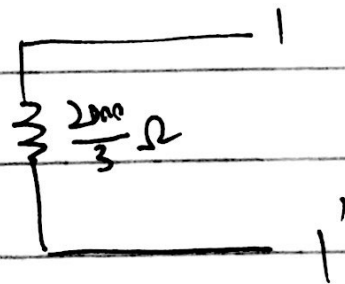

P3: a. Spanning tree

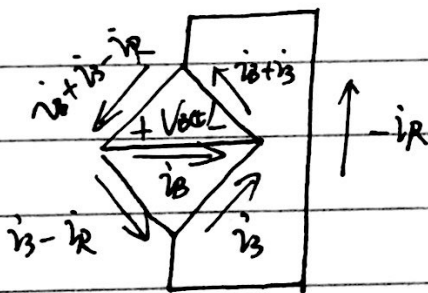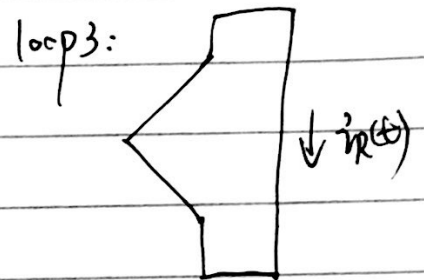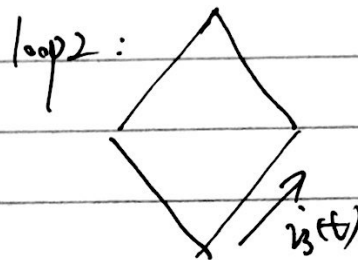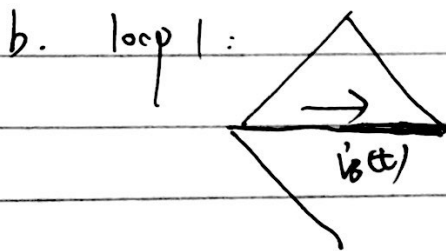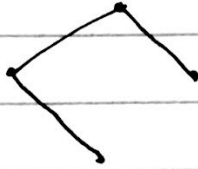

current in each branch
 (we also define the voltage across the current source as V_{ccL})


$$\text{KVL for loop 1: } \frac{1}{C} \int_{-\infty}^t [i_B(z) + i_3(z)] dz + [i_B(t) + i_3(t) - i_R(t)] R_1 + V_{ccL} = 0$$

$$\text{KVL for loop 2: } \frac{1}{C} \int_{-\infty}^t [i_B(z) + i_3(z)] dz + [i_3(t) + i_3(t) - i_R(t)] R_1$$

$$+ [i_3(t) - i_R(t)] R_2 + i_3(t) R_3 = 0$$

$$\text{KVL for loop 3: } -i_R(t) R + [i_B(t) + i_3(t) - i_R(t)] R_1 + [i_3(t) - i_R(t)] R_2 = 0$$

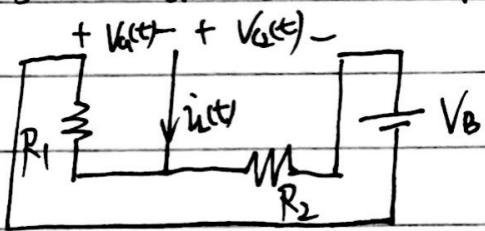P4: In steady state, C_1, C_2 behave like open circuit and L behaves like short circuit. So circuit can be simplified.



$$i(t) = 0 \text{ A}$$

$$V_a(t) = -V_B \frac{R_1}{R_1 + R_2} = -3 \cdot \frac{1 \times 10^3}{1 \times 10^3 + 2 \times 10^3} = -0.6 \text{ V}$$

PS. a. KVL: $L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i(z) dz = 0$

$$\frac{d^2 i(t)}{dt^2} + \frac{1}{LC} i(t) = 0$$

b. $i(0^+) = i(0^-) = 1 \text{ A}$

$$\left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{v(0^+)}{L} = \frac{v(0^-)}{L} = \frac{1}{0.25} = 4 \text{ A/s}$$

c. $\left. \frac{d^2 i(t)}{dt^2} \right|_{t=0^+} = -\frac{1}{LC} i(t) \Big|_{t=0^+} = -\frac{1}{LC} i(0^+) = -\frac{1}{0.25 \times 1} \times 1 = -4 \text{ A/s}^2$

d. $s^2 + 4 = 0$

$$s = \pm 2j \Rightarrow \sigma = 0, \omega = 2 \Rightarrow i_g(t) = 2|K| \cos(2t + 4K)$$

$$i_p(t) = 0 \Rightarrow i(t) = i_g(t) + i_p(t) = 2|K| \cos(2t + 4K) \quad \text{--- ①}$$

$$\frac{di(t)}{dt} = -4|K| \sin(2t + 4K) \quad \text{--- ②}$$

use boundary values:

plug $t=0$ to ①: $2|K| \cos 4K = 1$

plug $t=0$ to ②: $-4|K| \sin 4K = 4$

$$\Rightarrow \begin{cases} 4K = -\tan^{-1} 2 = -63^\circ \\ |K| = \frac{\sqrt{5}}{2} \end{cases}$$

$$\Rightarrow i(t) = \frac{\sqrt{5}}{2} \cos(2t - 63^\circ)$$