

**ECE 10, Winter 2020, Midterm – February 19, 2020**

**Instructions:** This exam booklet consists of five problems, blank sheets for the solutions, reference sheets with mathematical identities, and additional blank sheets. Please follow these instructions while answering your exam:

1. Write your name and student identification number below.
2. Write the names of students to your left and right as well.
3. You have 1 hour 45 minutes to finish your exam.
4. Write your solutions in the provided blank sheets after each problem.
5. The sheets marked “Scratch...” will NOT be graded. These sheets are provided for your rough calculations only.
6. Write your solutions clearly. Put a box around your final answer. Illegible solutions will not be graded.
7. Be brief.
8. Open book & open notes only. NO homework solution!
9. Regular, scientific, and graphing calculators are allowed.

NAME: \_\_\_\_\_

STUDENT ID: \_\_\_\_\_

NAMES OF ADJACENT STUDENTS:

LEFT: \_\_\_\_\_

RIGHT: \_\_\_\_\_

<b>Problem</b>	<b>Score</b>
<b>#1</b>	<b>/5</b>
<b>#2</b>	<b>/10</b>
<b>#3</b>	<b>/10</b>
<b>#4</b>	<b>/10</b>
<b>#5</b>	<b>/15</b>
<b>Total</b>	<b>/50</b>

**Problem 1:** Consider a capacitor whose capacitance  $C$  changes with the potential difference,  $V$ , applied across it in the following manner:

$$C = C(V) = C_0 - C_1 V$$

where  $C_0 = 20\text{F}$  and  $C_1 = 2\text{F/V}$  respectively. This capacitor was charged from  $2\text{V}$  to  $4\text{V}$ . Calculate the amount of work done in doing so.

**(5 points)**

**Solution :**

**Problem 2:** Derive the Norton's equivalent of the circuit shown in Figure 1.

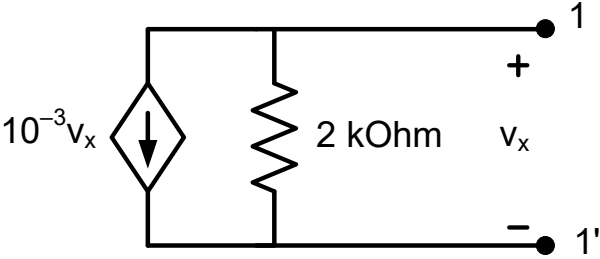


Figure 1

**(10 points)**

**Solution:**



**Problem 3:** Consider the circuit shown in Figure 2.

- Draw a spanning tree that does **not** include the branches  $R_3$  and  $R$ .
- Use mesh current method to write the equations for this circuit. Make sure that  $i_3(t)$  (current through  $R_3$ ) and  $i_R(t)$  (current through  $R$ ) are two of the unknowns. Assume that no energy is stored in any of the components.

(3 + 7 = 10 points)

**Solution:**

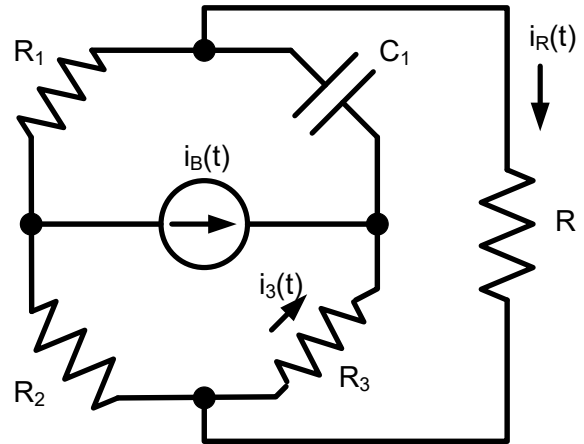


Figure 2.



**Problem 4:** Assume that the circuit shown in Figure 3 has reached steady state i.e. it has existed in this form for a very long time. Given  $R_1 = 1$  kiloOhms,  $R_2 = 4$  kiloOhms,  $L = 1$  nH,  $C_1 = 1$  nF,  $C_2 = 1$  nF, and  $V_B = 3$  V, calculate the steady state values of  $v_{C1}(t)$  and  $i_L(t)$ .

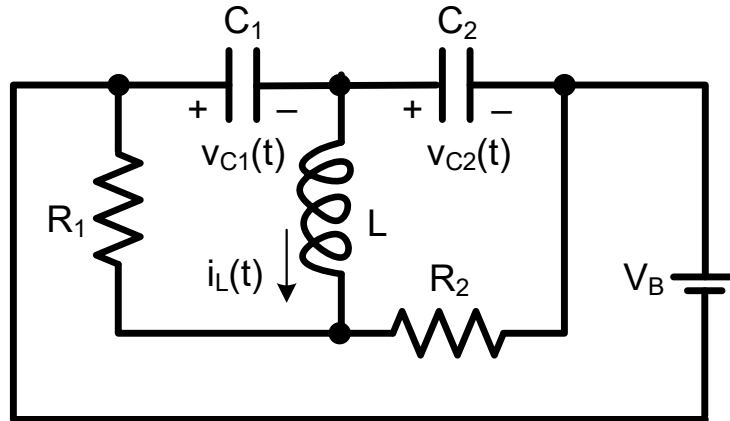


Figure 3.


(5 + 5 = 10 points)

**Solution:**





**Problem 5:** Refer to Figure 4 for this problem. The circuit came into existence at  $t = 0$ , prior to which,  $i_L(0^-) = 1\text{A}$  and  $v_C(0^-) = 1\text{V}$ . Assume that  $L = 0.25\text{H}$ ,  $C_1 = 1\text{F}$ .

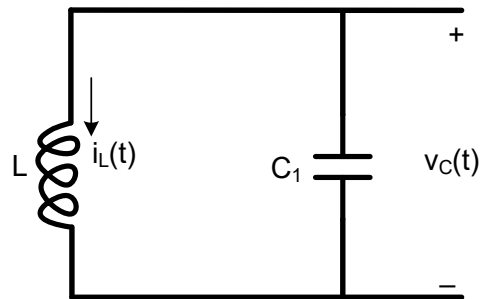

**Figure 4.**

- Derive a differential equation in terms of  $i_L(t)$  that characterizes circuit behavior for  $t \geq 0$ .
- Determine the values of  $i_L(0^+)$  and  $\left. \frac{di_L(t)}{dt} \right|_{t=0^+}$ .
- Determine the value of  $\left. \frac{d^2 i_L(t)}{dt^2} \right|_{t=0^+}$ .
- Derive an expression for the complete solution of  $i_L(t)$  in this circuit.

**(2 + 3 + 3 + 7 = 15 points)**

**Solution:**





## Reference Sheet #1

### Trigonometric Identities:

$$\sin A = \cos(A - 90^\circ) = \cos(A - \pi/2)$$

$$\cos A = \sin(A + 90^\circ) = \sin(A + \pi/2)$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos A + \cos B = 2 \cos\left(\frac{A+B}{2}\right) \cos\left(\frac{A-B}{2}\right)$$

$$\cos A - \cos B = -2 \sin\left(\frac{A+B}{2}\right) \sin\left(\frac{A-B}{2}\right)$$

$$\sin A + \sin B = 2 \sin\left(\frac{A+B}{2}\right) \cos\left(\frac{A-B}{2}\right)$$

$$\sin A - \sin B = 2 \cos\left(\frac{A+B}{2}\right) \sin\left(\frac{A-B}{2}\right)$$

$$\cos 2A = 2 \cos^2 A - 1 = \cos^2 A - \sin^2 A = 1 - 2 \sin^2 A$$

$$\sin 2A = 2 \sin A \cos A$$

$$\cos 3A = 4 \cos^3 A - 3 \cos A$$

$$\sin 3A = 3 \sin A - 4 \sin^3 A$$

$$a \cos A + b \sin A = \sqrt{a^2 + b^2} \cos\left(A - \tan^{-1}(b/a)\right)$$

### Complex Arithmetic:

$$\operatorname{Re}\{z_1 \pm z_2\} = \operatorname{Re}\{z_1\} \pm \operatorname{Re}\{z_2\}$$

$$\operatorname{Im}\{z_1 \pm z_2\} = \operatorname{Im}\{z_1\} \pm \operatorname{Im}\{z_2\}$$

$$\operatorname{Re}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Re}\{z_2\} - \operatorname{Im}\{z_1\} \operatorname{Im}\{z_2\}$$

$$\operatorname{Im}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Im}\{z_2\} + \operatorname{Im}\{z_1\} \operatorname{Re}\{z_2\}$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$x + jy = r e^{j\theta} \text{ where } r = \sqrt{x^2 + y^2}, \theta = \tan^{-1}(y/x)$$

$$r e^{j\theta} = x + jy \text{ where } x = r \cos \theta, y = r \sin \theta$$

$$|z_1 z_2| = |z_1| |z_2|, \quad \operatorname{angle}(z_1 z_2) = \operatorname{angle}(z_1) + \operatorname{angle}(z_2)$$

$$|1/z| = 1/|z|, \quad \operatorname{angle}(1/z) = -\operatorname{angle}(z)$$

$$(x + jy)^* = x - jy, \quad \operatorname{angle}(z^*) = -\operatorname{angle}(z)$$

### Quadratic Equations:

$$\text{The roots of } ax^2 + bx + c = 0 \text{ are } x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**Scratch Paper (Will NOT be graded)**



