

EE10

Midterm Exam

Fall 2012

Group 2

Time Limit: 1 hour and 50 minutes

Open Book, Open Notes

Calculators are allowed.

Your Name:

Solutions

Name of Person to Your Left:

Name of Person to Your Right:

1. 14



2. 15

3. 10


4. 6

45

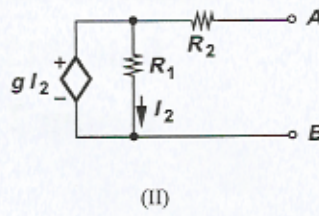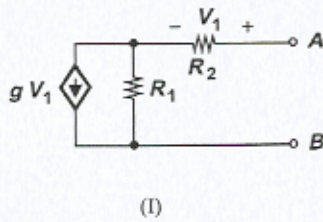1. (a) Consider the circuit shown in (I) below. Determine the equivalent resistance between terminals A and B.
 (b) What happens to the equivalent resistance as g approaches $1/R_2$? Can you explain intuitively why?
 (c) Consider the circuit shown in (II) below. Determine the equivalent resistance between terminals A and B.



(a). Apply test current source I_x .

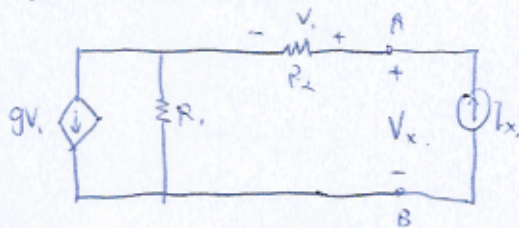

$$I_x = \frac{V_x}{R_2} = gV_1 + \frac{V_x - V_1}{R_1}$$

$$\Rightarrow \frac{V_x}{I_x} = R_1 + R_2 - gR_1R_2$$

$$R_{eq} = R_1 + R_2 - gR_1R_2$$

(5)


(b). when g approaches $1/R_2$, R_{eq} approaches R_2 .

That's because current through R_2 is $\frac{V_1}{R_2}$ which equals to gV_1 .

So there's no current flowing through R_1 . Therefore, $\frac{V_x}{I_x} = \frac{V_1}{\frac{V_1}{R_2}} = R_2$.

(4)

(c). Apply test current source I_x

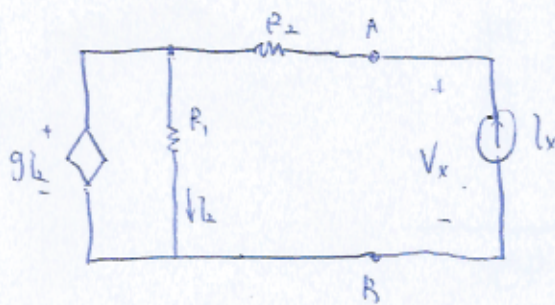

According to KCL,

$$I_x = \frac{V_x - gI_2}{R_2} \quad \dots \quad (1)$$

$$\text{where } I_2 = \frac{gI_2}{R_1} \quad \dots \quad (2)$$

For arbitrary choosing g and R_1 ,


we can only have $I_2 = 0$ to satisfy (2).

Therefore (1) is simplified to


$$I_x = \frac{V_x}{R_2} \Rightarrow R_{eq} = \frac{V_x}{I_x} = R_2$$

(5)

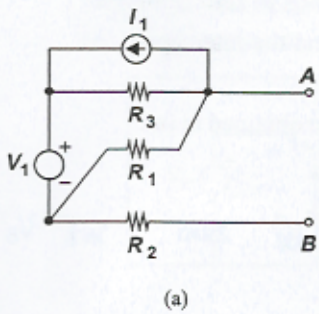
2. Determine the Thevenin equivalent circuit of each circuit shown below.



(a)

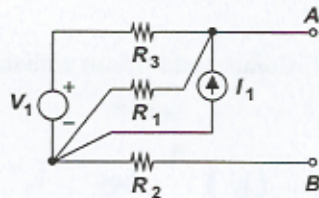

(b)


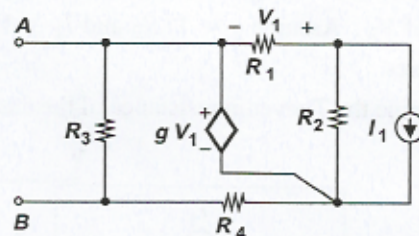


(c)

(a). First, let's determine V_{TH} :
 Superposition gives

$$V_{TH} = \frac{R_1}{R_1 + R_3} V_1 - I_1 \frac{R_1 R_3}{R_1 + R_3}$$
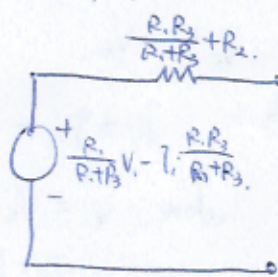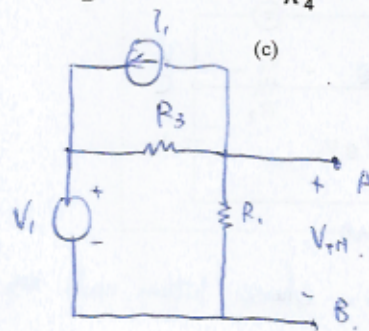
$$\text{Then } R_{TH} = R_1 // R_3 + R_2 = \frac{R_1 R_3}{R_1 + R_3} + R_2$$





5

(b). First, let's determine V_{TH} :

$$V_{TH} = \frac{R_1}{R_1 + R_3} V_1 + I_1 \frac{R_1 R_3}{R_1 + R_3}$$
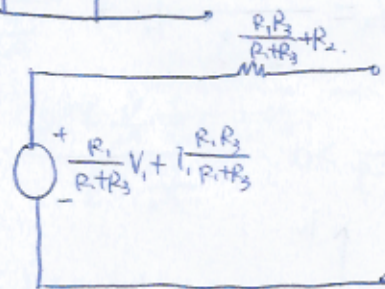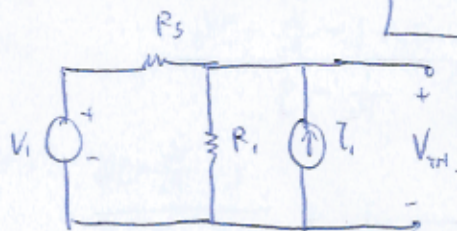
$$\text{Then } R_{TH} = R_1 // R_3 + R_2 = \frac{R_1 R_3}{R_1 + R_3} + R_2$$



4

(c). First, let's determine V_{TH} :


Choosing bottom node as GND, using nodal

Analysis: $V_a = gV_1$.

$$\text{KCL @ b: } \frac{V_b - V_a}{R_1} + \frac{V_b}{R_2} + I_1 = 0$$

$$\text{where } V_1 = \frac{V_b - V_a}{R_1} \Rightarrow V_1 = V_b - V_a$$
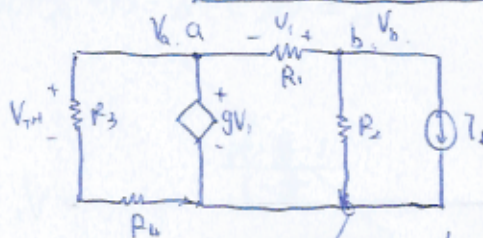
$$\Rightarrow V_a = -\frac{gI_1}{\frac{1}{R_1} + \frac{1+g}{R_2}} \Rightarrow V_{TH} = \frac{R_3}{R_3 + R_4} V_a = -\frac{gR_1 R_2 R_3 I_1}{(R_3 + R_4)(R_2 + (1+g)R_1)}$$



upon calculating R_{TH} , we find

$$V_1 = -gV_1 \frac{R_1}{R_1 + R_2} \Rightarrow V_1 = 0$$


$$\Rightarrow R_{TH} = R_3 // R_4 = \frac{R_3 R_4}{R_3 + R_4}$$

6

3. Consider the circuit shown in the dashed box below. We conduct two experiments.

(a) First, apply an external voltage, V_X , and measure I_X without setting any sources in the dashed box to zero. Plot I_X as a function of V_X . Assume $g < 1/R_2$ and $I_1 > V_B(-g + 1/R_2)$. Clearly show the slope and the intercepts with the x and y axes.

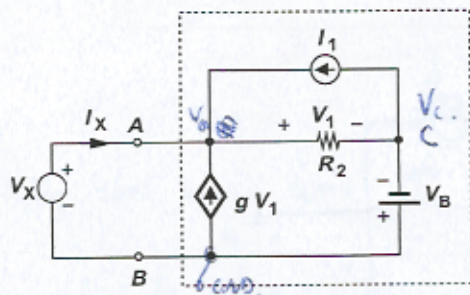(b) Second, determine the Thevenin resistance of the dashed box. Compare this result with the slope obtained in (a).



(a). Using Nodal Analysis, choose bottom node as GND.

$$V_c = -V_B$$

$$\text{KCL @ A: } I_x + gV_1 + I_1 + \frac{V_c - V_a}{R_2} = 0$$


$$\text{where } V_1 = V_a - V_c$$

$$\Rightarrow V_a = \frac{I_x + I_1 - \frac{V_a}{R_2} + gV_B}{\frac{1}{R_2} - g}$$

$$\Rightarrow V_x = V_a = \frac{1}{\frac{1}{R_2} - g} I_x + \frac{I_1 - \frac{V_B}{R_2} + gV_B}{\frac{1}{R_2} - g}$$


$$\text{where } \frac{1}{\frac{1}{R_2} - g} > 0, \quad \frac{I_1 - \frac{V_B}{R_2} + gV_B}{\frac{1}{R_2} - g} > 0$$
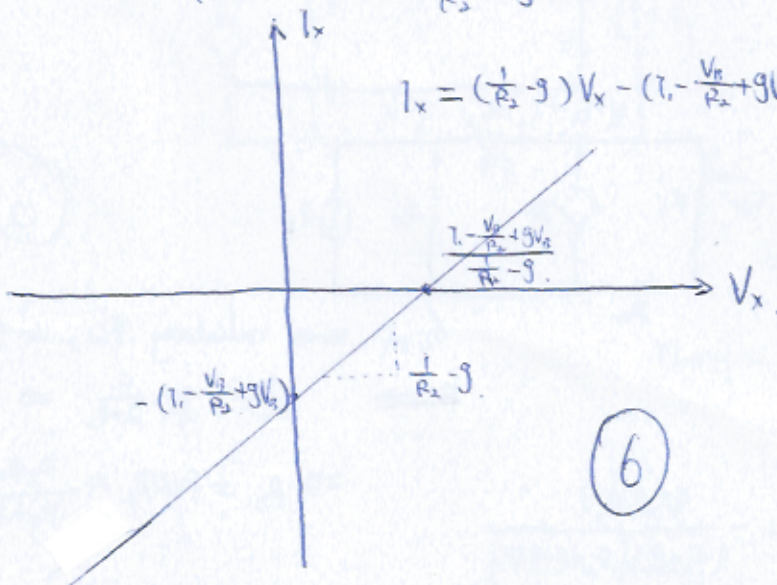
$$I_x = (\frac{1}{R_2} - g)V_x - (I_1 - \frac{V_B}{R_2} + gV_B)$$



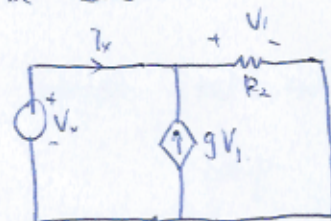(6)

(b). Set I_1 to be zero, set V_B to be zero.



$$R_{TH} = R_2 \parallel (-\frac{1}{g})$$

$$= \frac{1}{\frac{1}{R_2} - g}$$



$$\text{So } I_x = \frac{V_x}{R_{TH}} = (\frac{1}{R_2} - g)V_x$$

If plotting I_x versus V_x again, the slope are the same in these two conditions. Independent sources only add offset to V_x, I_x curve.

[Or simply saying, resistance is the inverse of $I_x - V_x$ curve.]

(4)

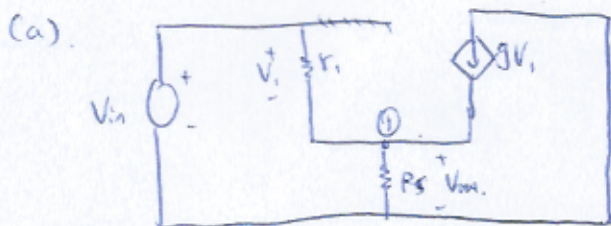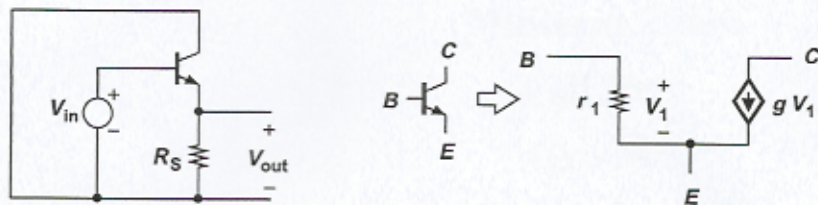4. (a) Shown below is an amplifier incorporating a transistor. Using the circuit model shown for the transistor, determine V_{out} in terms of V_{in} .
 (b) What happens as $R_S \rightarrow \infty$?



Using KVL, we have $V_1 = V_{in} - V_{out}$

Apply KCL @ (1):

$$\frac{V_1}{r_1} - \frac{V_{out}}{R_S} + gV_1 = 0.$$

$$\Rightarrow V_{out} = \frac{\frac{1}{r_1} + g}{\frac{1}{R_S} + \frac{1}{r_1} + g} \cdot V_{in}.$$

$$= \frac{(1 + gr_1)R_S}{r_1 + (1 + gr_1)R_S} \cdot V_{in}.$$

(5)

(b). when $R_S \rightarrow \infty$, $V_{out} \rightarrow V_{in}$. because $\frac{\frac{1}{r_1} + g}{\frac{1}{R_S} + \frac{1}{r_1} + g} \rightarrow 1$.

(1)