

EE10

Midterm Exam

Fall 2012

Group 2

Time Limit: 1 hour and 50 minutes


Open Book, Open Notes

Calculators are allowed.

Your Name:



Name of Person to Your Left:

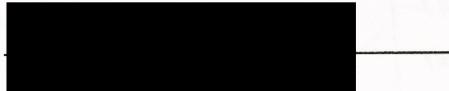

Name of Person to Your Right:



1. 9

2. 11


3. 8.5

4. 2+1


$$\begin{array}{r} 30.5 + 1 = 31.5 \\ \hline \end{array}$$

(a)

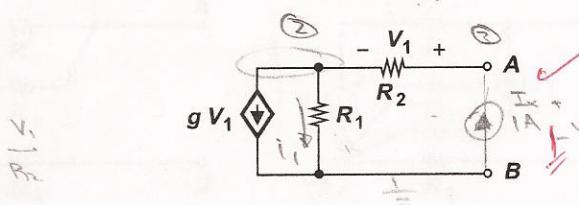- Consider the circuit shown in (I) below. Determine the equivalent resistance between terminals A and B.
- What happens to the equivalent resistance as g approaches $1/R_2$? Can you explain intuitively why?
- Consider the circuit shown in (II) below. Determine the equivalent resistance between terminals A and B.



(I)

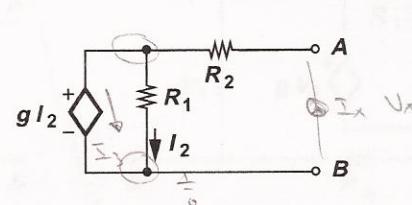

(II)

$$V_x - I_x R_2 - I_2 R_1 = 0$$

$$V_x - I_x R_2 - I_2 R_1 = 0$$

$$\frac{V_x - I_x R_2}{R_1} = I_2$$

$$2) \quad KCL \text{ at } 1: \quad -gV_1 - \frac{V_2}{R_1} + \frac{V_3 - V_2}{R_2} = 0 \quad V_3 = V_x$$

$$KCL \text{ at } 2: \quad \frac{V_2 - V_3}{R_2} + I = 0$$

$$V_1 = V_2 - V_3$$

$$\frac{V_3 - V_2}{R_1} = 1$$

$$-g(V_3 - V_2) - \frac{V_2}{R_1} + I = 0$$

$$-g(V_3 - V_2) = \frac{V_2}{R_1} - I$$

$$V_3 = -\left(\frac{V_2}{R_1} - I\right) + V_2 = R$$

$$I_x = I_2 + gV_1$$

$$I_x = \frac{V_x - I_x R_2}{R_1} + gV_1$$

$$I_x = I_2 + \frac{V_x - I_x R_2}{R_1} - I_2 R_1$$

$$R + R_2 - R_1 R_2 g$$

$$I_x R_1 (1 + \frac{R_2}{R_1} - g R_2) = V_x$$

$$\boxed{R_{eq} = R_1 + R_2 - g R_1 R_2}$$

$$R_1 I_2 = V_x - I_x R_2$$

$$I_2 = \frac{V_x - I_x R_2}{R_1}$$

b)

$$\begin{cases} g \rightarrow 1/R_2 \\ R_{eq} \rightarrow (R_2) \end{cases}$$

only current flowing through R_2 resistor. Current flows around R_1 resistor, so it's like you only have R_2 resistor in circuit.

$$I_x = I_2 + I_3$$

$$I_x = \frac{R_1 I_2}{R_1 + R_2}$$

$$V_3 - V_2 = V_1$$

$$KCL \text{ at } 2: \quad \frac{V_3 - V_2}{R_2} - \frac{V_1}{R_2} - \frac{V_2}{R_1} = 0$$

$$\frac{V_1}{R_2} - \frac{V_x}{R_2} - \frac{V_2}{R_1} = 0$$

$$V_2 = 0$$

$$I_1 = \frac{V_2}{R_1} = 0$$

$$c) \quad V_x = I_x R_2 + g I_2 \quad V_x = I_x R_2 + I_2 R_1 \quad I_x = I_2 + I_3$$

$$g I_2 = I_2 R_1$$

$$g = R_1$$


$$V_x = I_x R_2 + \frac{V_x - I_x R_2}{R_1} R_1$$

$$I_x = \frac{V_x}{R_3} + I_2 + I_4 + I$$

+11

$$V_x = I_3 R_1 + I_4 R_2 + I_2 R_4$$

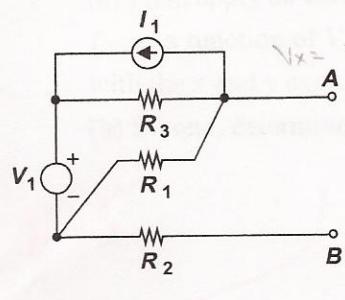2. Determine the Thevenin equivalent circuit of each circuit shown below.




(a)

$$I_2 = I_3 + I$$

$$I_4 = I_2 - I$$

$$V_x = I_3 R_1 + (I_3 - I) R_2 + (I_3 + I) R_4 + I R_1$$

for V_x

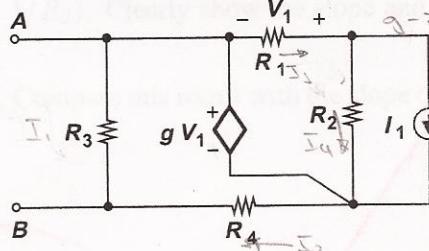

(c)


$$g(I_4 + I) R_1 = \frac{I_4 + I}{R_1} + \frac{I_4}{R_2}$$

$$g R_1 - \frac{I}{R_1} = I_4 \left(\frac{1}{R_1} + \frac{1}{R_2} - g R_1 \right)$$

$$I_4 = \frac{g - \frac{I}{R_1}}{\left(\frac{1}{R_1} + \frac{1}{R_2} - g R_1 \right)}$$

$$g V_1$$

a) $R_{TH} = (R_3 || R_1) + R_2$

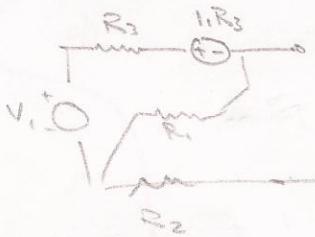

$$I = \frac{V_1 - I R_3}{R_2} = \frac{V_1 - I R_3}{R_2} \parallel \frac{R_3}{R_1 + R_3} \parallel R_1$$

$$V = \frac{V_1 - I R_3}{R_2} \left(\frac{R_1 R_3}{R_1 + R_3} \right) = \frac{(V_1 - I R_3) R_1}{R_1 + R_3}$$

$$R_{TH} = \frac{(V_1 - I R_3) R_1}{R_1 + R_3}$$

$$R_{TH} = \frac{R_1 R_3}{R_1 + R_3} + R_2$$

$$I = \frac{V_1}{R_2} + I_1 \parallel \frac{R_1 R_3}{R_1 + R_3} \parallel R_1$$

$$I = \frac{V_1}{R_2} + I_1 \parallel \frac{R_1 R_3}{R_1 + R_3} \parallel R_1$$

$$V = \frac{(V_1 - I R_3) R_1 R_3}{R_1 + R_3}$$

$$V = \frac{(V_1 - I) R_1 R_3}{R_1 + R_3}$$

$$R_{TH} = \frac{R_1 R_3}{R_1 + R_3 + R_2}$$

+4

$$KCL 1: 1 + \frac{V_2 - V_1}{R_3} + \frac{V_3 - V_1}{R_1} + \frac{V_3 - V_2}{R_2} + \frac{V_2 - V_3}{R_4} = 0$$

$$KCL 2: -1 + \frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} = 0$$

$$KCL 3: \frac{V_1 - V_3}{R_1} - \frac{V_3}{R_2} = 0$$

$$\sum_2 = \frac{V_x - g V_1}{R_4}$$

$$V_x - g V_1 - R_4 I_2 = 0$$

$$I_x = I_1 + I_2 + I_3$$

$$I_x = \frac{V_x}{R_3} + \frac{V_x - g(I_4 + I)}{R_4} + I_4 + I$$

$$I_x = \frac{V_x}{R_3} + \frac{V_x - g \left(\frac{I_4 + I}{R_1 + R_2 + R_4} \right) R_1}{R_4} +$$

$$g V_1 = I_3 R_1 + (I_3 - I) R_2$$

$$g I_3 R_1 = I_3 R_1 + (I_3 - I) R_2$$

Solve this for I_3

+2

$$I_x = \frac{V_x}{R_3} + \frac{V_x - g V_1}{R_4} + \frac{V_x}{R_1 + R_2 + R_4}$$

$$I_x = \frac{V_x}{R_3} + \frac{V_x - g \left(\frac{V_x - g V_1}{R_1 + R_2 + R_4} \right) R_1}{R_4} + \frac{V_x}{R_1 + R_2 + R_4}$$

$$R_{TH} = \frac{1}{R_3} + \frac{1 - g \left(\frac{R_1}{R_1 + R_2 + R_4} \right)}{R_4} + \frac{1}{R_1 + R_2 + R_4}$$

$$V_x = \frac{V_x - R_4 I_2}{g} R_1 + \left(\frac{V_x - R_4 I_2}{g} - 1 \right) R_2 + \left(\frac{V_x - R_4 I_2}{g} + 1 \right) R_4$$

$$V_x \left(1 + \frac{R_1}{g} + \frac{R_2}{g} + \frac{R_4}{g} \right) - \left(\frac{R_4 I_2}{g} \right) (R_1 + R_2 + R_4) - R_2 + R_4$$

$$V_x \left(1 + \frac{R_1}{g} + \frac{R_2}{g} + \frac{R_4}{g} \right) = - \frac{R_4 I_2}{g} (R_1 + R_2 + R_4) - R_2 + R_4$$


$$V_{TH} = - \frac{R_4 I_2}{g} (R_1 + R_2 + R_4) - R_2 + R_4$$

3. Consider the circuit shown in the dashed box below. We conduct two experiments.

(a) First, apply an external voltage, V_X , and measure I_X without setting any sources in the dashed box to zero. Plot I_X as a function of V_X . Assume $g < 1/R_2$ and $I_1 > V_B(-g + 1/R_2)$. Clearly show the slope and the intercepts with the x and y axes.

(b) Second, determine the Thevenin resistance of the dashed box. Compare this result with the slope obtained in (a).

8.5

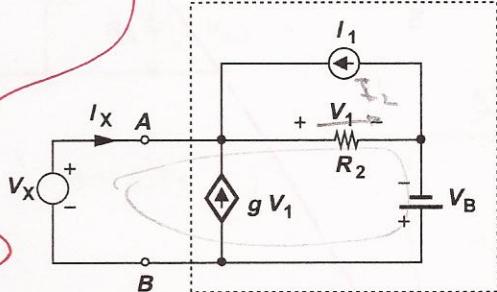

$$I_2 = \frac{V_1}{R_2}$$

a)

$$I_x + I_1 - I_2 + gI_2R_2 = 0$$

$$V_x - I_2R_2 + V_B = 0$$

$$I_x = -I_1 + I_2 - gI_2R_2$$

$$I_2 = \frac{V_x + V_B}{R_2}$$

$$I_x = -I_1 + \frac{V_x + V_B}{R_2} - g\left(\frac{V_x + V_B}{R_2}\right)R_2$$

$$I_x = -I_1 + \frac{V_x}{R_2} - gV_x + V_B$$

$$g < 1/R_2$$

$$\boxed{\frac{I_x + I_1}{(\frac{1}{R_2} - g)} - V_B = V_x}$$

b.




$$I_x + gV_1 - \frac{V_1}{R_2} = 0$$

$$KVL \quad V_x - V_1 = 0$$

$$V_x = V_1$$

$$I_x = \frac{V_x}{R_2} - gV_x$$

Intercept.

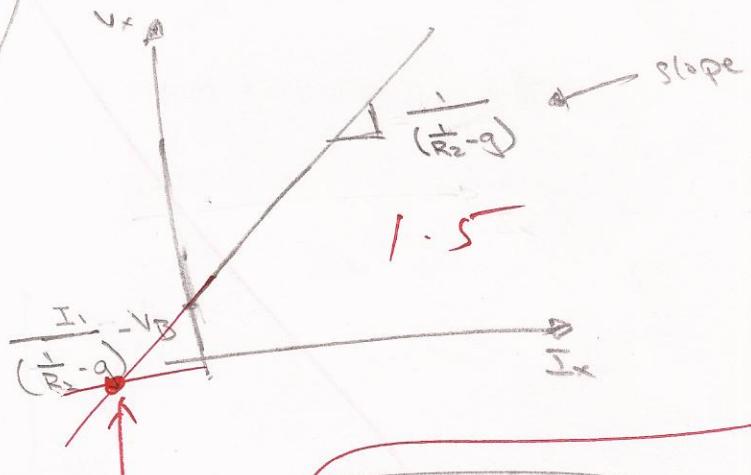



Compare?

$$V = IR \quad R_{Th} = \frac{V_x}{I_x} = \frac{V_x}{V_x(\frac{1}{R_2} - g)} = \frac{1}{\frac{1}{R_2} - g} = R_{Th}$$

$$R = \frac{V}{I}$$


Q +

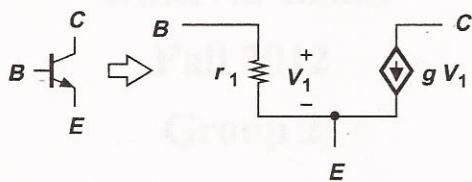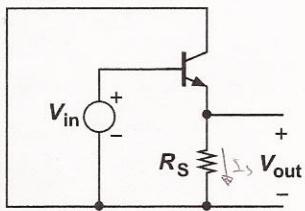4. (a) Shown below is an amplifier incorporating a transistor. Using the circuit model shown for the transistor, determine V_{out} in terms of V_{in} .
 (b) What happens as $R_S \rightarrow \infty$?



(a)

$$V_{out} = I_S R_S$$

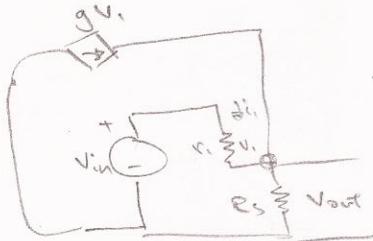

$$V_{in} - V_1 - V_{out} = 0$$

$$gV_1 + \frac{V_1}{R_i} - \frac{V_{out}}{R_S} = 0$$

$$-V_1 = I_S R_i$$

$$gI_S R_i + I_S - \frac{V_{out}}{R_S} = 0$$

$$V_{in} - I_S R_i - V_{out} = 0$$

| + |

$$I_S(gR_i + 1) = \frac{V_{out}}{R_S}$$

$$V_{in} - \frac{V_{out}}{R_S(gR_i + 1)} - V_{out} = 0$$

$$I_S = \frac{V_{out}}{R_S(gR_i + 1)}$$

$$V_{in} = V_{out} \left(\frac{1}{R_S(gR_i + 1)} + 1 \right)$$

$$V_{out} = \frac{V_{in}}{\left(\frac{1}{R_S(gR_i + 1)} + 1 \right)}$$

b)

$$\left\{ \begin{array}{l} \text{As } R_S \rightarrow \infty \\ V_{out} = V_{in} \end{array} \right. \quad \left. \begin{array}{l} V_{out} = \frac{V_{in}}{(0+1)} \end{array} \right|$$