

EE10

Midterm Exam

Fall 2012

Group 1

Time Limit: 1 hour and 50 minutes

Open Book, Open Notes

Calculators are allowed.

Your Name:

Emily Im

Name of Person to Your Left:

Zhibing Wu

Name of Person to Your Right:

Ahmed Hassan

1. 9
2. 10
3. 10
4. 6.

35

/ 14



/ 15

/ 10

/ 6

9

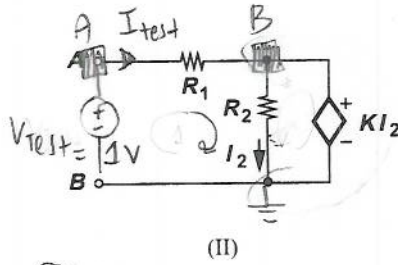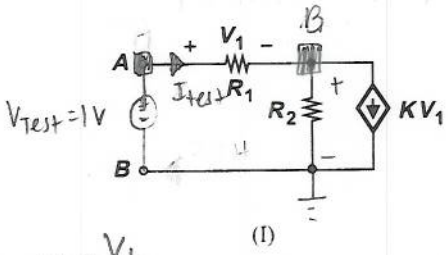1. (a) Consider the circuit shown in (I) below. Determine the equivalent resistance between terminals A and B.
- (b) What happens to the equivalent resistance as k approaches $1/R_1$? Can you explain intuitively why?
- (c) Consider the circuit shown in (II) below. Determine the equivalent resistance between terminals A and B.



(a) $I_{test} = \frac{V_1}{R_1}$ $V_1 = I_{test} R_1$

KCL @ B: $I_{test} = k V_1 + \frac{V_B}{R_2}$

$I_{test} = k I_{test} R_1 + \frac{V_B}{R_2}$

KVL: $+1 - V_B - V_1 = 0$

$V_B = 1 - V_1$

$V_B = 1 - I_{test} R_1$

$I_{test} = k I_{test} R_1 + \frac{1 - I_{test} R_1}{R_2}$

$(1 - k R_1 + \frac{R_1}{R_2}) I_{test} = \frac{1}{R_2}$

$I_{test} = \frac{1}{R_2 (1 - k R_1 + \frac{R_1}{R_2})}$

$R_{eq} = R_2 - k R_1 R_2 + R_1$

as $k \rightarrow \frac{1}{R_1}$, $R_{eq} \rightarrow R_1$

the current provided by this $k = \frac{1}{R_1}$ current source will be the same as the current going through the R_1 resistor so ~~there~~ no current would go through the R_2 resistor, (current source is ~~not~~ acting like a short in this specific case)

(c) KVL: $-1 + R_1 I_{test} + k I_2 = 0$

KVL: $-R_1 I_{test} = 1 - k I_2$

$I_{test} = \frac{1 - k I_2}{R_1}$


KVL @ node 2: $V_2 = 0$

$-I_2 R_2 + R_2 (I_{test} + I_2) = 0$

$I_2 R_2 = k I_2$

$k = R_2$

⊙ ⇒ 5 pts

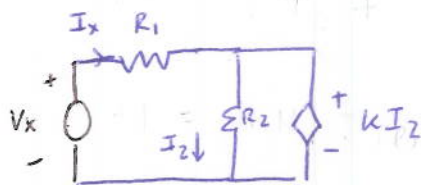


$\frac{k I_2}{R_2} = I_2 \Rightarrow I_2 = 0$


$\Rightarrow \frac{V_x}{I_x} = R_1$

+10

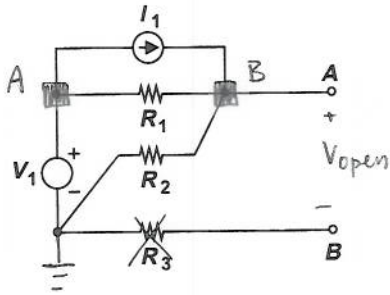
2. Determine the Thevenin equivalent circuit of each circuit shown below.



(a)

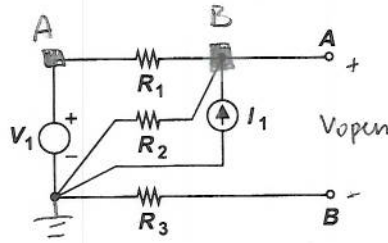

(b)

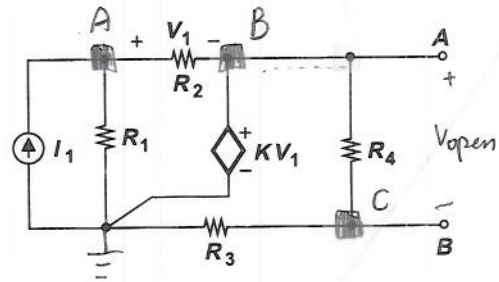

(c)


a) $V_A = V_1$ $V_B = V_{open}$

KCL @ B: $I_1 = \frac{V_B}{R_1} - \frac{V_A}{R_1} + \frac{V_B}{R_2}$


$I_1 = V_B \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_1}{R_1}$

$I_1 + \frac{V_1}{R_1} = V_B \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$

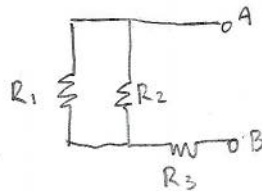$V_B = V_{open} = V_{TH} = \frac{I_1 + \frac{V_1}{R_1}}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right)}$ Volts



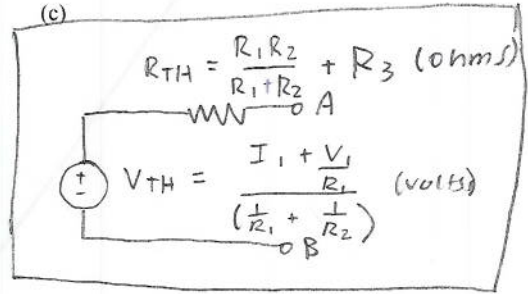$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} + R_3$




+J

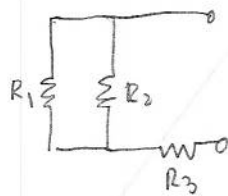
b) $V_A = V_1$ $V_B = V_{open}$

KCL @ B: $I_1 = \frac{V_B}{R_1} - \frac{V_A}{R_1} + \frac{V_B}{R_2}$

$V_{TH} = \frac{I_1 + \frac{V_1}{R_1}}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right)}$ Volts



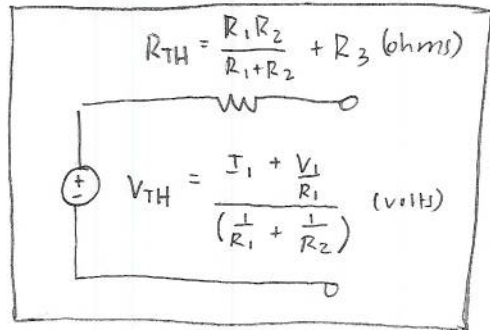$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} + R_3$



+Y

c) $V_B = kV_1$ $V_1 = V_A - V_B$


KCL @ A: $I_1 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_A - \frac{1}{R_2} V_B$

KCL @ C: $0 = \left(\frac{1}{R_4} + \frac{1}{R_3} \right) V_C - \frac{1}{R_4} V_B \Rightarrow V_C = \frac{1}{R_4} kV_1$
 $V_{open} = V_B - V_C = kV_1 - V_C$

$V_{TH} = kV_1 \left(1 - \frac{1}{R_4 \left(\frac{1}{R_4} - \frac{1}{R_3} \right)} \right)$ (volts)

4 pts in total

X
+1

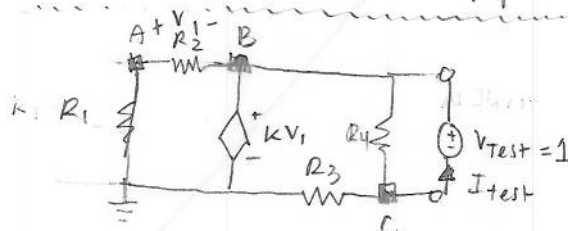


$V_B = kV_1$ $V_1 = V_A - V_B$ $V_A = V_1 + V_B$ $V_B - V_C = 1$ $V_C = V_B - 1$
 KCL @ A: $\left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_A - \frac{1}{R_2} kV_1 = 0 \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_1 + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) kV_1 - \frac{1}{R_2} kV_1 = 0 \Rightarrow$
 KCL @ C: $\left(\frac{1}{R_3} + \frac{1}{R_4} \right) V_C + I_{test} - \frac{1}{R_4} kV_1 = 0 \Rightarrow$

3. Consider the circuit shown in the dashed box below. We conduct two experiments.

(a) First, apply an external voltage, V_X , and measure I_X without setting any sources in the dashed box to zero. Plot I_X as a function of V_X . Assume $I_1 > V_B(K + 1/R_1)$. Clearly show the slope and the intercepts with the x and y axes.

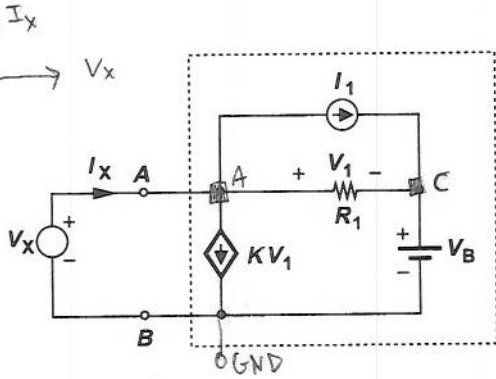(b) Second, determine the Thevenin resistance of the dashed box. Compare this result with the slope obtained in (a).



$$I_X = 0 \Rightarrow (k + \frac{1}{R_1})V_X = V_B(k + \frac{1}{R_1}) - I_1$$

$$V_X = \frac{V_B(k + \frac{1}{R_1}) - I_1}{(k + \frac{1}{R_1})}$$


$$V_X = V_B - \frac{I_1}{(k + \frac{1}{R_1})}$$

$$\textcircled{a} V_A = V_X \quad V_C = V_B$$


$$\text{KCL @ A: } I_X = kV_1 + I_1 + \frac{V_1}{R_1}$$

$$I_X = kV_X - kV_B + I_1 + \frac{V_X - V_B}{R_1}$$
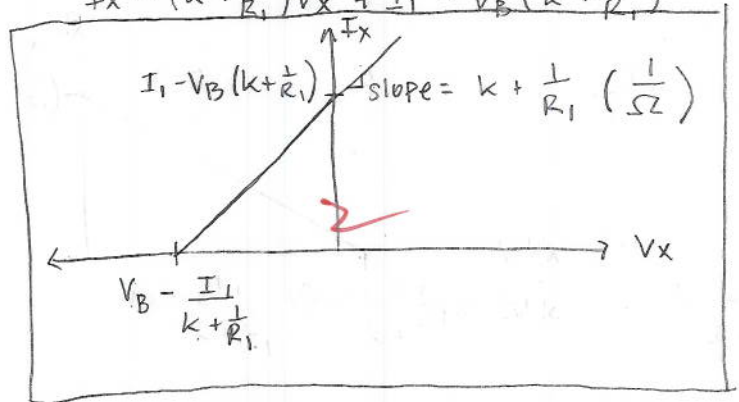
$$I_X = (k + \frac{1}{R_1})V_X + I_1 - V_B(k + \frac{1}{R_1})$$



(b)

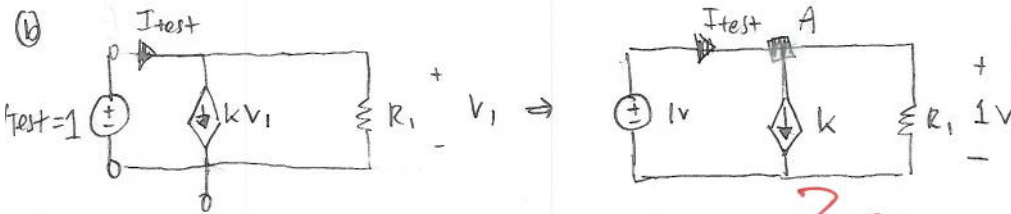

$$\text{KCL @ A: } I_{\text{test}} = k + \frac{1}{R_1}$$

$$V = IR \quad R = \frac{V_{\text{test}}}{I_{\text{test}}}$$





$$R_{\text{TH}} = \frac{1}{k + \frac{1}{R_1}} \text{ (}\Omega\text{)}$$

This is the inverse of the slope in part (a).

6.

4. (a) Shown below is an amplifier incorporating a transistor. Using the circuit model shown for the transistor, determine V_{out} in terms of V_{in} .

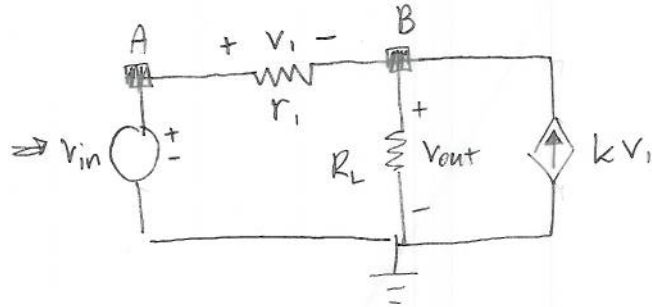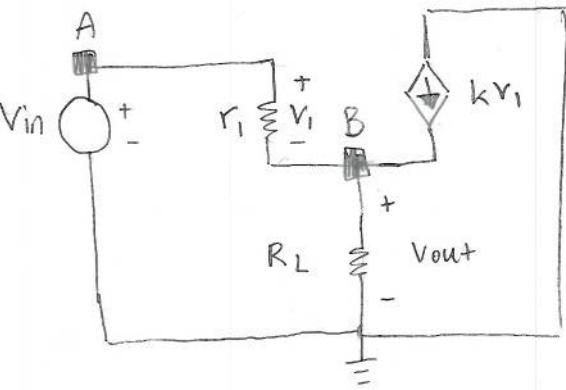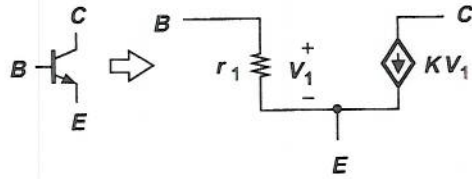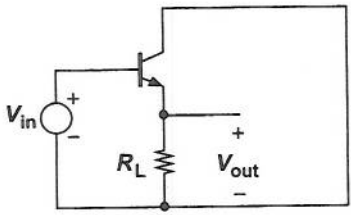(b) What happens as $R_L \rightarrow \infty$?



(a) $V_A = V_{in}$ $V_B = V_{out}$ $V_1 = V_A - V_B \Rightarrow V_1 = V_{in} - V_{out}$

$kV_1 = \frac{V_{out}}{R_L} - \frac{V_1}{r_1} \Rightarrow kV_{in} - kV_{out} = \frac{V_{out}}{R_L} - \frac{V_{in}}{r_1} + \frac{V_{out}}{r_1}$

$kV_{in} + \frac{1}{r_1}V_{in} = \frac{V_{out}}{R_L} + \frac{V_{out}}{r_1} + kV_{out}$

$(k + \frac{1}{r_1})V_{in} = (\frac{1}{R_L} + \frac{1}{r_1} + k)V_{out}$

$$V_{out} = \frac{(k + \frac{1}{r_1})}{(\frac{1}{R_L} + \frac{1}{r_1} + k)} V_{in}$$

5

(b) as $R_L \rightarrow \infty$ $\frac{1}{R_L} \rightarrow 0$

$V_{out} = \frac{(k + \frac{1}{r_1})}{(0 + \frac{1}{r_1} + k)} V_{in} = V_{in}$

as $R_L \rightarrow \infty$, value of V_{out} will approach the value of V_{in}