

EE10

Midterm Exam

Fall 2013

Group 1

Time Limit: 1 hour and 50 minutes

Open Book, Open Notes

Calculators are allowed.

Your Name:

Solutions

Name of Person to Your Left:

Name of Person to Your Right:


1. 10

2. 10


3. 10

4. 10

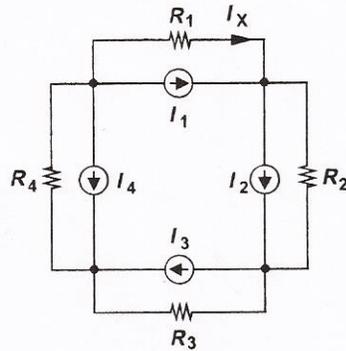1. Determine I_X in the circuit shown below.




Use superposition:

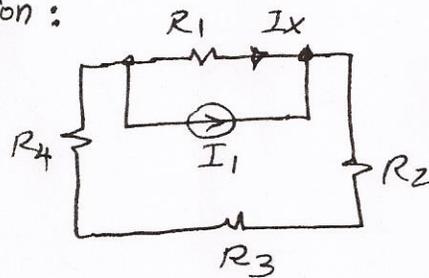

$$I_X|_{I_1} = -I_1 \frac{R_2 + R_3 + R_4}{\Sigma R}$$

$$\Sigma R = R_1 + \dots + R_4$$

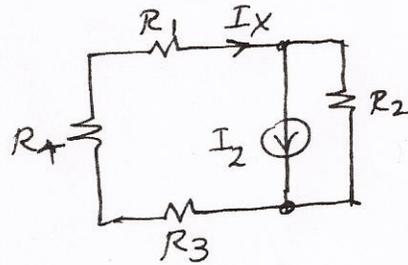


$$I_X|_{I_2} = I_2 \frac{R_2}{\Sigma R}$$

Similarly, $I_X|_{I_3} = I_3 \frac{R_3}{\Sigma R}$, $I_X|_{I_4} = -I_4 \frac{R_4}{\Sigma R}$


$$\Rightarrow I_{X, \text{tot}} = -I_1 \frac{R_2 + R_3 + R_4}{\Sigma R} + I_2 \frac{R_2}{\Sigma R} + I_3 \frac{R_3}{\Sigma R} - I_4 \frac{R_4}{\Sigma R}$$

$$= \frac{1}{\Sigma R} \left[-(R_2 + R_3 + R_4)I_1 + R_2 I_2 + R_3 I_3 - R_4 I_4 \right]$$

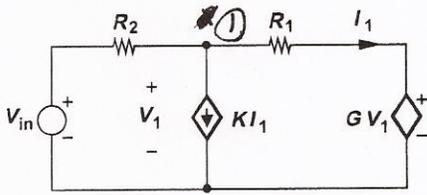2. Determine V_1 in each circuit shown below. (Your answers should not include I_1 .)



(a)

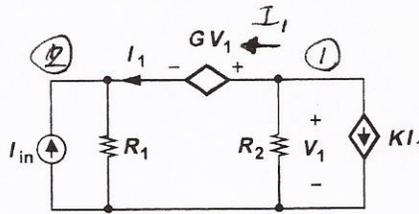

(b)

(a) KCL at ①:

$$\frac{V_1 - V_{in}}{R_2} + \frac{V_1 - GV_1}{R_1} + KI_1 = 0$$

$$I_1 = \frac{V_1 - GV_1}{R_1}$$

$$\Rightarrow \frac{V_1 - V_{in}}{R_2} + \frac{V_1 - GV_1 + K(V_1 - GV_1)}{R_1} = 0$$

$$\Rightarrow V_1 \left(\frac{1}{R_2} + \frac{(1+K)(1-G)}{R_1} \right) = \frac{V_{in}}{R_2}$$

$$\Rightarrow V_1 = \frac{V_{in}}{1 + (1+K)(1-G) \frac{R_2}{R_1}}$$

(b) KCL at ①: $\frac{V_1}{R_2} + KI_1 + I_1 = 0$

KCL at ②: Since $V_2 = V_1 - GV_1$, $\frac{V_1 - GV_1}{R_1} = I_1 + I_{in}$

$$\Rightarrow I_1 = \frac{V_1(1-G)}{R_1} - I_{in}$$

$$\Rightarrow \frac{V_1}{R_2} + (1+K) \left[\frac{V_1(1-G)}{R_1} - I_{in} \right] = 0$$

$$\Rightarrow V_1 \left[\frac{1}{R_2} + \frac{(1+K)(1-G)}{R_1} \right] = (1+K) I_{in}$$



$$\Rightarrow V_1 = \frac{(1+K) I_{in}}{\frac{1}{R_2} + \frac{(1+K)(1-G)}{R_1}}$$

3. In the circuit shown below, we wish to calculate V_{out} .

(a) Determine the Thevenin equivalent of the circuit in the dashed box. (Your answer should not include I_1 .)

(b) Use the Thevenin equivalent to find V_{out} .

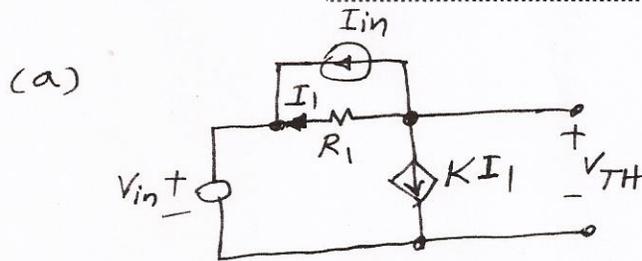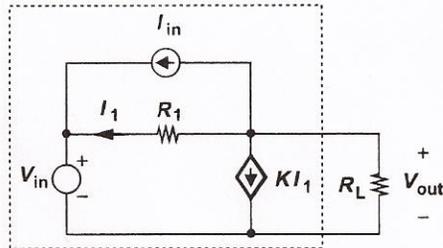(c) Check your answer for $K = 0$ and $I_{in} = 0$ and explain why it makes sense.



$$I_1 = \frac{V_{TH} - V_{in}}{R_1}$$

$$\frac{V_{TH} - V_{in}}{R_1} + I_{in} + K \frac{V_{TH} - V_{in}}{R_1} = 0$$

$$\Rightarrow V_{TH} \left(\frac{1+K}{R_1} \right) = V_{in} \frac{1+K}{R_1} - I_{in}$$

$$\Rightarrow V_{TH} = \cancel{V_{in}} V_{in} - R_1 \frac{I_{in}}{1+K}$$


For R_{TH} :



$$I_1 = \frac{V_X}{R_1}$$


$$I_X = (1+K) \frac{V_X}{R_1}$$

$$\Rightarrow R_{TH} = \frac{R_1}{1+K}$$

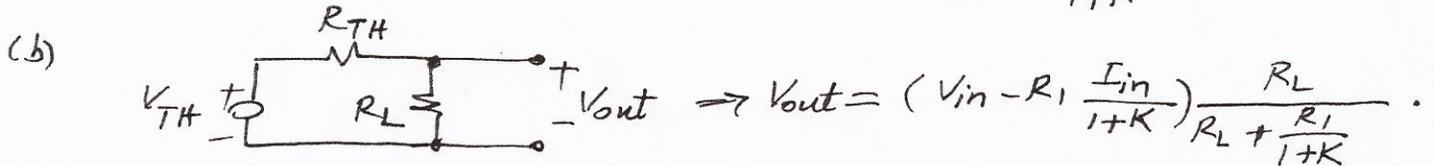

(c) If $K=0$, $I_{in}=0 \Rightarrow V_{out} = V_{in} \frac{R_L}{R_L + R_1}$: just a voltage divider.


4. The circuit shown below begins with an initial voltage of V_0 on C_1 . Determine V_{out} as a function of time. (Your answer should not include I_1 .)

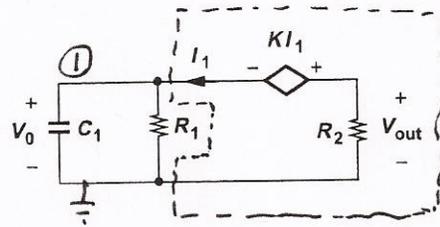

Method I:

Find the Thevenin equivalent of the circuit in the dashed box:

$$V_{TH} = 0.$$

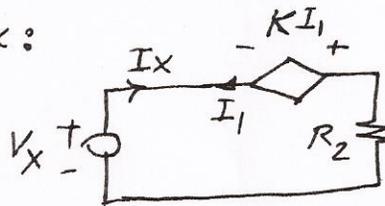

$$I_1 = -I_x \rightarrow \text{current through } R_2 = \frac{V_x + KI_1}{R_2}$$

$$= \frac{V_x - KI_x}{R_2}$$

$$= I_x$$

$$\Rightarrow \frac{V_x}{R_2} = \left(1 + \frac{K}{R_2}\right) I_x$$

$$\Rightarrow R_{TH} = R_2 + K$$


Thus, the voltage at node 1 can be expressed as:

$$V_1(t) = V_0 \exp\left(-\frac{t}{\tau}\right) \quad \tau = [R_1 \parallel (R_2 + K)] C_1$$

$$\text{We also have } \frac{V_1(t) + KI_1}{R_2} = \frac{V_{out}}{R_2} = -I_1$$


$$\Rightarrow -I_1 (R_2 + K) = V_1(t) \Rightarrow V_{out} = -I_1 R_2 = + \frac{V_1(t) R_2}{R_2 + K} = \frac{V_0 R_2 \exp\left(-\frac{t}{\tau}\right)}{R_2 + K}$$

Method II:

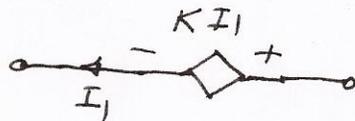

A two-terminal device whose voltage (KI_1) is proportional to its current (I_1) is a resistor:

$$R_{eq} = K$$

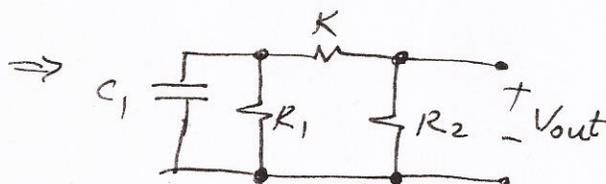

$$V_{out} = \frac{V_0 R_2}{R_2 + K} \exp\left(-\frac{t}{\tau}\right)$$

$$\tau = R_1 \parallel (K + R_2)$$