


**EE10 06W MidTerm #1**

Name \_\_\_\_\_

Last

First

1. (30 points)

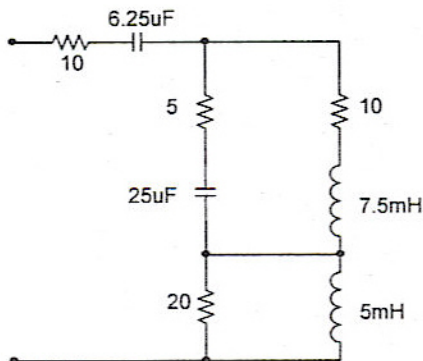

Student ID \_\_\_\_\_


Find the equivalent impedance of this network if  $\omega=4000$ .

$$X_{C_1} = \frac{1}{\omega C_1} = \frac{1}{(4e3)(6.25e-6)} = \frac{10^3}{25} = 40$$

$$X_{C_2} = \frac{1}{(4e3)(25e-6)} = \frac{10^3}{100} = 10$$

$$X_{L_1} = \omega L_1 = (4e3)(7.5e-3) = 30$$

$$X_{L_2} = (4e3)(5e-3) = 20$$

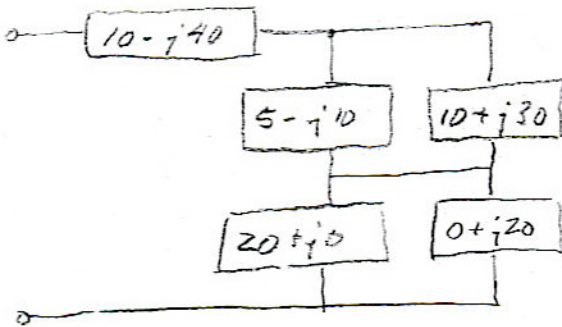


$$\frac{(5 - j10)(10 + j30)}{15 + j20} = 10 - j10$$

$$\frac{(20)(j20)}{20 + j20} = 10 + j10$$

$$Z_{eq} = 10 - j40 + 10 - j10 + 10 + j10 = 30 - j40 = 50 \angle -53.13^\circ$$

2. (15 points)

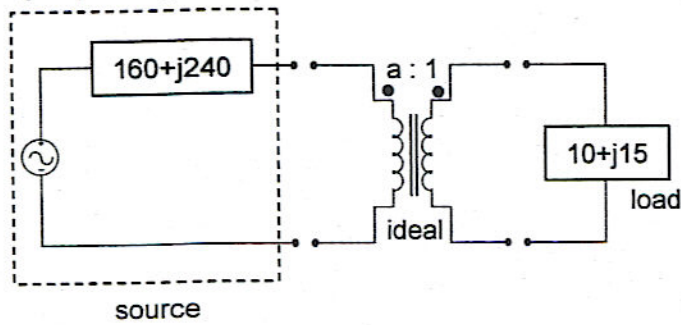

Student ID \_\_\_\_\_

The transformer is to be inserted between the source and the load with a turns ratio that makes the load impedance appear to be the same as the source impedance. Find the value of "a" necessary to make this happen. Assume that the voltages are plus at the top and the currents are clockwise.

$$\frac{V_1}{a} = \frac{V_2}{1} \text{ and } I_1 a = I_2$$

$$Z_L = \frac{V_2}{I_2} = 10 + j15$$

$$Z_S = \frac{V_1}{I_1} = 160 + j240$$


$$\frac{V_2}{I_2} = \frac{\frac{V_1}{a}}{I_1 a} = \frac{1}{a^2} \frac{V_1}{I_1}$$

$$a^2 = \frac{V_1/I_1}{V_2/I_2} = \frac{160 + j240}{10 + j15} = 16$$

$$a = 4$$

3. (40 points)

Student ID \_\_\_\_\_

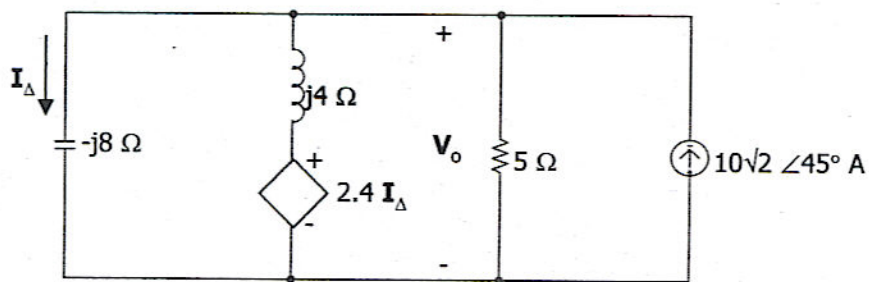

All voltages  
and currents  
are rms. Find  
 $V_o$ .

NODE-VOLTAGE METHOD

$$\frac{V_o}{-j8} + \frac{V_o - 2.4 I_{\Delta}}{j4} + \frac{V_o}{5} - (10 + j10) = 0$$

$$I_{\Delta} = \frac{V_o}{-j8}$$

$$\therefore V_o = j80$$

4. (15 points)

Student ID \_\_\_\_\_

A circuit element has voltage across it and current through it that are described by:

$$v(t) = 50 \cos(377t + 38^\circ)$$

and

$$i(t) = 10 \sin(377t + 75^\circ)$$

NOTE THE SINE FUNCTION!

Find the real power associated with that circuit element.

$$i(t) = 10 \cos(377t + 75^\circ - 90^\circ) = 10 \cos(377t - 15^\circ)$$

$$\text{By inspection, } P = \frac{V_{m} I_{m}}{2} \cos(\phi_v - \phi_i) = \frac{500}{2} \cos(38^\circ - (-15^\circ))$$

$$= 250 \cos 53^\circ = 150.45 \text{ W}$$