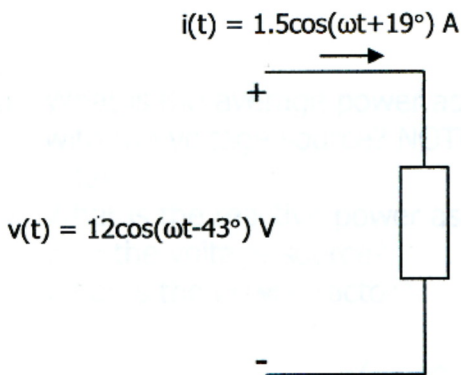


**DO NOT OPEN UNTIL
INSTRUCTED TO DO SO.**

- We will copy some graded exam papers for archival purposes!
- Put your name in the blank on EVERY page.
- Show your setup.
- Circle your answers.
- Add notes to help the graders determine your intentions.

1. (5/100)




- What is the instantaneous power associated with this circuit element?
- Is the element absorbing or providing reactive power?

$$\begin{aligned}
 a. \quad p(t) &= +v(t)i(t) = \frac{(12)(1.5)}{2} \cos(-43-19) + \frac{(12)(1.5)}{2} \cos(-43-19) \cos 2\omega t \\
 &\quad - \frac{(12)(1.5)}{2} \sin(-43-19) \sin 2\omega t \\
 &= 9 \cos(-62^\circ) + 9 \cos(-62^\circ) \cos 2\omega t - 9 \sin(-62^\circ) \sin 2\omega t \\
 p(t) &= 4.225 + 4.225 \cos 2\omega t + 7.997 \sin 2\omega t
 \end{aligned}$$

- b. ~~Absorbing~~, because ϕ is \ominus .
 Providing

2. (20/100)

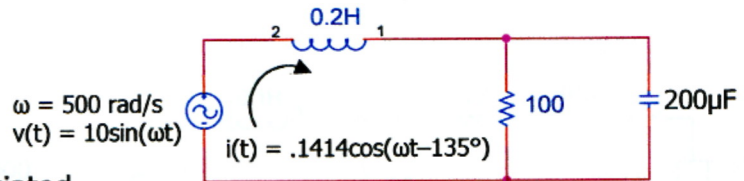

- What is the average power associated with the voltage source? NOTE the sine!
- What is the reactive power associated with the voltage source?
- What is the Power Factor?

$$v(t) = 10 \sin \omega t; \underline{V} = 10 \angle -90^\circ$$

$$a. P = -\frac{V_m I_m}{2} \cos(\phi_v - \phi_i) = -\frac{(10)(.1414)}{2} \cos(-90 - (-135)) = -0.707 \cos 45^\circ$$

$$P = -0.5 \text{ W}$$


$$b. Q = -\frac{V_m I_m}{2} \sin(\phi_v - \phi_i) = 0.707 \sin 45^\circ = 0.5 \text{ W}$$

$$c. pf = \cos(\phi_v - \phi_i) = \cos 45^\circ = 0.707$$

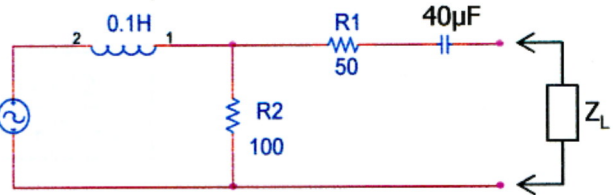3. (40/100)

Assuming that Z_L can be set to any complex value, what is the maximum power that can be delivered to Z_L ?


$\omega = 1000$
 $v_s(t) = 100\cos \omega t$



Find Theven E_{θ}

$$V_{th} = v_s(t) \frac{100}{j1000(.1) + 100} = 100 \angle 0 (.5 - j.5) = 50 - j50 = 50\sqrt{2} \angle -45^\circ$$
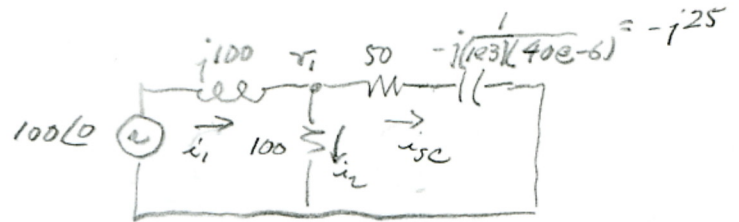
$$\frac{100 \angle 0 - v_1}{j100} = \frac{v_1}{100} + \frac{v_1}{50 - j25}$$



$$i_{sc} = \frac{v_1}{50 - j25}$$

$$\frac{100}{j100} = \frac{v_1}{j100} + \frac{v_1}{100} + \frac{v_1}{50 - j25} = v_1 (-j.01 + .01 + .016 + j.008) = v_1 (.026 - j.002)$$

$$v_1 = \frac{-j1}{.026 - j.002} = 2.941 - j38.235$$


$$i_{sc} = \frac{2.941 - j38.235}{50 - j25} = 0.353 - j0.598$$

$$Z_{th} = \frac{V_{th}}{i_{sc}} = \frac{50 - j50}{0.353 - j0.598} = 100 + j25$$

$$Z_{MPT} = 100 - j25$$

$$P_{max} = \frac{1}{8} \frac{V_{th,max}^2}{R_L} = \frac{1}{8} \frac{(50\sqrt{2})^2}{100} = \frac{5000}{800} = 6.25 \text{ W}$$

4. (10/100)

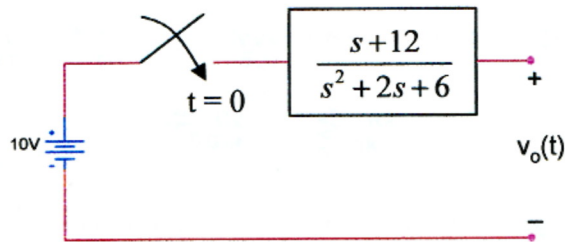


The output voltage in the s-domain $V_o(s)$ is described by the following expression:

$$V_o(s) = \left(\frac{10}{s}\right) \left(\frac{s+12}{s^2+2s+6}\right)$$

Find the final value of $v_o(t)$.

$$FV = \lim_{s \rightarrow 0} s V_o(s) = \lim_{s \rightarrow 0} s \left(\frac{10}{s}\right) \left(\frac{s+12}{s^2+2s+6}\right) = 20$$

5. (15/100)

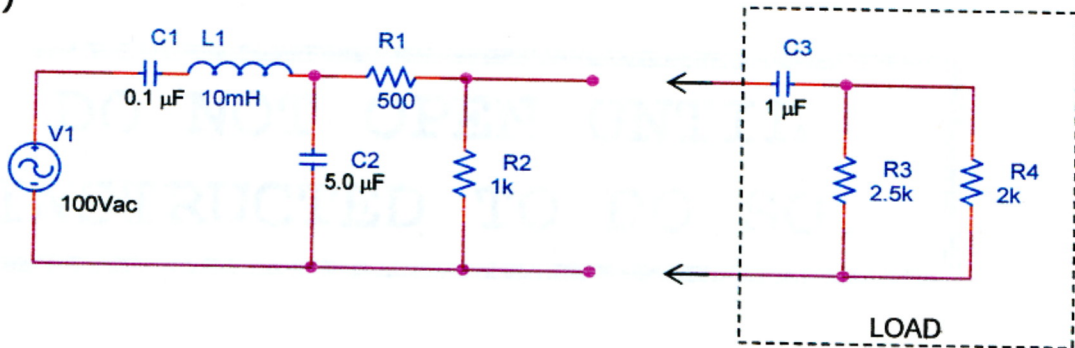

Assume that the designer wishes to manipulate the components in the load to maximize the power transfer to the load. Does the assumption in the text about the independence of R_L and X_L hold for this load? Explain how you arrived at your answer.

The assumption holds because the load can be

represented by $\frac{C}{1\mu F}$ in series with $R_3 \parallel R_4 = 1.11 K \Omega$, so $Z_C = (R_3 \parallel R_4) - i \frac{1}{\omega C}$.

If R_3 or R_4 changes, it does not affect the ^{load} reactance. If C changes, it does not affect the load resistance.