

Name: _____


UID: _____

Total of 3 questions


- **Open notes/book, but no internet, ccle, ...**
- **No calculator, MATLAB, ...**
- **Unless specifically stated, any method of analysis is acceptable.**
- **Submit your PDF at or before 2:30PM to Gradescope as <Last_First_UID>**

P1 (45)	
P2 (30)	
P3 (25)	
Total (100)	

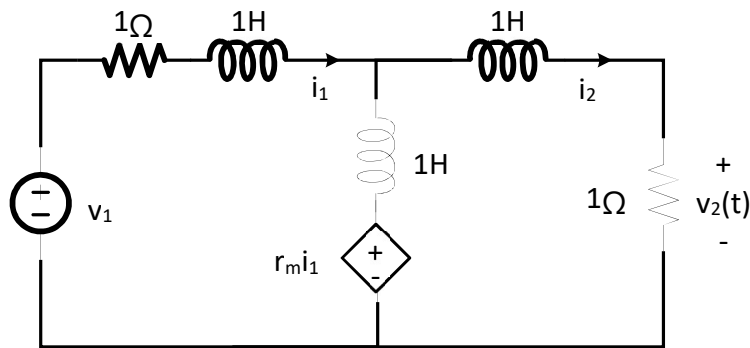1. Shown below is a zero-state circuit. $r_{mm} = 5\Omega$.
 - a. (5) Explain physically the number of natural frequencies of the circuit.
 - b. (10) Performing a mesh analysis, set up the integro-differential equations describing the circuit zero-input response (take i_1 and i_2 as the variables).
 - c. (8) Find the circuit natural frequencies.
 - d. (7) Calculate the network function, $H(s) = \frac{V_2(s)}{V_1(s)}$.
 - e. (5) Find the location of the circuit poles and zeros.
 - f. (10) Determine the impulse response of the circuit ($v_2(t)$, for $v_1(t) = \delta(t)$).



1) zero-state $r_m = 5 \Omega$

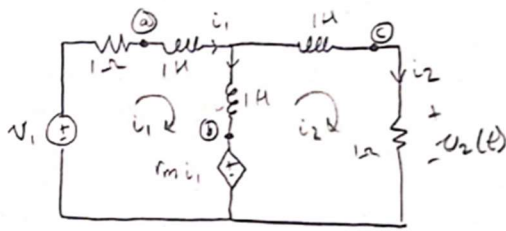

$$-v_1 + i_1 + \frac{di_1}{dt} + \frac{d(i_1 - i_2)}{dt} + r_m i_1 = 0$$

$$\frac{d i_2}{dt} + i_2 - r_m i_1 - \frac{d(i_1 - i_2)}{dt} = 0$$

for zero-input, $v_1 = 0$

$$\begin{cases} 6i_1 + 2i_1' - i_2' = 0 \\ -5i_1 - i_1' + i_2 + 2i_2' = 0 \end{cases}$$

$$\begin{bmatrix} 6+2s & -s \\ -5-s & 1+2s \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \end{bmatrix}$$

$$V_2 = I_2$$

$s = \text{line}$
 $s' = \text{letter}$

$$V_2 = \frac{\begin{vmatrix} 6+2s & V_1 \\ -5-s & 0 \end{vmatrix}}{\begin{vmatrix} 6+2s & -s \\ -5-s & 1+2s \end{vmatrix}} = \frac{V_1(s+5)}{(6+2s)(1+2s) - s(5+s)}$$


$$\frac{V_2}{V_1} = \frac{s+5}{4s^2 + 6 + 4s - 5s - s^2} = \frac{s+5}{3s^2 + 9s + 6} = \frac{s+5}{3(s^2 + 3s + 2)}$$

$$\frac{V_2}{V_1} = \frac{s+5}{3(s+1)(s+2)} = H(s)$$

$$\begin{cases} \text{poles at } s = -1, -2 \\ \text{zeros at } s = -5 \end{cases}$$

for natural frequencies: independent sources $\rightarrow 0$
determinant for denominator = $(6+2s)(1+2s) + s(-5-s)$
as solved above $= 3(s+1)(s+2)$
natural frequencies = $\{-1, -2\}$

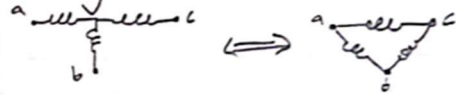2) There will be 2 natural frequencies. While there are 3 energy-storing elements in the circuit, there is an inductive loop. Using a delta to Y conversion,



So, there will be one fewer natural frequencies than energy-storing elements.
2 natural frequencies

$$(1) \quad u_2(t) = ? \quad \text{for } u_1(t) = \delta(t) \Leftrightarrow 1$$

$$\frac{V_2}{1} = \frac{1}{3} \frac{(s+5)}{(s+1)(s+2)} = \frac{k_1}{s+1} + \frac{k_2}{s+2}$$


$$k_1 = \frac{1}{3} \frac{(s+5)}{(s+2)} \Big|_{s=-1} = \frac{1}{3} \frac{4}{1} = \frac{4}{3}$$

$$k_2 = \frac{1}{3} \frac{(s+5)}{(s+1)} \Big|_{s=-2} = \frac{1}{3} \frac{3}{-1} = -1$$


$$V_2 = \frac{4/3}{s+1} + \frac{-1}{s+2}$$

$$\textcircled{f} \quad u_2(t) = \left(\frac{4}{3} e^{-t} - e^{-2t} \right) u(t) \quad \text{V}$$

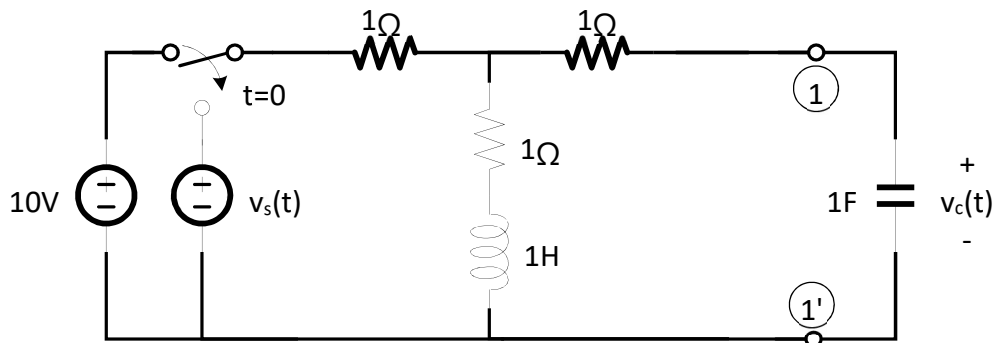
2. The network shown below has reached steady state for $tt < 0$. At $tt = 0$, the switch is flipped from position a to b. For $vv_{ss}(tt) = ee^{-tt}uu(tt)$,
- (20) Find the Norton equivalent of the circuit (in ss domain) at the left side of nodes 1-1'
 - (10) Calculate the capacitor voltage $vv_{cc}(tt)$ for $tt > 0$ using the Norton circuit in part a.



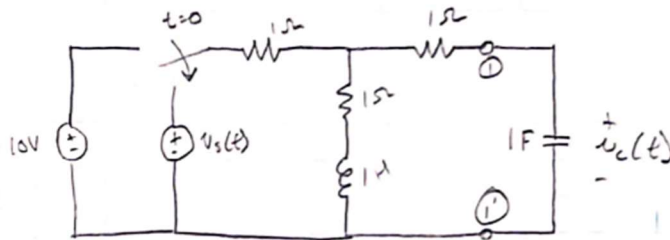2) steady state for $t < 0$ $v_s(t) = e^{-t}u(t) \Leftrightarrow \frac{1}{s+1}$




$t < 0$

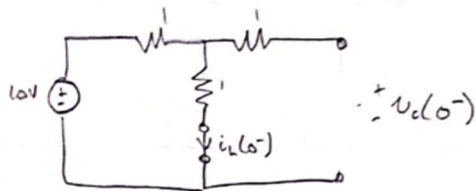


$$i_c(0^-) = \frac{10V}{2\Omega} = 5A$$

$$v_c(0^-) = 5A \cdot 1\Omega = 5V$$


$t \geq 0$

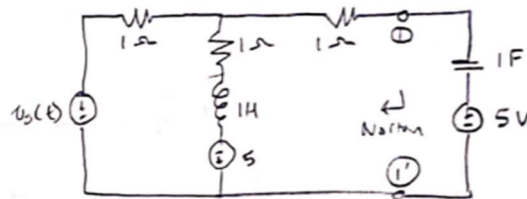

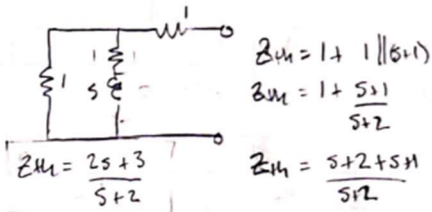$R_{th} \rightarrow$ all ind sources set to 0



Norton equivalent circuit:

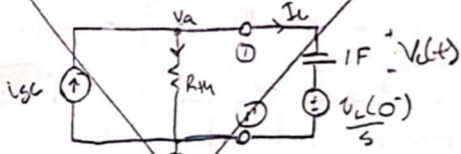

$V_a = V_c + 5$
 $i_c = C \frac{dV_c}{dt} \Rightarrow s V_c - 0$


$\frac{5s+6}{s+1} i_{sc} = \frac{V_a+5}{2} + s V_c$

$10(s+1) = V_c + 5 + 2s V_c - 10$

$V_c(2s+1) = 10s + 10 + 5$

$V_c = \frac{10s+15}{2s+1} = \frac{5s+15/2}{s+1/2}$

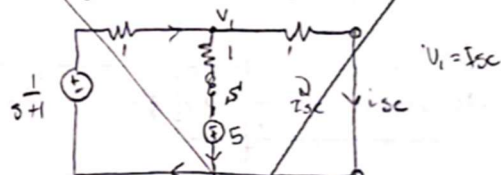$i_{sc} \rightarrow$ short output terminals



$V_1 = (s+1)5$

$V_1 = i_{sc} \cdot 1$

$i_{sc} = 5(s+1)$

$\frac{1}{s+1} - \frac{5}{s}(s+1) = \frac{5}{s} + i_{sc}$

$i_{sc} = \frac{1}{s+1} - \frac{5(s+1)}{s} - \frac{5}{s} = \frac{s - 5(s+1)^2 - 5s - 5}{s(s+1)}$

$i_{sc} = \frac{-4s - 5 - 5s^2 - 10s - 5}{s(s+1)}$

$i_{sc} = \frac{-5s^2 - 14s - 10}{s(s+1)}$


See next page!

$(2) \frac{V_{s+1} - I_{sc}}{1} = \frac{I_{sc} - 0}{1} + \frac{I_{sc} + 5}{s+1}$

$1 - (s+1)I_{sc} = (s+1)I_{sc} + I_{sc} + 5$


$-4 = (2s+3)I_{sc}$

$I_{sc} = \frac{-4}{2s+3}$

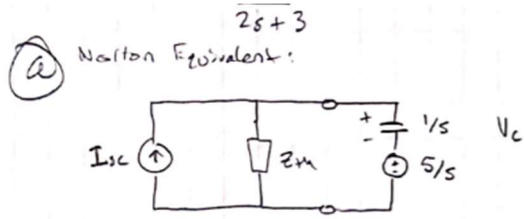

$$I_{sc} = \frac{-4}{2s+3}$$

$$Z_n = \frac{2s+3}{s+2}$$

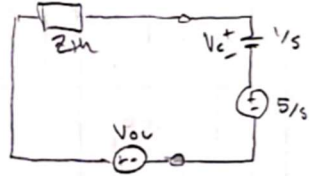

$$V_{oc} = I_{sc} Z_n$$

$$V_c = \frac{1/s}{1/s + Z_n} (V_{oc} - 5/s)$$

$$V_c = \frac{1/s}{\left(\frac{1}{s} + \frac{2s+3}{s+2}\right)} \left(\frac{-4}{2s+3} \cdot \frac{(2s+3)}{(s+2)} - \frac{5}{s} \right) = \frac{1/s}{\left(\frac{s+2+2s^2+3s}{s(s+2)}\right)} \left(\frac{-4s - 5s - 10}{(s+2) \cdot s} \right)$$

$$V_c = \frac{1}{s} \cdot \frac{s(s+2)}{2s^2+4s+2} \cdot \frac{-9s-10}{s(s+2)} = \frac{-9s-10}{2s(s^2+2s+1)} = \frac{-9/2s-5}{s(s+1)^2}$$

$$V_c = \frac{k_1}{s} + \frac{k_2}{(s+1)^2} + \frac{k_3}{s+1}$$

$$k_1 = \frac{-5}{1} \quad k_2 = \frac{9/2 - 5}{-1} = \frac{-1/2 - 5}{-1} = 5 + 1/2 = 11/2$$

$$V_c = \frac{-5}{s} + \frac{11/2}{(s+1)^2} + \frac{5}{s+1}$$

for 1st power terms,
 $2k_1s + k_2s + k_3 = -9/2s$
 $-10 + 11/2 + k_3 = -9/2$


$$k_3 = \frac{-9}{2} + \frac{11}{2} - \frac{1}{2} = \frac{1}{2} = 0.5$$

(b)
$$v_c(t) = -5u(t) + \left(5e^{-t} + \frac{1}{2}te^{-t}\right)u(t)$$


3. Shown below, the LTI two-port N with impedance matrix $ZZ = \begin{bmatrix} \frac{s+2}{s+1} & \frac{1}{s+1} \\ \frac{1}{s+1} & \frac{s+2}{s+1} \end{bmatrix}$ is

terminated with a source and 1Ω resistors as shown below.

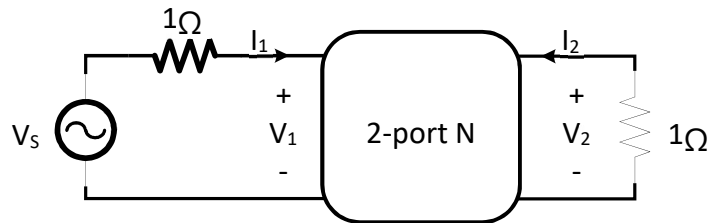- (15) Calculate the voltage transfer ratio, V_2/V_1 (V_2/V_1 in the s -domain).
- (10) Find the step response of the circuit ($v_2(t)$ for $t > 0$ with $v_{s1}(t) = u(t)$).



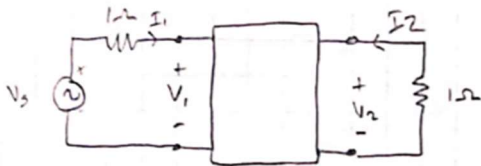3) $Z = \begin{bmatrix} \frac{s+2}{s+1} & \frac{1}{s+1} \\ \frac{1}{s+1} & \frac{s+2}{s+1} \end{bmatrix}$ LTI 2port



$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

WL

$$\begin{aligned} -V_3 + I_1 + V_2 &= 0 \\ -V_2 - I_2 &= 0 \end{aligned}$$

$$\begin{aligned} V_1 &= V_3 - I_1 \\ V_2 &= -I_2 \end{aligned}$$

$$\begin{aligned} V_3 - I_1 &= Z_{11} I_1 + Z_{12} (-V_2) & (-Z_{11} - 1) I_1 &= -V_3 - Z_{12} V_2 \\ V_2 &= Z_{21} I_1 + Z_{22} (-V_2) & I_1 &= \frac{V_3 + Z_{12} V_2}{Z_{11} + 1} \end{aligned}$$

$$V_2 = \frac{Z_{21} (V_3 + Z_{12} V_2)}{Z_{11} + 1} - V_2 Z_{22}$$

$$V_2 (1 + Z_{22}) = \left(\frac{Z_{21}}{Z_{11} + 1} \right) V_3 + \left(\frac{Z_{21} Z_{12}}{Z_{11} + 1} \right) V_2$$

$$V_2 \left(1 + Z_{22} - \frac{Z_{21} Z_{12}}{Z_{11} + 1} \right) = \left(\frac{Z_{21}}{Z_{11} + 1} \right) V_3$$

$$\frac{V_2}{V_3} = \frac{Z_{21}}{Z_{11} + 1} \left(\frac{Z_{11} + 1 + Z_{22} Z_{11} + Z_{22} - Z_{21} Z_{12}}{Z_{11} + 1} \right)^{-1}$$

$$\frac{V_2}{V_3} = \frac{Z_{21}}{Z_{22} Z_{11} - Z_{21} Z_{12} + Z_{11} + Z_{22} + 1} = \frac{1/s+1}{\frac{(s+2)^2}{(s+1)^2} - \frac{1}{(s+1)^2} + \frac{s+2}{s+1} + \frac{s+2}{s+1} + 1}$$

$$\frac{V_2}{V_3} = \frac{s+1}{(s+2)^2 - 1 + 2(s+2)(s+1) + (s+1)^2} = \frac{s+1}{s^2 + 4s + 4 - 1 + 2s^2 + 6s + 4}$$

$$\frac{V_2}{V_3} = \frac{s+1}{4s^2 + 12s + 8} = \frac{s+1}{4(s^2 + 3s + 2)} = \frac{s+1}{4(s+1)(s+2)}$$

(a)
$$\frac{V_2(s)}{V_3} = \frac{1}{4(s+2)}$$

(3) $u_2(t) = ? \quad u_3(t) = u(t) \Leftrightarrow 1/s$

$$V_2(s) = V_3 \cdot 1 = \frac{1/4}{s(s+2)} = \frac{k_1}{s} + \frac{k_2}{s+2} = \frac{1/8}{s} + \frac{-1/8}{s+2}$$

$$k_1 = \frac{1/4}{s+2} \Big|_{s=0} = \frac{1/4}{2} = \frac{1}{8}$$

$$k_2 = \frac{1/4}{s} \Big|_{s=-2} = \frac{-1}{8}$$

(b)
$$u_2(s) = 1/8 u(t) - 1/8 e^{-2t} u(t) \quad \checkmark$$

