
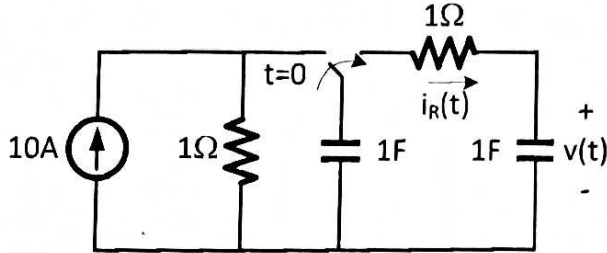
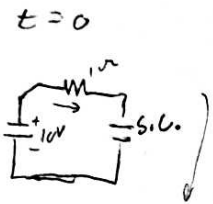


Total of 3 questions, 100 minutes.

<b>P1 (30)</b>	30
<b>P2 (40)</b>	28
<b>P3 (30)</b>	30
<b>Total (100)</b>	

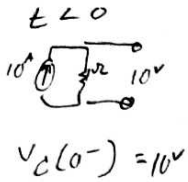
1. In the linear circuit below, the switch has been in the left position for a long time, and is flipped from left to right at  $t = 0$ . Assume  $v(0^-) = 0$ .

- Find the resistor current at  $t = 0^+$ :  $i_R(0^+)$ .
- Calculate the capacitor voltage  $v(t)$  for  $t > 0$ . Use your favorite method.
- What is the total energy stored in the two capacitors at  $t = 0^+$ ?
- What is the total energy stored in the two capacitors at  $t = \infty$ ?



(a)  $i_R(0^+) = \frac{10V}{1\Omega} = 10A$

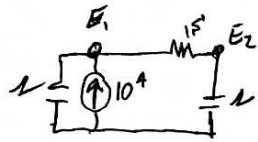(b) Laplace:  
 $i = C \frac{dv}{dt}$   
 $i = C[2 - v(0^-)]$



Node Voltage: solve  $E_2$

$$\begin{cases} 2E_1 - 10 + \frac{E_1 - E_2}{1} = 0 \\ 2E_2 + \frac{E_2 - E_1}{1} = 0 \rightarrow E_1 = (2+1)E_2 \end{cases}$$

solving:

$$4(2+1)E_2 + (2+1)E_2 - E_2 = 10$$

$$(2^2 + 2 + 2 + 1 - 1)E_2 = 10$$

$$(2+2)2E_2 = 10$$

$$E_2 = \frac{10}{(2+2)(2)} = \frac{K_1}{2+2} + \frac{K_2}{2}$$

$$e_2(t) = v(t) = (-5e^{-2t} + 5)u(t) \text{ (volts)}$$

cover up:

$$s = -2 \rightarrow K_1 = -5$$


$$s = 0 \rightarrow K_2 = 5$$

final value thm

$$\lim_{s \rightarrow 0} s E_2(s) = \lim_{s \rightarrow 0} \frac{10s}{2^2 + 2s} \rightarrow \frac{10}{2s+2} = 5$$

(c)  $w = \frac{1}{2} C V^2 \rightarrow \frac{1}{2}(1)(10^2) + \frac{1}{2}(1)(0^2) = 50J \text{ at } 0^+$

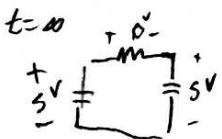(d)  $v(\infty) = 5$  for both  $C_1, C_2$ .



$$w = \frac{1}{2}(1)(25) + \frac{1}{2}(1)(25) = 25J \text{ at } t = \infty$$

2. In the linear time-invariant circuit shown below,  $r_m = 1\Omega$ ,  $v_C(0^-) = 1V$ , and  $i_L(0^-) = -1A$ .

a. Using **mesh analysis**, write the integro-differential equations of the circuit. You do not need to solve them.

b. Find the necessary initial conditions for  $i(t)$ :  $i(0^-)$  and  $\frac{d}{dt}i(0^-)$ .


c. If the circuit is already in **sinusoidal steady state**, with  $v_s(t) = 5\cos t$ , find the current  $i(t)$ . You can leave the phase of  $i(t)$  as an  $\tan^{-1}$  expression.

(a) DE'S

$$v_s(t) = 1 \cdot i_1 + \frac{1}{1F} \int_0^t i_1 dt + v_C(0^-) + (i_1 - i_2) \cdot 1$$


$$0 = (i_2 - i_1) \cdot 1 + 1 \cdot i_2' + 1 \cdot i_2 + 1 \cdot (i_1 - i_2)$$
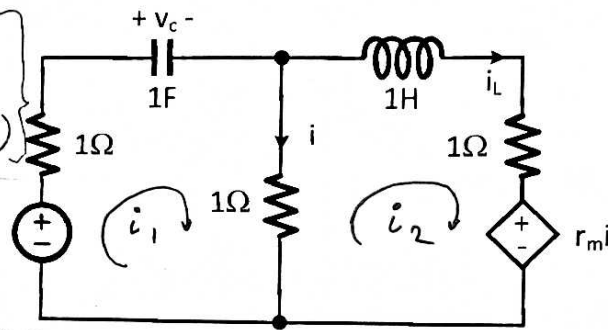
$$\begin{bmatrix} 2 + D^{-1} & -1 \\ 0 & 1 + D \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_s(t) - 1 \\ 0 \end{bmatrix}$$



(12)

(b) initial conditions: at  $t=0^-$

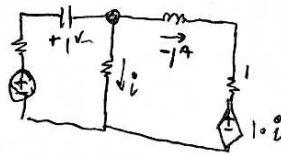

KVL left:


$$v_s^0 = i_1 + 1 + \dot{L} \Rightarrow 0 = -1 + 2\dot{i}$$

KCL top:  $i_1 = (-1) + i$

$$\dot{i}(0^-) = 0^+$$

$$\dot{i}'(0^-) = -1/5 \rightarrow \text{work (on next page)}$$

(these would help solve DE in part (a))

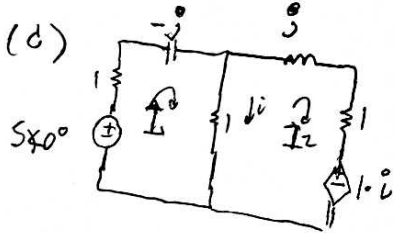

mesh:

$$s = I_1(1-j) + 1 \cdot (I_1 - I_2)$$

$$0 = I_2(1+j) + 1(I_1 - I_2) + (I_2 - I_1) \cdot 1$$

$$\Rightarrow I_2 = 0$$

$$\Rightarrow s = I_1(2-j)$$

$$I_1 = \frac{s}{2-j} \cdot \frac{2+j}{2+j} = \frac{s(2+j)}{5}$$

$$I_1 = \sqrt{5} \angle \tan^{-1}(1/2)$$

$$I = I_1 \angle 0^\circ$$

$$i(t) = \sqrt{5} \cos(t + \tan^{-1}(1/2))$$

(in SS) Amps

(10)

3. The network shown is in the steady state with switch closed. The switch opens at  $t = 0$ .  $v_s(t) = \delta(t)$ .

a. Find the inductor current  $i(t)$  for  $t > 0$  by directly solving the **time-domain** differential equation.

(a)

Derive ODE:

Left KVL:

$$v_s(t) = 1 \cdot i + \frac{1}{1F} \int_{-\infty}^{t} i + v_c(0^-) + 1 \cdot i' + 1 \cdot i$$

$$\delta(t) = 2i + \int i + i' + v_c$$

$$\delta'(t) = i'' + 2i' + i$$



$$\int_{-\infty}^t \delta(t) dt \rightarrow \delta(t) = i'(t) - i'(0^-) + 2i(t) - 2i(0^-) + \int_{-\infty}^t \delta(t) dt$$

$$\text{at } t=0^+ \rightarrow 0 = i'(0^+) + 2i(0^+)$$

$$\int_{-\infty}^t \delta(t) dt \rightarrow \int \delta(t) dt = i(t) = 1 \text{ (at } 0^+)$$

conditions
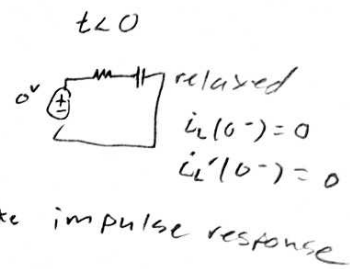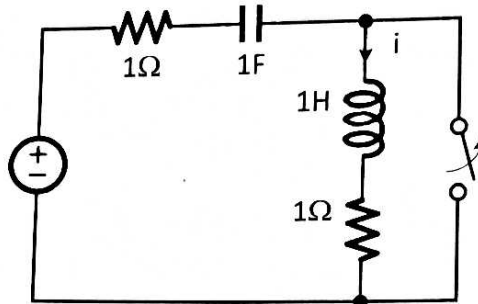
$$\left. \begin{aligned} i(0^+) &= 1 \text{ A} \\ i'(0^+) &= -2 \text{ A/s} \end{aligned} \right\}$$



Solving homogeneous

$$i'' + 2i' + i = 0$$

$$(s+1)^2 = 0$$

$\rightarrow s = -1$  repeated  
(critical damping)

$$i(t) = k_1 e^{-t} + k_2 t e^{-t}$$

$$i(0^+) = k_1 = 1$$


$$i'(0^+) = -k_1 e^{(0)} - k_2 t e^{-t} + k_2 e^{-t}$$

$$-2 = -1 + k_2 \Rightarrow k_2 = -1$$

$$i(t) = (e^{-t} - t e^{-t}) u(t)$$

(Amps)

(b)  
Redo using Laplace

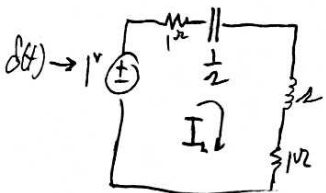

$$1 = (2 + \frac{1}{s} + 1) I_L$$

$$2 = (2s + 2s + 1) I_L$$

$$\frac{2}{2s^2 + 2s + 1} = I_L = \frac{A}{(s+1)} + \frac{B}{(s+1)^2}$$

$$I_L = \frac{1}{s+1} - \frac{1}{(s+1)^2}$$

$$\xrightarrow{\mathcal{L}^{-1}} i_L(t) = (e^{-t} - t e^{-t}) u(t)$$

(Amps)