

Name: \_\_\_\_\_

UID: \_\_\_\_\_


Total of 2 questions, 120 minutes (including scan/upload).

<b>P1 (40)</b>	
<b>P2 (60)</b>	
<b>Total (100)</b>	

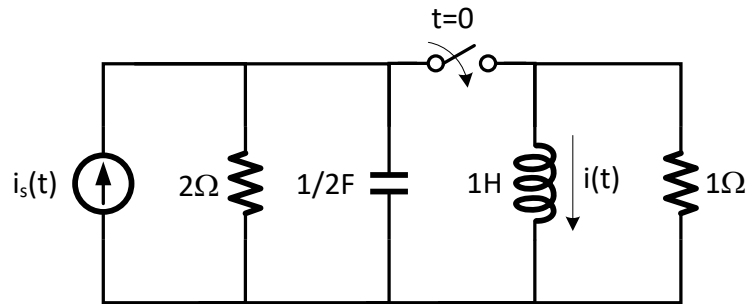1. The circuit shown is in the steady state with switch open. The switch closes at  $t = 0$ .

$$i_s(t) = \delta(t).$$

- Find the inductor current  $i(t)$  for  $t \geq 0$  by directly solving the time-domain differential equation.
- Redo part a using Laplace transform.





2. In the linear time-invariant circuit shown below,  $g_m = 1\text{S}$ ,  $v_c(0^-) = 1\text{V}$ , and  $i_L(0^-) = -1\text{A}$ . Assume  $i_s(t)$  is bounded, and is enforced at  $t = 0$ .
- Using node voltage analysis, write the integro-differential equations of the circuit. You do not need to solve them.
  - Indicate the necessary initial conditions for  $v_c(t)$  ( $v_c(0^-)$  and  $\frac{d}{dt}v_c(0^-)$ ).
  - If the circuit is in sinusoidal steady state, with  $i_s(t) = (2\cos t)u(t)$ , find the capacitor voltage,  $v_c(t)$ .

