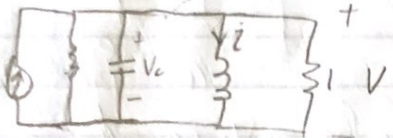


1110 Midterm Anthony Zhang 804750673

1. a)

$i_s(t) = \delta(t)$ $z(t) = \frac{1}{L} \int v dt$ $v(0^-) = v_c(0^-) = 0$ $i_L(0^-) = 0$



$$i_s(t) = \frac{1}{2}V + \frac{1}{2}\frac{dv}{dt} + \int v dt + V$$

$$\delta(t) = \frac{3}{2}V + \frac{1}{2}\frac{dv}{dt} + \int_0^{\infty} v dt$$

$$\delta(t) = \frac{3}{2}V + \frac{1}{2}V' + V$$

$$2\delta'(t) = V'' + 3V' + 2V$$

$s^2 + 3s + 2 = (s+2)(s+1)$ $s = -2, -1$

$V(t) = k_1 e^{-2t} + k_2 e^{-t}$

$$2 \int_0^{\infty} \delta(t) dt = \int_0^{\infty} 3V(t) dt + \int_0^{\infty} \frac{dV(t)}{dt} dt + \int_0^{\infty} V(t) dt$$

$Z = V(0^+)$

$$2\delta(0^+) = 3V(0^+) + V'(0^+) + \int_0^{\infty} V dt$$

initial conditions: $V(0^+) = 2V$, $V'(0^+) = -6 \frac{V}{s}$

$$0 = 6 + V'(0^+)$$


$\Rightarrow V(0^+) = k_1 + k_2 = 2$ $0 + 0 - k_1 = -4 \Rightarrow k_1 = 4$

$V'(0^+) = -2k_1 + k_2 = -6$ $k_2 = -2$

$V(t) = 4e^{-2t} - 2e^{-t}$ $i(t) = \frac{1}{L} \int (4e^{-2t} - 2e^{-t}) dt$

$$= (-2e^{-2t} + 2e^{-t}) u(t)$$

b)

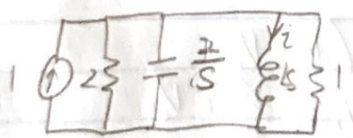

$1 = \frac{V}{2} + \frac{1}{2}V + \frac{V}{s} + V$

$1 = \frac{3}{2}V + \frac{1}{2}V + \frac{2V}{s}$

$2 = 3V + V + \frac{2V}{s}$

$2s = 3sV + s^2V + 2V = (s^2 + 3s + 2)V$

$V = \frac{2s}{s^2 + 3s + 2} = \frac{A}{s+2} + \frac{B}{s+1}$ $A = \frac{2s}{s+1} \Big|_{s=-2} = \frac{-4}{-1} = 4$

A+B=0

$= \frac{4}{s+2} - \frac{2}{s+1}$


$B = \frac{2s}{s+2} \Big|_{s=-1} = \frac{-2}{1} = -2$

$V(t) = (4e^{-2t} - 2e^{-t}) u(t)$

$z(t) = \frac{1}{L} \int V(t) dt$

$= (-2e^{-2t} + 2e^{-t}) u(t)$

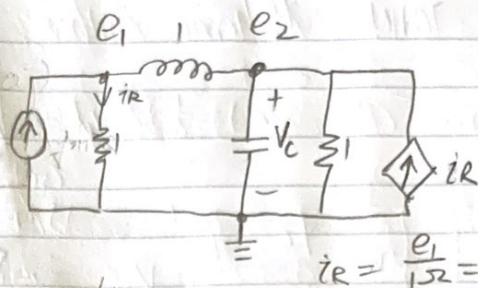2. a) e_1 $e_2 = V_c$ } node voltages
 $i_L(0^-) = -1A$ $V_c(0^-) = 1V$



$$i_s(t) = e_1 + \int_0^t (e_1 - e_2) dt + i_L(0^-)$$

$$\int_0^t (e_1 - e_2) dt + i_L(0^-) + e_1 = \frac{de_2}{dt} + e_2 \Rightarrow \int_0^t (e_1 - e_2) dt + e_1 - \frac{de_2}{dt} - e_2 = -i_L(0^-)$$

$$\begin{bmatrix} 1 + D^- & -D^- \\ 1 + D^- & -1 + D^- - D \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} i_s(t) + (1) \\ 1 \end{bmatrix}$$

b) $V_c(0^-) = 1V$ given

$$V_c = e_2 \rightarrow 0$$

$$\int_0^0 (e_1 - e_2) dt + e_1(0^-) - V_c'(0^-) - V_c(0^-) = 1 \Rightarrow V_c'(0^-) = 1 - e_1(0^-) + V_c(0^-)$$


$$i_s(0^-) = e_1(0^-) + \int_0^0 (e_1 - e_2) dt + i_L(0^-)$$

$$i_s(0^-) = 0 \quad i_L(0^-) = -1$$

$$\Rightarrow e_1(0^-) = 1$$

$$V_c'(0^-) = 1 - 1 + 1 = 1$$

$$dV_c/dt = 1 \text{ V/s}$$

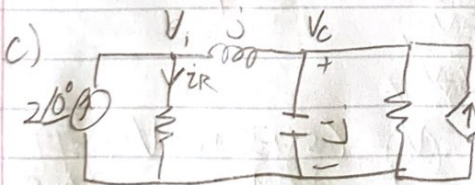

$$\omega = 1$$

$$L \Rightarrow j$$

$$C \Rightarrow \frac{1}{j} = -j$$

$$\textcircled{1} 2 = V_1 + \frac{1}{j} (V_1 - V_c)$$

$$\textcircled{2} (V_1 - V_c) \frac{1}{j} + V_1 = \frac{V_c}{j} + V_c$$

multiply by j

$$\textcircled{1} 2j = V_1 j + V_1 - V_c$$

$$\textcircled{2} -V_c + V_c j = V_1 j + V_1 - V_c$$

$$\textcircled{1} - \textcircled{2} \Rightarrow 2j + V_c - V_c j = 0$$

$$2j = V_c j - V_c$$

$$2j = j V_c (j - 1)$$

$$V_c(j\omega) = \frac{2j}{j-1} \frac{(j+1)}{(j+1)} = \frac{-2+2j}{-2} = 1-j$$

$$|V_c(j\omega)| = \sqrt{1+1} = \sqrt{2}$$

$$\angle V_c = \tan^{-1}(-1) = -45^\circ$$

$$= \sqrt{2} \angle -45^\circ \quad \tan^{-1}(-1)$$

$$\Rightarrow V_c(t) = \sqrt{2} \cos(t - 45^\circ) \text{ V in sss}$$