


40 / 40

Name: [REDACTED]  
Student ID: [REDACTED]


Quiz # 2

In the circuit below, a generator consisting of voltage source  $V_S$  and impedance  $Z_S$  is connected to a load  $Z_L$  through a mutual inductance as shown. Assume  $V_S = 120 \angle 0 \text{ V}_{\text{rms}}$ ,  $Z_S = 10 + j10$  and  $Z_L = R + j5$ , where  $R = 20$  minus the LAST DIGIT of your STUDENT ID. For example, if your ID is xxx-xxx-xx4, then  $R$  is 16 ohms.

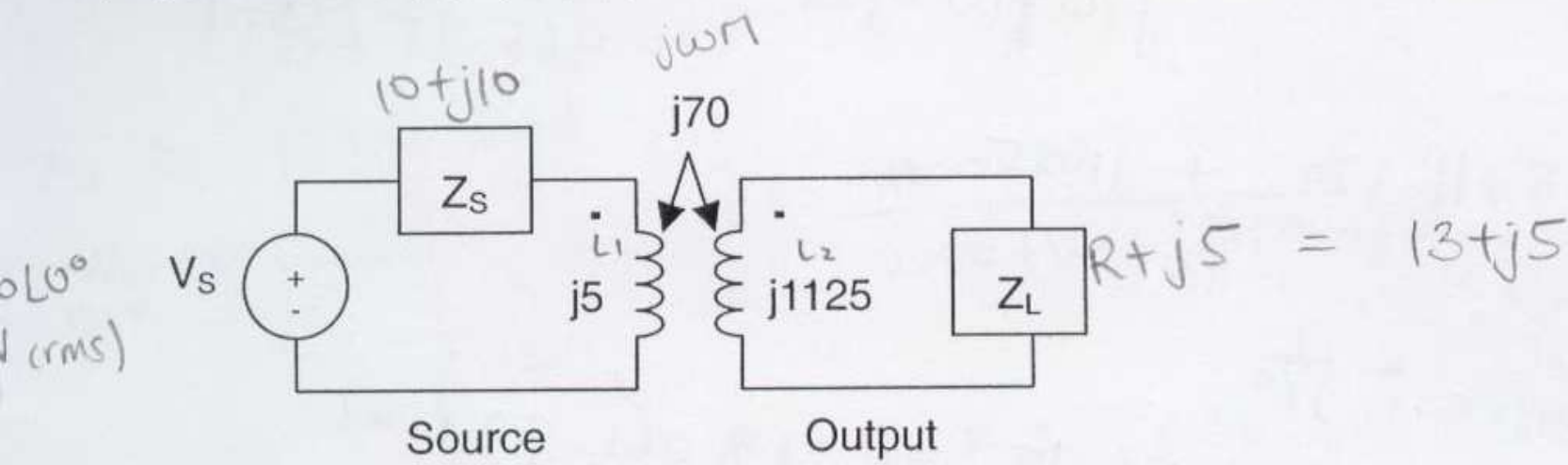- (a) Find the resistance  $R$  (this is to see if you have read the instructions). (2 pt.)
- (b) Find the coefficient of coupling  $k$  for the mutual inductance. (4 pts.)
- (c) If the inductors differ only in the number of turns in their windings, find the number of turns  $N_2$  in the output inductor if the number of turns in the input inductor  $N_1 = 10$ . (4 pts.)
- (d) Find the Thevenin equivalent circuit seen by the load. (5 pts.)
- (e) Find the RMS current, complex power, and power factor delivered to the load. (10 pts.)
- (f) Repeat (d) and (e) if the pair of inductors is replaced by an ideal transformer with the same turns ratio  $N_1:N_2$  calculated in (c). (15 pts.)



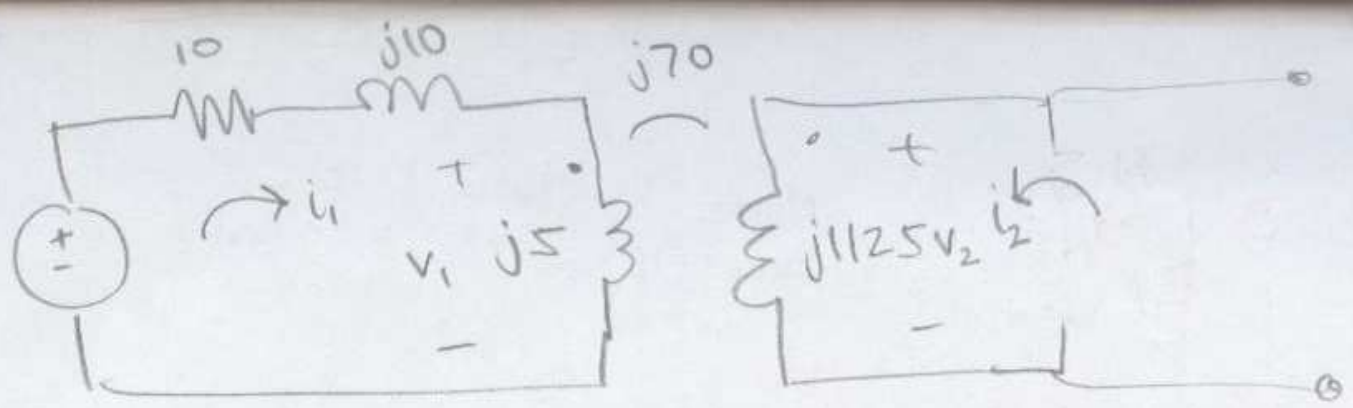$R = 13 \Omega$   
 $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{70}{\sqrt{5 \cdot 1125}} = 0.93$   
 $L_1 = \mu N_1^2$   
 $L_2 = \mu N_2^2$   
 $\mu = \frac{L_2}{N_2^2}$   
 $N_2^2 = \frac{L_2}{L_1} N_1^2 = \frac{\omega L_2}{\omega L_1} N_1^2 = \frac{1125}{5} (100) = 22500$   
 $N_2 = 150 \text{ # turns}$




$$Z_{th} R_n$$

$$V_{th}$$

$$L_2 = 0$$


$$V_2 = V_{th}$$

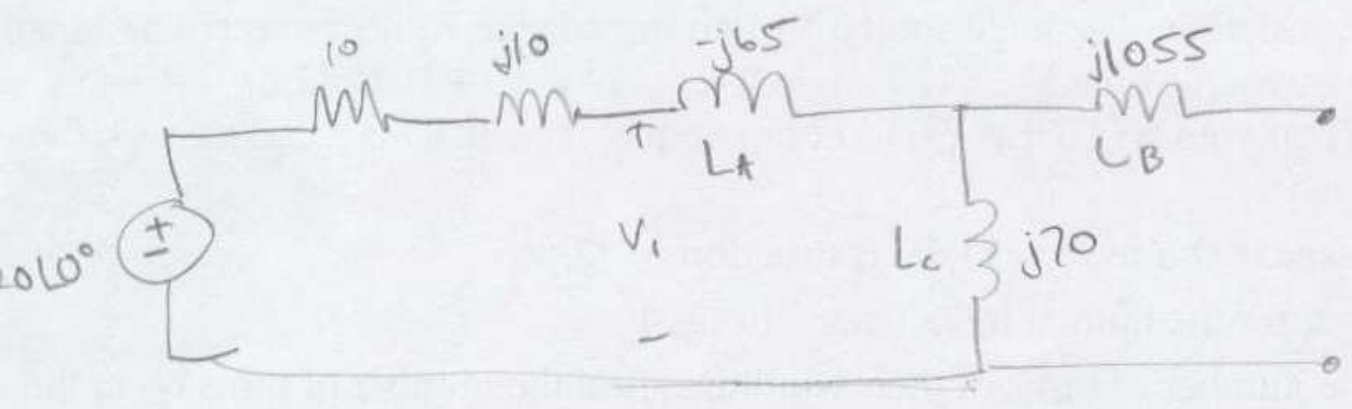

$$L_A = L_1 - M = j5 - j70 = -j65$$

$$L_B = L_2 - M = j1125 - j70 = j1055$$

$$L_C = M = j70$$

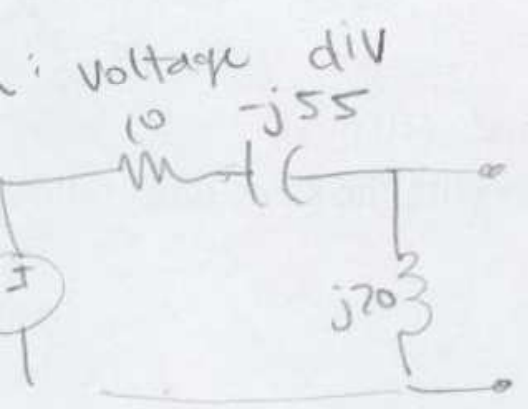

voltage div

$$V_{th} = \frac{120 \angle 0^\circ (j70)}{j70 + 10 - j55} = 387.69 + j258.44$$

$$= 465.95 \angle 0.588 \text{ rad}$$


$$= 465.95 \angle 33.7^\circ$$

$$Z_1 = (10 - j55) \parallel j70 + j1055$$

$$\frac{1}{Z_1} = \frac{1}{10 - j55} + \frac{1}{j70}$$

$$Z_1 = 150.77 - j156.15 = 217.06 \angle -0.8 \text{ rad}$$
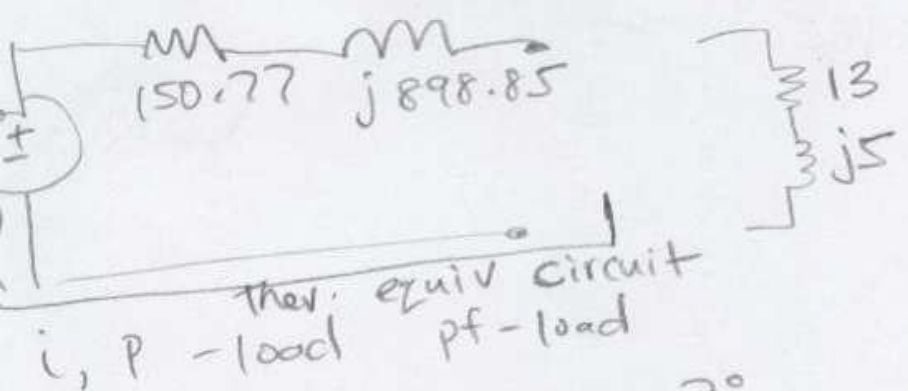
$$Z_{th} = Z_1 + j1055 = 150.77 + j898.85$$



$$I_{rms} = \frac{465.95 \angle 33.7^\circ}{150.77 + 13 + j898.85 + j5} = 0.507 \angle -0.8 \text{ rad}$$

$$= 0.507 \angle -46.04^\circ \text{ A (rms)}$$

$$P = I^2 R = (0.507)^2 (13) = 3.34 \text{ W}$$


$$Q = I^2 X = (0.507)^2 (5) = 1.285 \text{ Vars}$$

$$S = P + jQ = 3.34 + j1.285 \text{ VA} = 3.579 \angle 0.367 \text{ rad}$$

$$= 3.579 \angle 21.05^\circ$$


$$PF = \frac{P}{|S|} = \frac{3.34}{3.579} = 0.933$$

$$PF = \cos(\theta_v - \theta_i)$$

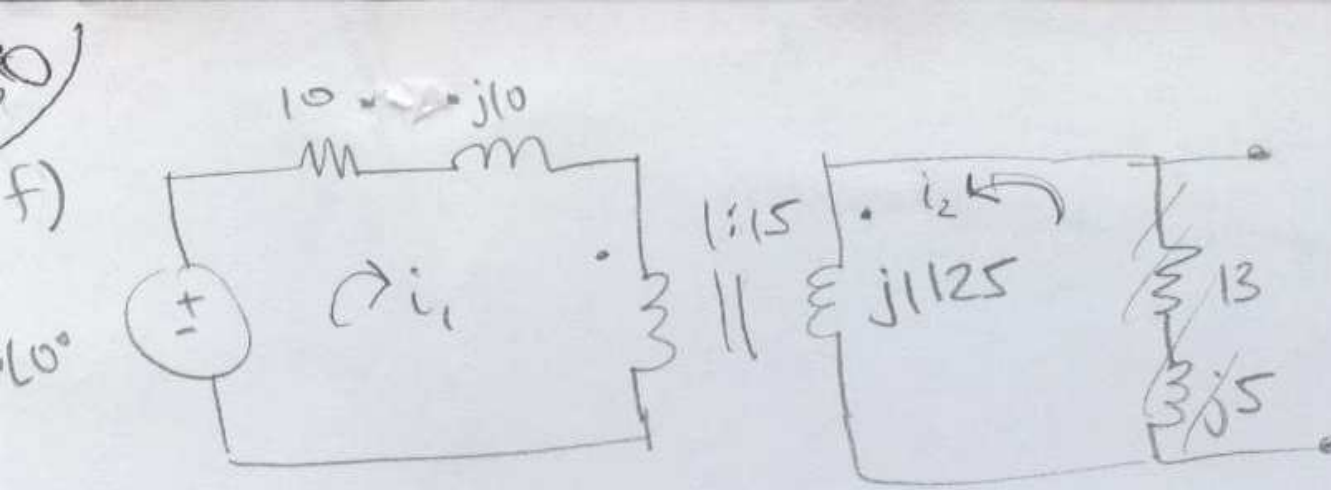


Vmshelli Ko  
 $n = \frac{N_2}{N_1} = \frac{150}{10} = 15$  802832

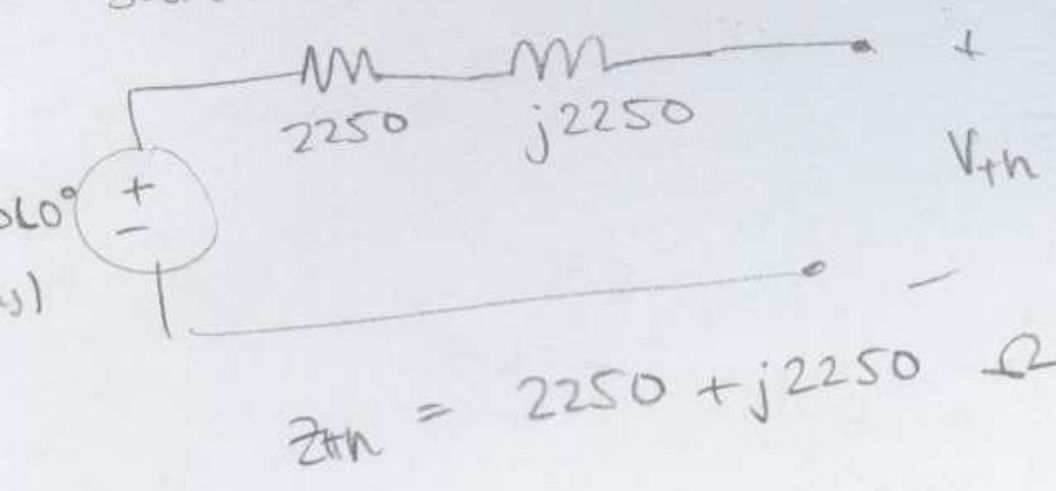(imp :  $\times n^2$   
 Source :  $\times n$        $n=15$



$i$ ,  $S$ , pf to load

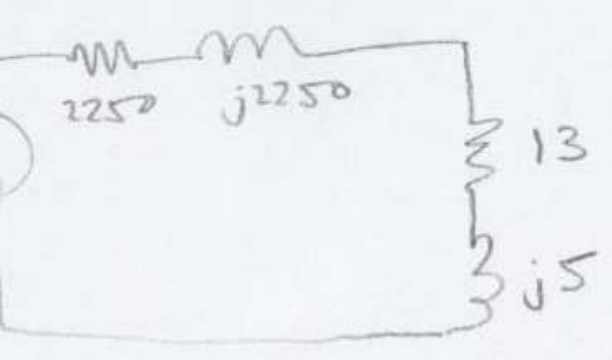

$$i = \frac{1800 \angle 0^\circ}{2250 + 13 + j2250 + j5} = 0.4 - j0.4 = 0.56 \angle -44.9^\circ$$


$$P = |i|^2 R = 0.56^2 (13) = 4.077 \text{ W}$$

$$Q = |i|^2 X = 0.56^2 (5) = 1.568 \text{ Vars}$$

$$S = P + jQ = 4.077 + j1.568 = 4.37 \angle 21.04^\circ \text{ VA}$$

$$PF = \frac{P}{|S|} = \frac{4.077}{4.37} = 0.933$$

2nd method

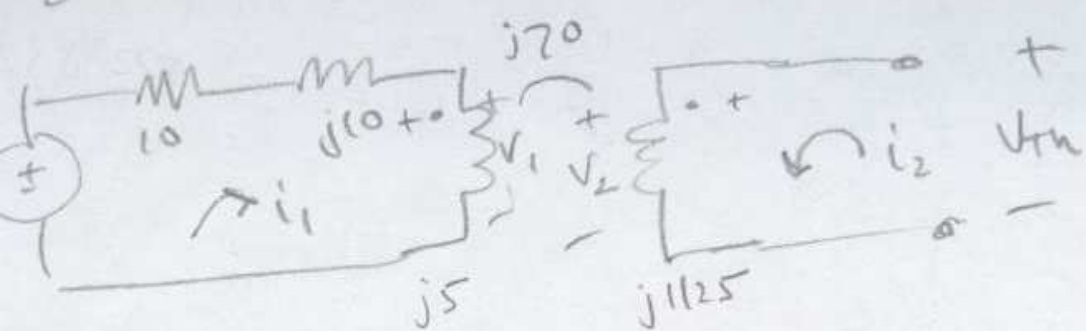

$$i_2 = 0$$
$$V_2 = V_{TH}$$

$$V_2 = 0 + j70i_1$$

$$V_1 = j5(i_1) + j70(i_2)$$

$$120\angle 0^\circ = (10 + j10)i_1 + V_1$$

$$120\angle 0^\circ = (10 + j10)i_1 + j5i_1$$

$$i_1 = \frac{120\angle 0^\circ}{10 + j15} = 3.7 - j5.54$$

$$= 6.656\angle -56.3^\circ$$

$$V_2 = j70i_1 = 387.8 + j259$$

Em: