

1- True or false?



- a) The voltage across a capacitor can never change abruptly. *False, if an infinite is applied or connected to a step voltage source*
- b) The response of an RLC network to a step function is always proportional to the height of the step. *False (it might not be zero-state)*
- c) The differential equation governing a circuit that includes 2 capacitors and 2 inductors is always a 4<sup>th</sup> order equation. *False, there might be a capacitive loop or inductive cut-set.*
- d) The Laplace Transform of all real functions is always convergent but it may or may not converge for complex functions. *False,  $f(t) = e^{t^2}$  is a real and divergent function. Laplace doesn't exist.*

(2.5+2.5+2.5+2.5=10 points)

10


2- Find  $v_{out}(t)$  for all  $t$  if the switch goes from position 1 to position 2 to at  $t = 0$  and back to position 1 at  $t = 1$  sec. The circuit had been at rest for a long time before  $t = 0$ .

(30 points)

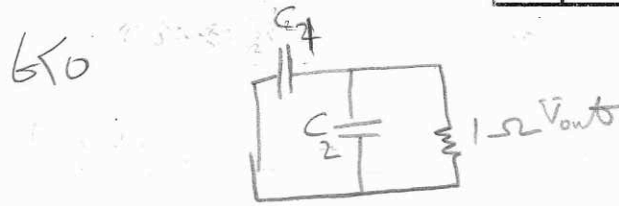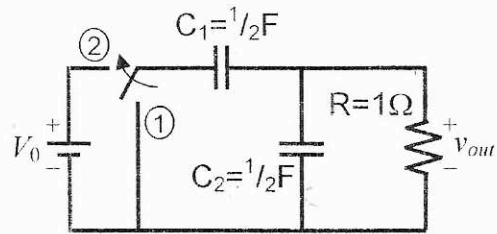

$V_{C_1}(0) = 0$   
 $V_{C_2}(0) = 0$

for  $t=0$  to  $t=1$ ,

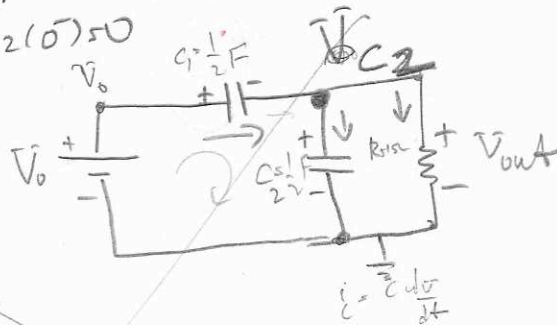

$V_C(0) = 0$  (No initial condition)


KCL at  $V_{C_2}$ :  $C_1 \frac{d(V_0 - V_{out})}{dt} = C_2 \frac{dV_{out}}{dt} + \frac{V_{out}}{R}$

$0 = C_1 \frac{dV_0}{dt} = C_1 \frac{dV_{out}}{dt} + C_2 \frac{dV_{out}}{dt} + \frac{V_{out}}{R} = (C_1 + C_2) \frac{dV_{out}}{dt} + \frac{V_{out}}{R}$

$\frac{dV_{out}}{dt} + V_{out} = 0 \Rightarrow s+1=0 \Rightarrow s=-1 \Rightarrow V_{out} = k e^{-st}$


Take into Laplace  
 Voltage divider

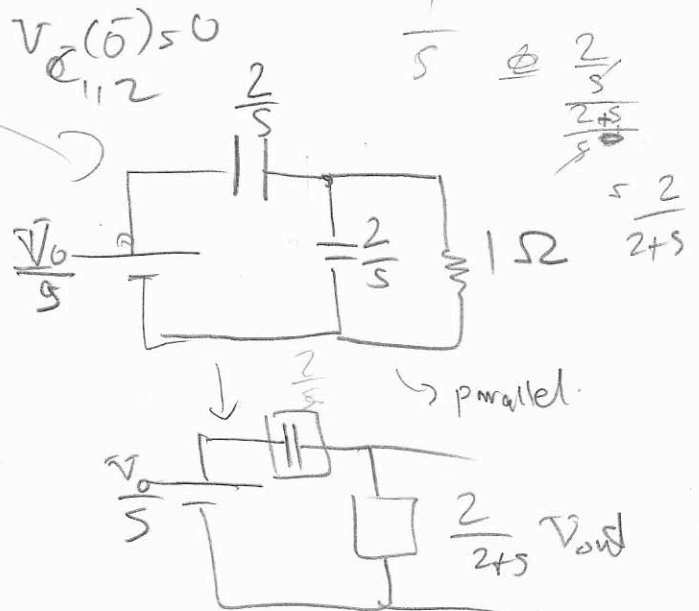$V_{out} = \left( \frac{\frac{2}{2+s}}{\left(\frac{2}{2+s}\right) + \frac{2}{s}} \right) \frac{V_0}{s}$



3- A) Without using the Laplace Transform, find the impulse response of a circuit, with input  $f(t)$  and output  $y(t)$ , governed by this equation:

$$y' = f'' + f$$

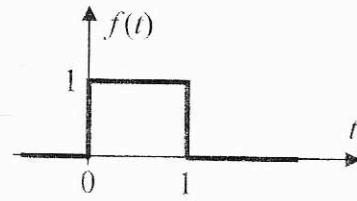

B) Without using the Laplace Transform, find the complete response of this circuit to the input  $f(t)$  shown here, if  $y(0^-) = 1$ .

(10+20=30 points)

find  $h(t)$ ?  $\Rightarrow$  when input  $f(t) = \delta(t)$   
 $h(t) \Rightarrow$  There is a delta  $\delta(t)$  and  $\delta'(t)$  in the response  
 $y'' = \delta''(t) + \delta(t)$

Find homogeneous response (characteristic equation):

$$\frac{dy}{dt} = 0 \Rightarrow k_1 s = 0 \Rightarrow s = 0 \Rightarrow k_1 u(t) + k_2 \delta(t) + k_3 \delta'(t)$$

$$k_1 \delta(t) + k_2 \delta'(t) + k_3 \delta''(t) = \delta''(t) + \delta(t) \Rightarrow k_1 = 1$$

$$\Rightarrow h(t) = u(t) + \delta'(t) \quad k_3 = 1$$

Use convolution:

$$y(0^-) = 1$$

$$y(t) = h(t) * f(t) = (u(t) + \delta'(t)) * f(t) = u(t) * f(t) + \delta'(t) * f(t)$$


$$\int_{-\infty}^t f(t-\tau) u(\tau) d\tau + \int_{-\infty}^t \delta(\tau) f(t-\tau) d\tau$$

1st integral: for  $t < 0 \Rightarrow y(t) = 0$  (no overlap)

$$0 < t < 1 \Rightarrow y(t) = t$$


$$t > 1 \Rightarrow y(t) = 1$$

2nd integral: for  $t < 0$  none

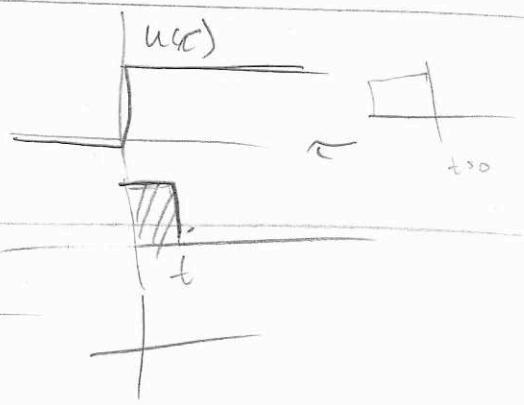

$$i(t) = i_{L1}(t) + i_{L2}(t)$$

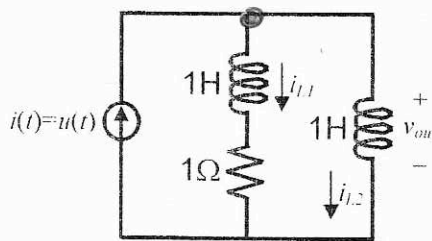4- A) Find the complete response for  $v_{out}(t)$  when the inductors have initial currents  $i_{L1}(0^-)$  and  $i_{L2}(0^-)$  at  $t=0^-$ . You can use the Laplace Transform if you choose to.  
 B) Determine the condition for  $i_{L1}(0^-)$  and  $i_{L2}(0^-)$  for which the exponential part of the response becomes equal to 0.



(20+10=30 points)


the shape has not changed  
 circuit remains the same

LS

change the circuit into laplace domain


KU at node A:
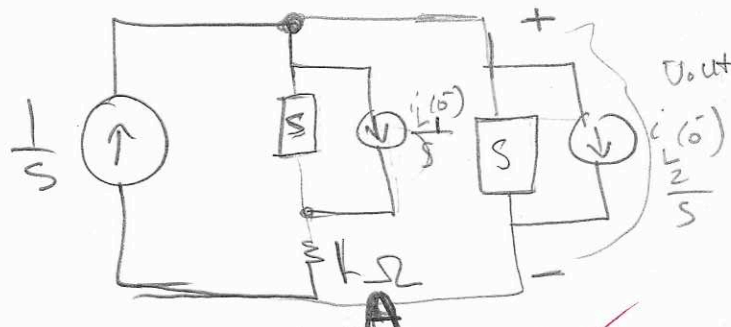
$$(1) \frac{1}{s} - \frac{i_{L1}(0^-)}{s} - \frac{i_{L2}(0^-)}{s} = \frac{V_{out}}{s} + \frac{V_{out} - V_B}{s}$$



KU at B:
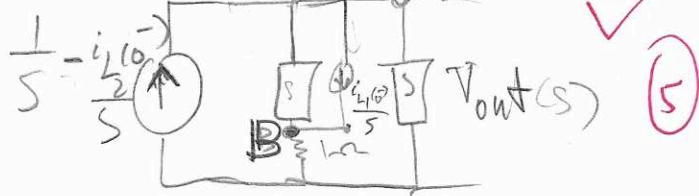
$$-\frac{i_{L1}(0^-)}{s} + \frac{V_{out} - V_B}{s} + V_B = 0$$



$$\Rightarrow -\frac{i_{L1}(0^-)}{s} - \frac{V_{out}}{s} = V_B \left( \frac{1}{s} - 1 \right) \Rightarrow V_B = \frac{-i_{L1}(0^-) - V_{out}}{\frac{1-s}{s}}$$

$$(2) V_B = \frac{-i_{L1}(0^-) - V_{out}}{1-s}$$

$$\frac{2V_{out}}{s} = \frac{1}{s} \left[ 1 - \frac{i_{L1}(0^-) - i_{L2}(0^-)}{s} + \left( \frac{-i_{L1}(0^-) - V_{out}}{1-s} \right) \right]$$

$$\frac{2V_{out}}{s} + \frac{V_{out}}{s(1-s)} = \frac{1}{s} \left[ 1 - \frac{i_{L1}(0^-) - i_{L2}(0^-)}{s} + \frac{-i_{L1}(0^-)}{1-s} \right]$$