

Name:

1- True or false?

- a) The voltage across a capacitor can never change abruptly.
- b) The response of an RLC network to a step function is always proportional to the height of the step.
- c) The differential equation governing a circuit that includes 2 capacitors and 2 inductors is always a 4th order equation.
- d) The Laplace Transform of all real functions is always convergent but it may or may not converge for complex functions.

(2.5+2.5+2.5+2.5=10 points)

a) False


x b) True

c) False

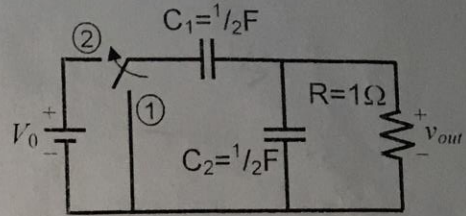d) False

+7.5

2- Find $v_{out}(t)$ for all t if the switch goes from position 1 to position 2 to at $t = 0$ and back to position 1 at $t = 1$ sec. The circuit had been at rest for a long time before $t = 0$.





(30 points)

$t < 0$, everything is uncharged

output

$$i = C \frac{dv}{dt}$$

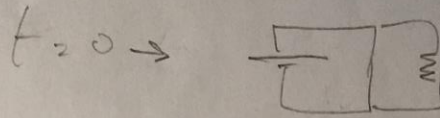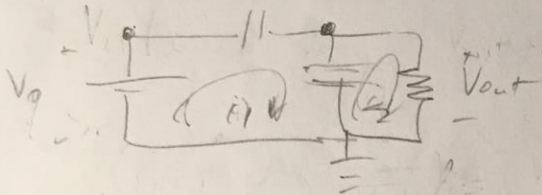

$$C \frac{dv_1}{dt} = C \left(\frac{dv_{out}}{dt} + \frac{v_{out}}{R} \right)$$

$$2v_1' = 2v_{out}' + v_{out}$$


$$v_1 + v_{out} = v_0$$

$$v_1 = v_0 - v_{out}$$

$$v_1' = -v_{out}'$$

$$2(v_0 - v_{out})' = 2v_{out}' + v_{out}$$

$$2v_0 \delta(t) = v_{out}$$

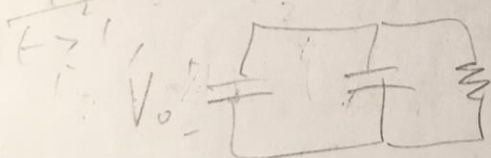

$$t > 1,$$

$$v_{out} = v_1 + (v_2 - v_1) e^{-\frac{t}{R(C_1 + C_2)}}$$


$$= v_{out}(1^-) e^{-t}$$

$$= v_{out}(1^-) e^{-t}$$

(3)

3- A) Without using the Laplace Transform, find the impulse response of a circuit, with input $f(t)$ and output $y(t)$, governed by this equation:

$$y' = f'' + f$$

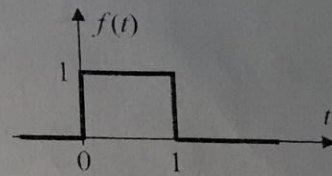

B) Without using the Laplace Transform, find the complete response of this circuit to the input $f(t)$ shown here, if $y(0^-) = 1$.

Zero state response

(10+20=30 points)

$$a) \quad f'' + f' = y' \quad , \quad s^2 + 1 = 0$$

$$s = \pm i$$

$$f(t) = Ae^{it} + Be^{-it}$$

$$f(t) = A \cos(t + \phi) u(t)$$

$$f'(t) = A \cos(\phi) \delta(t) - A \sin(t + \phi) u(t)$$

$$f''(t) = A \cos(\phi) \delta'(t) - A \sin(\phi) \delta(t) - A \cos(t + \phi) u(t)$$

$$A \cos(\phi) \delta'(t) - A \sin(\phi) \delta(t) = \delta'(t)$$

$$A \cos(\phi) = 1 \quad -A \sin(\phi) = 0$$

$$A = 1$$

$$\sin(\phi) = 0$$

$$\phi = 0$$

$$h(t) = \cos t u(t)$$


$$b) \quad h(t) * f(t) = y(t)$$

$$y(t) = \int_0^t h(\tau) f(t-\tau) d\tau$$

$$0 < t < 1, \quad y(t) = \int_0^t \cos \tau d\tau$$

$$= \sin \tau \Big|_0^t = \sin t$$

$$t > 1, \quad y(t) = \int_{t-1}^t \cos \tau d\tau = \sin \tau \Big|_{t-1}^t = \sin t - \sin(t-1)$$

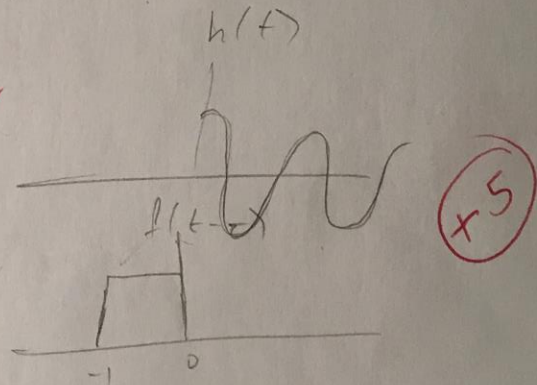


$$(\cos(0) = 1)$$

X3

X5

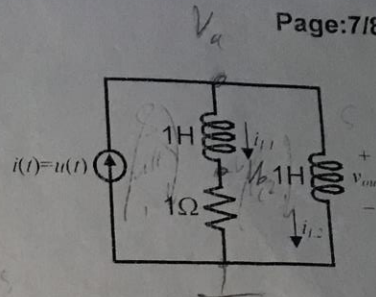4- A) Find the complete response for $v_{out}(t)$ when the inductors have initial currents $i_{L1}(0^-)$ and $i_{L2}(0^-)$ at $t=0^-$. You can use the Laplace Transform if you choose to.
 B) Determine the condition for $i_{L1}(0^-)$ and $i_{L2}(0^-)$ for which the exponential part of the response becomes equal to 0.



(20+10=30 points)

$$i_{L1} + i_{L2} = u(t) \rightarrow i_{L2} = u(t) - i_{L1}(t)$$

$$\frac{di_{L1}}{dt} + i_{L1} = \frac{di_{L2}}{dt} \quad i_{L2}' = u'(t) - i_{L1}'(t)$$

$$i_{L1}' + i_{L1} = u'(t) - i_{L1}'(t)$$

$$2i_{L1}' + i_{L1} = u'(t)$$

$$2sI_{L1}(s) - 2i_{L1}(0^-) + I_{L1}(s) = 1$$

$$I_{L1}(s)(2s+1) = 1 + 2i_{L1}(0^-)$$

$$I_{L1}(s) = \frac{1 + 2i_{L1}(0^-)}{2s+1} = \frac{1}{2} + i_{L1}(0^-) \cdot \frac{1}{s + \frac{1}{2}}$$

$$i_{L1}(s) = \frac{\frac{1}{2} + i_{L1}(0^-)}{s + \frac{1}{2}}$$

$$i_{L1}(t) = \left(\frac{1}{2} + i_{L1}(0^-)\right) e^{-\frac{1}{2}t} u(t)$$

$$i_{L2}(t) = u(t) - i_{L1}(t)$$


$$= u(t) - \left(\frac{1}{2} + i_{L1}(0^-)\right) e^{-\frac{1}{2}t} u(t)$$

$$= \left(1 - \frac{1}{2} - i_{L1}(0^-)\right) e^{-\frac{1}{2}t} u(t)$$

$$i_{L2}(t) = \left(\frac{1}{2} - i_{L1}(0^-)\right) e^{-\frac{1}{2}t} u(t)$$

$$v_{out} = \frac{L di_{L2}}{dt} = \left(\frac{1}{2} - i_{L1}(0^-)\right) u'(t) - \frac{1}{2} \left(\frac{1}{2} - i_{L1}(0^-)\right) e^{-\frac{1}{2}t} u(t)$$

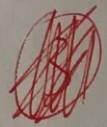B) $i_{L1}(0^-) = \frac{1}{2} A$, $i_{L2}(0^-) = \frac{1}{2} A$



(5)

(3)