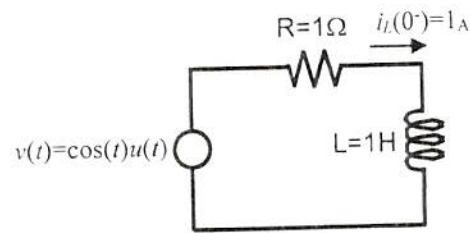


1- In the RL circuit shown:

A) Use your favorite method to find the complete response for $i_L(t)$.

B) After the transient part of the response dies out, find the energy delivered to the resistor in one cycle.



(15+10=25 points)

a) zero input:

$$iR + Li' = 0 \quad i(0^-) = 1$$

$$iR = -Li'$$

$$i = e^{-\frac{R}{L}t}$$

zero state:

$$iR + Li' = \cos(t)$$

$$i_h = K_1 e^{-\frac{R}{L}t}$$

$$i_p = A \cos t + B \sin t$$

$$i_p' = -A \sin t + B \cos t$$

$$A + B = 1$$

$$A - B = 0$$

$$2A = 1$$

$$A = \frac{1}{2}$$

$$B = \frac{1}{2}$$

$$i = K_1 e^{-\frac{R}{L}t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t$$

$$i(0^-) = 0 = K_1 + \frac{1}{2}$$

$$K_1 = -\frac{1}{2}$$

$$i = -\frac{1}{2} e^{-\frac{R}{L}t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t$$

complete: $i(t) = \frac{1}{2} e^{-t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t$

$$b) E_R = \int_0^T v(t) i(t) dt$$

$$E_R = \int_0^{2\pi} \left[\frac{1}{2} (\cos t + \sin t) \right]^2 dt$$

$$E_R = \frac{1}{2} \left[\int_0^{2\pi} \cos^2 t dt + \int_0^{2\pi} \sin^2 t dt + \int_0^{2\pi} \sin t \cos t dt \right]$$

$$E_R = \frac{1}{2} \left[\int_0^{2\pi} \cos^2 t dt + \int_0^{2\pi} \sin^2 t dt + \int_0^{2\pi} \sin t \cos t dt \right]$$

$$E_R = \frac{1}{2} \left[2\pi + \int_0^0 u du \right]$$

let $u = \sin t$
 $du = \cos t dt$
 $\cos t = 0$
 $\sin t = 0$

$$E_R = \pi$$

+15

+7


Name:

Student ID:

Page:4/9


2- Use Laplace Transform to find the complete response for $v_c(t)$ if:

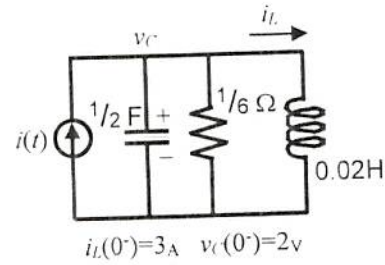- A) $i(t)=u(t)$
- B) $i(t)=\delta(t)$
- C) Is the response in part B the derivative of the response in Part A and why?



(10+10+5=25 points)

A.)

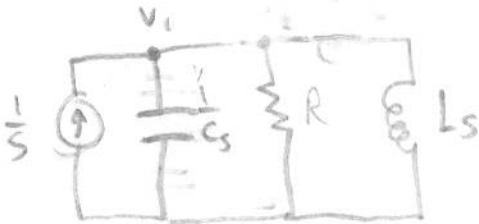

x 10

$$V_c \left(\frac{1}{s} \right) + \frac{V_c}{R} + \frac{V_c}{Ls} = \frac{1}{s} = \frac{i_L(0^-)}{s}$$

$$\frac{s}{2} \left(V_c + \frac{2}{s} \right) + 6V_c + \frac{50V_c}{s} = \frac{1-3}{s}$$

$$V_c \left(\frac{s}{2} + 6 + \frac{50}{s} \right) = -\frac{2}{s} + 1$$

$$V_c (s^2 + 12s + 100) = -4 + 2s$$

$$V_c = \frac{2s - 4}{s^2 + 12s + 100}$$

$$V_c = \frac{2s - 4}{s + 6 + 64}$$

$$V_c = 2 \left(\frac{s+6}{(s+6)^2 + 64} \right) - 2 \frac{8}{(s+6)^2 + 64}$$

$$V_c = 2e^{-6t} \cos 8t - 2e^{-6t} \sin 8t$$

$$B.) V_1(s^2 + 12s + 100) = 1 - \frac{3}{s} + 1, 2s$$

same but replace
 $\frac{1}{s}$ for $u(t)$ with 1 for $\delta(t)$

$$V_1(s^2 + 12s + 100) = 4s - 6$$

$$V_1 = \frac{4s - 6}{(s+6)^2 + 64}$$

$$V_1 = 4 \left(\frac{s+6}{(s+6)^2 + 64} \right) - \frac{15}{4} \left(\frac{8}{(s+6)^2 + 64} \right)$$

+10

$$V_1(t) = 4e^{-6t} \cos 8t - \frac{15}{4} e^{-6t} \sin 8t$$

$$C.) V_A = 2e^{-6t} \cos 8t - 2e^{-6t} \sin 8t$$

$$V_A' = -12e^{-6t} \cos 8t - 16e^{-6t} \sin 8t + 12e^{-6t} \sin 8t - 16e^{-6t} \cos 8t$$

$$= -28e^{-6t} \cos 8t - 4e^{-6t} \sin 8t \rightarrow V_B$$

Part B is not the derivative of part A. This is because of the initial conditions. Impulse response is only the derivative of step response for zero-state circuits.


+5

Name:

Student ID:

Page: 6/9

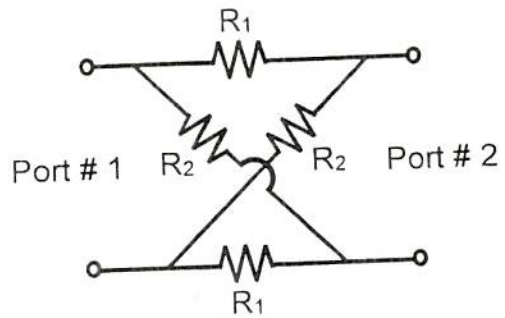3- Find the Y-parameters of the two-port network shown here.




16 (25 points)

$$I_1 = V_1 Y_{11} - V_2 Y_{12}$$

$$I_2 = V_2 Y_{22} - V_1 Y_{21}$$
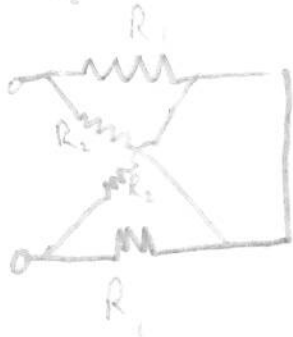
$$Y_{11} = \frac{I_1}{V_1} \text{ when } V_2 = 0$$



$$V_{R1A} = V_{R2A}$$

$$V_{R2B} = V_{R1B}$$

$$I_{R1A} = I_{R2A} = I_{R2B} = I_{R1B} = I_1$$

so

$$V_{R2A} = V_{R2B} \quad V_{R1A} = V_{R1B}$$

$$R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_1 = V_{R1A} + V_{R2B} = V_{R1B} + V_{R2A} = I_1 \cdot 2(R_1 // R_2)$$

$$\frac{I_1}{V_1} = \frac{1}{R_1 // R_2} = \frac{R_1 + R_2}{2R_1 R_2} = Y_{11}$$

X

~~8~~ 8


Circuit is symmetric so for Y_{22} we get an identical circuit. So

$$Y_{22} = \frac{R_1 + R_2}{2R_1 R_2}$$

X

Y_{12} and Y_{21} on back of page
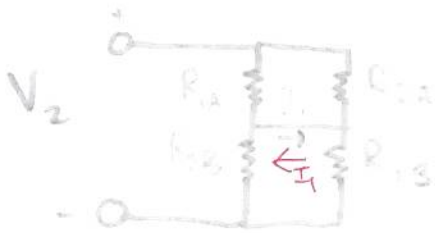
$$Y_{12} = \frac{I_1}{V_2} \text{ when } V_1 = 0$$



Can make same conclusions as before but now need to find how much current is in each resistor

$$\begin{aligned} i_{1A} R_{1A} &= i_{2A} R_{2A} \\ i_{1A} &= \frac{i_{2A} R_{2A}}{R_{1A}} \end{aligned}$$

$$\begin{aligned} i_{1B} &= i_{1A} \\ i_{2A} &= i_{2B} \end{aligned}$$

$$I_1 = i_{1B} - i_{2A}$$

$$= \frac{i_{2A} R_{2A}}{R_{1A}} - i_{2A} = i_{2A} \left(\frac{R_2}{R_1} - 1 \right)$$

$$V_2 = i_{1A} R_{1A} + i_{2B} R_{2B} = i_{2A} R_2 + i_{2A} \frac{R_2}{R_1} R_1$$

$$\frac{I_1}{V_2} = \frac{\frac{R_2}{R_1} - 1}{2R_2} = \frac{-(R_2 - R_1)}{2R_1 R_2} = \frac{1}{2} \quad \times$$

~~8~~ 8

Again, by symmetry $Y_{12} = Y_{21}$ so


$$Y_{21} = \frac{-(R_2 - R_1)}{2R_1 R_2} \quad \times$$

4- Without using Laplace Transform:

A) Write the integro-differential equations in time domain relating $v_C(t)$ to $v_{in}(t)$.

B) For $v_{in}(t) = u(t)$ find the homogenous and particular responses.

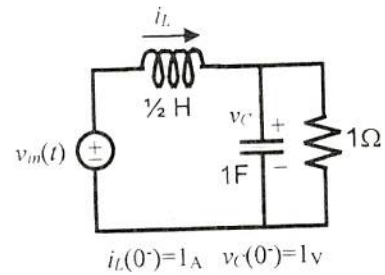C) Find the complete response by applying the initial conditions.



(10+10+5=25 points)

a.)
$$v_{in}(t) = L \frac{di_L}{dt} + \frac{1}{C} \int i_C dt + v_C(0^-)$$

$$i_L + i_L(0^-) = i_C + i_R$$

$$\frac{1}{C} \int i_C dt = i_R R \quad i_R = \frac{1}{RC} \int i_C dt$$

$$v_{in}(t) = C \frac{d^2 v_C}{dt^2} + \frac{L}{R} \frac{dv_C}{dt} + v_C \cdot v_C(0^-)$$

with numerical values

$$i_L = i_C - \frac{1}{RC} \int i_C dt - i_L(0^-)$$

$$i_L = C \frac{dv_C}{dt} + \frac{1}{R} v_C - i_L(0^-)$$

$$\frac{di_L}{dt} = C \frac{d^2 v_C}{dt^2} + \frac{1}{R} \frac{dv_C}{dt}$$

$$v_{in}(t) = \frac{1}{2} v_C'' + \frac{1}{2} v_C' + v_C \cdot v_C(0^-)$$

X 5

B) Since part C wants complete, I will assume zero-state.

$$v(t) = \frac{1}{2} v_C'' - \frac{1}{2} v_C' - v_C$$
 homogeneous X 0

$$V_P = 1 \text{ for } t > 0$$
 ✓ 5

Since $v_C(0^+) = 0$ (no current at $t=0$; all V dropped across inductor)
and $v_C(\infty) = 1$ (inductor is short, cap is open, so all V across cap)

$$v_C = (V_E - V_F) e^{-t/\tau} + V_F \quad V_F = V_P \text{ so } V_H = (V_E - V_F) e^{-t/\tau} = -e^{-t/\tau}$$

based on our diff. eq., $\tau =$

$$V_H = -e^{-t/\tau}$$

c.) With the initial conditions, we are already in the final state from part B

so

$$V_C(t) = 1 \quad \checkmark \quad \tau$$

Find by solving diff. eq.?