

EE110 – Circuit Analysis II
Winter 2018 – Dr. Shervin Moloudi
Mid-Term Exam – Wednesday February 14, 2018

Instructions

- 1- You have 1 hour and 50 minutes.**
- 2- Do not attach your own paper. Ask the proctors for extra paper**
- 5- The exam is closed book. No formula sheets, electronic devices, tablets, smart phones/watches allowed. Regular wrist watches allowed.**

Question	
1	10 / 10
2	20 / 20
3	15 / 30
4	10 / 40
Grade	55 / 100

1- True or false?

- The current through an inductor can never change abruptly.
- A reciprocal network only contains R, L, C, and linear dependent sources.
- The immittance network function for an RLC network cannot have zeros on the right hand side of the complex plane.
- No two networks have the same 2-port Z-parameters

(2.5+2.5+2.5+2.5=10 points)


a) $V = L \frac{di}{dt} \Rightarrow I = \frac{1}{L} \int_0^t v dt$

False (could have infinite voltage across inductor)

b) False

c) True (otherwise e^{at} where $a > 0$ could be a solution, leading to constantly rising V & I)

d) False

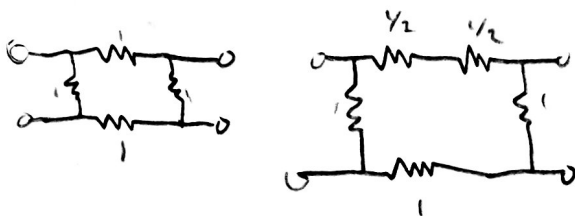

These both have same Z-parameters

2- Prove the integration property for the n^{th} derivative of the impulse function:

$$\int_{-\infty}^{+\infty} f(t) \delta^{(n)}(t - t_0) dt = (-1)^n f^{(n)}(t_0)$$

(20 points)

$$\int_{-\infty}^{\infty} f(t) \delta^{(n)}(t - t_0) dt$$

$$\int_{-\infty}^{\infty} f(t) \delta'(t - t_0) dt = \int_{-\infty}^{\infty} f(t_0) \delta'(t - t_0) dt$$

$$\mathcal{L}\left\{\frac{dx}{dt}\right\} = s\mathcal{L}\{x\} - x(0)$$

$$\int_{-\infty}^{\infty} f(t) \delta^{(n)}(t - t_0) dt \quad \text{let } u = f(t) \quad dv = \delta^{(n)}(t - t_0)$$

$$du = f'(t) \quad v = \delta^{(n-1)}(t - t_0)$$

$$\left[f(t) \delta^{(n-1)}(t - t_0) \right]_{-\infty}^{\infty} - \int_{-\infty}^{\infty} \delta^{(n-1)}(t - t_0) f'(t) dt$$

$$\begin{aligned} & \int_{-\infty}^{\infty} \delta^{(n-1)}(t - t_0) f'(t) dt \quad \text{let } u = f'(t) \quad dv = \delta^{(n-1)}(t - t_0) \\ & \quad du = f''(t) \quad v = \delta^{(n-2)}(t - t_0) \\ & \quad - \left[f'(t) \delta^{(n-2)}(t - t_0) \right]_{-\infty}^{\infty} + \int_{-\infty}^{\infty} \delta^{(n-2)}(t - t_0) f''(t) dt \end{aligned}$$


This is equivalent to $(-1)^n$

Following this pattern set by integration by parts, since we take the n^{th} integral of $\int_{-\infty}^{\infty} f(t) \delta^{(n)}(t - t_0) dt$, we get $\int_{-\infty}^{\infty} (-1)^n f^{(n)}(t_0) \delta(t - t_0) dt$

$$(-1)^n f^{(n)}(t_0) \int_{-\infty}^{\infty} \delta(t - t_0) dt$$

$$\boxed{= (-1)^n f^{(n)}(t_0)}$$

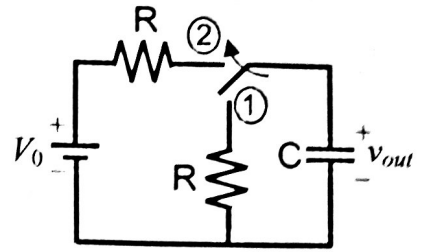3- In this circuit the switch has been toggling between positions 1 and 2 periodically for a very long time. Within the period T , the switch spends half the time in position 1 and the rest of the time in position 2. Find and plot $v_{out}(t)$ for one cycle and calculate the average power delivered by the battery in the same cycle. Note that there is no relationship between T and RC .



Hint: A periodic cycle of T starts and ends at the same voltage.

(30 points)

Switch at pos 2

First half, $0 < t < \frac{T}{2}$:

$$I = C \frac{dv}{dt}$$

$$\frac{1}{C} \int_0^t i dt = V$$

$$\frac{v_{out} - V_0}{R} + C \frac{dv_{out}}{dt} = 0$$

$$v_{out} - V_0 + RC \frac{dv_{out}}{dt} = 0$$

$$-RC \frac{dv_{out}}{dt} = -V_0 + v_{out}$$

$$\int_{v_{out} - V_0}^{\infty} \frac{1}{v_{out} - V_0} dv_{out} = \int -\frac{1}{RC} dt$$

$$\ln |v_{out} - V_0| = -\frac{1}{RC} t + A$$

$$v_{out} = V_0 + B e^{-\frac{t}{RC}}$$

$$v_{out}(0) = v_i$$


$$v_i = V_0 + B$$

$$B = v_i - V_0$$

$$v_{out} = V_0 + (v_i - V_0) e^{-\frac{t}{RC}}$$

$$v_{out}(\frac{T}{2}) = V_0 + (v_i - V_0) e^{-\frac{T}{2RC}}$$

\checkmark

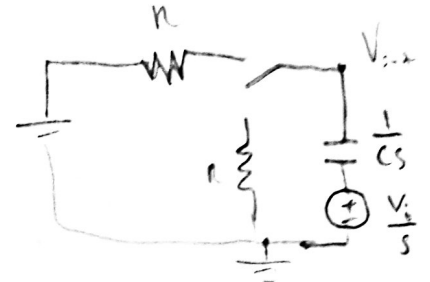

$$\frac{v_{out} - \frac{V_0}{2}}{R} + \frac{v_{out} - \frac{V_0}{2}}{CS} = 0$$

$$v_{out} - \frac{V_0}{2} + CS R v_{out} - CR \frac{V_0}{2} = 0$$

$$v_{out} (1 + CSR) = \frac{V_0}{2} + CR \frac{V_0}{2}$$

$$v_{out} = \frac{V_0 + CR V_0 S}{S(1 + RC S)}$$

$$v_{out} = \frac{V_0 + CR V_0 S}{RC S (\frac{1}{RC} + S)}$$

Second half, $\frac{T}{2} < t < T$:

Switch at pos 1

$$\frac{v_{out}}{R} + C \frac{dv_{out}}{dt} = 0$$

$$RC \frac{dv_{out}}{dt} = -v_{out}$$

$$\int_{v_{out}}^{\infty} \frac{1}{v_{out}} dv_{out} = \int -\frac{1}{RC} dt$$

$$v_{out} + (v_i - V_0) e^{-\frac{t}{RC}} \ln |v_{out}| = -\frac{(t - \frac{T}{2})}{RC} + A$$

$$v_{out}(T) = v_i$$

$$v_{out} = B e^{-\frac{(t - \frac{T}{2})}{RC}}$$

$$V_{\text{out}} = V_0 e^{-\frac{t}{\tau}}$$

plug in $V_{\text{out}}(T/2) = V_0 + (V_i - V_0) e^{-\frac{T}{2\tau}}$ ~~X~~

$$V_0 + (V_i - V_0) e^{-\frac{T}{2\tau}} = \beta$$


$$V_{\text{out}} = (V_0 + (V_i - V_0) e^{-\frac{T}{2\tau}}) e^{-\frac{t}{\tau}}$$

$$V_{\text{out}} = (V_0 e^{\frac{T}{2\tau}} + V_i - V_0) e^{-\frac{t}{\tau}}$$

(check $V_{\text{out}}(T) = 0$) $V_i = V_0 e^{-\frac{T}{2\tau}} + V_i e^{-\frac{T}{\tau}} - V_0 e^{-\frac{T}{\tau}}$

$$V_i (1 - e^{-\frac{T}{\tau}}) = V_0 e^{-\frac{T}{2\tau}}$$

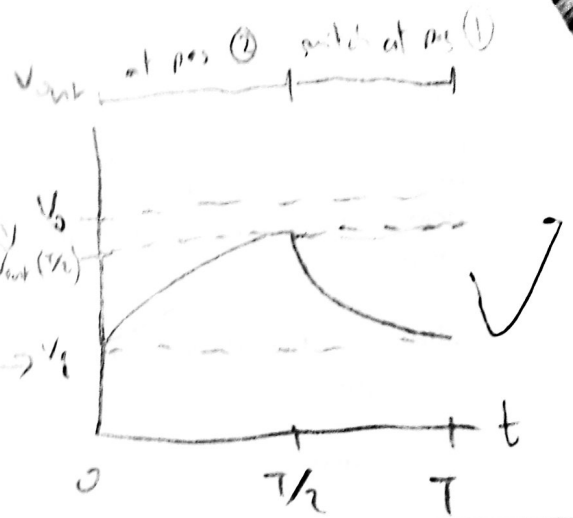~~$$V_i = \frac{V_0 e^{-\frac{T}{2\tau}}}{(1 - e^{-\frac{T}{\tau}})}$$~~



$$V_{\text{out}} = \left(V_0 e^{\frac{T}{2\tau}} + \frac{V_0 e^{-\frac{T}{2\tau}}}{(1 - e^{-\frac{T}{\tau}})} - V_0 \right) e^{-\frac{t}{\tau}} \quad \text{for } \frac{T}{2} \leq t < T$$

Average power delivered by battery only occurs during charging, i.e., $0 < t < T/2$

$$P = IV = IV_0 = \frac{V_0 - V_{\text{out}}(t)}{R} V_0 = V_0 (V_0 + (V_i - V_0)) e^{-\frac{t}{\tau}}$$

$$P_{\text{avg}} = \frac{1}{T} \int_0^{T/2} V_0 (V_0 + V_i - V_0) e^{-\frac{t}{\tau}} dt$$

$$= \frac{1}{T} (V_0) \int_0^{T/2} V_0 + (V_i - V_0) e^{-\frac{t}{\tau}} dt$$

$$= \frac{V_0}{T} (V_0) \left(\frac{T}{2} \right) + \frac{V_0 (V_i - V_0)}{T} (-\tau) \left[e^{-\frac{t}{\tau}} \right]_0^{T/2}$$

$$P_{\text{avg}} = \frac{V_0^2 T}{2T} - \frac{\tau V_0}{T} \left(\frac{V_0 e^{-\frac{T}{2\tau}}}{(1 - e^{-\frac{T}{\tau}})} - V_0 \right) (e^{-\frac{T}{2\tau}} - 1)$$


Name:

Student ID:

Page: 6/8


4- In the network shown $i_L(0^-) = I_0$.

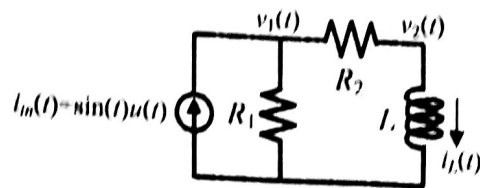- A) Draw an equivalent circuit in Laplace domain.
- B) Express the node equations in Laplace domain in the matrix form $Y(s)V(s) = F(s)$ where $Y(s)$ is the network admittance matrix, $V(s)$ is the vector of node voltages, and $F(s)$ contains the inputs and the initial states.




- C) Find the zero-state response ($t \geq 0$) of $v_2(t)$ if $R_1 = R_2 = 2\Omega$ and $L = 1H$.
- D) Find the zero-input response ($t \geq 0$) of $v_2(t)$ if $R_1 = R_2 = 2\Omega$ and $L = 1H$.
- E) Find the complete response ($t \geq 0$) of $v_2(t)$ if $R_1 = R_2 = 2\Omega$ and $L = 1H$ and determine the value of I_0 such that the exponential part of the response becomes equal to zero.

(5+10+10+10+5=40 points)

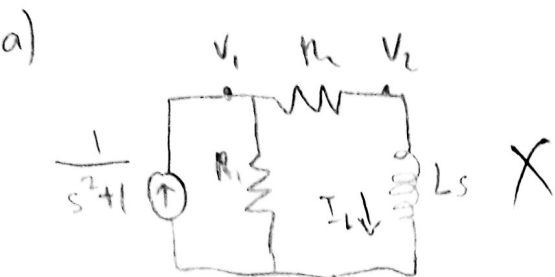
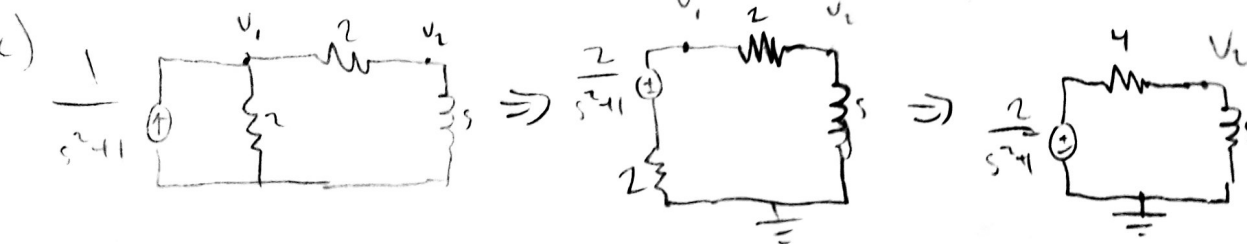
$$\begin{bmatrix} \frac{1}{R_1} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{Ls} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{s^2+1} - \frac{I_0}{s} \\ 0 \end{bmatrix}$$



$$V_2 - \frac{2}{s^2+1} + \frac{V_2}{s} = 0$$

$$V_2 s - \frac{2s}{s^2+1} + 4V_2 = 0$$

$$V_2 (s+4) = \frac{2s}{s^2+1}$$

$$V_2 = \frac{2s}{(s^2+1)(s+4)} = \frac{As+B}{s^2+1} + \frac{C}{s+4}$$

$$V_2 = \frac{\frac{8}{17}s + \frac{2}{17}}{s^2+1} + \frac{\frac{8}{17}}{s+4}$$

$$\begin{aligned} As^2 + Bs + 4As + 4B + Cs^2 + C &= 2s \\ C + A &= 0 & B + C &= 0 & 4A + B &= 2 \\ A &= -C & 4B + C &= 0 & -4C - \frac{C}{4} &= 2 \\ A &= \frac{8}{17} & B &= \frac{-C}{4} & \frac{-17C}{4} &= 2 \\ & & C &= \frac{2}{17} & C &= -\frac{8}{17} \end{aligned}$$

$$v_2 = \frac{8}{17} \frac{1}{s^2+1} + \frac{2}{17} \frac{1}{s^2+1} - \frac{8}{17} \frac{1}{s+4}$$

$$\stackrel{\mathcal{L}^{-1}}{\Rightarrow} \left[\frac{8}{17} \cos(t) + \frac{2}{17} \sin(t) - \frac{8}{17} e^{-4t} \right] u(t)$$

$$v(t) = \frac{8}{17} \cos(t) + \frac{2}{17} \sin(t) - \frac{8}{17} e^{-4t} \quad t \geq 0$$

d)



$$i(t) = I_0 e^{-\frac{1}{4}t} = I_0 e^{-\frac{1}{4}t}$$

$$v_2 = \frac{i(t)}{4} \Rightarrow v_2(t) = \frac{I_0}{4} e^{-\frac{1}{4}t}, \quad t \geq 0$$

X

e) complete response is $v_{zs}(t) + v_{zi}(t)$, which were found in (c) + (d)

$$v_2(t) = \frac{8}{17} \cos(t) + \frac{2}{17} \sin(t) - \frac{8}{17} e^{-4t} + \frac{I_0}{4} e^{-\frac{1}{4}t}$$

For exponential to be zero,

$$\frac{I_0}{4} = \frac{8}{17}$$

$$I_0 = \frac{32}{17}$$

X