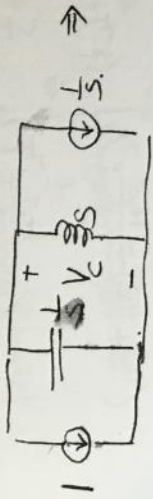


f. Method 1. the equivalent Laplace circuit is.



$$V_c = \left(\frac{1}{s} + 1\right) \cdot \frac{1}{s} \parallel s$$

$$= -\left(\frac{1}{s} + 1\right) \cdot \frac{1}{s + s}$$

$$\Rightarrow -\left(\frac{s+1}{s}\right) \frac{s}{s^2+1} = -\frac{s+1}{s^2+1}$$

$$\text{For } I_L = \frac{1}{s} + \frac{V_c}{s} = \frac{1}{s} - \frac{s+1}{(s^2+1)s}$$

$$= \frac{s^2+1-s-1}{s(s^2+1)} = \frac{s-1}{s^2+1}$$

$$\Rightarrow V_c = \frac{-s}{s^2+1} \downarrow -\cos t$$

These inverse Laplace transform

\downarrow -sint

can be find in the

table of the book !!!


$$I_L = \frac{s}{s^2+1} \downarrow \cos t$$

$$\Rightarrow V_c(t) = -(\cos t + \sin t)$$

$$i_L(t) = \cos t - \sin t$$

Method 2

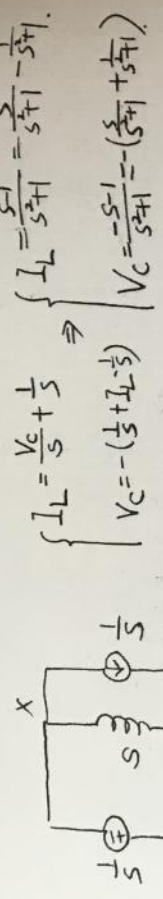1. Draw S-domain circuit and do node analysis @ X.



$$I_L = \frac{V_C}{s} + \frac{1}{s}$$


$$V_C = -(\frac{1}{s} + I_L \cdot \frac{1}{s})$$

$$\Rightarrow \begin{cases} I_L = \frac{s-1}{s^2+1} = -\frac{s}{s^2+1} - \frac{1}{s^2+1} \\ V_C = \frac{-s-1}{s^2+1} = -(\frac{s}{s^2+1} + \frac{1}{s^2+1}) \end{cases}$$

take the inverse Laplace transform of $I_L(s), V_C(s)$

$$\Rightarrow i(t) = \cos t - \sin t$$


$$V_C(t) = -(\cos t + \sin t)$$

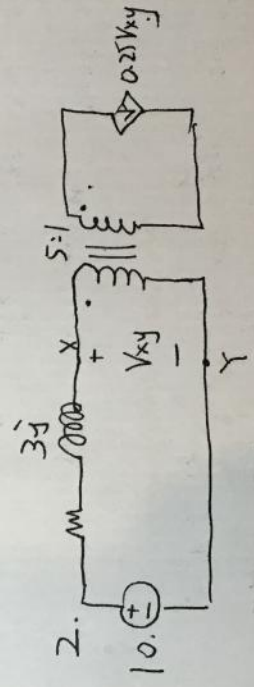

Take Thevenin equivalent circuit at port X-Y.

(1) $V_{eq} = 0$ ∴ no independent source

X, Y is open circuit.


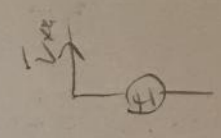


$$\Rightarrow V_{eq} = 0$$

$$\Rightarrow Z_{eq} = \frac{V_{xy}}{i_{xy}}$$


$$i_{xy} = \frac{V_{xy}}{4} / 5 = \frac{V_{xy}}{20}$$

$$\Rightarrow Z_{eq} = 20$$

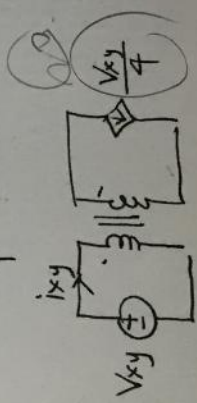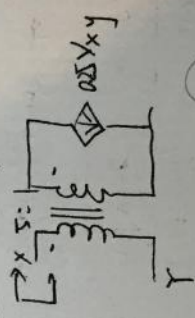

$$Z_{xy} = \frac{V_{xy}}{i_{xy}}$$

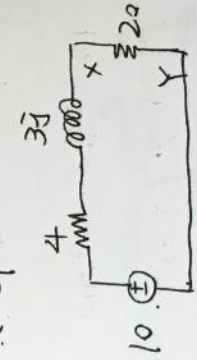port X, Y
 \Rightarrow the equivalent CT of the right side is just a resistor.
 \therefore equivalent CT is



$$\Rightarrow I = \frac{10}{24 + 3j} = \frac{16}{39} - \frac{2}{39}j$$


$$V_{XY} = I \cdot 20 = 8.2 - 1.02j$$

\Rightarrow Complex power is $S = V_{XY} \cdot I^* = 3.42 \text{ W}$.

\therefore ideal transformer doesn't consume power

b. now since the load is X therefore, the all the complex power at load X, Y will be the power consumed by load

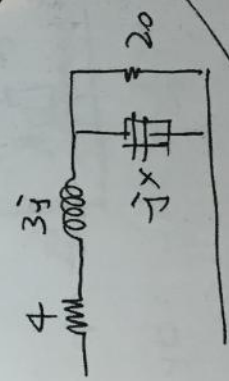b. Now, since the load is fixed (at X, Y side just 20 resistor) we can do best is adding a ~~comp~~ component to cancel the complex imaginary part of source impedance.



$$Z_L = \frac{jX \cdot 20}{jX + 20} = \frac{20Xj(20 - jX)}{20^2 + X^2}$$

$$= \frac{400Xj + 20X^2}{20^2 + X^2}$$

\therefore to cancel imaginary part

$V = 75$

rms phasor.

Problem 2: Refer to the circuit shown in Figure 2. The source is an rms phasor.

- Determine the complex power delivered to the load.
- What passive component should you connect between the terminals x and y such that maximum power is transferred to the load. What should be the value of this component?

(Yes Inc Cap Just one at time)


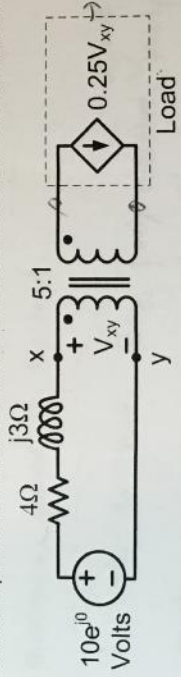


Figure 2.


(7 + 8 = 15 points)

Solution:

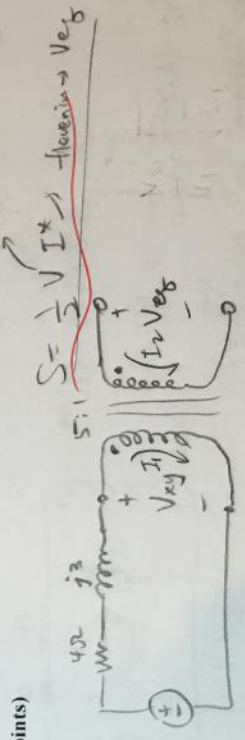

We need to find V_{o2}

$$\frac{V_{xy}}{5} = V_{o2}$$

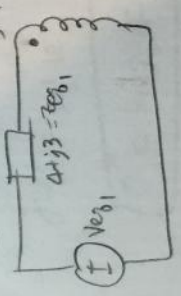


$$V_{o2} = \frac{N_2}{N_1} V_{o1}, \quad z_{o2} = \left(\frac{N_2}{N_1}\right)^2 z_{o1}$$

$$V_{o2} = \frac{1}{5} 10 \angle 0^\circ = 2, \quad z_{o2} = \frac{1}{25} (4+j3) = 0.2 \angle 36.87^\circ$$


$$S = \frac{V \cdot I^*}{z^*} = \frac{V \cdot V^*}{z^*} = \frac{1}{z^*} \cdot |V|^2 \Rightarrow$$

$$S = 20 \angle 36.87^\circ$$

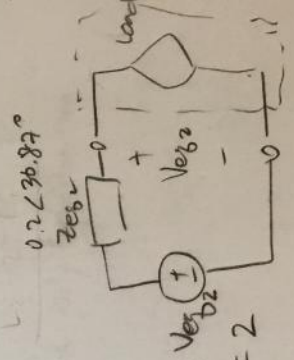


$$z_{o2}^* = 0.2 \angle -36.87^\circ$$

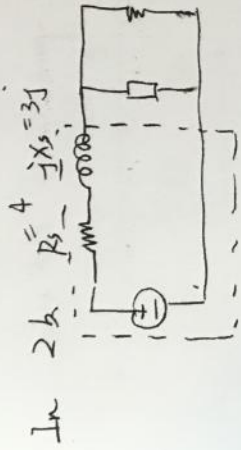
$$\frac{1}{(0.2 \angle -36.87^\circ)} \cdot 4$$



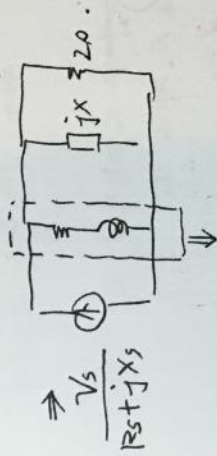The dashed line part can be Norton equivalent.


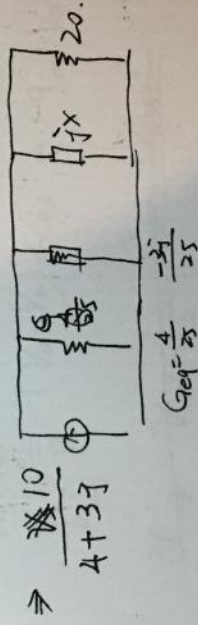
$$Z_{eq} = R_s + jX_s \quad Y_{eq} = \frac{1}{R_s + jX_s} = G_{seq} + jB_{eq} = \frac{1}{4 + 3j} = \frac{4 - 3j}{25}$$




$\therefore jX = \frac{3}{25}j$ to cancel the imaginary part.

for real susceptance, only cap can achieve.

$$jB = j\omega C = \frac{3}{25}j \quad \therefore \omega = 1 \Rightarrow C = \frac{3}{25}$$

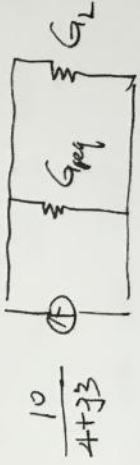If choose $C = \frac{3}{25}$ the imaginary part cancels each other.





$$P_{av} = I_s^2 \frac{G_L}{(G_{eq} + G_L)^2}$$


$$= \left| \frac{10}{4+j3} \right|^2 \frac{1}{\left(\frac{4}{25} + \frac{1}{20} \right)^2}$$

$$= \frac{10^2}{25} \times \frac{1}{20} \times \left(\frac{100}{21} \right)^2 = 4.53 \text{ W}$$

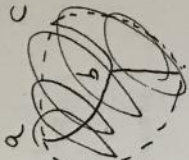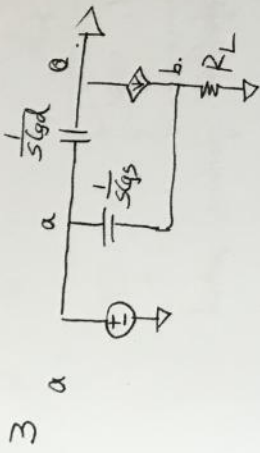This is the optimum ~~power~~ transmitted power.



branch β . tree.

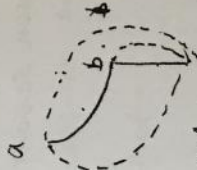

node. 3 $3-1 \Rightarrow 2$ equation

a voltage is known only need 1

Chord $5-2=3 \rightarrow 3$ equation for mesh analysis

\Rightarrow node analysis is good.

$$V_a = V_{in}$$

$$\frac{V_b}{R_L} = g_m (V_a - V_b) + s C_g (V_a - V_b)$$

~~$$V_b \Rightarrow V_b = \frac{1}{2} \left(\frac{1 + s/5 \times 10^9}{1 + s/10 \times 10^9} \right) V_a$$~~

$$V_b \left(\frac{1}{R_L} + s C_g + g_m \right) = (g_m + s C_g) V_a$$

$$\Rightarrow V_b = \left(\frac{g_m + s C_g}{\frac{1}{R_L} + s C_g + g_m} \right) V_a \quad \text{①}$$


$$= \frac{1}{2} \left(\frac{1 + s/5 \times 10^9}{1 + s/10 \times 10^9} \right) \left(\frac{10^{10}}{s^2 + 10^9} \right)$$

From ①, we can see.

V_b is not related to C_{gd} .


This can be shown as ~~follows~~ follows, which
is a ~~second~~ second method. ~~this~~

3. a.

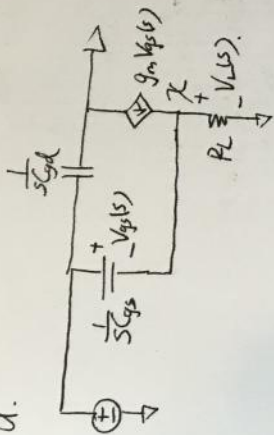

b. The circuit looks complicated, we can simplify it.

redraw the circuit, ~~we can find~~ as

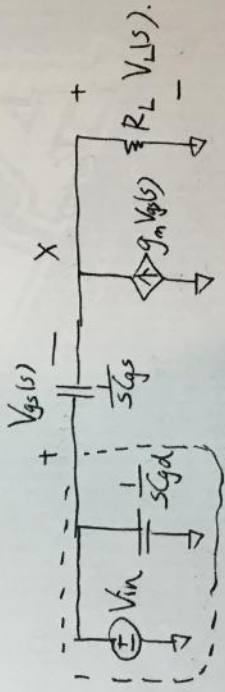


We only care about $V_{L(s)}$.

In the dot line circle, an impedance is in parallel with a voltage source. The dash line totally can be regarded as just a single voltage source (based on EE10 knowledge)

We can also do the thevenin equivalent CKT for

the dashed line part.

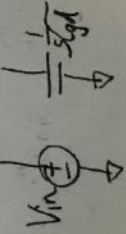open the part g, we find $V_{eq} = V_{in}$




Then set $V_{in} = 0$ We try to find Z_{eq} .

$\therefore V_{in} = 0$ in a short CKT $\Rightarrow Z_{eq} = 0$

above all the ~~gate~~ dash line part ^{part} thevenin equivalent CKT is just

a voltage source

$$+ V_{gs}(s) = V_{in} - V_L(s)$$

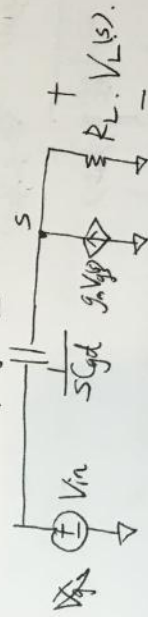

Now the CKT is very simple.

$$\text{do KCL at } s: \quad V_{gs}(s) / s g_m + g_m V_{gs}(s) = \frac{V_L(s)}{R_L} \quad \text{①}$$

$$V_{gs}(s) + V_L(s) = V_{in}(s) \quad \text{②}$$

$$\text{Combine ①, ②} \Rightarrow V_L(s) = \frac{1}{2} \left(\frac{1 + s(5 \times 10^9)}{1 + s(10 \times 10^9)} \right) \left(\frac{10^{10}}{s^2 + 10^{20}} \right)$$

C. Now doing the partial derivative of \$V_L(s)\$

$$V_L(s) = \frac{k_1}{1 + s/10 \times 10^9} + \frac{k_2}{s + 10^{10}j} + \frac{k_2^*}{s - 10^{10}j}$$

$$k_1 = V_L(s) \cdot (1 + s/10 \times 10^9) \Big|_{s=10 \times 10^9} =$$

$$V_L(s) = 5 \times 10^9 \times \frac{2s + 10^{20}}{(s + 10^{10})(s + 10^{10}j)(s + 10^{10}j)} = 5 \times 10^9 \times \left(\frac{2}{s^2 + 10^{20}} - \frac{10^{10}}{(s + 10^{10}j)(s + 10^{10}j)} \right)$$

$$\Rightarrow \frac{10^{10}}{s^2 + 10^{20}} - \frac{1}{2} \frac{10^{20}}{(s + 10^{10}j)(s + 10^{10}j)} \xrightarrow{L^{-1}} \sin 10^{10} t - \left(\frac{e^{-10^{10}t}}{4} + \frac{\sin 10^{10} t - \cos 10^{10} t}{4} \right)$$