

EE 110, Winter 2016, Midterm Exam – February 3, 2016

Instructions: This exam booklet consists of three problems, blank sheets for the solutions, reference sheets with mathematical identities, and additional blank sheets. Please follow these instructions while answering your exam:

1. Write your name and student identification number below.
2. Write the names of students to your left and right as well.
3. You have 1 hour 45 minutes to finish your exam.
4. Write your solutions in the provided blank sheets after each problem.
5. The sheets marked "Scratch..." will NOT be graded. These sheets are provided for your rough calculations only.
6. Write your solutions clearly. Illegible solutions will NOT be graded.
7. Be brief.

NAME: _____



STUDENT ID: _____



NAMES OF ADJACENT STUDENTS:

LEFT: _____

RIGHT: _____



| Problem | Score |
|----------------|--------------|
| #1 | 7 / 10 |
| #2 | 8 / 15 |
| #3 | 21 / 25 |
| Total | 36 / 50 |

+7

Problem 1: Refer to Figure 1 for this problem. Given that $L=1\text{H}$, $C=1\text{F}$, $v_C(0^-) = -1\text{V}$ and $i_L(0^-) = 1\text{A}$, determine $v_C(t)$ and $i_L(t)$ for all $t \geq 0$. Do not leave any imaginary numbers in your answers.

(10 points)


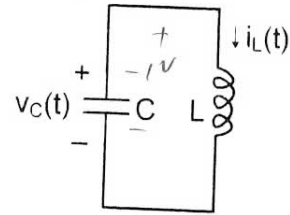
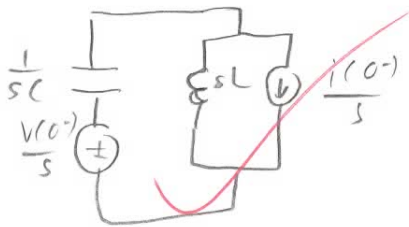


Figure 1

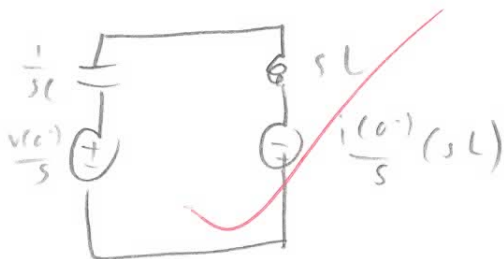

$$\frac{v_C(0^-)}{s} + \frac{i(0^-)}{s}(sL) = I(s) \left(\frac{1}{sC} + sL \right)$$

$$-\frac{1}{s} + 1 = I(s) \left(\frac{1}{s} + s \right)$$

$$\frac{s-1}{s} \left(\frac{1}{s+s} \right) = I(s)$$

$$I(s) = \frac{s-1}{s^2+1} = \frac{s-1}{(s+j)(s-j)} = \frac{k_1}{s+j} + \frac{k_2}{s-j}$$

$$s-1 = k_1(s-j) + k_2(s+j)$$

$$s = +j$$

$$+j-1 = k_1(2j)$$

$$k_1 = \frac{j-1}{2j} = \frac{1}{2} \left(1 - \frac{1}{j} \right) = \frac{1}{2} (1+j)$$

$$k_2 = \frac{1}{2} (1-j)$$

$$I(s) = \frac{\frac{1}{2} + \frac{1}{2}j}{s+j} + \frac{\frac{1}{2}(1-j)}{s-j} = \frac{1}{4} \left(\frac{(1+j)(s-j) + (1-j)(s+j)}{s^2+1} \right)$$

$$= \frac{1}{4} \left(\frac{s - j + sj + 1 + s + j - sj + 1}{s^2+1} \right) = \frac{1}{4} \left(\frac{2s+2}{s^2+1} \right)$$

- Problem 2:** Refer to the circuit shown in Figure 2. The source is an rms phasor.
- Determine the complex power delivered to the load.
 - What passive component should you connect between the terminals "x" and "y" such that maximum power is transferred to the load. What should be the value of this component?

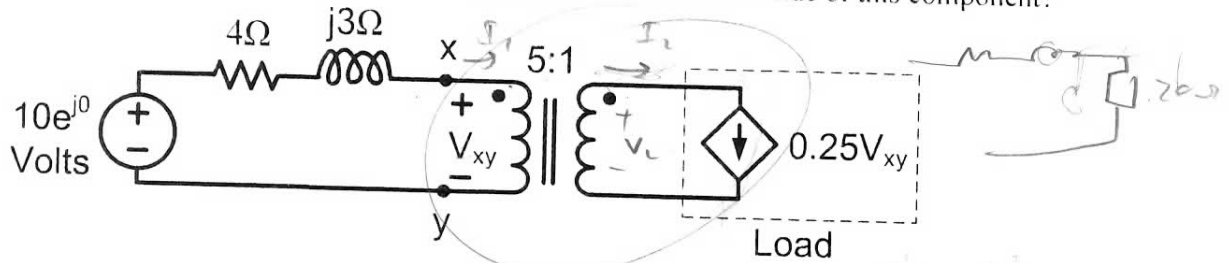


Figure 2.

(7 + 8 = 15 points)

Solution:

a)

$$\frac{V_{xy}}{V_L} = \frac{5}{1} \quad V_{xy} = 5V_L$$

$$\frac{I_1}{I_2} = \frac{1}{5} \quad I_1 = \frac{I_2}{5} = \frac{0.25V_{xy}}{5}$$

$$10 = I_1(4 + j3) + V_{xy}$$

$$10 = I_1(4 + j3) + \frac{5I_1}{0.25} = I_1(4 + j3) + 20I_1$$




$$I_1 = \frac{10}{24 + j3} = 0.41 - j0.051 \text{ A}$$

$$V_{xy} = \frac{I_1 \cdot 5}{0.25} = 8.205 - j1.026 \text{ V}$$

$$V_L = \frac{V_{xy}}{5} = 1.641 - j0.205 \text{ V}$$

$$I_2 = I_1 \cdot 5 = 2.0512 - j0.2564 \text{ A}$$
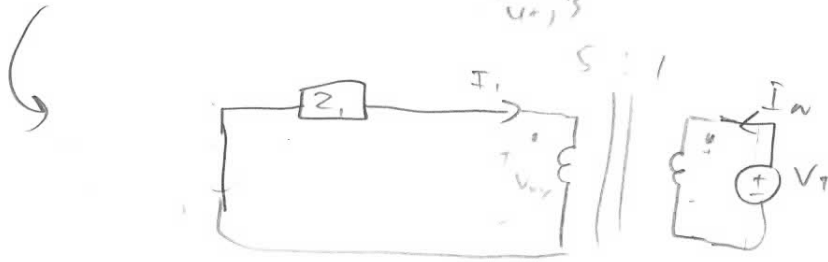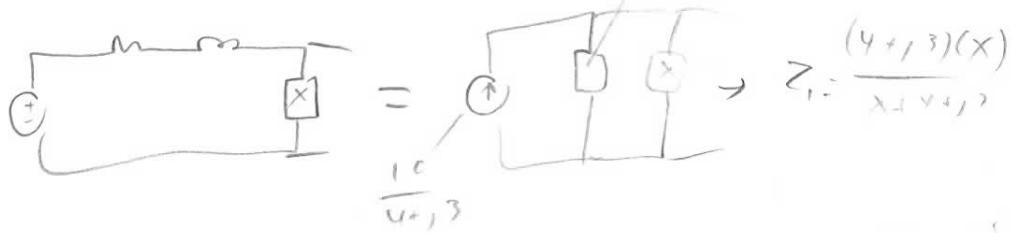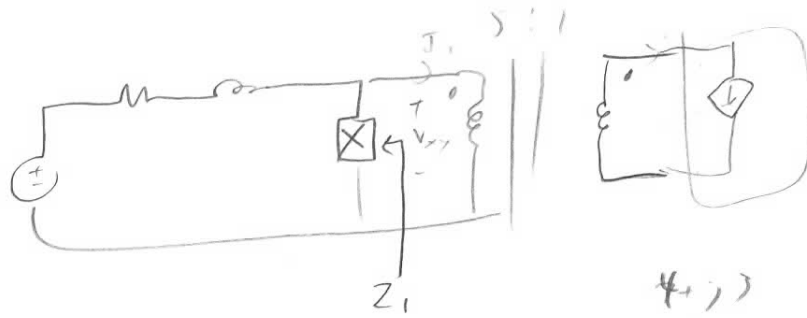
$$S = \frac{1}{2} V_L I_2^* = 1.71 - j(2.564 \cdot 10^{-2}) \text{ VAS}$$



$$I_1 = -\frac{I_N}{5} \quad V_{xy} = 5 V_T$$

$$V_{xy} = -I_1 Z_1$$

$$V_{xy} = -\left(-\frac{I_N}{5}\right) Z_1$$

$$\frac{5 V_T}{I_N} = \frac{Z_1}{5} \quad Z_{TH} = \frac{V_T}{I_N} = \frac{Z_1}{25} = \left(\frac{4+j3}{X+4+j3}\right) \left(\frac{X}{25}\right)$$

must be
→

$$0.8 - j1.2 = \left(\frac{4+j3}{X+4+j3}\right) \left(\frac{X}{25}\right)$$

$$(20 - j30)(X + 4 + j3) = X(4 + j3)$$

$$X(4 + j3 - 20 + j30) = 20 - j120 + j60 + 90$$

$$X(-16 + j33) = 110 - j60$$

$$X = -2.78 - j1.985 \, \Omega$$

for max power

Problem 3: Refer to Figure 3 for this problem.

- Draw a Laplace-domain equivalent for the circuit shown.
- Obtain an expression for $V_L(s)$ i.e. the Laplace transform of $v_L(t)$.
- Compute $v_L(t)$. Do not leave any imaginary numbers in your answers.

Note: If you are unable to derive $V_L(s)$ from parts (a) and (b), are if you are unsure of it, you can use the following expression instead for part (c).

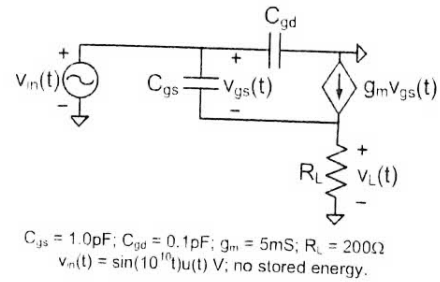


Figure 3


$$V_L(s) = \frac{1}{2} \left(\frac{1 + s(5 \times 10^9)}{1 + s/(10 \times 10^9)} \right) \left(\frac{10^{10}}{s^2 + 10^{20}} \right)$$

Notes:

- There will be a 3 point penalty if you use this expression instead of using what you get from part (b).
- Do not assume that $\bar{V}_L(s)$ is the answer to part (b).

(5 + 7 + 13 = 25 points)

Solution:

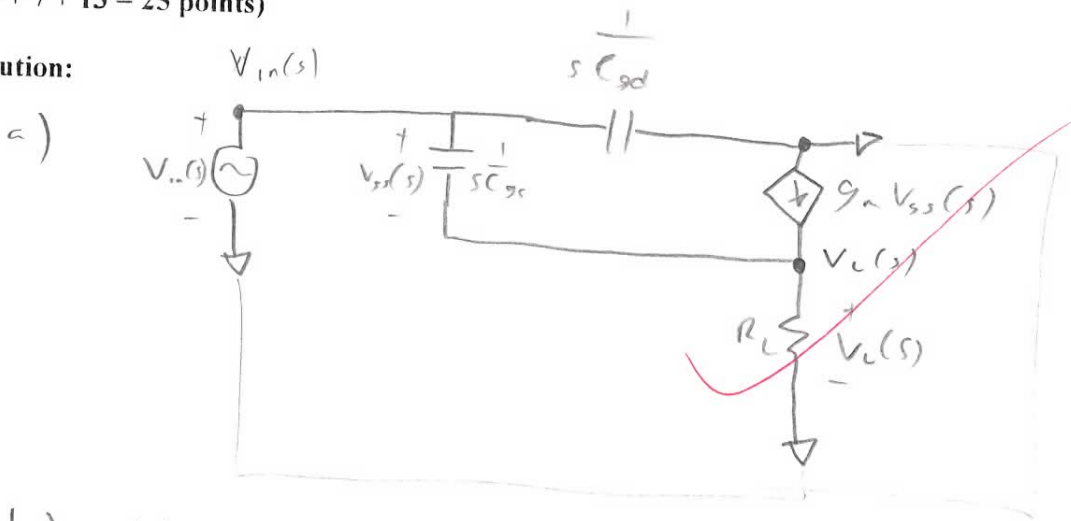

b) $V_{gs} = V_{in} - V_L$

KCL:

$$\frac{V_L(s) - V_{in}(s)}{\frac{1}{sC_{gs}}} + \frac{V_L}{R_L} = g_m V_{gs}(s)$$

$$[V_L(s) - V_{in}(s)] sC_{gs} + \frac{V_L}{R_L} = g_m (V_{in} - V_L)$$

$$V_L(s) \left(sC_{gs} + \frac{1}{R_L} + g_m \right) = V_{in} (g_m + sC_{gs})$$

$$V_L(s) = \frac{V_{in}(s) (g_m + sC_{gs})}{sC_{gs} + \frac{1}{R_L} + g_m} \rightarrow$$

~~$V_{in}(s) = \sin(10^{10}t)u(t)$~~

$$V_{in}(s) = \frac{10^{10}}{s^2 - 10^{20}}$$

$$V_c(s) = \frac{10^{10} [0.005 + (1 \cdot 10^{12})s]}{(s^2 - 10^{20}) [(1 \cdot 10^{12})s + \frac{1}{200} + 0.005]}$$

$$V_c(s) = \frac{(5 \cdot 10^7) + 0.01s}{(s^2 - 10^{20})(1 \cdot 10^{12}s + 0.01)} = \frac{(5 \cdot 10^{19}) + 1 \cdot 10^{10}s}{(s^2 - 10^{20})(5 + 10^{10})}$$

$$= \frac{k_1}{s + j10^{10}} + \frac{k_1^*}{s - j10^{10}} + \frac{k_2}{s + 10^0}$$

$$\rightarrow (5 \cdot 10^{19}) + 10^{10}s = k_1(s - j10^{10})(s + 10^0) + k_1^*(s + j10^{10})(s + 10^0) + k_2(s^2 + 10^{10})$$

$$0 + 10^{10} = 9.999 \cdot 10^9 + k_2 \quad k_2 = 1 \cdot 10^0$$



$$s = j10^{10}$$

$$(5 \cdot (10^9)) + j10^{20} = K_1^* (2j10^{10})(j10^{10} + 10^{10})$$

$$K_1^* = .25 - j.25$$

$$K_1 = .25 + j.25$$

$$5 \cdot 10^{19} + 10^{10}s = K_1 (s - j10^{10})(s + 10^{10}) + K_1^* (s + j10^{10})(s + 10^{10}) + K_2 (s^2 + 10^{20})$$

$$s = -10^{10}$$

$$5 \cdot 10^{19} - 1 = K_2 (2 \cdot 10^{20})$$

$$K_2 = .25$$

$$V_L(s) = \frac{.25 + j.25}{s + j10^{10}} + \frac{.25 - j.25}{s - j10^{10}} + \frac{.25}{s + 10^{10}} \quad V$$

$$c) \frac{(.25 + j.25)(s - j10^{10}) + (.25 - j.25)(s + j10^{10})}{s^2 + 10^{20}} \quad \& \quad \frac{.25}{s + 10^{10}}$$

$$= \frac{1.5s + .25(2)(10^{10})}{s^2 + 10^{20}} + \frac{.25}{s + 10^{10}}$$

$$\mathcal{L}^{-1} \rightarrow V_L(t) = 1.5 \cos(10^{10}t) + .5 \sin(10^{10}t) + .25 e^{-(10^{10})t} \quad V$$

Reference Sheet #1

Trigonometric Identities:

$$\sin A = \cos(A - 90^\circ) = \cos(A - \pi/2)$$

$$\cos A = \sin(A + 90^\circ) = \sin(A + \pi/2)$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(A \pm B) = \cos A \cos B \pm \sin A \sin B$$

$$\cos A + \cos B = 2 \cos((A+B)/2) \cos((A-B)/2)$$

$$\cos A - \cos B = -2 \sin((A+B)/2) \sin((A-B)/2)$$

$$\sin A + \sin B = 2 \sin((A+B)/2) \cos((A-B)/2)$$

$$\sin A - \sin B = 2 \cos((A+B)/2) \sin((A-B)/2)$$

$$\cos 2A = 2 \cos^2 A - 1 = \cos^2 A - \sin^2 A = 1 - 2 \sin^2 A$$

$$\sin 2A = 2 \sin A \cos A$$

$$a \cos A + b \sin A = \sqrt{a^2 + b^2} \cos(A - \tan^{-1}(b/a))$$

Complex Arithmetic:

$$\operatorname{Re}\{z_1 \pm z_2\} = \operatorname{Re}\{z_1\} \pm \operatorname{Re}\{z_2\}$$

$$\operatorname{Im}\{z_1 \pm z_2\} = \operatorname{Im}\{z_1\} \pm \operatorname{Im}\{z_2\}$$

$$\operatorname{Re}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Re}\{z_2\} - \operatorname{Im}\{z_1\} \operatorname{Im}\{z_2\}$$

$$\operatorname{Im}\{z_1 z_2\} = \operatorname{Re}\{z_1\} \operatorname{Im}\{z_2\} + \operatorname{Im}\{z_1\} \operatorname{Re}\{z_2\}$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$x + jy = re^{j\theta} \text{ where } r = \sqrt{x^2 + y^2}, \theta = \tan^{-1}(y/x)$$

$$re^{j\theta} = x + jy \text{ where } x = r \cos \theta, y = r \sin \theta$$

$$|z_1 z_2| = |z_1| |z_2|, \text{ angle}(z_1 z_2) = \text{angle}(z_1) + \text{angle}(z_2)$$

$$|1/z| = 1/|z|, \text{ angle}(1/z) = -\text{angle}(z)$$

$$(x + jy)^* = x - jy, \text{ angle}(z^*) = -\text{angle}(z)$$

$$(z_1 z_2)^* = (z_1)^* (z_2)^*$$

Quadratic Equations:

$$\text{The roots of } ax^2 + bx + c = 0 \text{ are } x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2}$$

Reference Sheet #2

Laplace Transforms:

$$\delta(t) \leftrightarrow 1$$

$$u(t) \leftrightarrow 1/s$$

$$tu(t) \leftrightarrow 1/s^2$$

$$e^{-at}u(t) \leftrightarrow \frac{1}{s+a}$$

$$te^{-at}u(t) \leftrightarrow \frac{1}{(s+a)^2}$$

$$\sin(\omega t)u(t) \leftrightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\cos(\omega t)u(t) \leftrightarrow \frac{s}{s^2 + \omega^2}$$

$$e^{-at} \sin(\omega t)u(t) \leftrightarrow \frac{\omega}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cos(\omega t)u(t) \leftrightarrow \frac{s+a}{(s+a)^2 + \omega^2}$$

Operational Laplace Transforms:

$$k_1 f_1(t) + k_2 f_2(t) \leftrightarrow k_1 F_1(s) + k_2 F_2(s)$$

$$\frac{df(t)}{dt} \leftrightarrow sF(s) - f(0^-)$$

$$\frac{d^2 f(t)}{dt^2} \leftrightarrow s^2 F(s) - sf(0^-) - \frac{df(0^-)}{dt}$$

$$\int_0^t f(x) dx \leftrightarrow \frac{F(s)}{s}$$

$$f(t-a)u(t-a), a > 0 \leftrightarrow e^{-as} F(s)$$

$$e^{-at} f(t) \leftrightarrow F(s+a)$$

$$tf(t) \leftrightarrow -\frac{dF(s)}{ds}$$

$$t^2 f(t) \leftrightarrow (-1)^n \frac{d^n F(s)}{ds^n}$$

$$\frac{f(t)}{t} \leftrightarrow \int_s^\infty F(u) du$$