

November 10, 2005

MID-TERM EXAMINATION

Do all work in this examination packet. There are three questions. Each counts 10 points. Good luck!

6

1. Switch S1 has been closed and switch S2 has been open for $t < 0$. At $t = 0$, S1 is opened and S2 is closed. (Both voltage sources are DC voltage sources.)


- 0 a.) (2 points) Find the characteristic equation for the sub-system governing $i(t)$ for $t > 0$.

- 0 b.) (1 point) Find the roots of the sub-system's characteristic equation.

- 1 c.) (1 point) For $t > 0$, the sub-system is (check one box): undamped; underdamped; critically damped; overdamped.

- 2 d.) (2 points) Find the quality factor (Q) of the sub-system.

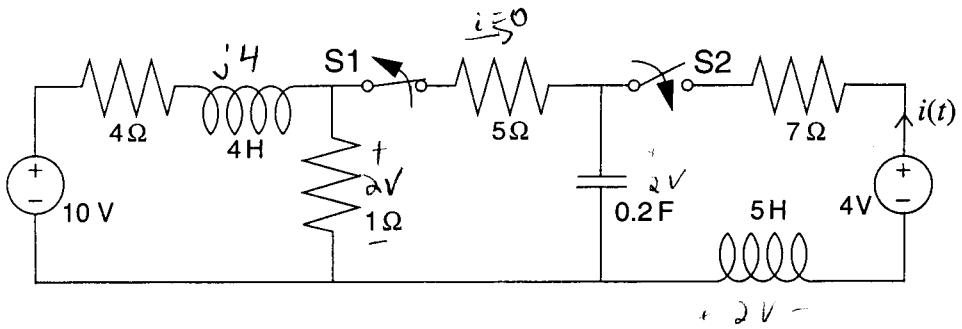- 3 e.) (4 points) Obtain $i(t)$ for $t > 0$.



$$a) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5H \cdot 0.2F}} = 1 \quad \omega_0^2 = 1 \quad \omega_0^2 > \omega^2 \text{ means} \\ \omega = \frac{R}{2L} = \frac{2\Omega}{2 \cdot 5H} = 0.7 \frac{\text{rad}}{\text{s}} \quad \omega^2 = 0.49 \quad \text{it is underdamped.}$$

$$i(t) = I_f + B_1 e^{-\omega t} \cos \omega_d t + B_2 e^{-\omega t} \sin \omega_d t$$

$$\text{where: } \omega = 0.7 \frac{\text{rad}}{\text{s}} \quad \omega_d = \sqrt{\omega_0^2 - \omega^2} = 0.714 \frac{\text{rad}}{\text{s}}$$

- b) $i_f(0) = 0$ bc no current flowed through the capacitor before the switches open.

If $i_f(0) = 0$ bc the whole voltage drop will be across the capacitor

$$\frac{dI_f(t)}{dt} = \frac{V_f}{L} = \frac{2V}{5H} = -0.4$$

$$i_f(0) = I_f + B_1(0) + 0 \\ \boxed{0 = I_f} \quad \checkmark$$

$$S_1, S_2 - \omega = \sqrt{\omega_0^2 - \omega^2} \\ \left| \begin{array}{l} S_1 = 12^\circ - 134.4^\circ \\ S_2 = 12^\circ + 134.4^\circ \end{array} \right. \quad \text{don't need these}$$

$$\frac{di(t)}{dt} = -\omega B_1 e^{-\omega t} \cos \omega_d t + B_1 e^{-\omega t} (-\omega \sin \omega_d t) \\ + -\omega B_2 e^{-\omega t} \sin \omega_d t + B_2 \omega d e^{-\omega t} \cos \omega_d t$$

$$\left| \begin{array}{l} -0.4 = B_2 \omega d \\ -0.560 = B_2 \end{array} \right.$$

d)

$$Q = \frac{\omega_0}{\beta}$$

$$\beta = \frac{1}{1.40}$$

$$\boxed{Q = .714} \quad \checkmark$$

$$\omega_{c1}, \omega_{c2} = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c1} = .521$$

$$\omega_{c2} = 1.92$$

$$\beta = \omega_{c2} - \omega_{c1}$$

$$\beta = 1.40$$


$$R = 7\Omega$$

$$L = 5H$$

$$C = .2F$$

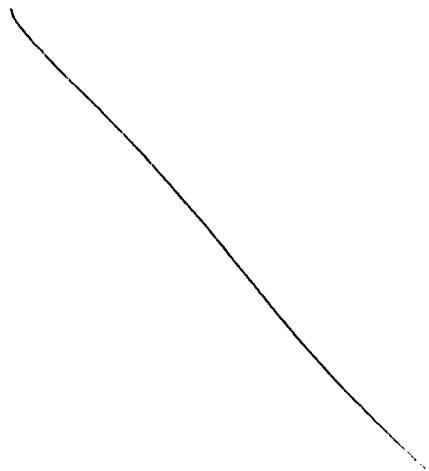e) we have all the parts from part b (see work there) so we can substitute them into our characteristic equation for our final answer

$$i(t) = -.560 e^{.7t} \sin(.714t) \quad (t > 0)$$



2. For the circuit shown, find the Thévenin equivalent with respect to the terminals c, d.


$$\text{Ansatz: } I_1 \text{ short circuit (L2)} \quad 8/10$$

$$\left\{ \begin{array}{l} 4j5 + I_1 5 + I_2 j5 + I_2 j20 = 0 \\ 45I_2 + I_2 j125 + I_1 j20 = 0 \end{array} \right.$$

$$\left\{ \begin{array}{l} I_1 (5 + j5) + I_2 (j20) = 425 \\ I_1 (j20) + I_2 (45 + j125) = 0 \end{array} \right.$$

$$\left\{ \begin{array}{l} I_1 (5 + j5) + I_2 (j20) = 425 \\ I_1 (j20) + I_2 (45 + j125) = 0 \end{array} \right.$$

$$I_1 = \frac{425 - I_2 (j20)}{5 + j5}$$

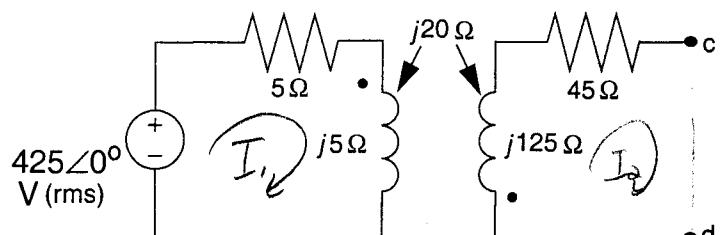

$$I_2 = -10 \quad -10 \angle 180^\circ$$

$$\left(\frac{4j5 - I_2 (j20)}{5 + j5} \right) (j20) + I_2 (45 + j125) = 0$$

$$\frac{4j5}{5 + j5} (j20) = -\frac{I_2 (j20)}{5 + j5} - I_2 (45 + j125)$$

find Z_{eq}

$$Z_{LOAD} = 5 + 5j$$

$$Z_{LOAD}^* = 5 - 5j$$

$$Z_{eq} = 45 + 125j + \left(\frac{-j20}{|5 + 5j|} \right)^2 (5 - 5j)$$

$$Z_{eq} = 45 + 125j + \left(\frac{-j20}{5\sqrt{2}} \right)^2 (5 - 5j)$$


$$Z_{eq} = 45 + 125j + (-8)(5 - 5j)$$


$$Z_{eq} = 45 + 125j + 40(-40j)$$

$$Z_{eq} = \frac{85}{85} + \frac{165j}{85} = +165 \angle 88.3^\circ \Omega$$

$$V_{th} = I_2 \cdot Z_{eq} = -850 \angle 180^\circ$$
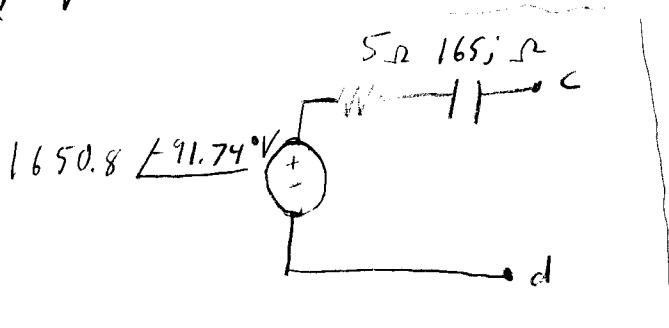
$$V_{th} = 1650.8 \angle -91.74^\circ V$$



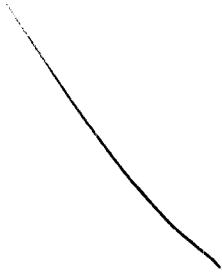


7

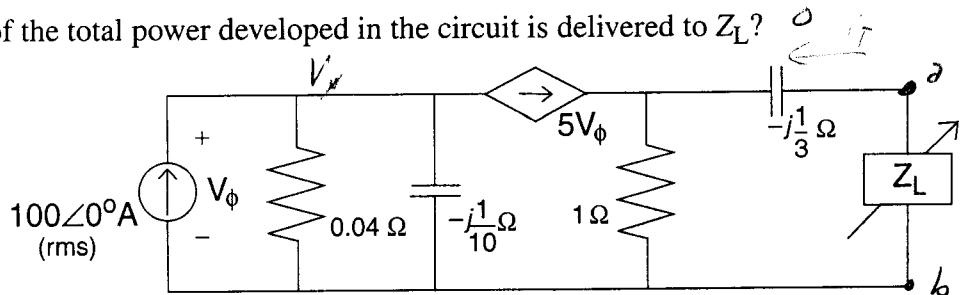3. The load impedance Z_L for the circuit shown is adjusted until maximum average power is delivered to Z_L .

a.) (8 points) Find the maximum average power delivered to Z_L . 7

b.) (2 points) What percentage of the total power developed in the circuit is delivered to Z_L ? 7



first find thevenin equivalent circuit.

$$-100 + \frac{V_\phi}{0.04} + \frac{V_\phi}{-j\frac{1}{10}} - 5V_\phi = 0 \quad (1)$$

$$V_\phi \left(\frac{1}{0.04} - \frac{1}{j} - 5 \right) = 100$$

$$V_\phi = 4.47 \angle -26.57^\circ = 4 - j2$$

$$V_{ab} : V_{12} = V_\phi = 4 - j2$$


apply a test voltage between a:b to find the test current

$$V_T = i_T \cdot -j\frac{1}{3} \Omega + (5V_\phi + i_T) \cdot 1\Omega \quad \frac{V_\phi}{0.04} + \frac{V_\phi}{-j\frac{1}{10}} - 5V_\phi = 0$$

$$V_T = i_T \cdot -j\frac{1}{3} \Omega + i_T \cdot 1\Omega \quad V_0 = 0$$

$$\frac{V_T}{i_T} = Z_{th} = 1 + \frac{j}{3}$$

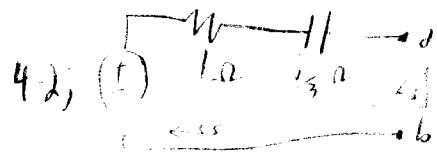using V_{th} and Z_{th} we can reduce the circuit:



Thus, Z_L maximum power at $Z_L^* = \left(1 - \frac{j}{3} \right) \Omega$

$$i_s = \frac{4-j}{12-\frac{1}{3}+j2+\frac{1}{3}} = \frac{4-j}{2} = 2-j$$

$$P = |I_{rms}|^2 R$$

$$P = (\sqrt{2^2 + 1^2})^2 R$$

$$P = (\sqrt{5})^2 / R$$

$$\boxed{P = 5 \text{ W}}$$

b) $S_{0.04\Omega} = V_p^2 / 0.04\Omega$

$$S_{0.04\Omega} = 48 - j64 \text{ VA}$$

$$S_{j\frac{1}{10\Omega}} = V_p^2 / -j\frac{1}{10\Omega}$$

$$S_{j\frac{1}{10\Omega}} = -\frac{8}{5} - \frac{6}{5}j$$