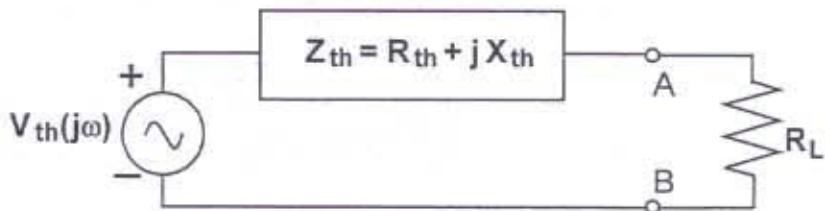


MID-TERM EXAMINATION

Do all work in this examination packet. There are four questions. Each counts 25 points. Good luck!


- 1A. (10 points) The circuit to the left of nodes A and B has a Thevenin impedance Z_{th} for which $R_{th} > 0$ and $X_{th} \neq 0$. The resistor R_L is required to have a value that will maximize the power that will be delivered to it.




a.) Derive a formula for the required value of R_L as a function of the R_{th} and X_{th} components of the Thevenin impedance Z_{th} .

b.) Let $R_{th} = 12 \Omega$ and $X_{th} = 5 \Omega$, and use your derived formula to find this optimum value of R_L .

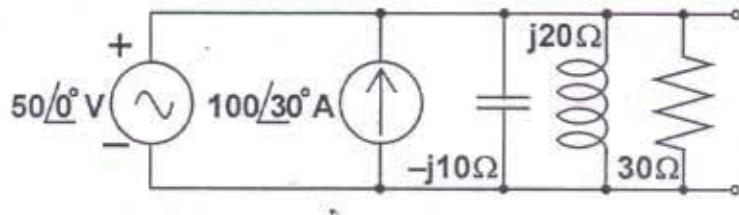
- 1B. (5 points) Find the Thevenin equivalent circuit for this circuit:



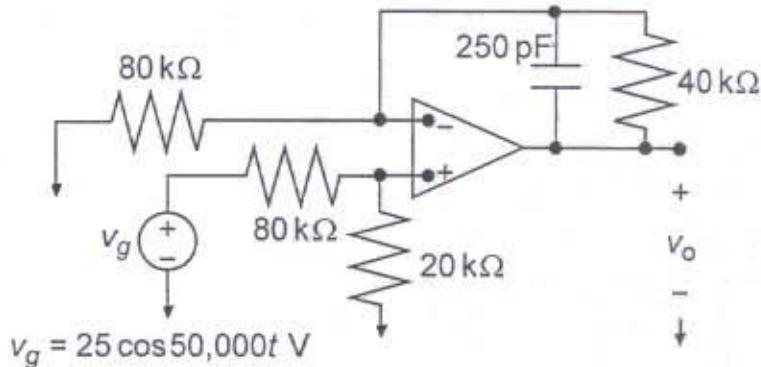
- 1C. (5 points) The op amp in this circuit is ideal. Find the steady-state expression for $v_o(t)$.



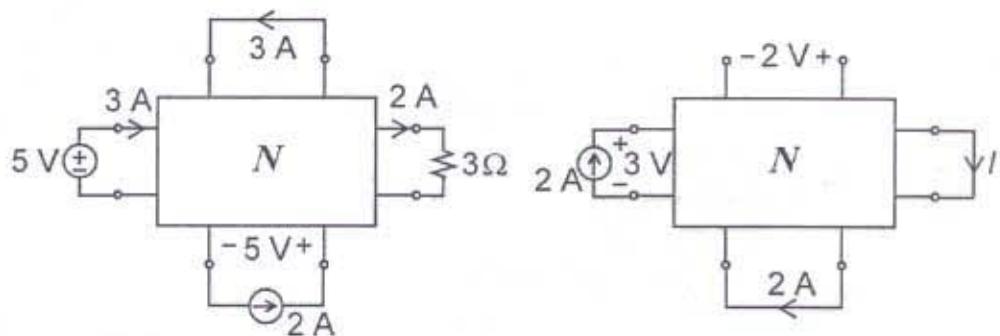- 1D. (5 points) When an eight-terminal resistive network N is subjected to various external connections, the results are as indicated in the figure below. Determine the current I .



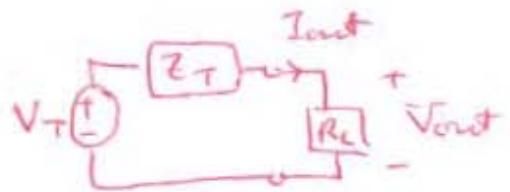1A. a) $V_{out} = \frac{R_L}{R_T + jX_T + R_L} V_T$



Power delivered = $P = \frac{1}{2} \operatorname{Re}(V_{out} * I_{out}^*)$

$$= \frac{1}{2} \operatorname{Re} \left(\frac{R_L}{R_T + jX_T + R_L} V_T \frac{V_T^*}{(R_T + jX_T + R_L)^*} \right)$$

$$= \frac{1}{2} |V_T|^2 \frac{R_L}{|R_T + jX_T + R_L|^2} \quad \begin{matrix} \text{To maximize this,} \\ \text{set deriv w.r.t. } R_L \\ \Leftarrow \text{to zero.} \end{matrix}$$

$$\frac{\partial P}{\partial R_L} = \frac{1}{2} \frac{1^2 \times 1 - R_L 2(R_T + R_L)}{[(R_T + R_L)^2 + X_T^2]^2}$$

$$\begin{aligned} |R_T + jX_T + R_L|^2 &= (R_T + R_L)^2 + X_T^2 \\ &= R_T^2 + 2R_T R_L + R_L^2 + X_T^2 \end{aligned}$$

$$= 0 \Leftrightarrow (R_T + R_L)^2 + X_T^2 = 2R_T R_L + 2R_L^2$$

$$\Leftrightarrow R_T^2 + 2R_T R_L + R_L^2 = 2R_T R_L + 2R_L^2 + X_T^2$$

$$\Leftrightarrow R_T^2 + X_T^2 = R_L^2 \Leftrightarrow R_L = \sqrt{R_T^2 + X_T^2}$$

$$\Leftrightarrow R_L = |R_T + jX_T|$$

$$\Leftrightarrow R_L = |Z_T|$$

b) $R_L = \sqrt{12^2 + 5^2} = \sqrt{144 + 25} = \sqrt{169} = 13,$


$$\boxed{R_L = 13 \Omega}$$

1B. To get Th. Impedance: 1) Set midday sources to zero



2) Get open-circ. voltage: $V_{oc} = 50 \angle 0^\circ$

\Rightarrow Th. Eq. Ch. i

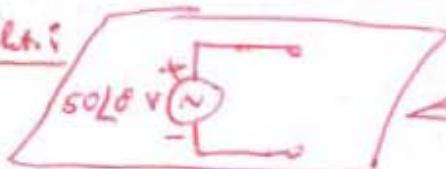

That's IT !!

1c. $V_g = 25 \angle 0^\circ V \Rightarrow V_+ = \frac{20}{100} V_g = 5 \angle 0^\circ$

~~At node 0~~ $V_- = V_+ = 5 \angle 0^\circ V$

$$S_0: \frac{5}{80,000} + \frac{5 - V_0}{Z_p} = 0$$

$$Z_p = -j80,000 \parallel 40,000$$


$$= 32,000 - j16,000 \Omega$$

$$V_0 = \frac{5Z_p}{80,000} + 5 = 7 - j1 = 7.07 \angle -8.13^\circ V$$

$$\Rightarrow V_o(t) = 7.07 \cos(50,000t - 8.13^\circ) V$$

$$j\omega C = \frac{1}{5 \times 10^4 \parallel 250 \times 10^{-12}} = -j80,000$$

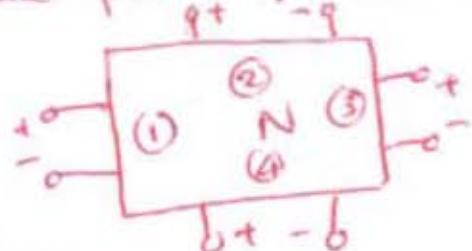1d. Use same port polarities for both circuits:



Use Thévenin's Theorem

$$\sum_{\text{4 ports}} N_L i_{12} = \sum_{\text{4 ports}} N_R i_L$$


ports							
①	②	③	④	①	②	③	④
N_L	5 0 6 -5			N_R	3 -2 0 0		
i_L	3 3 -2 -2			i_R	2 0 -1 2		

$$\sum N_L i_R = 5 \times 2 + 0 \times 0 + 6 \times (-1) + (-5) \times 2 = -6 I$$

$$\sum N_R i_L = 3 \times 3 + (-2) \times 3 + 0 \times (-2) + 0 \times (-2) = 9 - 6 = 3$$

$$\text{So: } -6 I = 3 \Rightarrow I = -\frac{1}{2} A$$

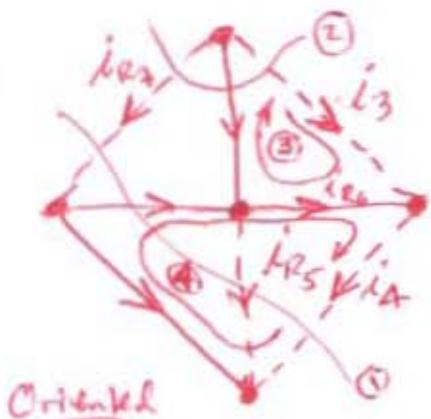2. (25 points) Write state equations for this circuit.




Graph of circuit having a proper tree.

State variables are
 V_1, V_2, i_3, i_4

We need to express some resistor currents and/or voltages in terms of state variables.


We need $(i_{e5}, i_{e7}, V_{R6} \text{ & } V_{R8})$.

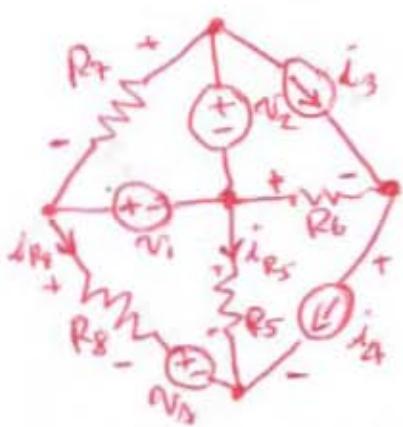This "graph" containing "sources" & resistors can help:



Easy ones: $i_{R7} = \frac{1}{R7}(V_2 - V_1)$; $V_{R6} = R6(i_4 - i_3)$

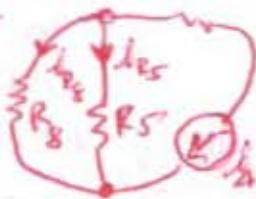
The others:
We can write two simultaneous eqns. in order to solve for i_{e5} & i_{e7} . Here's another way: (Use superposition) First, just turn on source i_4 . Then, we have this circuit



By current division:

$$i_{e5} = -\left(\frac{R8}{R5+R8}\right)i_4$$
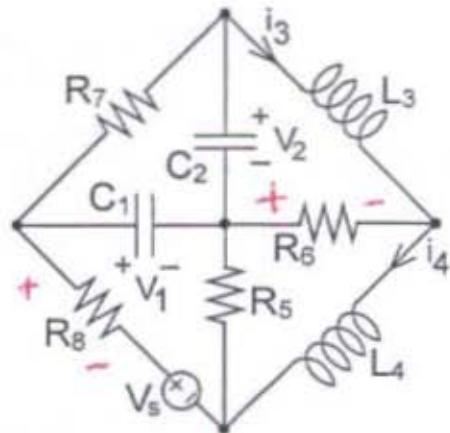
$$i_{e7} = -\left(\frac{R5}{R5+R8}\right)i_4$$



Fundamental cut-set equations:
(for the selected tree)

$$\textcircled{1} \quad C_1 \frac{dv_1}{dt} = i_4 + i_{e5} + i_{R7}$$


$$\textcircled{2} \quad C_2 \frac{dv_2}{dt} = -i_3 - i_{e7}$$

Fundamental loop eqns (for tree):

$$\textcircled{3} \quad L_3 \frac{di_3}{dt} = V_2 + V_{R6}$$

$$\textcircled{4} \quad L_4 \frac{di_4}{dt} = -V_1 - V_{R6} + V_{R8} + V_5$$

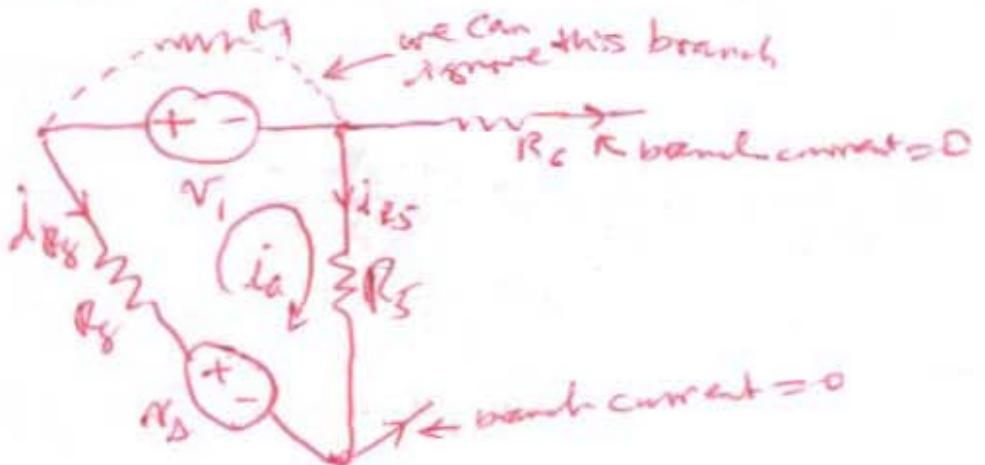Similarly, if we just turn on V_1 and V_8 , we have



$$\text{Loop current } i_A = \frac{V_8 - V_1}{R_5 + R_8} = -i_{R_8} = i_{R_5}$$

The other two sources (V_2 & i_3), if turned on exclusively ^(by themselves) will not cause currents i_{R_5} & i_{R_8} to flow.

Thus, the sought after resistor currents are:

$$i_{R_5} = -\left(\frac{R_8}{R_5 + R_8}\right) i_A + \left(\frac{1}{R_5 + R_8}\right) (V_s - V_1)$$

$$i_{R_8} = -\left(\frac{R_5}{R_5 + R_8}\right) i_A - \left(\frac{1}{R_5 + R_8}\right) (V_s - V_1)$$

$$\begin{cases} C_1 \frac{dV_1}{dt} = i_A - \left(\frac{R_8}{R_5 + R_8}\right) i_A + \left(\frac{1}{R_5 + R_8}\right) V_s - \left(\frac{1}{R_5 + R_8}\right) V_1 + \frac{1}{R_7} V_2 - \frac{1}{R_7} V_1 \\ C_2 \frac{dV_2}{dt} = -i_3 - \frac{1}{R_7} V_2 + \frac{1}{R_7} V_1 \\ L_3 \frac{di_3}{dt} = V_2 + R_6 i_4 - R_6 i_3 \\ L_4 \frac{di_4}{dt} = -V_1 + R_6 i_3 - R_6 i_4 - \left(\frac{R_5 R_8}{R_5 + R_8}\right) i_A + \left(\frac{R_8}{R_5 + R_8}\right) V_1 + \left(\frac{R_8}{R_5 + R_8}\right) V_s + V_0 \end{cases}$$

This can be "cleaned up" a bit by combining some terms:

$$\left\{ \begin{array}{l} C_1 \frac{dV_1}{dt} = \frac{R_5}{R_5+R_8} i_4 - \frac{R_5+R_8+R_7}{(R_5+R_8)R_7} V_1 + \frac{1}{R_7} V_2 + \frac{1}{R_5+R_8} V_3 \\ C_2 \frac{dV_2}{dt} = -i_3 + \frac{1}{R_7} V_1 - \frac{1}{R_7} V_2 \\ L_3 \frac{di_3}{dt} = V_2 - R_6 i_3 + R_6 i_4 \\ L_4 \frac{di_4}{dt} = -\frac{R_5}{R_5+R_8} V_1 + R_6 i_3 - \frac{R_6(R_5+R_8)+R_5 R_8}{(R_5+R_8)R_7} i_4 + \frac{R_5}{R_5+R_8} V_3 \end{array} \right.$$

And finally, in matrix form:


$$\begin{pmatrix} \frac{dV_1}{dt} \\ \frac{dV_2}{dt} \\ \frac{di_3}{dt} \\ \frac{di_4}{dt} \end{pmatrix} = \begin{pmatrix} -\frac{R_5+R_8+R_7}{C_1(R_5+R_8)R_7} & \frac{1}{C_1 R_7} & 0 & \frac{R_5}{C_1(R_5+R_8)} \\ \frac{1}{C_2 R_7} & -\frac{1}{C_2 R_7} & -\frac{1}{C_2} & 0 \\ 0 & \frac{1}{L_3} & -\frac{R_6}{L_3} & -\frac{R_6}{L_3} \\ -\frac{R_5}{L_4(R_5+R_8)} & 0 & \frac{R_6}{L_4} & -\frac{R_6(R_5+R_8)+R_5 R_8}{L_4(R_5+R_8)} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ i_3 \\ i_4 \end{pmatrix} + \begin{pmatrix} 0 \\ 0 \\ i_3 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} \frac{1}{C_1(R_5+R_8)} \\ 0 \\ 0 \\ \frac{R_5}{L_4(R_5+R_8)} \end{pmatrix} \begin{pmatrix} V_3 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

3. (25 points) The load impedance Z_L for this circuit is adjusted until maximum average power is delivered to Z_L .


a) Find the maximum average power delivered to Z_L .

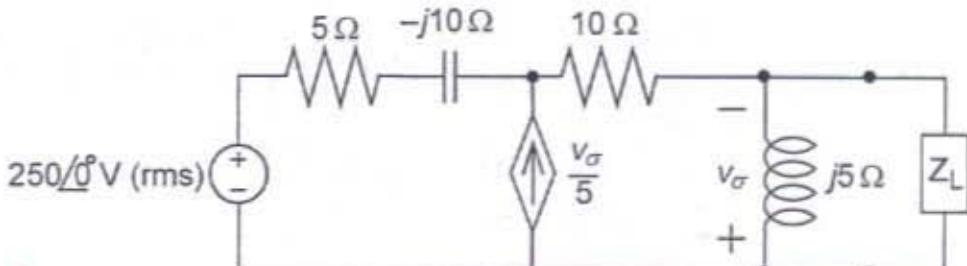b) What percentage of the total power developed in the circuit is delivered to Z_L ?



(a)

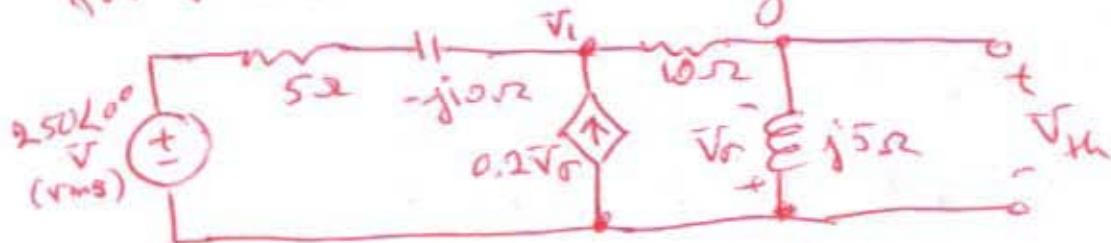First let's get the Thevenin's equivalent circuit for the circuit seen by the load impedance:




$$\left\{ \begin{array}{l} \frac{V_1 - 250}{5 - j10} - 0.2 V_o + \frac{V_1}{10 + j5} = 0 \\ V_o = \frac{-j5}{10 + j5} V_1 = \frac{-jV_1}{2 + j1} \\ -0.2 V_o = \frac{j0.2 V_1}{2 + j1} \end{array} \right. \Rightarrow V_1 [\frac{1}{5 - j10} + \frac{j0.2}{2 + j1} + \frac{1}{10 + j5}] = \frac{250}{5 - j10}$$


$$\Rightarrow V_1 = 10(10 + j5)$$

$$\therefore V_{th} = \frac{j5}{10 + j5} V_1 = j50 = 50∠90^\circ \text{ V (rms)}$$

Short-circuit currents:

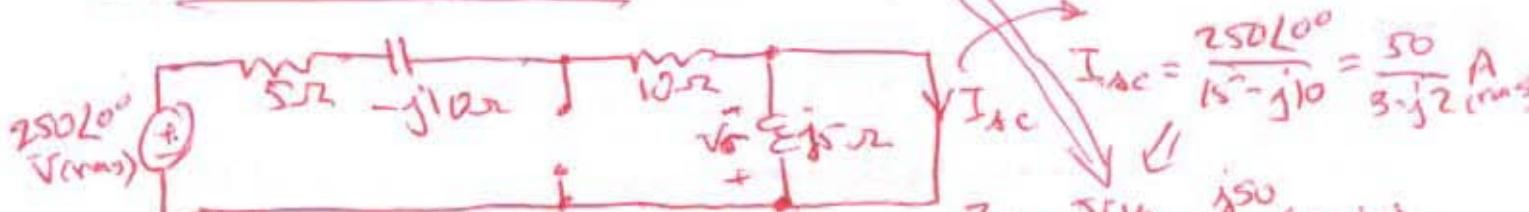

For max avg. power delivered to Z_L :

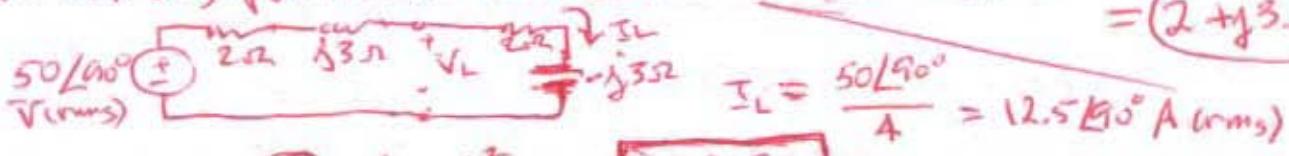


$$\Rightarrow P = (12.5)^2 (2) = 312.5 \text{ W}$$

$$I_L = \frac{50∠90^\circ}{4} = 12.5∠90^\circ \text{ A (rms)}$$

$$Z_{th} = \frac{V_{th}}{I_{sc}} = \frac{j50}{50} (3 - j2) = (2 + j3) \Omega$$

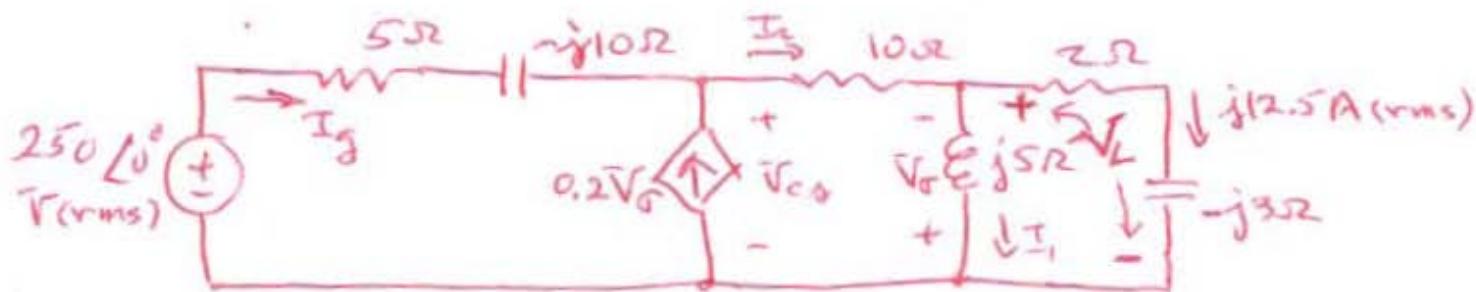(b) In the original circuit, with the optimized Z_L we have:



$$V_L = (2 - j3)(j12.5) = 37.5 + j25 \text{ V(rms)}$$

$$\Rightarrow I_1 = \frac{V_L}{j5} = \frac{37.5 + j25}{j5} = 5 - j7.5 \text{ A (rms)}$$

$$\Rightarrow I_2 = I_1 + I_L = 5 - j7.5 + j12.5 = 5 + j5 \text{ A (rms)}$$

$$\Rightarrow V_{cr} = V_L + 10I_2 = 37.5 + j25 + 50 + j50 \\ \Rightarrow V_r = -V_L = -37.5 - j25 \\ \Rightarrow 0.2V_r = -7.5 - j5 = I_{cs}$$

So complex power absorbed by the dependent source is

$$S_{cr} = V_{cr}(-I_{cs})^* = (87.5 + j75)(7.5 - j5)^* \\ = (87.5 + j75)(7.5 - j5) = (656.25 + 375) \\ + j(562.5 - 437.5) \\ = \underline{1031.25 + j125 \text{ VA}}$$

Therefore, in this circuit the dependent source is absorbing 1031.25 W and 125 magnetizing vars.

(Only the independent voltage source is developing power.)



$$I_g = -0.2V_r + I_2 = 7.5 + j5 + 5 + j5 = 12.5 + j10 \text{ A (rms)}$$

$$S_d = (250)(-I_g)^* = (250)(-12.5 + j10) = -3125 + j2500 \text{ VA}$$

$$\therefore P_{dev} = 3125 \text{ W} \Rightarrow \% \text{ of dev. per det.} = \frac{3125}{3125}(100) = \boxed{100\%}$$

4. (25 points) This circuit is in the sinusoidal steady state with angular frequency ω .

- a) Write the circuit's mesh equations in matrix form, with matrix and vector elements made explicit in terms of R , L , C , ω , etc., variables.
- b) Determine the driving-point impedance Z_{in} when $\omega = 2$ rad/sec. and $R = 2 \Omega$, $L_1 = 2 H$, $L_2 = 4 H$, $|M| = 1 H$, $C = 1/2 F$, $\mu = 10$.

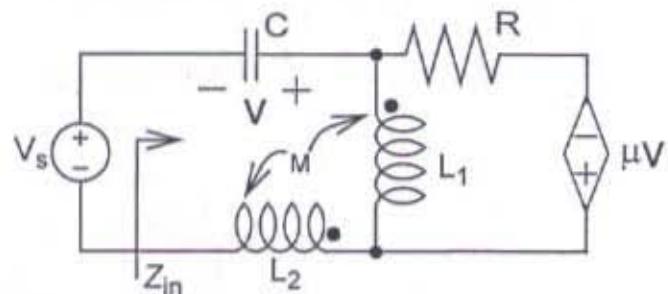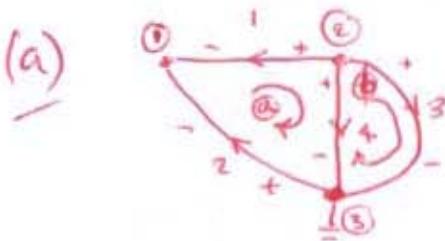

$$\begin{aligned} -V_1 + V_2 + V_4 &= 0 \\ V_3 - V_4 &= 0 \end{aligned} \quad \left. \begin{array}{l} \text{from } \Sigma \text{ of mesh KVL} \\ \text{from } \Sigma \text{ of mesh KCL} \end{array} \right.$$

$$\left\{ \begin{array}{l} I_1 = -I_a \\ I_2 = I_a \\ I_3 = I_b \\ I_4 = I_a - I_b \end{array} \right. \quad \begin{array}{l} \text{branch currents} \\ \text{in terms of} \\ \text{mesh currents} \end{array}$$

$$V_1 = \left(\frac{1}{j\omega C} \right) I_1 = -\frac{1}{j\omega C} I_a$$

$$V_2 = (j\omega L_2) I_2 + (j\omega M) I_{4,1} = j\omega L_2 I_a + j\omega M (I_a - I_b) - V_4$$

$$V_3 = R I_3 - \mu V \quad (\text{where } V = V_1) \Rightarrow V_3 = R I_b + \mu \left(\frac{1}{j\omega C} \right) I_a$$

$$V_4 = (j\omega L_1) I_4 + (j\omega M) I_2 = j\omega L_1 (I_a - I_b) + j\omega M I_a$$

Solving Σ of mesh KVL:

$$\frac{1}{j\omega C} I_a + j\omega L_2 I_a + j\omega M (I_a - I_b) - V_4 + j\omega L_1 (I_a - I_b) + j\omega M I_a = 0$$

$$R I_b + \mu \left(\frac{1}{j\omega C} \right) I_a - j\omega L_1 (I_a - I_b) - j\omega M I_a = 0$$

$$\Rightarrow \boxed{\begin{bmatrix} \frac{1}{j\omega C} + j\omega L_2 + j\omega M + j\omega L_1 & -j\omega L_1 - j\omega M \\ \frac{\mu}{j\omega C} - j\omega L_1 - j\omega M & R + j\omega L_1 \end{bmatrix} \begin{pmatrix} I_a \\ I_b \end{pmatrix} = \begin{pmatrix} V_4 \\ 0 \end{pmatrix}}$$

(b) Substituting specific numerical values into the mesh eqns.:

$$\left[\begin{array}{cc|c} \frac{1}{j(2)(\frac{1}{2})} + j2(4+2+1+2) & -j2(2+1) \\ \frac{-10}{j(2)(\frac{1}{2})} - j2(2+1) & 2+j(2)(2) \end{array} \right] \begin{pmatrix} I_a \\ I_b \end{pmatrix} = \begin{pmatrix} V_s \\ 0 \end{pmatrix}$$

$$\Rightarrow \left[\begin{array}{cc|c} -j + j16 & -j6 \\ -j10 - j6 & 2 + j4 \end{array} \right] \begin{pmatrix} I_a \\ I_b \end{pmatrix} = \begin{pmatrix} V_s \\ 0 \end{pmatrix}$$

$$\Rightarrow \left[\begin{array}{cc|c} j15 & -j6 \\ -j16 & 2+j4 \end{array} \right] \begin{pmatrix} I_a \\ I_b \end{pmatrix} = \begin{pmatrix} V_s \\ 0 \end{pmatrix}$$

Using Cramer's rule: $I_a = \frac{\begin{vmatrix} V_s & -j6 \\ 0 & 2+j4 \end{vmatrix}}{\begin{vmatrix} j15 & -j6 \\ -j16 & 2+j4 \end{vmatrix}}$

$$\Rightarrow I_a = \frac{(2+j4)V_s}{j30 - 60 + 96} = \frac{(2+j4)V_s}{36 - j30}$$

$$= \frac{(2+j4)(36 - j30)}{36^2 + 30^2} V_s$$

$$= \frac{(72 + 120) + j(144 - 60)}{2196} V_s$$

$$= \frac{192 + j84}{2196} V_s = \left(\frac{48 + j21}{549} \right) V_s$$

$$\text{Clearly, } Z_{in} = \frac{V_s}{I_a} = \frac{549}{48 + j21} = \frac{549(48 - j21)}{48^2 + 21^2}$$

$$= \frac{26,352 - j11,529}{2,304 + 441} = \frac{26,352}{2,745} - j \frac{11,529}{2,745}$$

$$\boxed{Z_{in} = 9.6 - j4.2}$$

Reference Sheet

Trigonometric Identities

$$\sin \theta = \cos(\theta - 90^\circ) = \cos\left(\theta - \frac{\pi}{2}\right)$$

$$\cos \theta = \sin(\theta + 90^\circ) = \sin\left(\theta + \frac{\pi}{2}\right)$$

$$\cos(\theta + \phi) = \cos \theta \cos \phi - \sin \theta \sin \phi$$

$$\cos(\theta - \phi) = \cos \theta \cos \phi + \sin \theta \sin \phi$$

$$\sin(\theta + \phi) = \sin \theta \cos \phi + \cos \theta \sin \phi$$

$$\sin(\theta - \phi) = \sin \theta \cos \phi - \cos \theta \sin \phi$$

$$\cos \theta + \cos \phi = 2 \cos \frac{(\theta + \phi)}{2} \cos \frac{(\theta - \phi)}{2}$$

$$\cos \theta - \cos \phi = -2 \sin \frac{(\theta + \phi)}{2} \sin \frac{(\theta - \phi)}{2}$$

$$\sin \theta + \sin \phi = 2 \sin \frac{(\theta + \phi)}{2} \cos \frac{(\theta - \phi)}{2}$$

$$\sin \theta - \sin \phi = 2 \cos \frac{(\theta + \phi)}{2} \sin \frac{(\theta - \phi)}{2}$$

$$\cos 2\theta = 2 \cos^2 \theta - 1 = 1 - 2 \sin^2 \theta = \cos^2 \theta - \sin^2 \theta$$

$$A \cos \theta + B \sin \theta = (A^2 + B^2)^{1/2} \cos(\theta - \text{atan}(B/A))$$

Complex Arithmetic

$$\operatorname{Re}(z_1 + z_2) = \operatorname{Re}(z_1) + \operatorname{Re}(z_2)$$

$$\operatorname{Im}(z_1 + z_2) = \operatorname{Im}(z_1) + \operatorname{Im}(z_2)$$

$$\operatorname{Re}(z_1 z_2) = \operatorname{Re}(z_1)\operatorname{Re}(z_2) - \operatorname{Im}(z_1)\operatorname{Im}(z_2)$$

$$\operatorname{Im}(z_1 z_2) = \operatorname{Re}(z_1)\operatorname{Im}(z_2) + \operatorname{Im}(z_1)\operatorname{Re}(z_2)$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$Z = X + jY \Rightarrow Z = Re^{j\theta}, \text{ where } R = (X^2 + Y^2)^{1/2} \text{ and } \theta = \operatorname{atan}(Y/X)$$

$$Z = Re^{j\theta} \Rightarrow Z = X + jY \text{ where } X = R\cos\theta \text{ and } Y = R\sin\theta$$

$$|X + jY| = (X^2 + Y^2)^{1/2}$$

$$\angle(X + jY) = \operatorname{atan}(Y/X)$$

$$|Z_1 Z_2| = |Z_1||Z_2|; \quad \angle(Z_1 Z_2) = \angle Z_1 + \angle Z_2$$

$$|1/Z| = 1/|Z|; \quad \angle(1/Z) = -\angle Z$$

$$(X + jY)^* = X - jY$$

$$(Re^{j\theta})^* = Re^{-j\theta}$$

$$(Z_1 Z_2)^* = (Z_1^*)(Z_2^*); \quad (Z_1/Z_2)^* = (Z_1^*)/(Z_2^*); \quad (Z_1 \pm Z_2)^* = (Z_1^*) \pm (Z_2^*)$$