
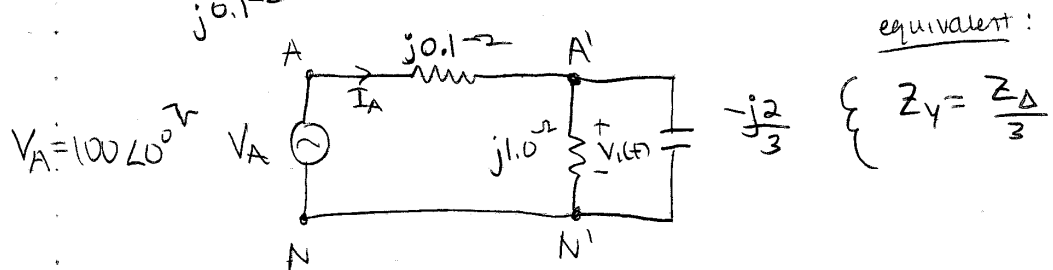


5/11

Midterm Exam Solutions

#1

Multiple choice

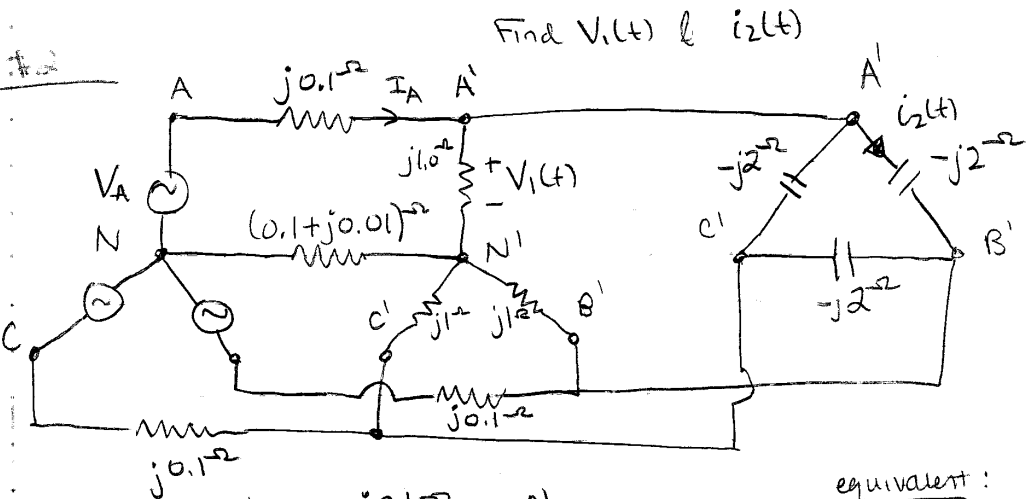

$$I_A = \frac{100 \angle 0^\circ}{j0.1 + \frac{(j1.0)(-j\frac{2}{3})}{j1.0 - j\frac{2}{3}}} = \frac{100 \angle 0^\circ}{j0.1 - j2} = j52.63 \text{ A}$$

$$\rightarrow I_A = 52.63 \angle 90^\circ \text{ A}$$

$$V_1 = (j52.63)(-j2) = 105.26 \angle 0^\circ \text{ V}$$

$$V_1(t) = 105.26 \sqrt{2} \cos(2\pi(60)t) \text{ V}$$


$$V_{AB'} = \sqrt{3} V_{A'N'} \angle 30^\circ = \sqrt{3} (105.26) \angle 30^\circ \text{ V}$$

$$\underline{V_{A'B'}} = 182.15 \angle 30^\circ \text{ V}$$

$$\underline{I_2} = \frac{V_{A'B'}}{-j2} = \frac{182.15 \angle 30^\circ}{2 \angle -90^\circ} = 91 \angle 120^\circ \text{ A}$$

$$i_2(t) = -91\sqrt{2} \cos(\omega t + 120^\circ) \text{ A}$$

Problem #3

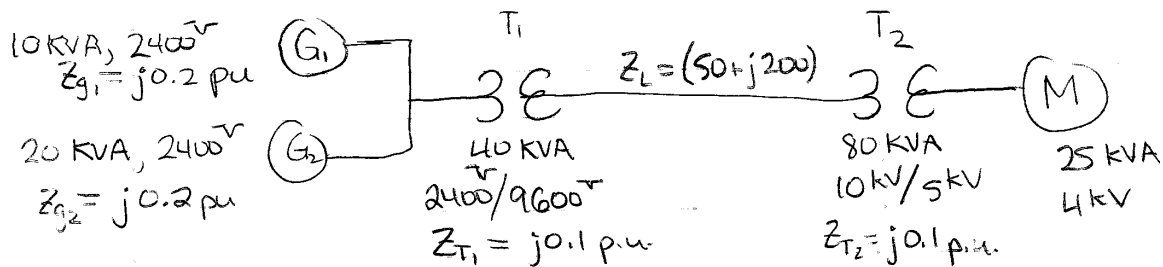

$$S_B = 100 \text{ kVA}, V_{B(G)} = 2400 \text{ V} \text{ (at generator-side)}$$

$$V_{B(L)} = 2400 \left(\frac{9600}{2400} \right) = \underline{9600 \text{ V}} \text{ (base at line)}$$

$$V_{B(M)} = 9600 \left(\frac{5 \text{ kV}}{10 \text{ kV}} \right) = \underline{4800 \text{ V}} \text{ (at motor)}$$

New
p.u.
impedances

$$Z_{g1} = j0.2 \left(\frac{100 \text{ kVA}}{10 \text{ kVA}} \right) \left(\frac{2400 \text{ V}}{2400 \text{ V}} \right)^2 = j2 \text{ p.u.}$$

$$Z_{g2} = j0.2 \left(\frac{100 \text{ kVA}}{20 \text{ kVA}} \right) \left(\frac{2400 \text{ V}}{2400 \text{ V}} \right)^2 = j1 \text{ p.u.}$$

$$Z_{T1} = j0.1 \left(\frac{100 \text{ kVA}}{40 \text{ kVA}} \right) \left(\frac{2400 \text{ V}}{2400 \text{ V}} \right)^2 = j0.25 \text{ p.u.}$$

$$Z_{B(L)} = \frac{V_{B(L)}^2}{S_B} = \frac{9600^2}{100,000 \text{ VA}} = \underline{\underline{921.6^{-2}}}$$

$$\hookrightarrow Z_{(L)} = \frac{50 + j200^{-2}}{921.6^{-2}} = \underline{\underline{0.054 + j0.217 \text{ p.u.}}}$$


$$Z_{T_2} = j0.1 \left(\frac{100 \text{ kVA}}{80 \text{ kVA}} \right) \left(\frac{5000 \text{ kV}}{4800 \text{ kV}} \right)^2 = \underline{\underline{j0.1356 \text{ p.u.}}}$$

OR $\frac{10000^{\text{V}}}{9600^{\text{V}}}$


Motor:


$$\bullet S_M = \frac{25 \text{ kVA}}{100 \text{ kVA}} = 0.25 \text{ p.u.}$$

$$\bullet V_M = \frac{4000^{\text{V}}}{4800^{\text{V}}} = 0.833 \text{ p.u.}$$

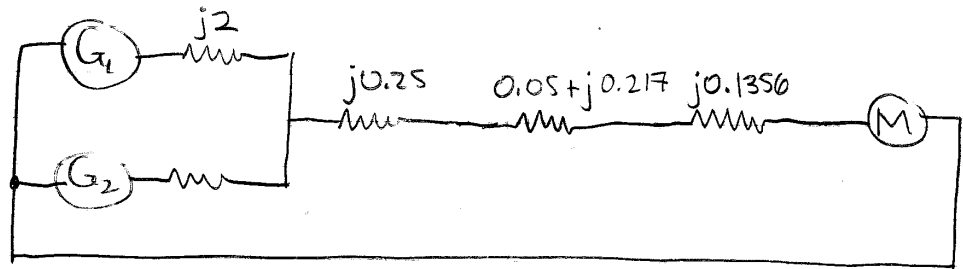

Problem 4

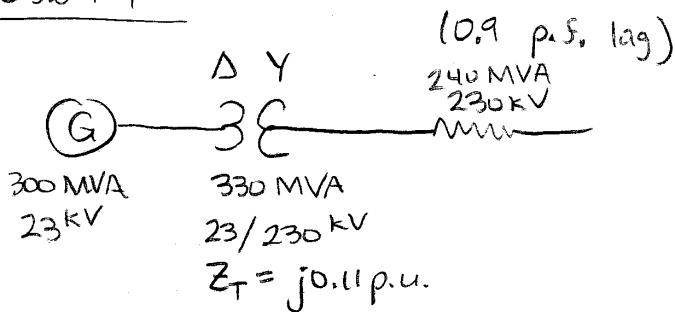

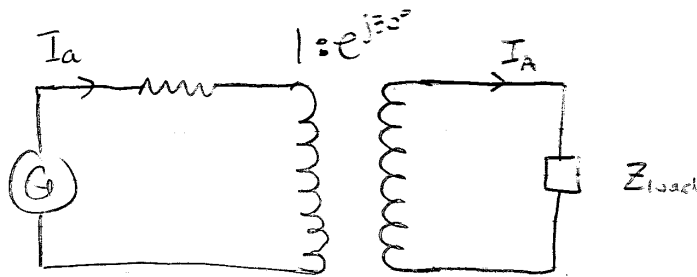

$$S_B = 100 \text{ MVA}$$

$$V_{B(L)} = 230 \text{ kV}$$

$$V_{B(G)} = 230 \text{ kV} \left(\frac{23 \text{ kV}}{230 \text{ kV}} \right) = 23 \text{ kV}$$

$$Z_T = (0.11 \text{ pu}) \left(\frac{100 \text{ MVA}}{330 \text{ MVA}} \right) \left(\frac{23 \text{ kV}}{23 \text{ kV}} \right)^2 = j0.033 \text{ p.u.}$$

Find

(a) I_A, I_B, I_C

$$I_A = I_{load} = \frac{240 \text{ MVA}}{\sqrt{3} \times 230} \angle -\cos^{-1}(0.9)$$

$$\text{OR } I_A = \frac{(240 \text{ MVA}/3)}{\frac{230}{\sqrt{3}}} \angle -\cos^{-1}(0.9)$$

$$\rightarrow I_A = 602.47 \angle -25.84^\circ \text{ A}$$

$$I_{B(L)} = \frac{100,000,000 \text{ VA}}{\sqrt{3} \times 230 \text{ kV}} = 251.03 \text{ A}$$

$$\rightarrow I_A = \frac{602.47 \angle -25.84^\circ \text{ A}}{251.03 \text{ A}} = \boxed{2.4 \angle -25.84^\circ \text{ p.u.}}$$

$$\left. \begin{aligned} I_B &= 2.4 \angle -25.84^\circ - 120^\circ \\ I_C &= 2.4 \angle -25.84^\circ - 240^\circ \end{aligned} \right\} \text{ p.u.}$$


(b) I_a, I_b, I_c

$$I_a = I_A \angle -30^\circ = 2.4 \angle -25.84^\circ - 30^\circ$$

$$\rightarrow \boxed{I_a = 2.4 \angle -55.84^\circ \text{ p.u.}}$$

$$\underline{I_b = I_B \angle -30^\circ} \quad \underline{I_c = I_C \angle -30^\circ}$$

(c)

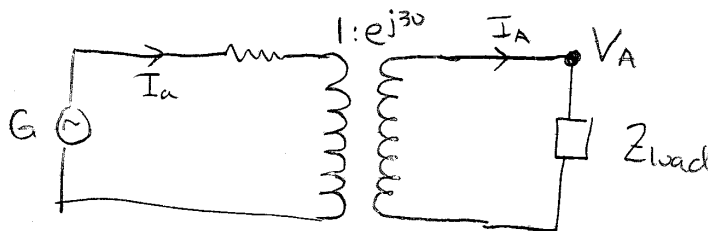

$$V_A = 1 \angle 0^\circ \quad (V_A \text{ taken as reference})$$

$$V_G = V_A + j X_T I_a = 1 \angle 0^\circ + (j0.033)(2.4 \angle -55.84^\circ)$$

$$V_G = 1.0374 \angle -26.02^\circ \text{ p.u.}$$

$$V_G = (1.0374 \angle -26.02^\circ)(23 \text{ kV})$$

$$\rightarrow \boxed{|V_G| = 23.86 \text{ kV}}$$

$$S = VI^* = (1.0374 \angle -26.02^\circ)(2.4 \angle -55.84^\circ)^*$$

$$S = 2.489 \angle 29.82^\circ$$

Real power supplied by generator:

$$P = 2.489 \cos(29.82^\circ) = 2.16 \text{ p.u.}$$

$$P = (2.16 \times 100) = \boxed{216 \text{ MW}}$$

Ignoring 30° phase shift:

$$(d) I_a = I_A = 2.4 \angle -25.84^\circ \text{ p.u.}$$

$$V_G = 1.0 + (j0.033)(2.4 \angle -25.84^\circ)$$

$$V_G = 1.0374 \angle 3.94^\circ$$

$$S = V_G \cdot I_a^* = (1.0374 \angle 3.94^\circ)(2.4 \angle -25.84^\circ)^*$$


$$= 2.489 \angle 29.78^\circ \text{ p.u.}$$

$$P = 2.489 \cos(29.78^\circ) = \underline{2.16 \text{ p.u.}}$$

↳ phase shift does not affect real power supplied by generator

(P is the same as in part (c))

Problem 5

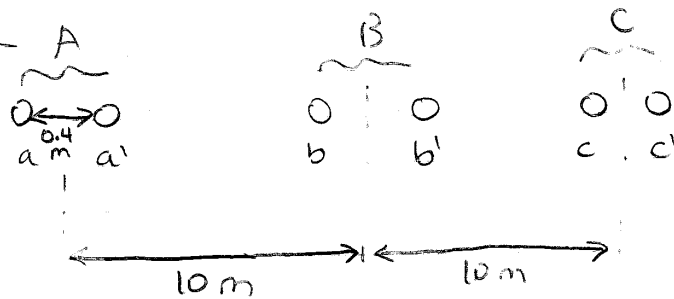

$$d = 1.108'' \quad \text{GMR} = 0.0375 \text{ ft.} \quad (D_s)$$

(a) Find $X_L = \omega L$

$$L = 2 \times 10^{-7} \ln \left(\frac{D_{eq}^B}{D_{sL}} \right)$$

$$D_{eq} = \sqrt[3]{D_{ab} D_{bc} D_{ca}} \quad \leftarrow \text{not true for bundled conductors}$$

$$D_{eq}^B = \sqrt[3]{D_{AB} D_{BC} D_{CA}}$$

$$\begin{aligned} \bullet D_{AB} &= \sqrt[4]{D_{ab} D_{ab'} D_{a'b} D_{a'b'}} \\ &= \sqrt[4]{(10)(10.4)(9.6)(10)} = \underline{\underline{9.996 \text{ m}}} \end{aligned}$$

$$\bullet D_{BC} = \underline{\underline{9.996 \text{ m}}} \text{ (by symmetry)}$$

$$\bullet D_{CA} = \sqrt[4]{D_{ca} D_{ca'} D_{c'a} D_{c'a'}} = \underline{\underline{19.99 \text{ m}}}$$

$$D_{eq}^B = \sqrt{(9.996)(9.996)(19.99)} = \underline{\underline{12.595 \text{ m}}}$$

two
bundle
conductors

$$\left\{ \begin{aligned} D_{SL} &= \sqrt{D_s \cdot d} & D_s &= 0.0114 \text{ m} \end{aligned} \right.$$

$$\rightarrow D_{SL} = \sqrt{(0.0114 \text{ m})(0.4 \text{ m})} = \underline{\underline{0.0676 \text{ m}}}$$

$$L = 2 \times 10^{-7} \ln \left(\frac{12.595 \text{ m}}{0.0676 \text{ m}} \right) \text{ H/m}$$

$$\rightarrow L = 10.455 \times 10^{-7} \text{ H/m}$$

$$L_b = 0.0010455 \text{ H/km}$$

$$X_L = (2\pi)(60)(0.0010455 \text{ H/km}) = \boxed{0.394 \frac{\Omega}{\text{km}}}$$

$$(b) \quad Y_L = \omega C$$

$$C = \frac{2\pi\epsilon}{\ln\left(\frac{D_{eq}}{D_{sc}}\right)}$$

$$\therefore D_{eq} = 12.595 \text{ m}$$

$$D_{sc}: \quad r = \frac{d}{2} = \frac{1.108}{2} \times 0.0254 = 0.0141 \text{ m}$$

$$D_{sc} = \sqrt{(0.0141 \text{ m})(0.4 \text{ m})} = 0.075 \text{ m}$$

$$C = \frac{2\pi\epsilon}{\ln\left(\frac{12.595 \text{ m}}{0.075 \text{ m}}\right)} = \boxed{10.852 \times 10^{-12} \text{ F/m}}$$

$$\therefore Y = \omega C = (2\pi)(60)(10.852 \times 10^{-9} \text{ F/km})$$