
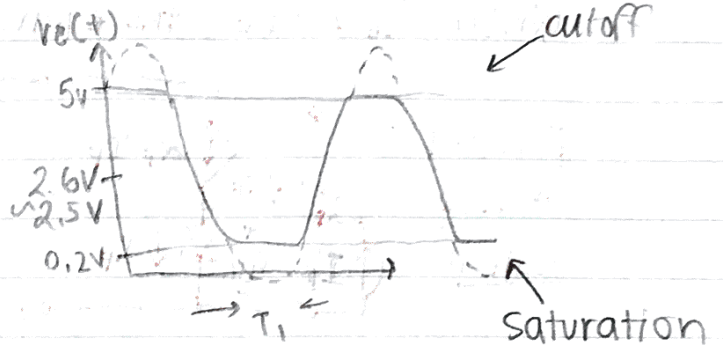


MIDTERM SOLUTIONS

5/4/18

PROBLEM 3.

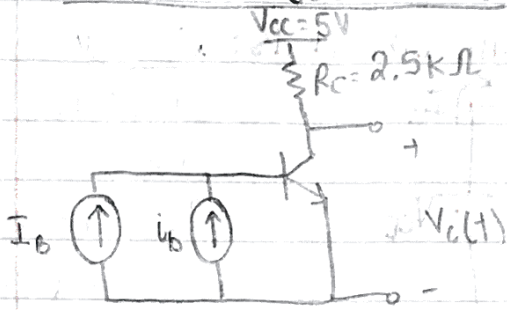

a). find I_B , I_C

$$i_b = -I_0 \sin \omega t$$

$I_0 > I_B$ ← causes cutoff

bias voltage

$$2.5 = V_{CC} - R_C I_C$$

$$I_C = \frac{2.5}{2.5k\Omega} = 1mA$$

$$I_B = 10mA$$

b). plot $V_C(t)$ if $I_0 = 8.8mA$ and $I_B = 10mA$

$$i_b = I_B - I_0 \sin \omega t$$

assume EA mode


$$I_C = \beta I_B = 1mA$$

$$V_C = V_{CC} - I_C R_C$$

$$\begin{aligned} V_{Cmin} &= V_{CC} - I_{Cmax} R_C \\ &= V_{CC} - (1.58mA)(2.5k\Omega) \\ &= 0.3V \end{aligned}$$

$$\begin{aligned} V_{Cmax} &= V_{CC} - I_{Cmin} R_C \\ &= 4.7V \end{aligned}$$

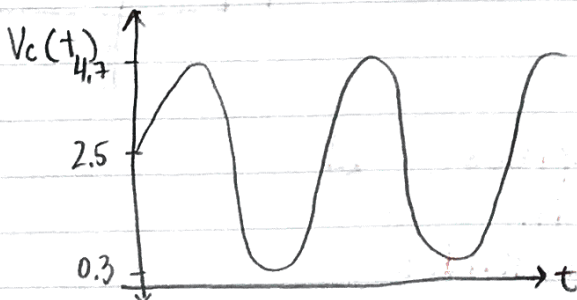
since $I_0 < I_B$, won't go into cutoff or saturation



← does not go to cutoff

← does not go to saturation

Problem 4

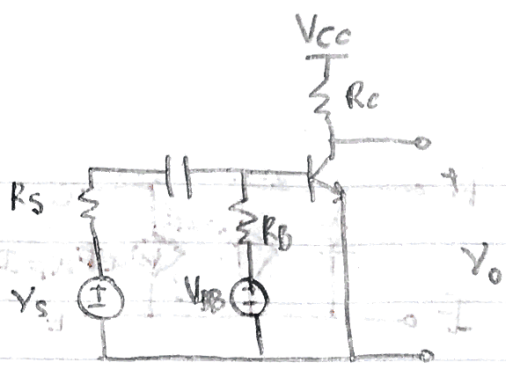

V_{CC} is biased optimally


$R_B, R_C \sim \times 10 R_S$

optimum bias point


Prove $\frac{V_O}{V_S} \approx -\frac{V_{CC}}{2V_T}$

$\frac{1}{2}V_{CC} = V_{CC} - I_C R_C \rightarrow I_C = \frac{V_{CC}}{2R_C}$

small signal equivalent:

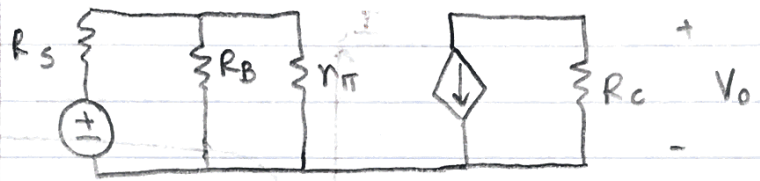

can neglect R_B

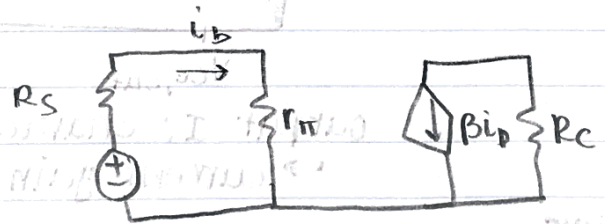

$i_b = \frac{V_S}{R_S + r_{\pi}}$

$V_O = -\beta i_b R_C$

$\frac{V_O}{V_S} = \frac{-\beta R_C}{R_S + r_{\pi}}$

$\frac{V_O}{V_S} = -\frac{\beta R_C}{R_S + \frac{V_T}{I_B}}$

$I_B = \frac{I_C}{\beta}$

$\frac{V_O}{V_S} \approx -\frac{\beta R_C}{R_S + \frac{V_T \beta^2 R_C}{V_{CC}}} \leftarrow \text{this is equal to } R_C$

$$\frac{V_o}{V_s} = \frac{-1}{R_s + R_c} \beta R_c \approx -\frac{\beta R_c}{R_c} = -\beta$$


gain is 100 ← this is equal to $\frac{V_{cc}}{2V_T}$

to get the expression:

$$\frac{V_o}{V_s} = -\frac{\beta R_c}{r_{\pi}} = -\frac{\beta R_c}{R_c \frac{2V_T}{V_{cc}}} = -\frac{V_{cc}}{2V_T}$$


← this is what we wanted

Problem 1:

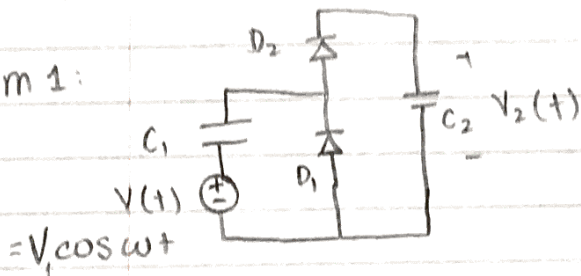


Plot $v_2(t)$ in steady state.

when $v(t) > 0$

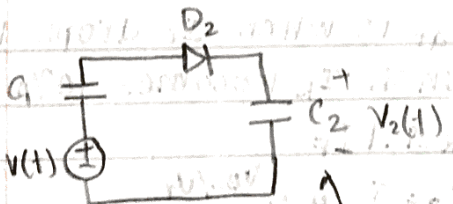

when $v(t) < 0$

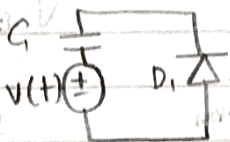



← C_1 is getting discharged

C_2 is always charging


max voltage across C_1 : V_1

max voltage across C_2 : $2V_1$


steady state for v_2 must be constant since it is always being charged

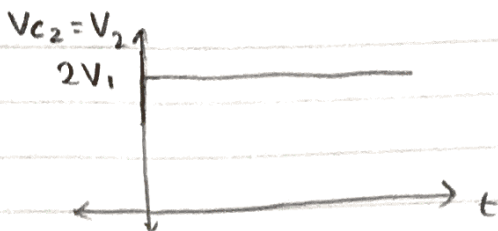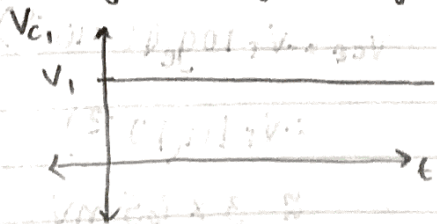

Problem 2

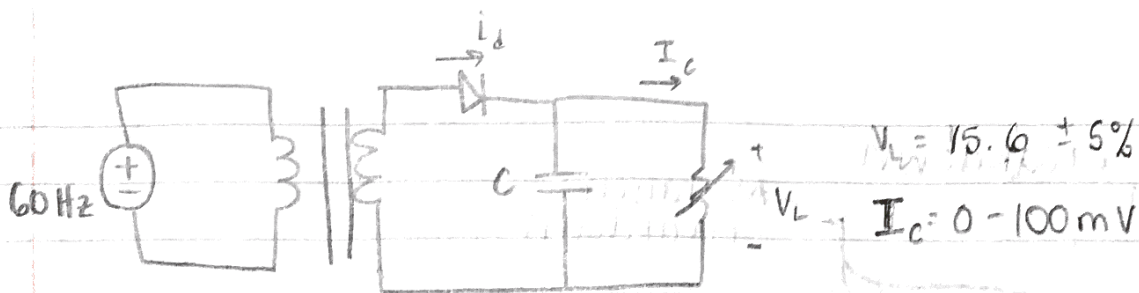


a) calculate the smallest C.

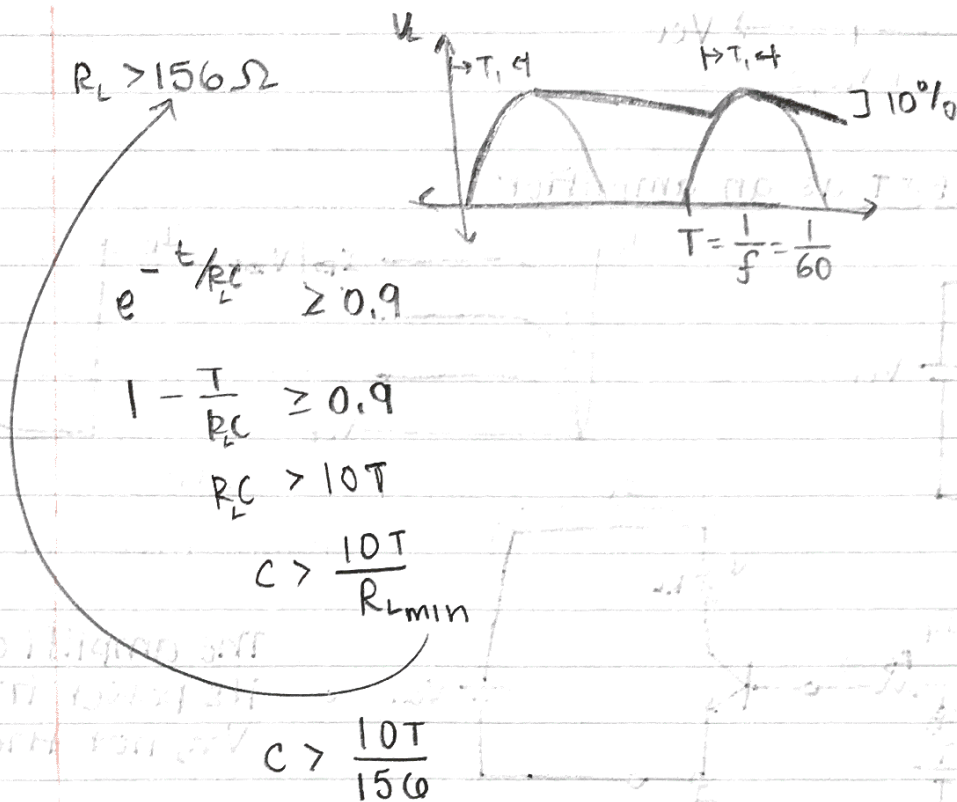

b)

$i_d(t) = I_L$ at DC

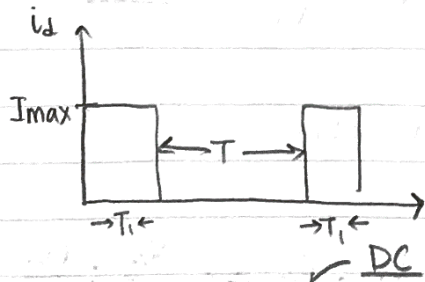

diode only conducts during T_i , when diode is on

$I_{max} T_i = I_L T$

$\cos \theta = 0.9$

$\rightarrow \theta$

$\frac{\theta}{2\pi} = \frac{T_i}{T} \rightarrow \frac{T_i}{T} = \frac{I_L}{I_{max}} = \frac{\theta}{2\pi}$